

Republic of Iraq
Ministry of Higher Education
and Scientific Research
Al-Mustaqbal University College
Computer Engineering Techniques Department



Subject: Fundamentals of Electrical Engineering

First Class

Lecture Seven

By

Dr. Jaber Ghaib


MSc. Sarah Abbas

نظرية ثيفنين Thevenin's Theorem


نظرية ثيفنين هي نظرية لتحليل الدوائر الكهربائية.

فائرة ثيفنين هي دائرة تحتوي على مقاومة تسمى مقاومه ثيفنين (R_{Th}) ومصدر جهد ثيفنين (E_{Th}), اي ان اي دائرة كهربائية ذات تيار مستمر يمكن استبدالها بدائرة ثيفنين وهي عبارة عن حاوية لها مخرجين (a) و (b) كما بالشكل:

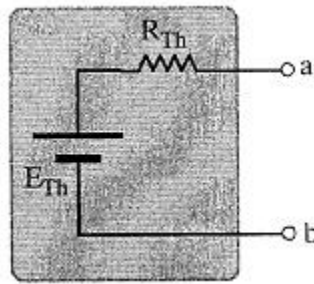المقاومة (R_{Th}) موصله على التوالي مع المصدر (E_{Th}).



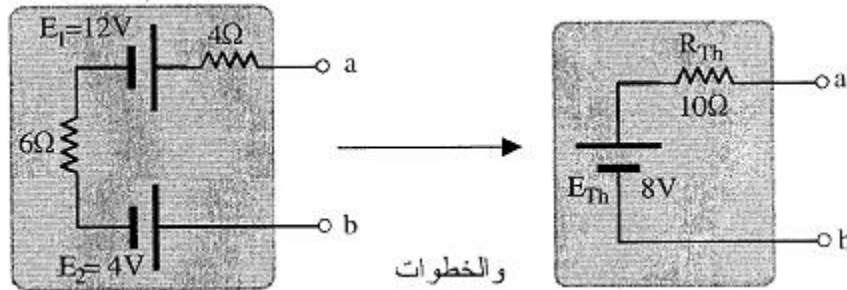والشكل التالي يوضح كيفية اختزال دائرة كهربائية لتصبح دائرة ثيفنين




والخطوات التالية توضح طريقة تحويل دوائر كهربائية للوصول الى دائرة ثيفنين:


١. اقطع الجزء من الدائرة المراد تحديد مكافئ ثيفنين له.
٢. حدد المخرجين a و b للدائرة.
٣. اوجد قيمة (R_{Th}) وذلك باستبدال جميع المصادر في الدائرة, حيث يستبدل مصدر الجهد بدائرة مغلقة (Short circuit) مصدر التيار بدائرة مفتوحة (Open circuit) وبالتالي يمكن حساب المقاومة (R_{Th}) ما بين النقطتين a و b.

٤. احسب الجهد (E_{Th}) وذلك بارجاع جميع المصادر الى حالتها الاصلية ومن ثم ايجاد فرق الجهد ما بين النقطتين a و b.
- وفي حال وجود اكثر من مصدر جهد نستخدم طريقة التراكيب لاجاد (E_{Th}) الكلية.
٥. نرسم دائرة ثيفنين المكافئة مع ارجاع الجزء المحذوف من الدائرة الاصلية.

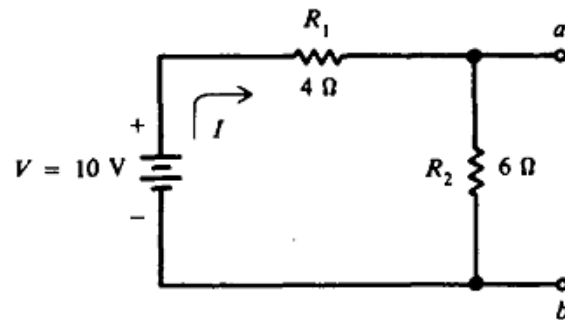Example 1: Find the Thevenin equivalent to the circuit at terminals a and b



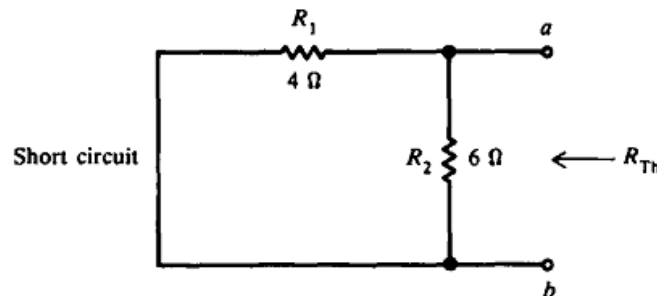
Sol: Step 1. Find R_{Th} . Short-circuit the voltage source $V = 10V$. R_1 and R_2 are in parallel.




$$R_{Th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{4(6)}{4 + 6} = \frac{20}{10} = 2.4\Omega$$

Find V_{Th} . V_{Th} is the voltage across terminals a and b, which is the same as the voltage drop across resistance R_2 .


$$I = \frac{V}{R_1 + R_2} = \frac{10}{4 + 6} = \frac{10}{10} = 1 \text{ A}$$
$$V_{\text{Th}} = V_2 = IR_2$$
$$V_{\text{Th}} = 1(6) = 6 \text{ V} \quad \text{Ans.}$$

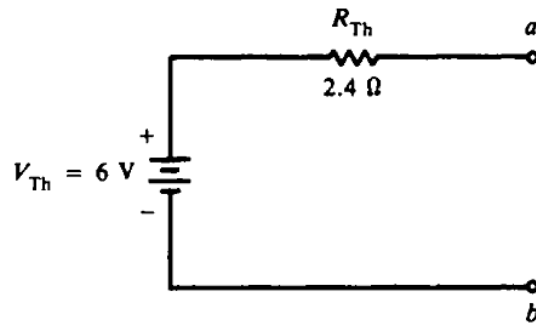

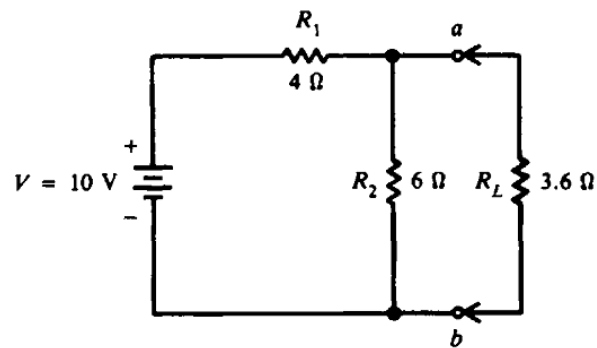Example 2: To the circuit of Example 1, add a resistor load R_L of **3.60** and find the current I_L through the load and voltage V_L across the load.




Sol:

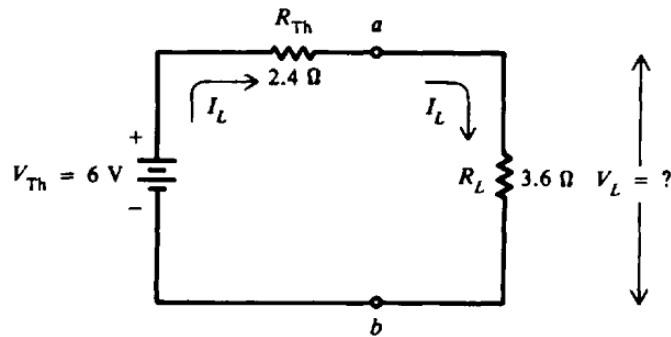


$$I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{6}{2.4 + 3.6} = \frac{6}{6} = 1 \text{ A}$$

$$V_L = I_L R_L = 1(3.6) = 3.6 \text{ V} \quad \text{Ans.}$$

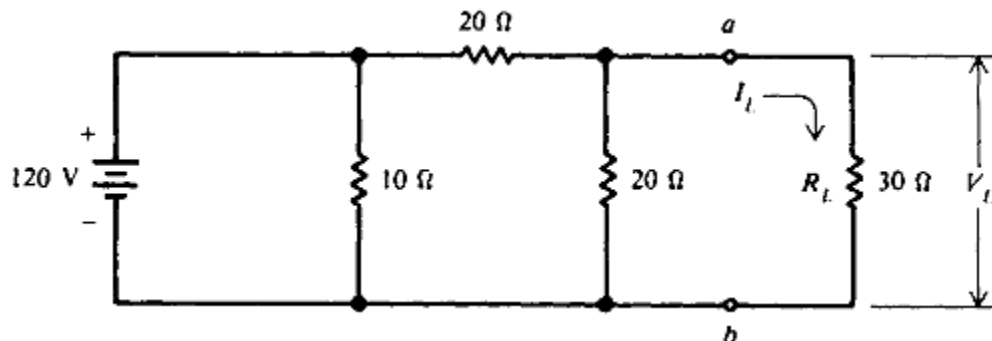Example 3: Find the load current I_L and the load voltage V_L in the circuit of fig below by use of Thevenin's theorem.



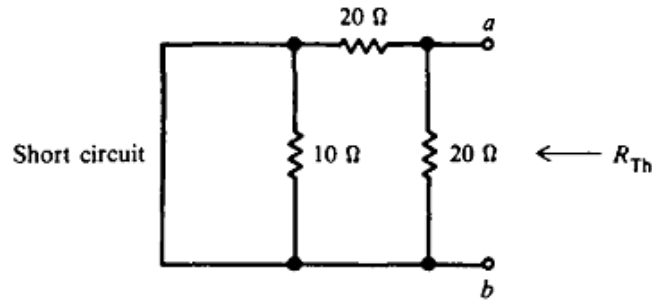Sol: **Step 1.** Find R_{Th} . Remove the load R_L . Short-circuit the voltage source of 120V. Short-circuiting the battery also short-circuits the 10Ω resistor, leaving two 20Ω resistors in parallel.




$$R_{Th} = \frac{20}{2} = 10\Omega$$

Step 2: Find V_{Th} . The two 20Ω resistors are in series across the 120-V line. Since the voltage is the same across equal resistances and V_{Th} is the open-circuit voltage at **a** and **b** across the 20Ω resistor,

$$V_{Th} = \frac{120}{2} = 60\text{V}$$

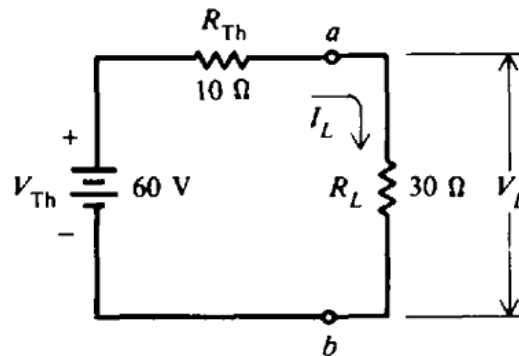Step 3. Draw the equivalent circuit with R_L and find I_L and V_L .




$$I_L = \frac{V_{Th}}{R_L + R_{Th}} = \frac{60}{30 + 10} = \frac{60}{40} = 1.5 \text{ A}$$

Ans.


$$V_L = I_L R_L = 1.5(30) = 45 \text{ V}$$

Ans.

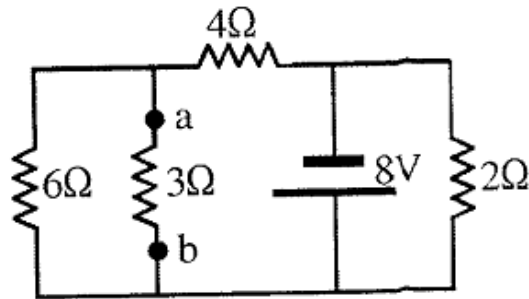Example 4: Find the Thevenin equivalent to the circuit at terminals a and b



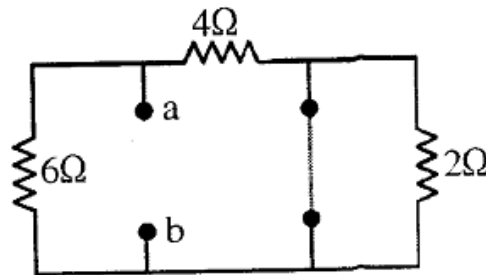
Sol: Step 1. Find R_{Th} by replace the voltage source with short circuit




$$R_{Th} = 4 // 6$$

$$R_{Th} = \frac{4 \times 6}{4 + 6} = \frac{24}{10} = 2.4\Omega$$

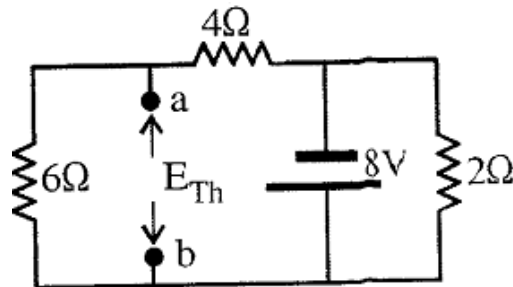
Step 2: find V_{Th} which is the voltage across the 6Ω resistance




$$E_{Th} = \frac{8V \times 6\Omega}{6\Omega + 4\Omega} = \frac{48}{10} = 4.8V$$

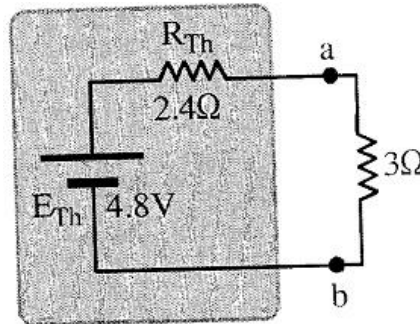

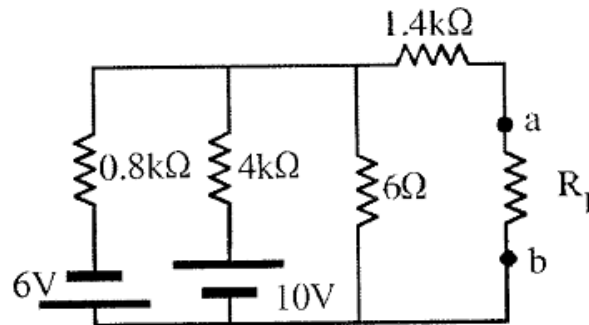Example 5: Find the Thevenin equivalent to the circuit at terminals a and b



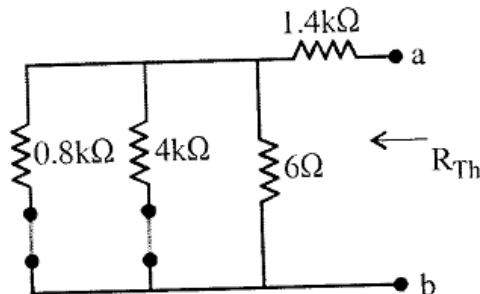
Sol: Step 1. Find R_{Th} by replace the voltage source with short circuit



$$0.8k\Omega // 4k\Omega // 6k\Omega = 0.6k\Omega$$

$$R_{Th} = 0.6k\Omega + 1.4k\Omega = 2k\Omega$$

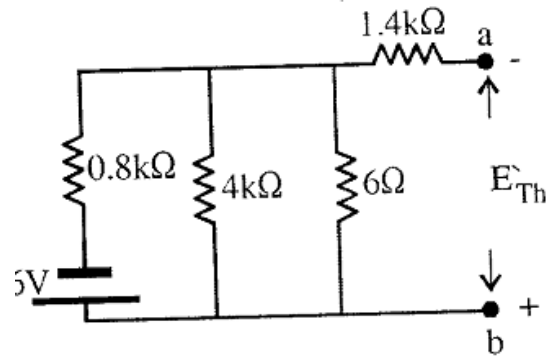Step 2: find V_{Th} with the effect of (6V) voltage source




The resistance (1.4k Ω) neglected because the circuit is open. So V_{Th} is the voltage across the 6 Ω resistance

$$4k\Omega // 6k\Omega = 2.4k\Omega$$

By using voltage divider rule

$$E'_{Th} = \frac{6V \times 2.4k\Omega}{2.4k\Omega + 0.8k\Omega} = \frac{14.4}{3.2} = 4.5V$$

the effect of (10V) voltage source

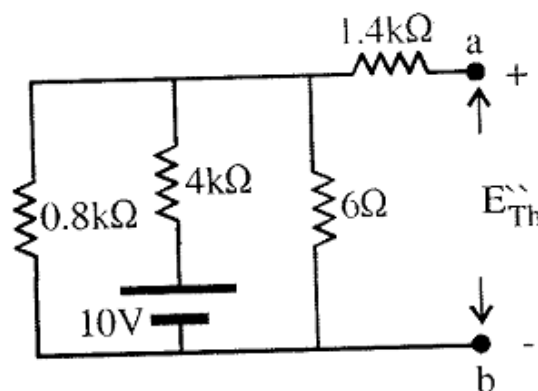

$$0.8k\Omega // 6k\Omega = 0.706k\Omega$$

$$E''_{Th} = \frac{10V \times 0.706k\Omega}{0.760k\Omega + 4k\Omega} = \frac{7.06}{4.706} = 1.5V$$

Since E'_{Th} and E''_{Th} are opposite to each other the

$$E_{Th} = E'_{Th} - E''_{Th}$$

$$E_{Th} = 4.5 - 1.5 = 3V$$

