

**Republic of Iraq**  
**Ministry of Higher Education**  
**and Scientific Research**  
**Al-Mustaqbal University College**  
**Computer Engineering Techniques Department**



**Subject: Fundamentals of Electrical Engineering**

**First Class**

**Lecture Four**


**By**

**Dr. Jaber Ghaib**

**MSc. Sarah Abbas**
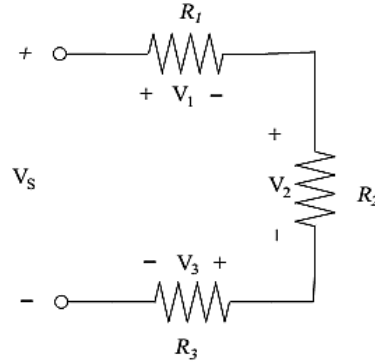
## قانون كير شوف للجهود (Kirchhoff's Voltage Law (KVL))

ينص على " في اي مسار مغلق يكون المجموع الجبري للجهود مساوياً صفرًا "



$$V_s = V_1 + V_2 + V_3$$


$$V_s - V_1 - V_2 - V_3 = 0$$

خطوات الحل بطريقة كير شوف:-

١- نترض اتجاه التيار في كل فرع (مسار مغلق)

٢- كتابة معادلة الجهد لكل مسار مغلق

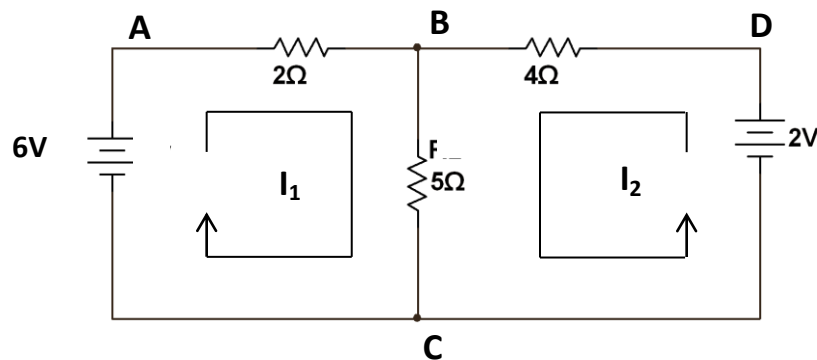**Example 1:** In the following circuit, calculate the current in each element of the circuit using Kirchhoff's Law





Sol:

In the first loop  $I_1$ :

$$6 = 2 \times I_1 + 5 \times (I_1 + I_2)$$

In the second loop  $I_2$ :

$$2 = 4 \times I_2 + 5 \times (I_1 + I_2)$$

Solving the two equations

$$30 = 35 \times I_1 + 25 \times I_2$$

$$-14 = -35 \times I_2 - 63 \times I_2$$

---

$$16 = 0 - 38 I_2$$

$$\therefore I_2 = \frac{16}{-38} = -0.421 A$$

Sub. The value of  $I_2$  in the second equation we get:

$$2 = 5 \times I_1 - 9 \times 0.421$$

$$I_1 = \frac{5.789}{5} = 1.16 A$$

So the current flow in  $R_{BC}$  is:

$$I_3 = I_1 + I_2$$

$$= 1.16 + (-0.421) = 0.739 A$$

## قانون تقسيم الجهد (Voltage divider Rule)

بما ان التيار المار في مقاومات موصلة على التوالي يكون متساوياً فان هذا يؤدي الى ان هبوط الجهد على مقاومة حسب قانون اوم يعتمد على قيمة المقاومة.

فمن هذا البيان يتضح لنا، ان الجهد المطبق في الدائرة الموصلة على التوالي سوف يتسم على المقاومات حسب قيمة كل منها، فالاكبر يكون هبوط الجهد عليها كبيراً وهكذا.

ولحساب قيمة الجهد على مقاومة في الدائرة فاننا نطبق العلاقة التالية:

$$V_x = \left( \frac{R_x}{R_T} \right) V_s$$


حيث:

$V_x$ : هبوط الجهد المجهول على المقاومة  $R_x$ .

$R_T$ : المقاومة الكلية

$V_s$ : جهد المصدر

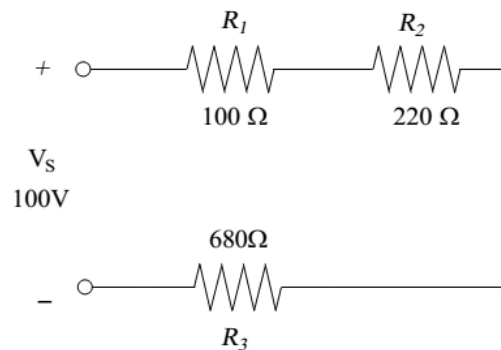**Example 2:** In the following circuit find the value of voltage drop through the resistance  $R_3$



Sol:

$$V_{R3} = V_S \left( \frac{R_X}{R_T} \right)$$


$$R_T = R_1 + R_2 + R_3$$

$$R_T = 100\Omega + 220\Omega + 680\Omega = 1K\Omega$$

$$V_{R3} = 100 * \frac{680}{1000} = 68 V$$
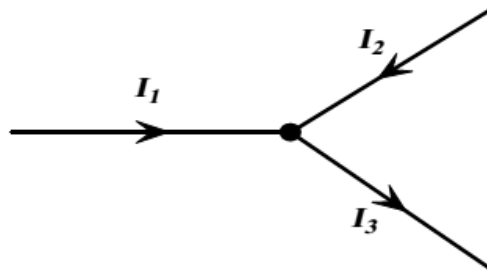
### قانون كيرشوف للتيار ((Kirchhoff's Current Law (KCL))

في اي نقطة في الدائرة فان المجموع الجبري للتيارات يساوي الصفر. اي ان مجموع التيارات الداخلة الى النقطة والخارجة من النقطة تساوي الصفر. ويتضح هذا من الشكل التالي:




ويمكن اعتبار ان اشارة التيار الداخل الي النقطة تكون سالبة و اشارة التيار الخارج من النقطة تكون موجبة و بالتالي:

$$I_3 - I_2 - I_1 = 0$$



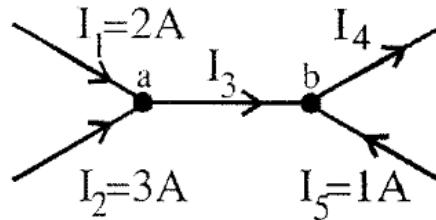**Example 3:** Find the value  $I_3$  and  $I_4$  using Kirchoff's Current Law (KCL).



Sol:

At node (a)


$$I_3 = I_1 + I_2$$
$$I_3 = 2A + 3A = 5A$$

At node (b)

$$I_4 = I_3 + I_5$$

$$I_4 = 5A + 1A = 6A$$

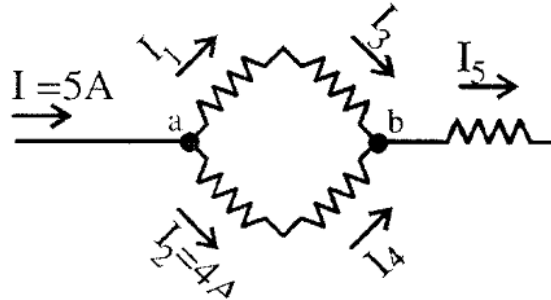**Example 4:** From the figure below find the value of  $I_1$ ,  $I_3$ ,  $I_4$ , and  $I_5$



Sol: at node (a)

$$I = I_1 + I_2$$

$$5A = I_1 + 4A$$

$$I_1 = 1A$$

At node (b)

$$I_3 + I_4 = I_5$$

Since  $I_1$  is not divide so its equal to  $I_3$

$$I_3 = I_1 = 1A$$


So that for  $I_4 = I_2$

$$I_4 = I_2 = 4A$$


$$I_5 = I_3 + I_4 = 1A + 4A = 5A$$
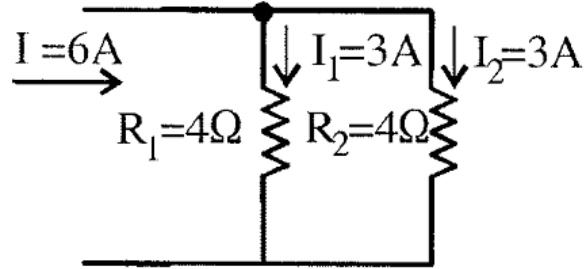
## قانون تجزئة التيار (Current Divider Rule(CDR) )


١- يتجزأ التيار المار في مقاومتين على التوازي، و يتجزأ قيمته بالتساوي على مقاومتين في حالة تساويهما في القيمة



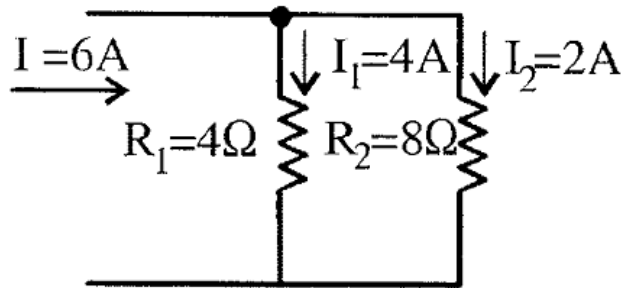٢- اما التيار المار في مقاومتين مختلفتين فيتجزأ بحيث يكون للمقاومة الاصغر تيار أكبر، ويكون للمقاومة الاكبر قيمة تيار أصغر.



في حالة مقاومتين متصلتين على التوازي

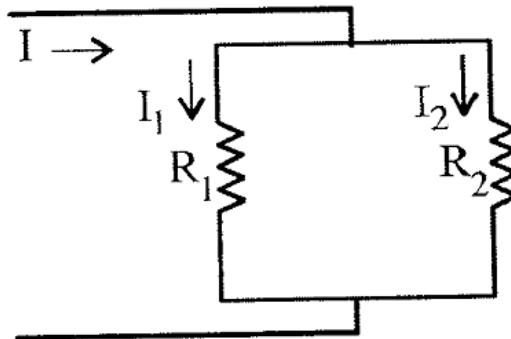



$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

$$I_1 = \frac{R_T}{R_1} I$$


$$\therefore = \frac{[(R_1 R_2) / (R_1 + R_2)]}{R_1} I$$

$$\therefore I_1 = \frac{R_2}{R_1 + R_2} I$$

وبنفس الكيفية تكون قيمة  $I_2$

$$\therefore I_2 = \frac{R_1}{R_1 + R_2} I$$

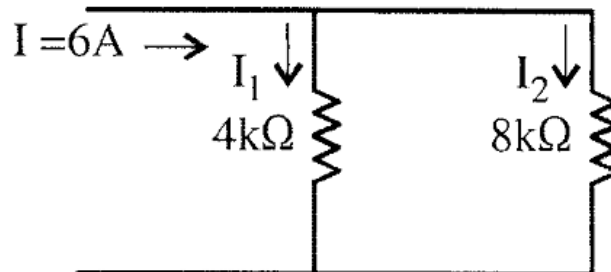**Example 5:** find the value of the current  $I_2$  in the following circuit using (CDR):




Sol:



$$I_2 = \frac{R_1}{R_1 + R_2} I = \frac{(4k\Omega)(6A)}{4k\Omega + 8k\Omega}$$

$$I_2 = \frac{24}{12} = 2A$$

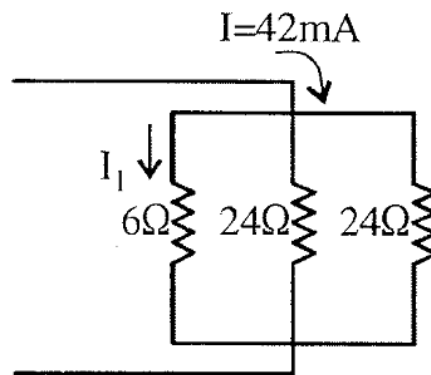**Example 6:** Find the value of the current  $I_1$  in the circuit below.



Sol:

$$R_T = 6\Omega // 24\Omega // 24\Omega \\ = 6\Omega // 12\Omega$$


$$= \frac{6 \times 12}{6 + 12} = \frac{72}{18}$$

$$R_T = 4\Omega$$

$$I_1 = \frac{R_T}{R_1} I$$

$$I_1 = \frac{(4\Omega)(42 \times 10^{-3} A)}{6\Omega} = 28\text{mA}$$

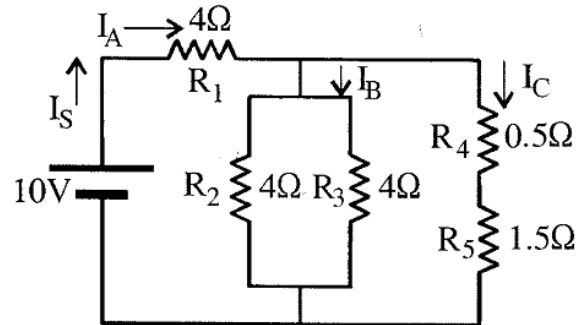**Example 7:** from the circuit in the following figure find the value of the current and voltage in each resistance.



**Sol:** by simplification the circuit we get


$$R_A = R_1 = 4\Omega$$

$$R_B = R_2 // R_3 = 4\Omega // 4\Omega$$

$$R_B = 2\Omega$$

$$R_C = R_4 + R_5 = 0.5 + 1.5$$

$$R_C = 2\Omega$$

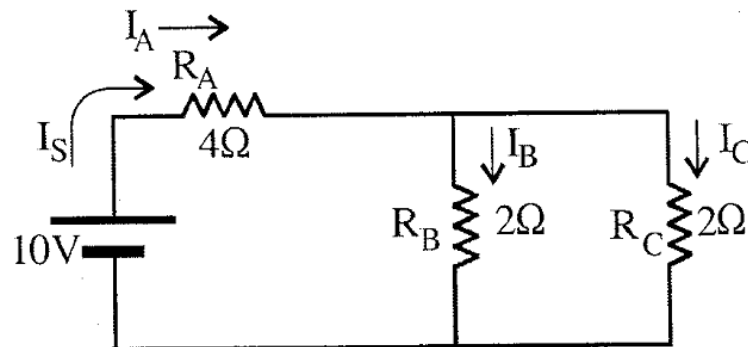

The resistance  $R_B$  and  $R_C$  are in parallel

$$\therefore R_{B//C} = \frac{R}{N} = \frac{2\Omega}{2} = 1\Omega$$

The total resistance is

$$R_T = R_A + R_{B//C}$$



$$R_T = 4\Omega + 1\Omega = 5\Omega \quad \longrightarrow \quad I_S = \frac{E}{R_T} = \frac{10V}{5\Omega} = 2A$$

We can find currents in the circuit  $I_A, I_B, I_C$


$$I_A = I_S = 2A$$

Since  $R_B, R_C$  are equal, so the current will be divided between them

$$I_B = I_C = \frac{I_A}{2} = \frac{2A}{2} = 1A$$

By return to the original shape of the circuit, we can find the current following through the resistance  $R_2, R_3$
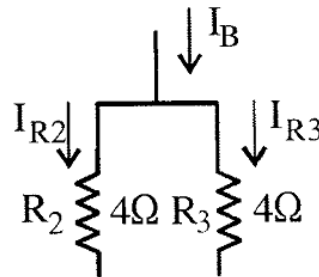
$$I_{R_2} = I_{R_3} = \frac{I_B}{2} = \frac{1A}{2} = 0.5A$$



The voltages  $V_A, V_B, V_C$  can be found as:

$$V_A = I_A R_A = (2A)(4\Omega) = 8V$$

$$V_B = I_B R_B = (1A)(2\Omega) = 2V$$

$$V_C = I_C R_C = (1A)(2\Omega) = 2V$$

By using KVL to prove the solution

$$\sum V = 0$$


$$E - V_A - V_B = 0$$

$$10 - 8 - 2 = 0$$

$$10 - 10 = 0$$

$$0 = 0$$

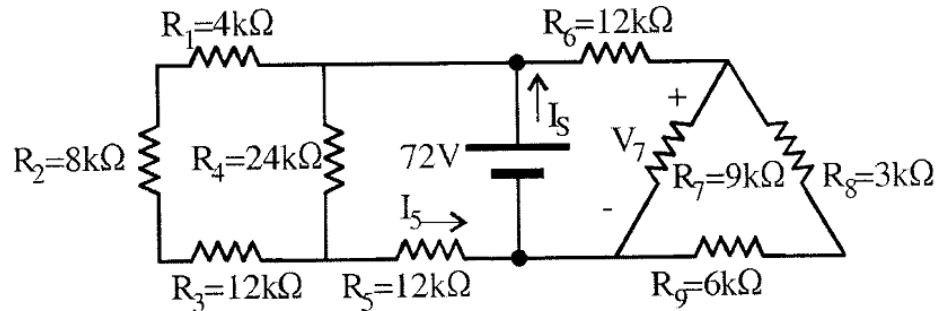
**Example 8:** In the following circuit find the two currents  $I_s$  and  $I_5$  and the voltage  $V_7$ .



**Sol:**

The resistances  $R_1$ ,  $R_2$  and  $R_3$  are connected in series and its equivalent  $24 \text{ k}\Omega$ . The resistance  $R_8$  and  $R_9$  are connected in series and their equivalent is  $9 \text{ k}\Omega$ .

So the circuit can be drawn as

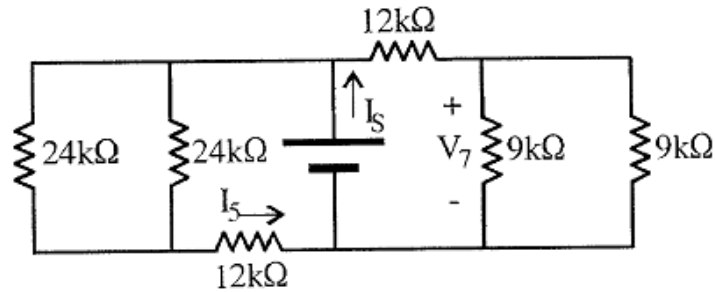


$$12k\Omega \longleftarrow 24k\Omega // 24k\Omega$$

$$24k\Omega \longleftarrow 12k\Omega + 12k\Omega$$

$$4.5k\Omega \longleftarrow 9k\Omega // 9k\Omega$$

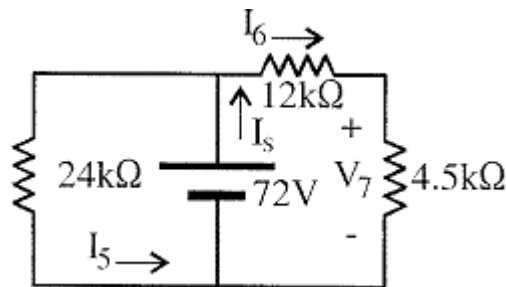The voltage of the 24 kΩ resistance equal to 72V in parallel with the voltage source



$$\therefore I_s = \frac{72V}{24k\Omega} = 3mA$$


To calculate the value of  $V_7$  we use Voltage Divided Rule

$$V_7 = \frac{(72V)(4.5k\Omega)}{4.5k\Omega + 12k\Omega} = \frac{324V}{16.5} = 19.6V$$

To find the current  $I_6$

$$I_6 = \frac{19.6V}{4.5k\Omega} = 4.35mA$$

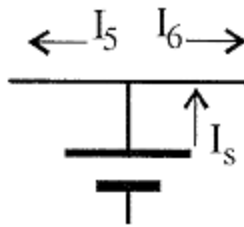To calculate the current  $I_s$  we use Kirchhoff's Voltage Law(KVL)



$$I_s = I_5 + I_6$$

$$= 3\text{mA} + 4.35\text{mA} = 7.35\text{mA}$$

**Example 2.19.** A circuit consists of two parallel resistors, having resistance of  $20\ \Omega$  and  $30\ \Omega$  respectively, connected in series with  $15\ \Omega$ . If current through  $15\ \Omega$  resistor is  $3\ \text{A}$ , find (i) the current through  $20\ \Omega$  and  $30\ \Omega$  resistors (ii) the voltage across the whole circuit and (iii) total power.

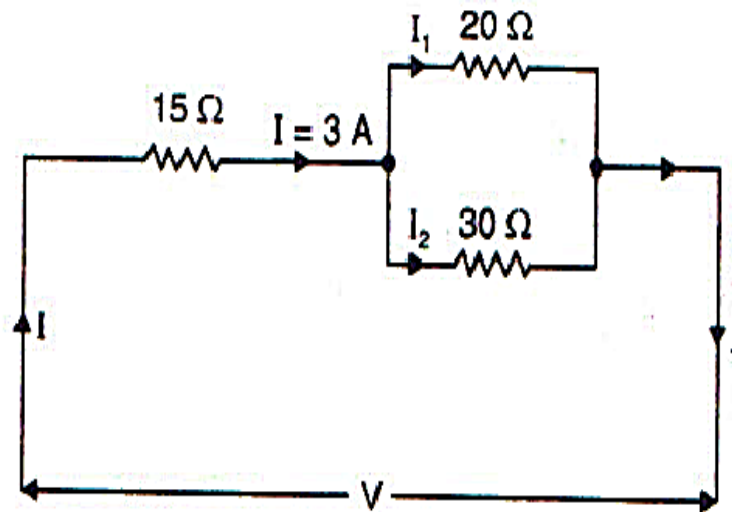


Fig. 2.25

**Solution.** Fig. 2.25 shows the circuit arrangement.

(i) The total current of  $3\ \text{A}$  will divide between  $20\ \Omega$  and  $30\ \Omega$  as under :  
 Current through  $20\ \Omega$ ,

$$I_1 = 3 \times \frac{30}{20 + 30} = 1.8\ \text{A}$$

Current through  $30 \Omega$ ,  $I_2 = 3 \times \frac{20}{20 + 30} = 1.2 \text{ A}$


(ii) For parallel circuit,  $R_p = \frac{20 \times 30}{20 + 30} = 12 \Omega$

Total circuit resistance =  $15 + 12 = 27 \Omega$

$\therefore$  Supply voltage,  $V = 3 \times 27 = 81 \text{ V}$


(iii) Total power =  $V I = 81 \times 3 = 243 \text{ watts}$

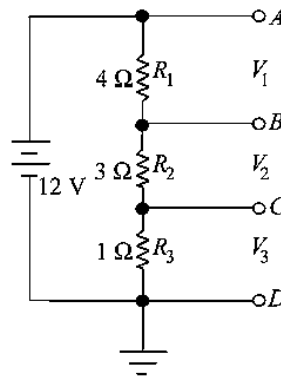**Q1:** find the value of different voltages that can be obtained from a 12-V battery ( $V_{AB}$ ,  $V_{BC}$ ,  $V_{CD}$ ,  $V_{AC}$ ,  $V_{AD}$ ) with the help of voltage divider circuit shown below



Ans.[6 V, 4.5 V, 1.5 V, 10.5 V, 12 V]

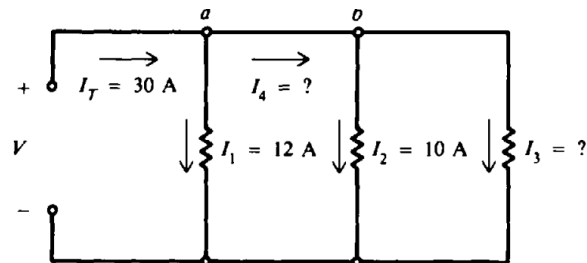**Q2:** Find the value of  $I_3$  and  $I_4$  using KCL



Ans.[8 A, 18 A]