



Analog electronics

Third lecture

Characteristic Curves, Hybrid Parameters, Equivalent Circuit

Dr. Mohammed Hashim

MS. Noor Hayder

Third stage

Department of medical physics

Al-Mustaqbal University-College

2022- 2023

Outline

1. Characteristic curves
2. hybrid parameters
3. equivalent circuit
4. References

3.1 Characteristic curves

The I-V Characteristic Curves, which is short for Current-Voltage Characteristic Curves or simply I-V curves of an electrical device or component, are a set of graphical curves which are used to define its operation within an electrical circuit. As its name suggests, I-V characteristic curves show the relationship between the current flowing through an electronic device and the applied voltage across its terminals. I-V characteristic curves are generally used as a tool to determine and understand the basic parameters of a component or device and which can also be used to mathematically model its behavior within an electronic circuit. But as with most electronic devices, there are an infinite number of I-V characteristic curves representing the various inputs or parameters and as such we can display a family or group of curves on the same graph to represent the various values. Figure below show characteristic curves of an ideal resistor.

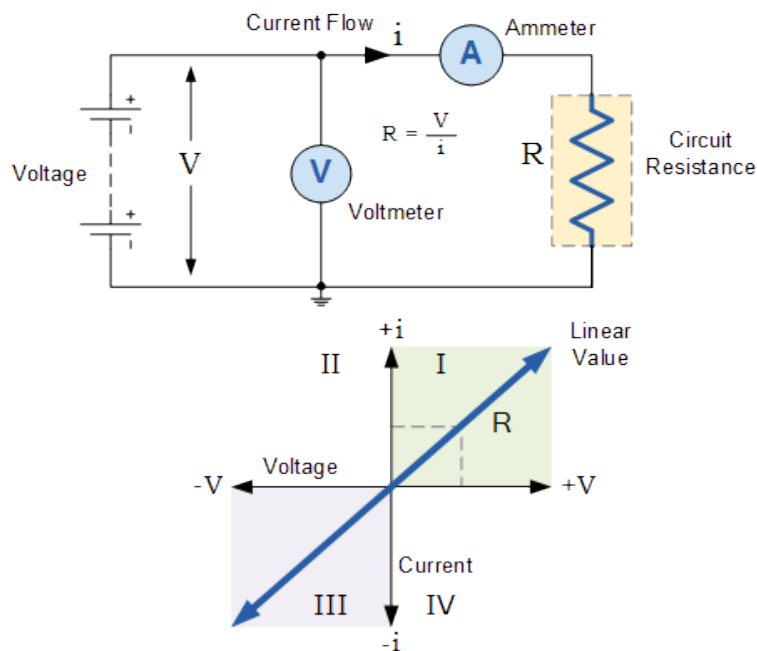


Figure 1: Characteristic curves of an ideal resistor circuit.

Figure below show Characteristic Curve of a Diode.

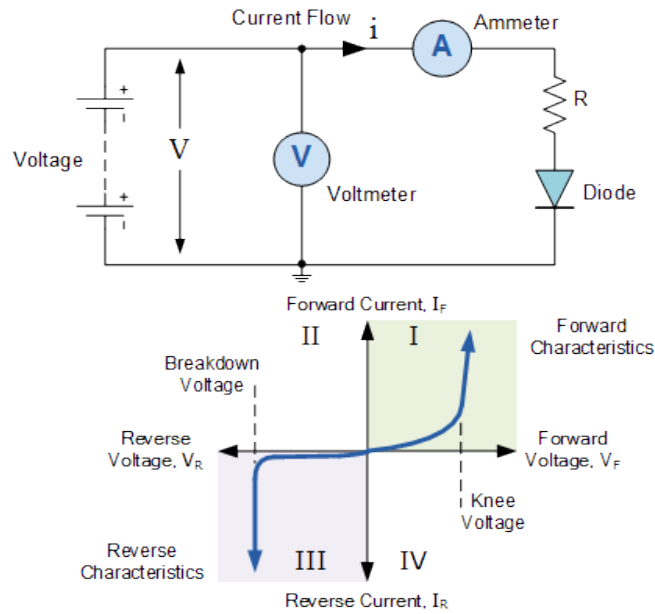


Figure 2: Characteristic curves of an diode circuit..

Characteristic Curves of Transistor

Figure 3 below shows a simple circuit of a transistor, in which the 1.5 V battery and the resistance R_B determine the base current I_B , and the 24 V battery together with R_C define the collector current I_C . We are interested in determining the variation of the collector current I_C . This current can be varied either by changing the base current I_B or the collector-emitter voltage V_{CE} (the voltage between the collector C and the emitter E). The base current can be varied by the variable resistor R_B .

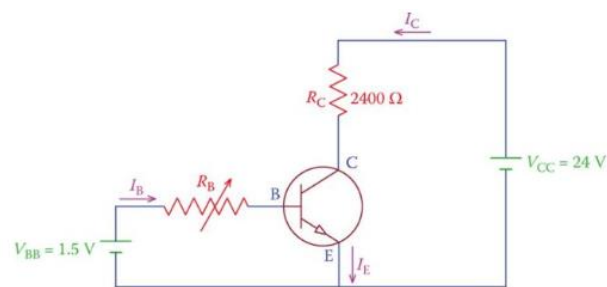


Figure 3: Simple circuit for a transistor operation.


The characteristic curves of a transistor provide the relationship between collector-emitter voltage and collector current for different values of the base current. Because there are two parameters that affect I_C , a set of individual curves shown together denote various operating conditions.

A typical curve is shown in Figure 4a, and a set of these curves are depicted in Figure 4b. Each individual curve depicts the variation of I_C versus the value of collector-emitter voltage (VCE) for a fixed value of base current I_B .


Cut Off Region: When I_B is zero, a transistor is **cut off**, and it does not conduct no matter how much voltage is applied to the collector; any collector current is due to leaks, is very small, and is negligible. In both Figure 4a and b, the curve corresponding to $I_B = 0$ is exaggerated for clarity. The area under the curve corresponding to $I_B = 0$, shaded in Figure 4a, represents the region where a transistor is cut off and is not conducting.

Saturation Region: For each nonzero value of I_B , the collector current starts from zero when the collector-emitter voltage is zero. A transistor starts conducting and the collector current increases rapidly when $V_{CE} > 0$. The area around this abrupt change in I_C also shaded in Figure 4a, corresponds to when a transistor is in saturation.

Saturation implies that the collector current has reached its maximum value for that collector-emitter voltage and cannot increase further by increasing the base current I_B . For example, consider point M corresponding to $V_{CE} = V_M$ in Figure 4b. For this point, I_C has reached its maximum and cannot be increased by increasing I_B . In contrast, an increase in I_B can move point N to N' , both corresponding to a collector-emitter voltage V_N .

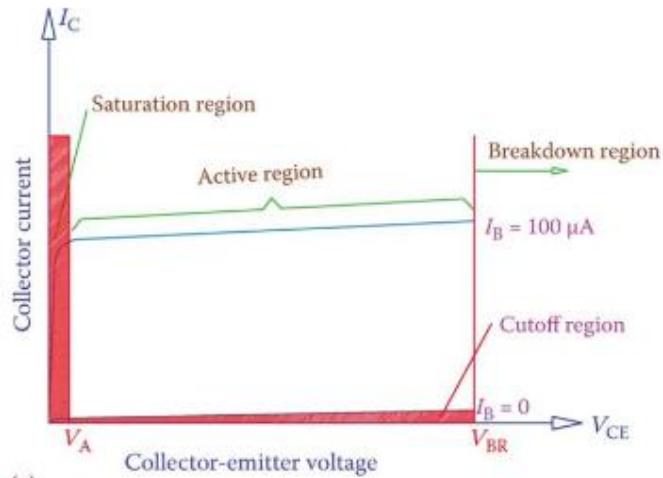

(a)

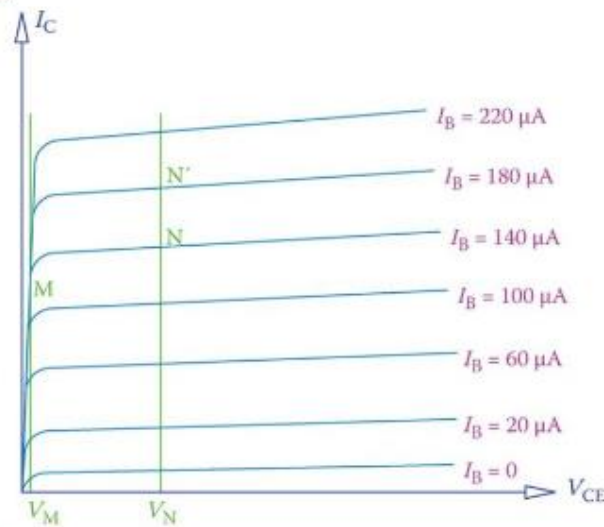

(b)

Figure 4: Collector current versus collector voltage characteristic curve of a transistor. (a) For one value of base current. (b) For multiple values of base current.

Saturation (in a transistor): The state of a transistor at which the collector current has reached its maximum value for the present collector-emitter voltage, and cannot increase further by only increasing the base current I_B .

Active Region: When saturated, a transistor cannot operate as expected. In normal operation, transistors function in the active region, the area that the characteristic curve is a segment of an almost horizontal straight line. In this region increasing collector-emitter voltage has little effect on the collector current. In other words, the transistor exhibits a large resistance in this region, so that increasing voltage has little effect on the current through it. This resistance is variable because it depends on the value of I_B (for each value of I_B the ratio V_{CE}/I_C is different).

Active region: An area in the characteristic curve of a transistor, in terms of collector-emitter voltage and collector current values that the transistor can function. If any of these values falls outside of its range a transistor falls in the saturation region or cutoff region and cannot function (see Figure 4a).

Breakdown voltage: Voltage at which a semiconductor device changes behavior or gets damaged.

3.2 hybrid parameters

For analyzing circuits containing active devices such as transistors, it is more convenient to think of the input terminals of a four-terminal coupling network as an equivalent voltage source and the output terminals as a Norton-equivalent current source. **We then describe the coupling network in terms of four hybrid parameters (h-parameters).**

To find the open-circuit voltage of the equivalent source at input terminals (port 1) in Figure 5(a), we feed V_2 into the output terminals (port 2). In this circuit, we consider the equivalent source to be a voltage-controlled voltage source. **The parameter that represents the fraction of the output voltage**

appearing at the input terminals is V_1/V_2 , which is a ratio without units. This parameter is the open-circuit reverse-voltage ratio, h_{12} .

Since we are treating the dependent source as a voltage-controlled voltage source, we short-circuit the output terminals while we measure the input voltage and current, as shown in Figure 5(b). The parameter h_{11} is V_1/I_1 , which is expressed in ohms and represents the short-circuit input impedance of the network. Since $h_{12}V_2$ is a voltage source, the equivalent input circuit for the coupling network shows the dependent voltage source and input impedance in series, as in Figure 5(c).

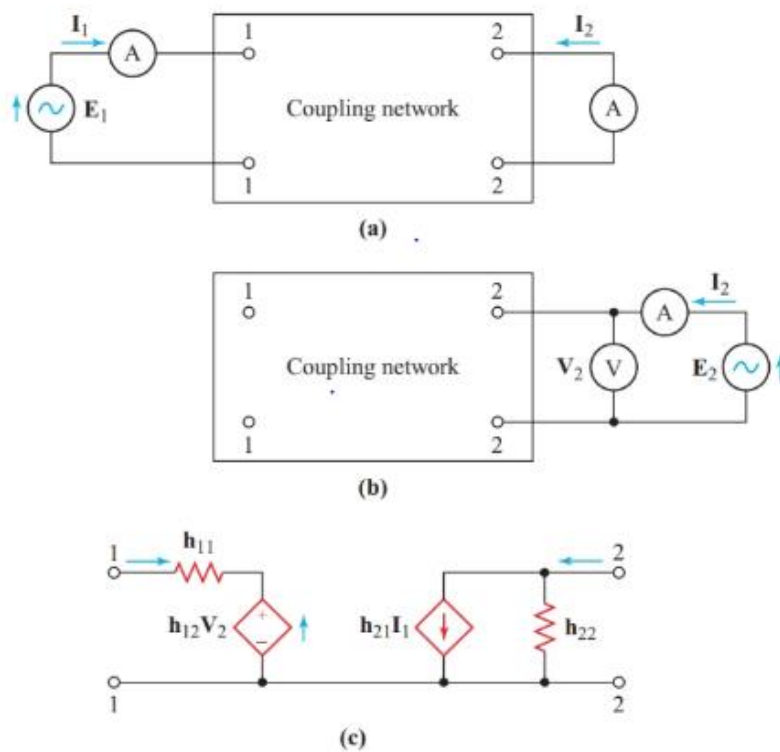


Figure 5: Figure 2 Finding the Norton-equivalent output circuit of a four-terminal network: (a) short-circuit forward current; (b) output admittance; (c) complete hybrid parameters.

To determine the short-circuit current of the Norton-equivalent source at the output terminals (port 2) in Figure 5(a), we feed I_1 into the input terminals and short-circuit the output terminals through the ammeter measuring I_2 . As long as the network impedances are linear (independent of voltage and current), I_2 will be a constant fraction of the input current I_1 . **The ratio I_2/I_1 is the short-circuit forward-current ratio, h_{21} .**

Short-circuit input impedance:

$$h_{11} = \frac{V_1}{I_1} \text{ (with } V_2=0) \quad (1)$$

Open-circuit reverse-voltage ratio:

$$h_{12} = \frac{V_1}{V_2} \text{ (with } I_1=0) \textit{ Open - Circuit} \quad (2)$$

Short-circuit forward-current ratio:

$$h_{21} = \frac{I_2}{I_1} \text{ (with } V_2=0) \textit{ Short - Circuit} \quad (3)$$

Open-circuit output admittance:

$$h_{22} = \frac{I_2}{V_2} \text{ (with } I_1=0) \quad (4)$$

The two unknowns in these equations are I_1 and V_2 .

$$h_{11}I_1 + h_{12}V_2 = E_1 \quad (5)$$

$$h_{21}I_1 + h_{22}V_2 = I_2 \quad (6)$$

The transistor amplifier equivalent circuit of Figure 6 is a typical example of hybrid parameters.

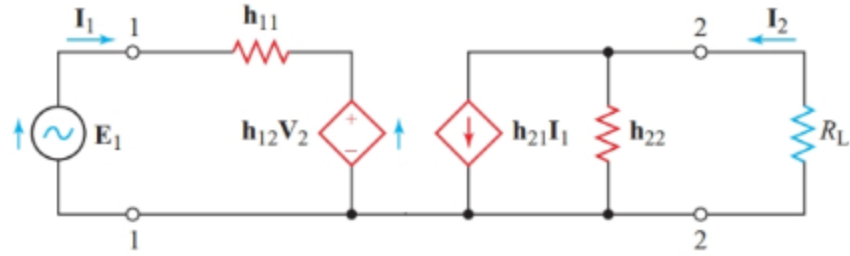


Figure 6: Hybrid parameters of a simple transistor amplifier.

3.3 Equivalent Circuit

Equivalent Circuit of transistor: An electric circuit made up of the basic elements resistance, inductance, and capacitance in a simple arrangement such that its performance would duplicate that of a more complicated circuit or network

A network of voltage sources, current sources, and resistors can be replaced by an equivalent circuit which has identical terminal properties (I-V characteristics) without affecting the operation of the rest of the circuit.

Let us identify a pair of nodes, say node a and b, such that the circuit can be partitioned into two parts as shown in figure 7.

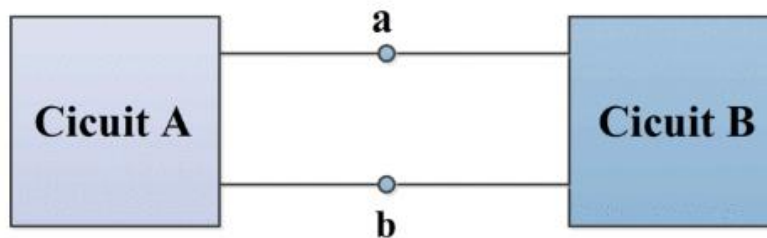


Figure.7: Circuit partitioned into two parts

Furthermore, suppose that circuit A contains no dependent source that is dependent on a variable in circuit B and vice versa. Then, we can model circuit A by an appropriate independent voltage source, call it V_{oc} that is connected in series with an appropriate resistance, call it R_{TH} . This series combination of a voltage source and a resistance is called the equivalent of circuit A. in other words, **circuit A in figure 7 and the circuit in the shaded box in figure 8 have the same effect on circuit B. Circuit B (which is often called a load) may consist of many circuit elements, a single element (a load resistor), or no element.**

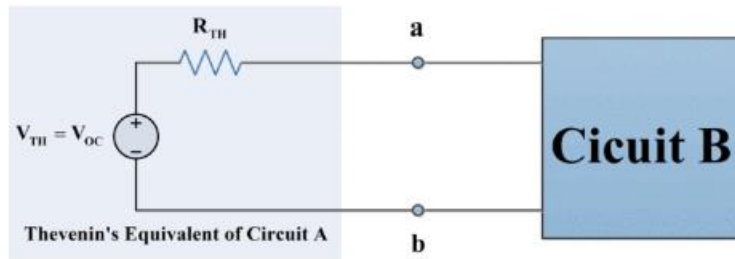


Figure.8: Equivalent Circuit

3.4 References

Electronics principles (fourth edition) by Malvino.