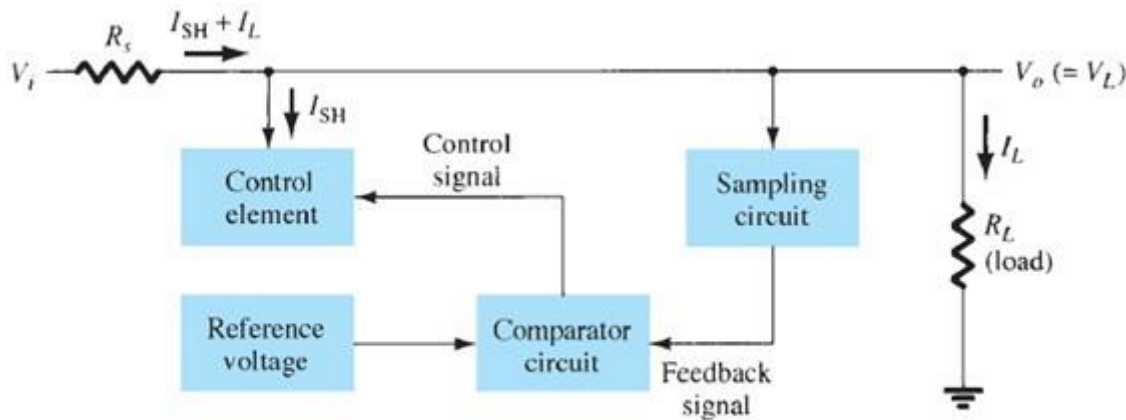





**A shunt voltage regulator** provides regulation by shunting current away from the load to regulate the output voltage. Figure below shows the block diagram of such a voltage regulator. The input unregulated voltage provides current to the load. Some of the current is pulled away by the control element to maintain the regulated output voltage across the load.



Block diagram of shunt voltage regulator.


**Basic Transistor Shunt Regulator** A basic shunt regulator circuit is shown in Fig. below. Resistor  $R_s$  drops the unregulated voltage by an amount that depends on the current supplied to the load  $R_L$ . The voltage across the load is set by the Zener diode and transistor base-emitter voltage. If the load resistance decreases, a reduced drive current to the base of  $Q_1$  results, shunting less collector current. The load current is thus larger, thereby maintaining the regulated voltage across the load. The output voltage to the load is

$$V_o = V_{in} - IR_s$$

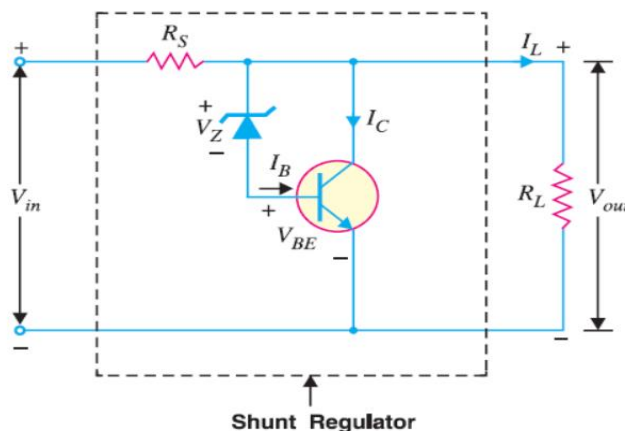



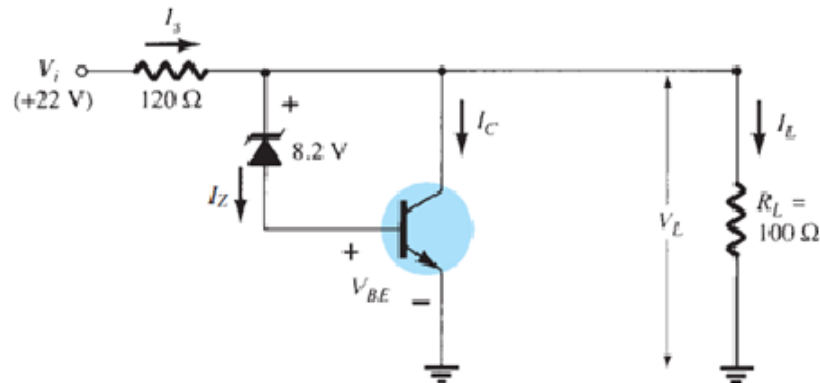**EXAMPLE** Determine the regulated voltage and circuit currents for the shunt regulator of Fig.



**Solution:** The load voltage is

$$V_L = 8.2 \text{ V} + 0.7 \text{ V} = 8.9 \text{ V}$$

For the given load,

$$I_L = \frac{V_L}{R_L} = \frac{8.9 \text{ V}}{100 \Omega} = 89 \text{ mA}$$

With the unregulated input voltage at 22 V, the current through  $R_S$  is

$$I_S = \frac{V_i - V_L}{R_S} = \frac{22 \text{ V} - 8.9 \text{ V}}{120} = 109 \text{ mA}$$


so that the collector current is

$$I_C = I_S - I_L = 109 \text{ mA} - 89 \text{ mA} = 20 \text{ mA}$$





**Shunt Voltage Regulator Using Op-Amp** Figure shows another version of a shunt voltage regulator using an op-amp as voltage comparator. The Zener voltage is compared to the feedback voltage obtained from voltage divider  $R_1$  and  $R_2$  to provide the control drive current to shunt element  $Q_1$ . The current through resistor  $R_S$  is thus controlled to drop a voltage across  $R_S$  so that the output voltage is maintained.

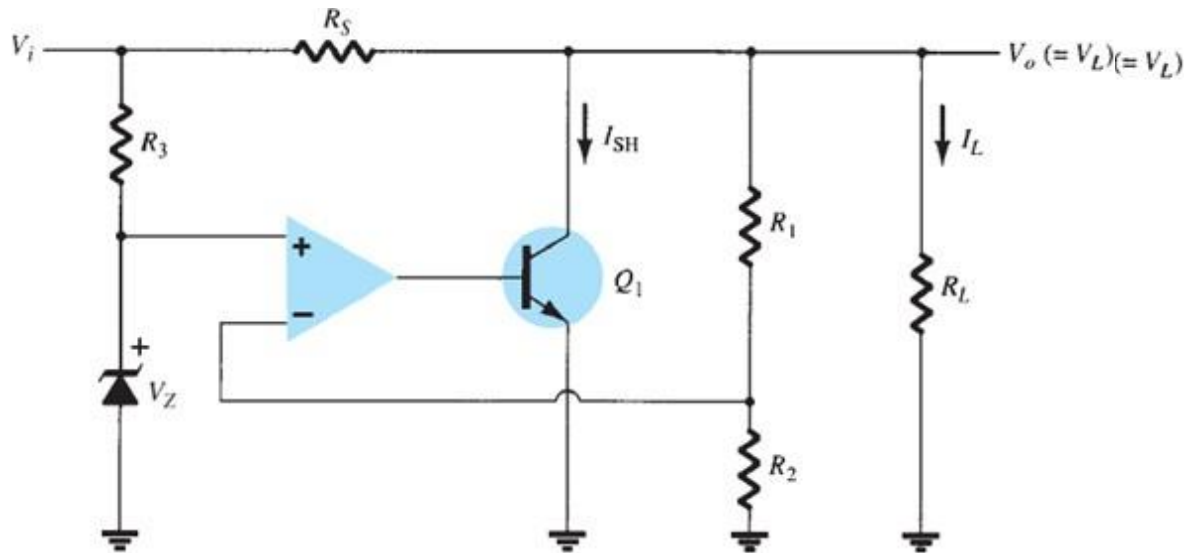

*Shunt voltage regulator using an op-amp.*

### H.W.

What is the output voltage of the Shunt Voltage Regulator Using Op-Amp ( $V_o = ?$ )