



Ministry of Higher Education

and Scientific Research

Al- Mustaqbal University College

Department of Medical Instrumentation Techniques Engineering

تكنولوجيا الكهرباء

Electrical Technology

Lecture 6

Lecture Name: TRANSFORMER


By

Dr. Jaber Ghaib Talib



Equivalent Circuit of Transformer

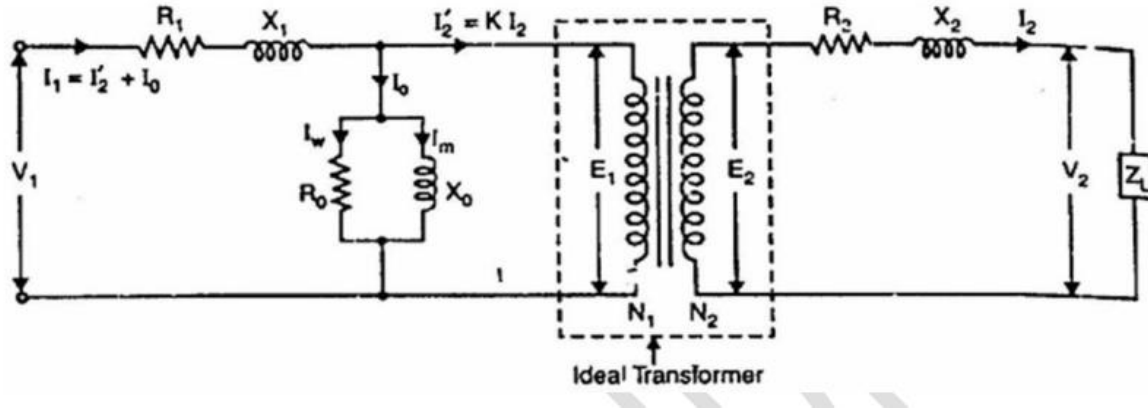(The equivalent circuit of transformer is shown in the figure)



Where:

R1: primary winding resistance

R2: secondary winding resistance

X1: leakage reactance of primary winding

X2: leakage reactance of the secondary winding

R0: represents the core losses (hysteresis and eddy current losses)

X0: represents magnetizing reactance of the core

Im: magnetizing current (to create magnetic flux in the core)

Iw: active current (required to supply the core losses)

I0 = no load primary current

NOTE1: Parallel circuit R0 - X0 is the no-load equivalent circuit of the transformer or called exciting circuit

No load Components



The no-load primary current I_0 has two components, namely I_m and I_w .

Where $I_m =$ magnetizing component $= I_0 \sin \phi_0$
and $I_w =$ core-loss component $= I_0 \cos \phi_0$.

I_w supplies for the no-load losses and is assumed to flow through the no-load resistance which is also known as core-loss resistance (R_0).

The magnetizing component, I_m is assumed to be flowing through a reactance which is known as magnetizing reactance, X_0 .

The parallel combination of R_0 and X_0 is also known as the exciting circuit.

From the equivalent circuit of transformer,

$$R_0 = V_1/I_w \text{ and } X_0 = V_1/I_m.$$

NOTE2:

The equivalent circuit has created two normal electrical circuits separated only by an ideal transformer whose function is to change values according to the equation:

$$\frac{E_2}{E_1} = \frac{N_2}{N_1} = \frac{I'_2}{I_2}$$

NOTE3:



If Z_L is the external load across the secondary circuit, voltage E_2 induced in the secondary by mutual flux will produce a secondary current I_2 , hence

$$V_2 = E_2 - I_2(R_2 + jX_2) = E_2 - I_2Z_2$$

Similarly supply voltage can be given as:

$$V_1 = -E_1 + I_1(R_1 + jX_1) = -E_1 + I_1Z_1$$

NOTE4:


When the transformer is loaded to carry the secondary current I_2 , the primary current consists of two components: ► I_0 to provide magnetizing current and the current required to supply the core losses.

► primary current $I'_2 (= K I_2)$ required to supply the load connected to the secondary





Simplified Equivalent Circuit of a Loaded Transformer (حفظ)

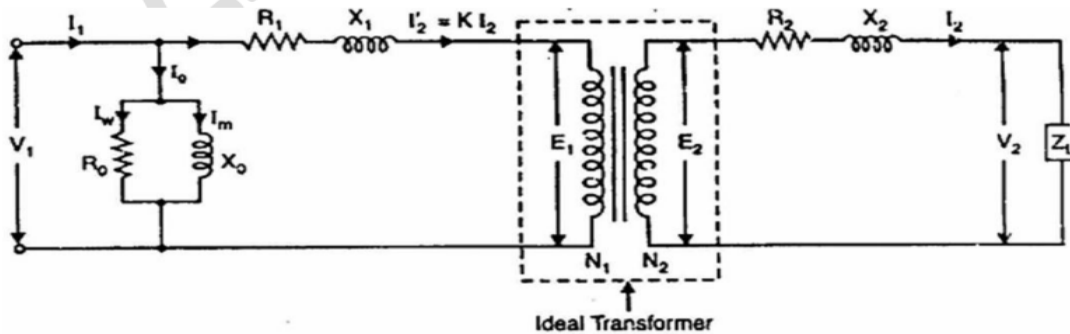If I_0 of a transformer is small as compared to the rated primary current I_1 , voltage drops in R_1 and X_1 due to I_0 are negligible. Hence, the exact equivalent circuit can be simplified by transferring the shunt circuit $R_0 - X_0$ to the input terminals as shown below:



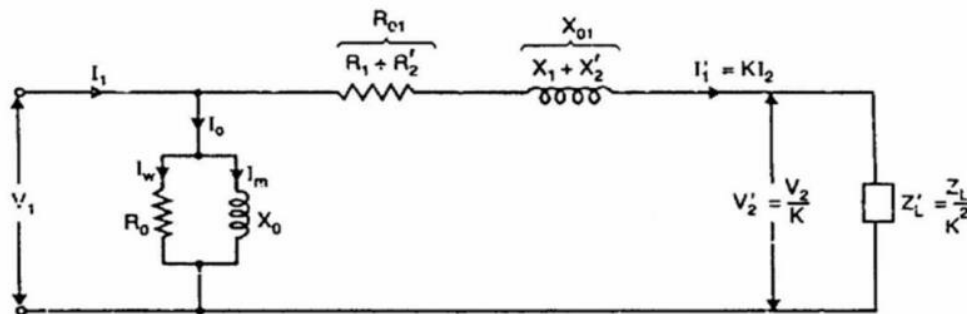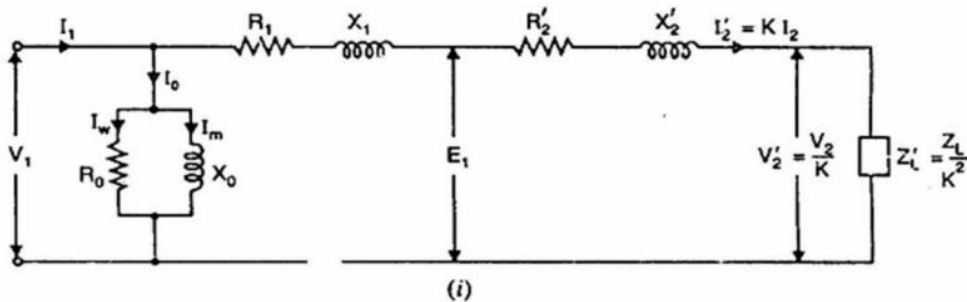If all the secondary quantities are referred to the primary, we can get the **simplified equivalent circuit of the transformer referred to the primary** as shown below (حفظ)





Exp: A transformer has 1200 primary turns and 200 secondary turns. The primary and secondary resistances are 0.2Ω and 0.02Ω respectively and the corresponding leakage reactance are 1.2Ω and 0.05Ω respectively. Calculate (a) the equivalent resistance, reactance and impedance referred to the primary winding, and (b) the phase angle of the impedance

$$(a) \text{ Equivalent resistance, } R_e = R_1 + R_2 \left(\frac{V_1}{V_2} \right)^2 = 0.2 + 0.02 \left(\frac{1200}{200} \right)^2 = \mathbf{0.92 \Omega}$$

$$\text{Equivalent reactance, } X_e = X_1 + X_2 \left(\frac{V_1}{V_2} \right)^2 = 1.2 + 0.05 \left(\frac{1200}{200} \right)^2 = \mathbf{3.0 \Omega}$$

$$\text{Equivalent impedance, } Z_e = \sqrt{R_e^2 + X_e^2} = \sqrt{0.92^2 + 3.0^2} = \mathbf{3.138 \Omega \text{ or } 3.14}$$

Ω

$$(b) \cos \phi_e = \frac{R_e}{Z_e} = \frac{0.92}{3.138} \quad \text{and} \quad \text{phase angle of impedance, } \phi_e = \cos^{-1} \left(\frac{0.92}{3.138} \right) =$$

72.95°