



Ministry of Higher Education

and Scientific Research

Al- Mustaqbal University College

Department of Medical Instrumentation Techniques Engineering

تكنولوجيا الكهرباء

Electrical Technology

Lecture 5

Lecture Name: TRANSFORMER

By


Dr. Jaber Ghaib Talib


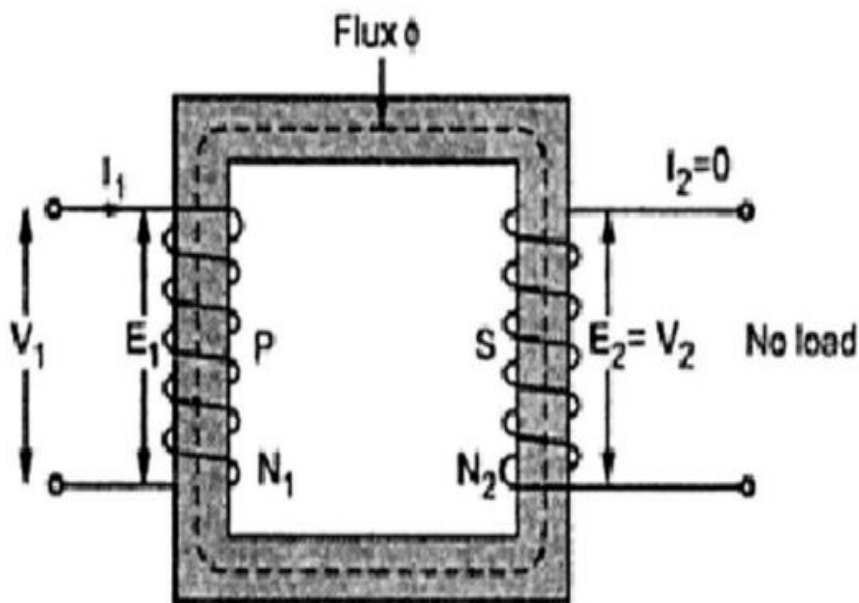
## Ideal Transformer on No Load


For no load  $I_2 = 0$ .  $I_1$  is just necessary to produce flux in the core, which is called magnetizing current denoted as  $I_m$ .

$I_m$  is very small Hence  $E_1$  and  $E_2$  are in antiphase with  $V_1$  but equal in magnitude and  $E_1$  and  $E_2$  are in phase.





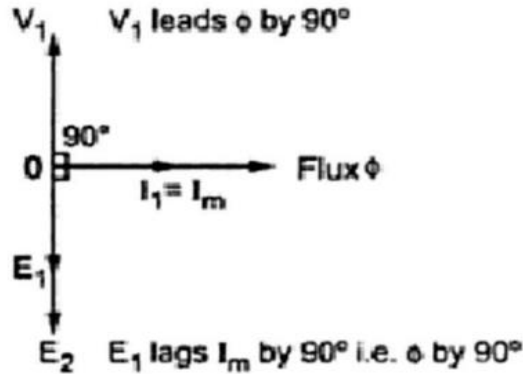
This can be illustrated in the phase diagram as shown below:



### Phasor diagram for ideal transformer on no load
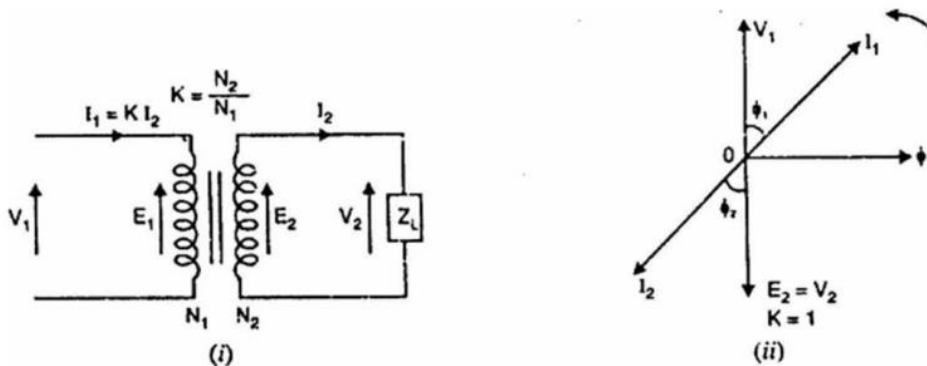
### Ideal Transformer on Load

Let us connect a load  $Z_L$  across the secondary of an ideal transformer as shown in Figure below: The secondary emf  $E_2$  will cause a current  $I_2$  to flow through the load:






$$I_2 = \frac{E_2}{Z_L} = \frac{V_2}{Z_L}$$

## **PRACTICAL TRANSFORMER**


**A differs from the ideal transformer in many respects. The practical transformer has**

- (i) iron losses**
  - (ii) winding resistances and**
  - (iii) magnetic leakage, giving rise to leakage reactance.**
- (i) Iron losses. Since the iron core is subjected to alternating flux, there occurs eddy current and hysteresis loss in it.**
- (ii) Winding resistances. Since the windings consist of copper conductors, it immediately follows that both primary and secondary will have winding resistance.**

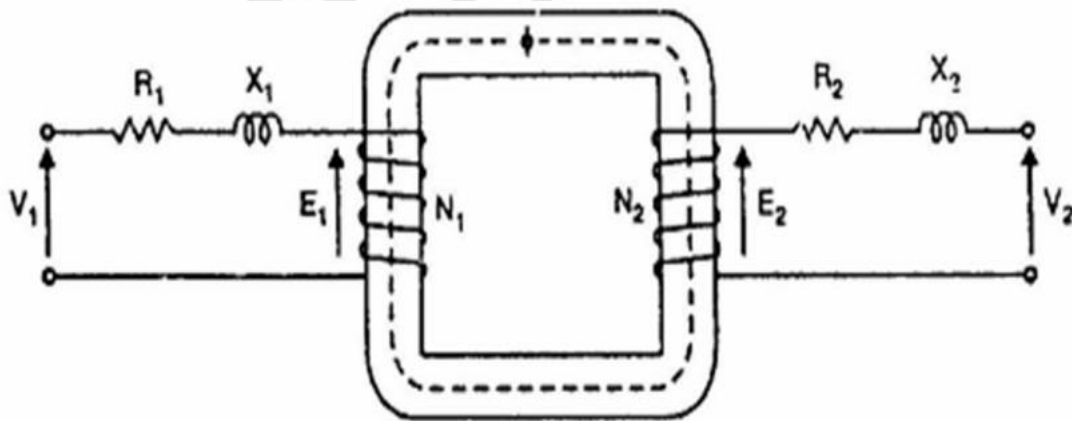**The primary resistance R1 and secondary resistance R2 act in series with the respective windings as shown below:**




(iii) **Leakage reactance.** Both primary and secondary currents produce flux. The flux  $\Phi$  which links both the windings is the useful flux. However, primary current would produce some flux  $\Phi$  which would not link the secondary winding and is called mutual flux.

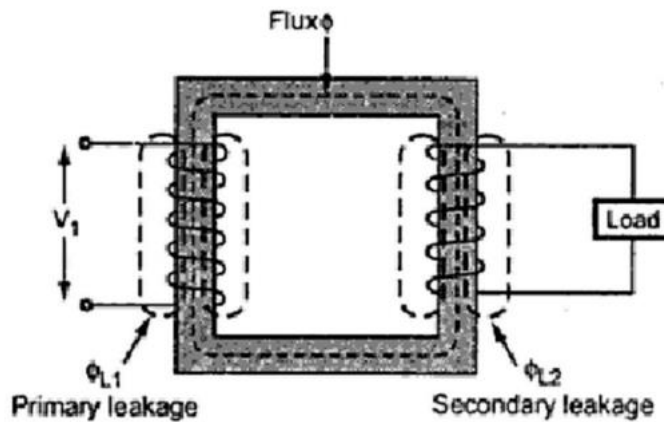

**Figure : Leakage reactance**

### Practical Transformer on No Load

Consider the figure below:

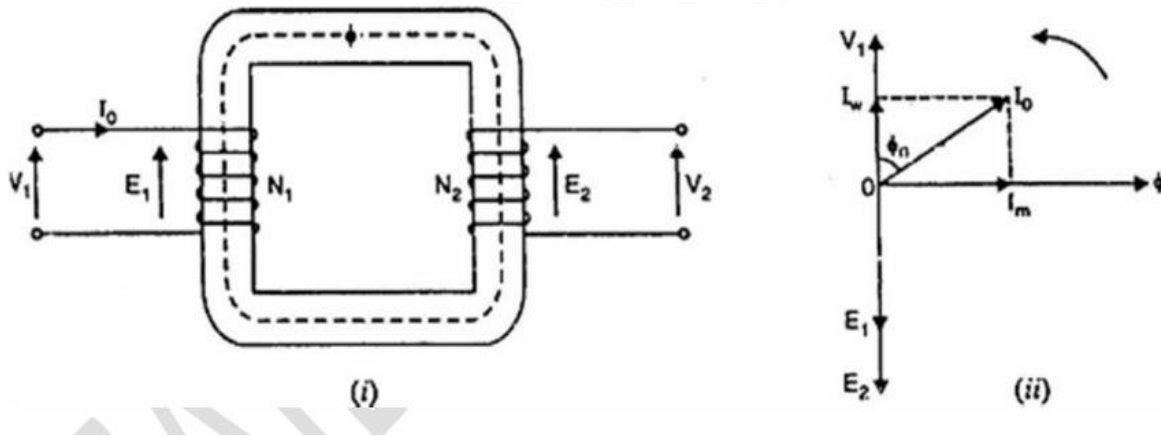

The primary will draw a small current  $I_0$  to supply (i) the iron losses and (ii) a very small amount of copper loss in the primary.

The no-load primary current  $I_0$  can be resolved into two rectangular components:

- (i) The component  $I_w$  in phase with the applied voltage  $V_1$ . This is known as active or working or iron loss component and supplies the iron loss and a very small primary copper loss.

$$I_w = I_0 \cos \phi_0$$

- (ii) The component  $I_m$  lagging behind  $V_1$  by  $90^\circ$  and is known as magnetizing component. It is this component which produces the mutual flux  $\phi$  in the core.

$$I_m = I_0 \sin \phi_0$$

Clearly,  $I_0$  is phasor sum of  $I_m$  and  $I_w$ ,

$$\therefore I_0 = \sqrt{I_m^2 + I_w^2}$$

No load p.f.,  $\cos \phi_0 = \frac{I_w}{I_0}$



## Summary

Working component  $I_w = I_0 \cos \phi_0$

No load current  $I_0 = \sqrt{I_w^2 + I_m^2}$

Magnetizing component  $I_m = I_0 \sin \phi_0$

Power factor  $\cos \phi_0 = \frac{I_w}{I_0}$

No load power input  $P_0 = V_1 I_0 \cos \phi_0$

### Exp.

**A 3300 V/440 V, single-phase transformer takes a no-load current of 0.8 A and the iron loss is 500 W. Draw the no-load phasor diagram and determine the values of the magnetizing and core loss components of the no-load current.**


$$V_1 = 3300 \text{ V}, \quad V_2 = 440 \text{ V} \quad \text{and} \quad I_0 = 0.8 \text{ A}$$

$$\text{Core or iron loss} = 500 = V_1 I_0 \cos \phi_0 \quad \text{i.e.} \quad 500 = (3300)(0.8) \cos \phi_0$$



from which,  $\cos \phi_o = \frac{500}{(3300)(0.8)} = 0.1894$  and  $\phi_o = \cos^{-1} 0.1894 = 79.08^\circ$

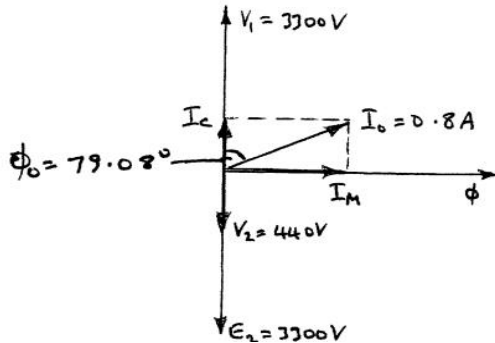The no-load phasor diagram is shown below.




**Magnetizing component,  $I_M = I_o \sin \phi_o = 0.8 \sin 79.08^\circ = 0.786 \text{ A}$**

**Core loss component,  $I_C = I_o \cos \phi_o = 0.8(0.1894) = 0.152 \text{ A}$**

### Practical Transformer on Load

We shall consider two cases (i) when such a transformer is assumed to have no winding resistance and leakage flux (ii) when the transformer has winding resistance and leakage flux.
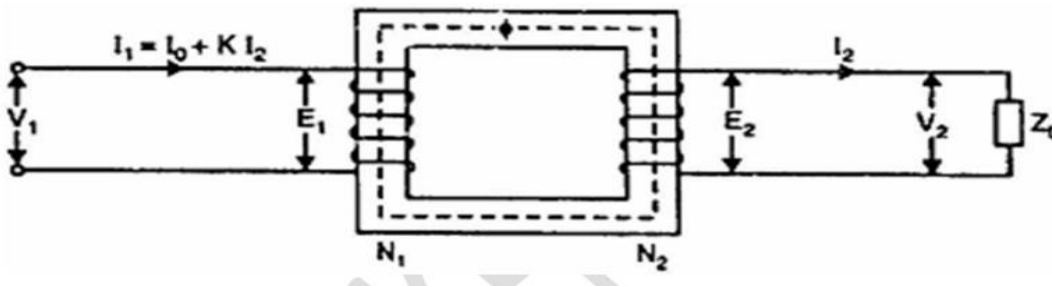
#### **No winding resistance and leakage flux**







From Figure above shows a practical transformer with the assumption that resistances and leakage reactance's of the windings are negligible. With this assumption,  $V_2 = E_2$  and  $V_1 = E_1$ .

Let us take the usual case of inductive load which causes the  $I_2$  to lag  $V_2$  by  $\Phi_2$ .

The total primary current  $I_1$  must meet two requirements:

- It must supply the no-load current  $I_0$  to meet the iron losses in the transformer and to provide flux in the core.
- It must supply a current  $I'_2$  to counteract the demagnetizing effect of secondary current  $I_2$ . The magnitude of  $I'_2$  will be such that:

$$N_1 I'_2 = N_2 I_2$$

or 
$$I'_2 = \frac{N_2}{N_1} I_2 = K I_2$$

The total primary current  $I_1$  is the phasor sum of  $I'_2$  and  $I_0$  i.e.,


$$I_1 = I'_2 + I_0$$

where 
$$I'_2 = -K I_2$$

Note that  $I'_2$  is  $180^\circ$  out of phase with  $I_2$ .
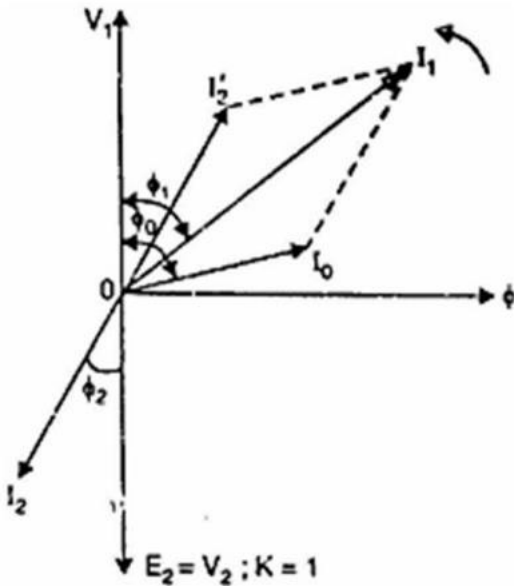
### Phasor Diagram:

Both  $E_1$  and  $E_2$  lag behind the mutual flux  $\Phi$  by  $90^\circ$ . The current  $I'_2$  represents the primary current to neutralize the demagnetizing effect of secondary current  $I_2$ . Now  $I'_2 = K I_2$  and is antiphase with  $I_2$ .  $I_0$  is the no-load current of the transformer. The phasor sum of  $I'_2$  and  $I_0$  gives the total primary current  $I_1$ . Note that in drawing the phasor diagram, the value of  $K$  is assumed to be unity so that primary phasors are equal to secondary phasors.




**Transformer with resistance and leakage reactance The total primary current  $I_1$  must meet two requirements:**

- It must supply the no-load current  $I_0$  to meet the iron losses in the transformer and to provide flux in the core.
- It must supply a current  $I'_2$  to counteract the demagnetizing effect of secondary current  $I_2$ . The magnitude of  $I'_2$  will be such that:

$$N_1 I'_2 = N_2 I_2$$

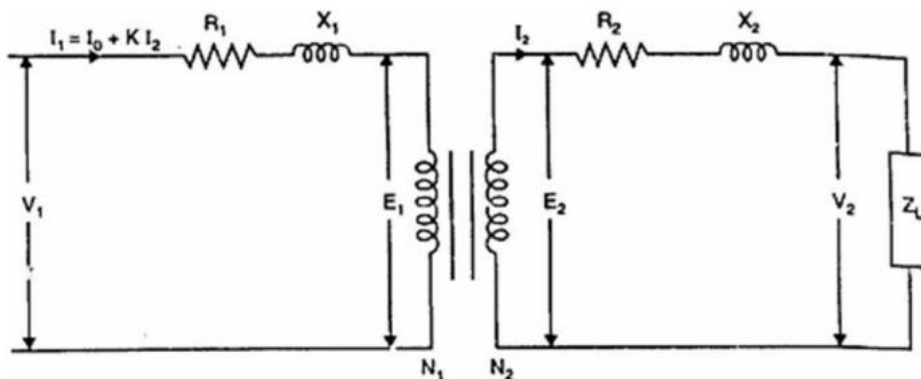or 
$$I'_2 = \frac{N_2}{N_1} I_2 = K I_2$$





The total primary current  $I_1$  will be the phasor sum of  $I'_2$  and  $I_0$  i.e.,

$$I_1 = I'_2 + I_0 \quad \text{where} \quad I'_2 = -KI_2$$

$$V_1 = -E_1 + I_1(R_1 + jX_1) \quad \text{where} \quad I_1 = I_0 + (-KI_2)$$
$$= -E_1 + I_1Z_1$$

$$V_2 = E_2 - I_2(R_2 + jX_2)$$
$$= E_2 - I_2Z_2$$

**Phasor Diagram** Note that counter emf that opposes the applied voltage  $V_1$  is  $-E_1$ . Therefore, if we add  $I_1R_1$  (in phase with  $I_1$ ) and  $I_1 X_1$  ( $90^\circ$  ahead of  $I_1$ ) to  $-E_1$ , we get the applied primary voltage  $V_1$ . The phasor  $E_2$  represents the induced emf in the secondary by the mutual flux. The secondary terminal voltage  $V_2$  will be what is left over after subtracting  $I_2R_2$  and  $I_2X_2$  from  $E_2$ .

