



LECTURE 5

Full-Wave Rectifier (FWR)

Analog Electronics

31.10.2022

By

Dr. Basim Al-Qargholi

Outline and Aim

After completing this lecture, you should be able to:

- Analyze the operation of a full-wave rectifier
- Describe how the diodes function in a rectifier
- Determine the average value of a full-wave rectified voltage
- Describe the Center-Tapped Full-Wave Rectifier
- Describe the effect of the Turns Ratio n on Full-Wave Output Voltage
- Determine the peak inverse voltage (PIV)

The Full-Wave Rectifier (FWR)

The result of full-wave rectification is a dc output voltage that pulsates every half-cycle of the input, as shown in Fig. 9.

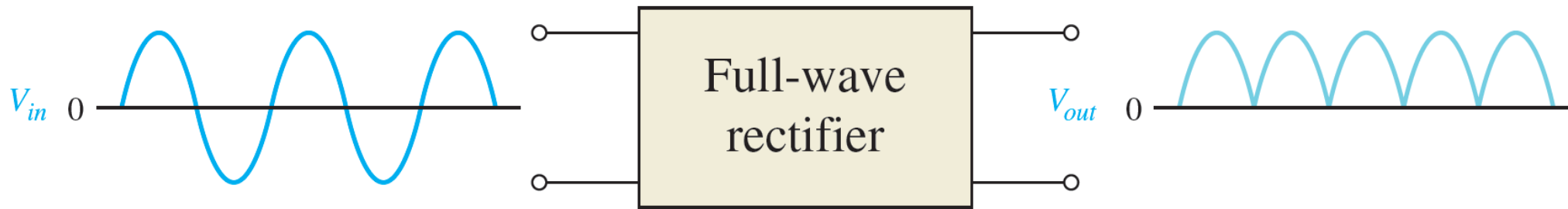


Fig. 9: Full-wave rectification

The average value for a full-wave rectified output voltage is twice that of the half-wave rectified output voltage, expressed as follows:

$$V_{AVG} = \frac{2V_{p(out)}}{\pi}$$

The Full-Wave Rectifier (FWR)

The **difference** between half-wave and full-wave rectification is that:

Half-wave rectifier:

Allows only one-half of the current to the load during the entire input cycle.

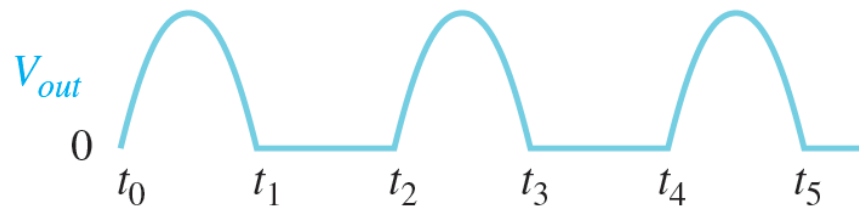


Fig. 10: Output of a half-wave rectifier

$$V_{AVG} = \frac{V_{p(out)}}{\pi}$$

Full-wave rectifier :

Allows unidirectional current to the load during the entire input cycle.

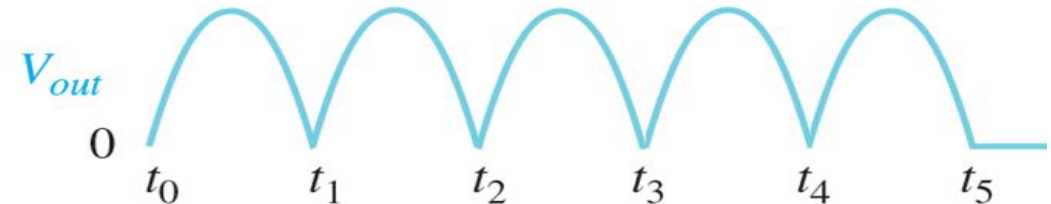


Fig. 11: Output of a full-wave rectifier

$$V_{AVG} = \frac{2V_{p(out)}}{\pi}$$

The Full-Wave Rectifier (FWR)

EXAMPLE 5:

Find the average value of the full-wave rectified output voltage in Fig. 12

Solution:

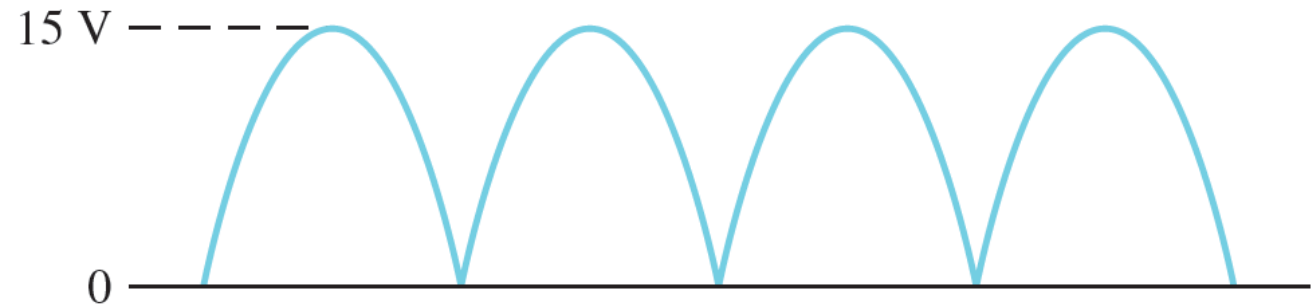



Fig. 12: Output of a half-wave rectifier

$$V_{AVG} = \frac{2V_{p(out)}}{\pi} = \frac{2*15}{3.14} = 9.55 V$$

The Full-Wave Rectifier (FWR)


1. Center-Tapped Full-Wave Rectifier

Fig. 13: Center-Tapped Full-Wave Rectifier

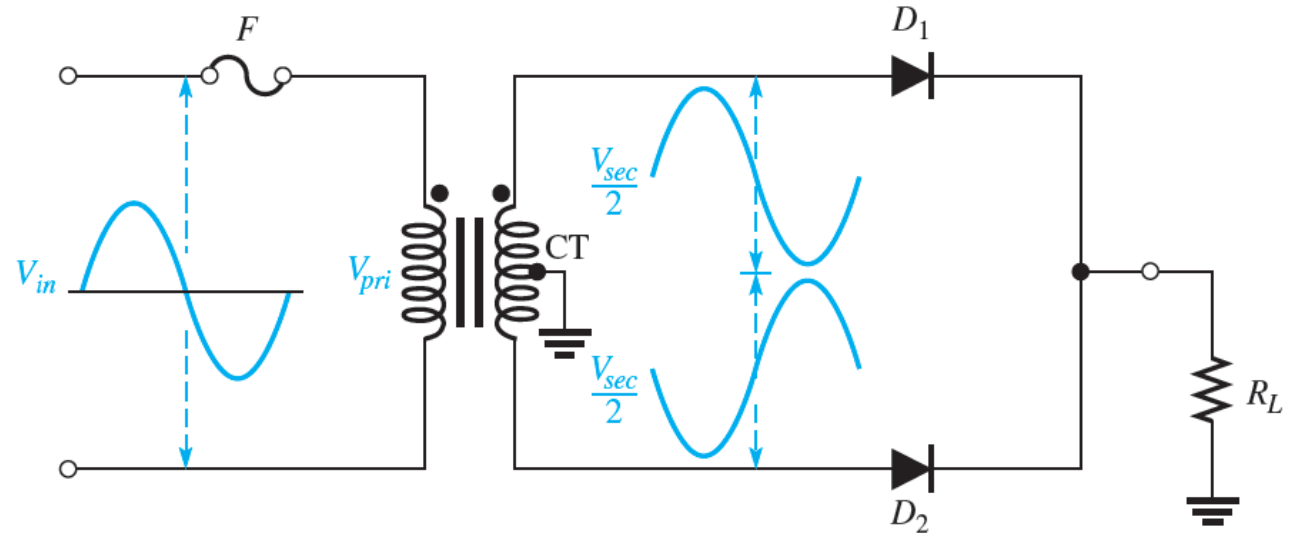

2. Full-Wave Bridge Rectifier

Fig. 14: Full-Wave Bridge Rectifier

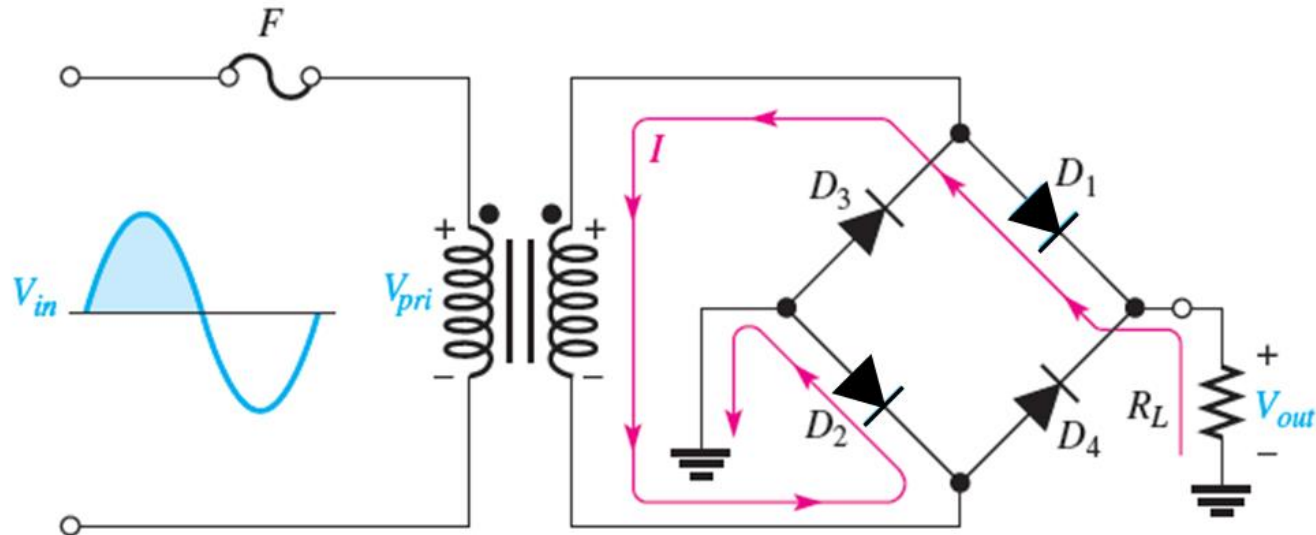

The Full-Wave Rectifier (FWR)

1. Center-Tapped Full-Wave Rectifier

- The center-tapped (CT) full-wave rectifier uses two diodes connected to the secondary of a center-tapped transformer.
- The input signal is coupled through the transformer to the secondary.
- Half of the secondary voltage appears between the center tap and each end of the secondary winding, as shown in Fig. 13.

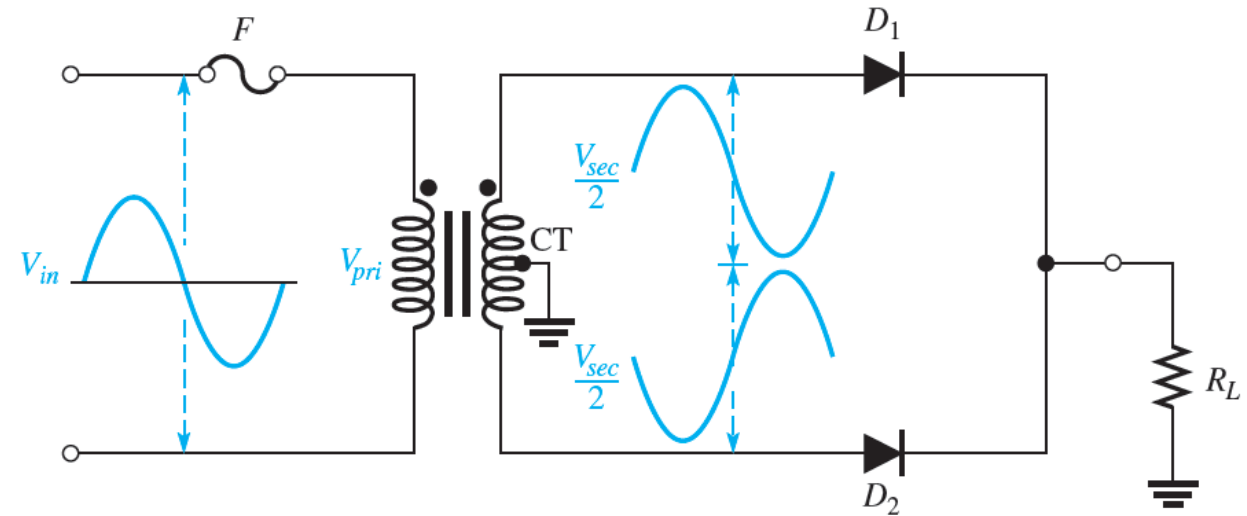


Fig. 13: Center-Tapped Full-Wave Rectifier

The Full-Wave Rectifier (FWR)

1. Center-Tapped Full-Wave Rectifier

For a **positive half-cycle** of the input voltage, the polarities of the secondary voltages are shown in Fig 15.

a) Forward-biases the upper diode D_1

b) Reverse-biases the lower diode D_2 .

The current path is through D_1 and the load resistor R_L , as indicated.

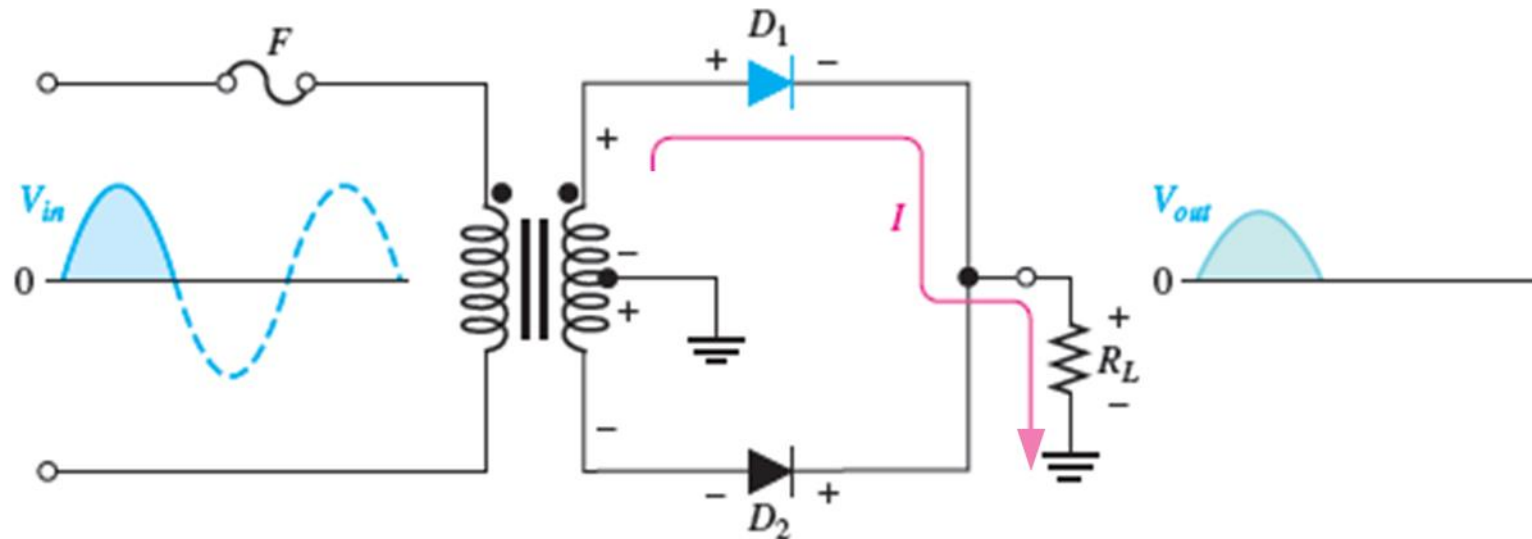


Fig. 15: During positive half-cycles, D_1 is forward-biased and D_2 is reverse-biased.

The Full-Wave Rectifier (FWR)

1. Center-Tapped Full-Wave Rectifier

For a **negative half-cycle** of the input voltage, the polarities of the secondary voltages are shown in Fig 15.

a) Forward-biases the lower diode D_2

b) Reverse-biases the upper diode D_1 .

The current path is through D_2 and the load resistor R_L , as indicated.

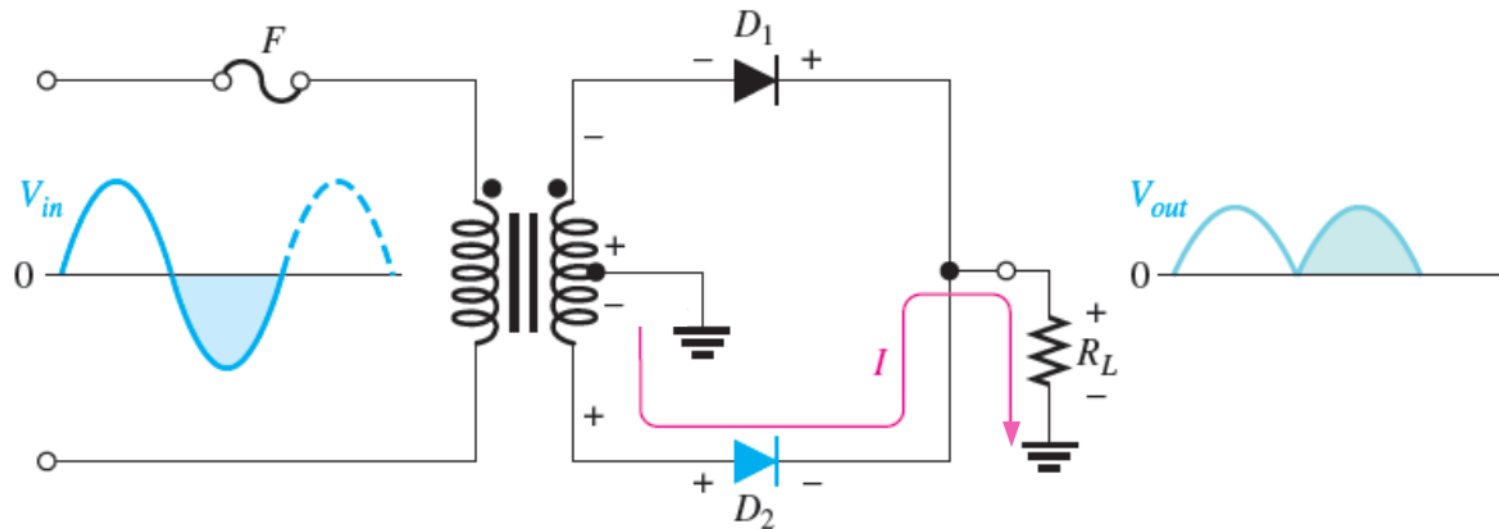


Fig. 15: During negative half-cycles, D_2 is forward-biased and D_1 is reverse-biased.

Center-Tapped Full-Wave Rectifier

Effect of the Turns Ratio n on Full-Wave Output Voltage:

- The output voltage is determined by the **turns ratio, n** , of the transformer.
- The peak output voltage is one-half the peak secondary voltage.

$$n = \frac{N_{sec}}{N_{pri}}$$

$$V_{p(out)} = \frac{nV_{p(in)}}{2}$$

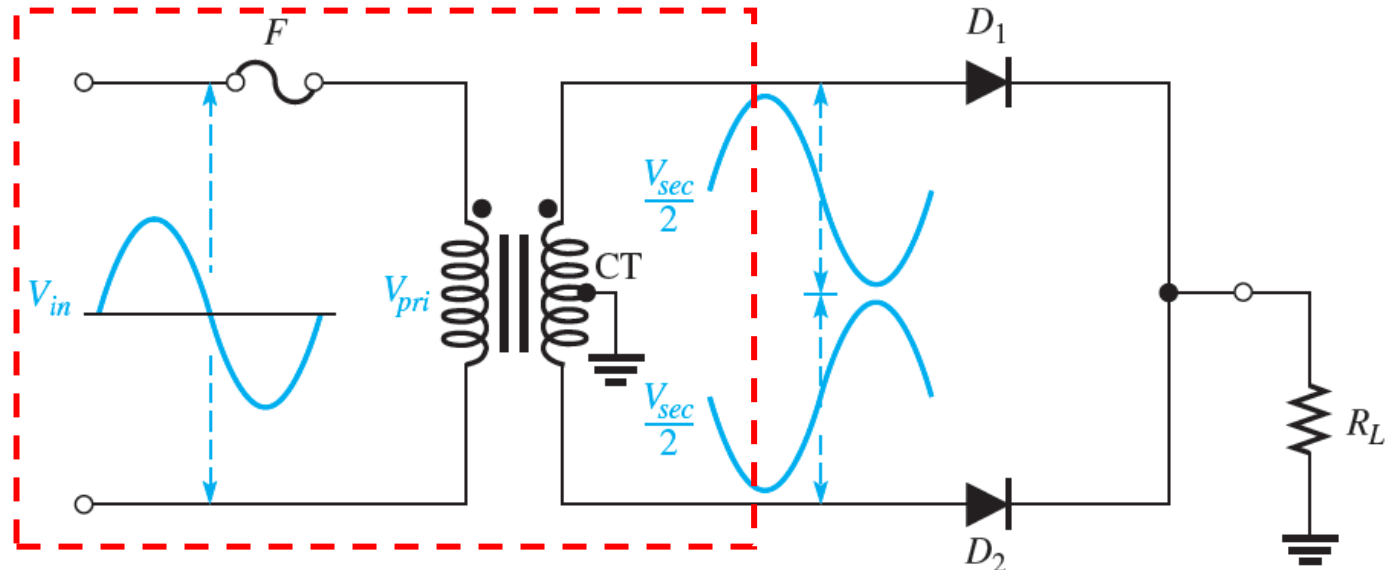


Fig. 16: Center-Tapped Full-Wave Rectifier

The primary voltage V_{pri} is the same as the input voltage V_{in} .

Center-Tapped Full-Wave Rectifier

Example 1: To obtain an output voltage $V_{p(out)}$ with a peak value approximately equal to the input peak $V_{p(in)}$, what would be the turn ratio n of a transformer?

Solution:

$$V_{p(out)} = \frac{nV_{p(in)}}{2}$$

$$n = \frac{2V_{p(out)}}{V_{p(in)}}$$

Since, $V_{p(out)}$ equal $V_{p(in)}$

$$n = 2$$

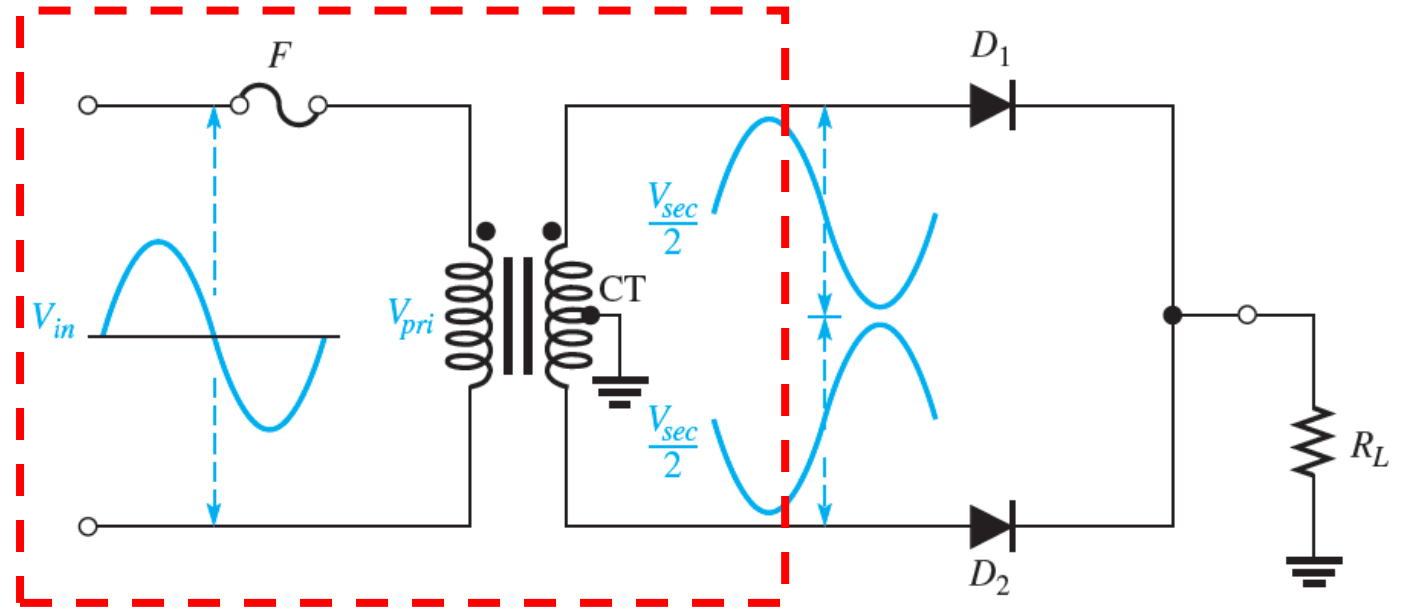


Fig. 16: Center-Tapped Full-Wave Rectifier

Center-Tapped Full-Wave Rectifier

Example2: Specify the turns ratio of a transformer required for a center-tapped full-wave rectifier if the input voltage is $220 \text{ V}_{\text{rms}}$ and the required output is 12 V peak?

Solution:

$$V_{p(in)} = \frac{V_{rms(in)}}{0.707}$$

$$V_{p(in)} = \frac{220 \text{ V}}{0.707} = 311 \text{ V}$$

$$n = \frac{2V_{p(out)}}{V_{p(in)}}$$

$$n = \frac{2 \times 12}{311} = 0.0771$$

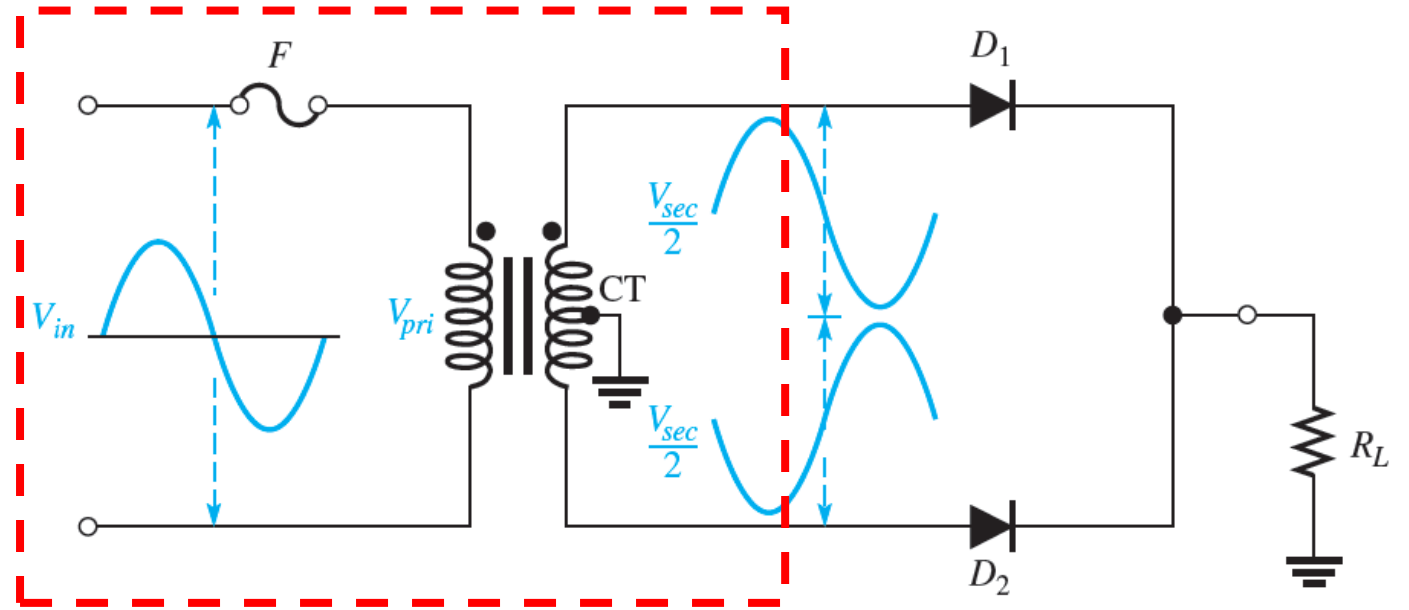


Fig. 16: Center-Tapped Full-Wave Rectifier

Center-Tapped Full-Wave Rectifier

Example 3: For a center-tapped full-wave rectifier if the input voltage is $220 \text{ V}_{\text{rms}}$, What is the peak output if the turns ratio is 0.15?

Solution:

$$V_{p(in)} = \frac{V_{rms(in)}}{0.707}$$

$$V_{p(in)} = \frac{220 \text{ V}}{0.707} = 311 \text{ V}$$

$$V_{p(out)} = \frac{nV_{p(in)}}{2}$$

$$V_{p(out)} = \frac{0.15 \times 311}{2} = 23.3 \text{ V}$$

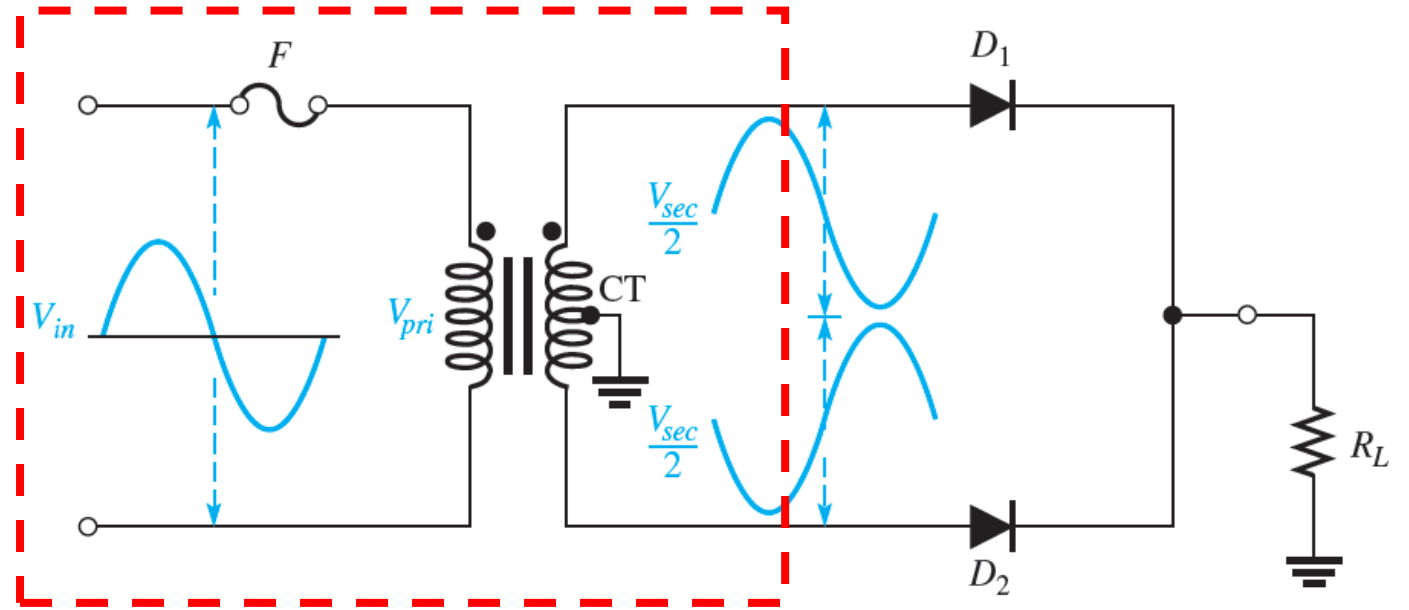


Fig. 16: Center-Tapped Full-Wave Rectifier

Center-Tapped Full-Wave Rectifier

Peak Inverse Voltage (PIV)

Each diode in the FWR is alternately forward-biased and then reverse-biased.

The maximum reverse voltage V_R that each diode must withstand is the peak value of the total secondary voltage $V_{p(sec)}$.

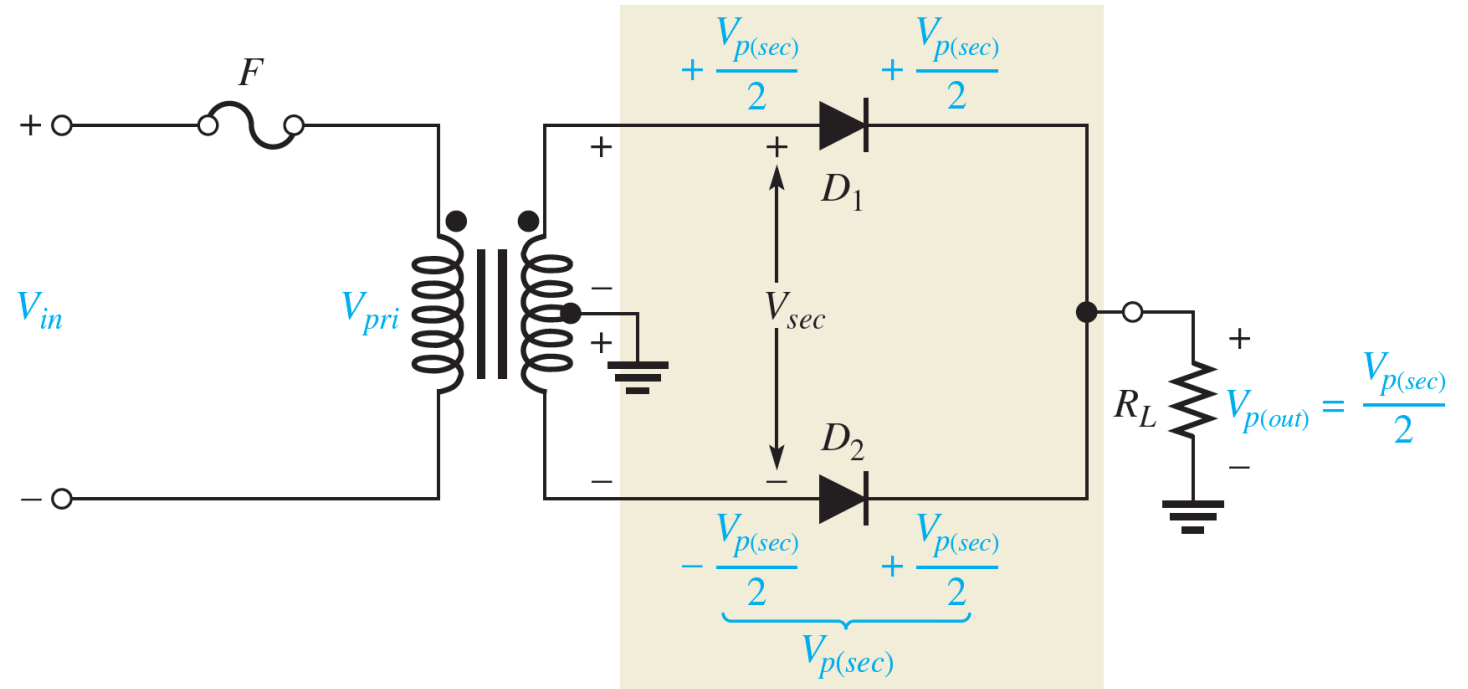


Fig. 17: Center-Tapped Full-Wave Rectifier showing the Peak Inverse Voltage PIV

Center-Tapped Full-Wave Rectifier

Peak Inverse Voltage (PIV)

When the total secondary voltage has the polarity shown in Fig. 17,

The anode of D_1 is $+\frac{V_{p(sec)}}{2}$ Which is equal to the cathode voltage

The anode of D_2 is $-\frac{V_{p(sec)}}{2}$

$$V_{D2} = \frac{V_{p(sec)}}{2} - \frac{-V_{p(sec)}}{2}$$

$$V_{D2} = V_{p(sec)}$$

$$PIV = V_{p(sec)}$$

$$PIV = 2V_{p(out)}$$

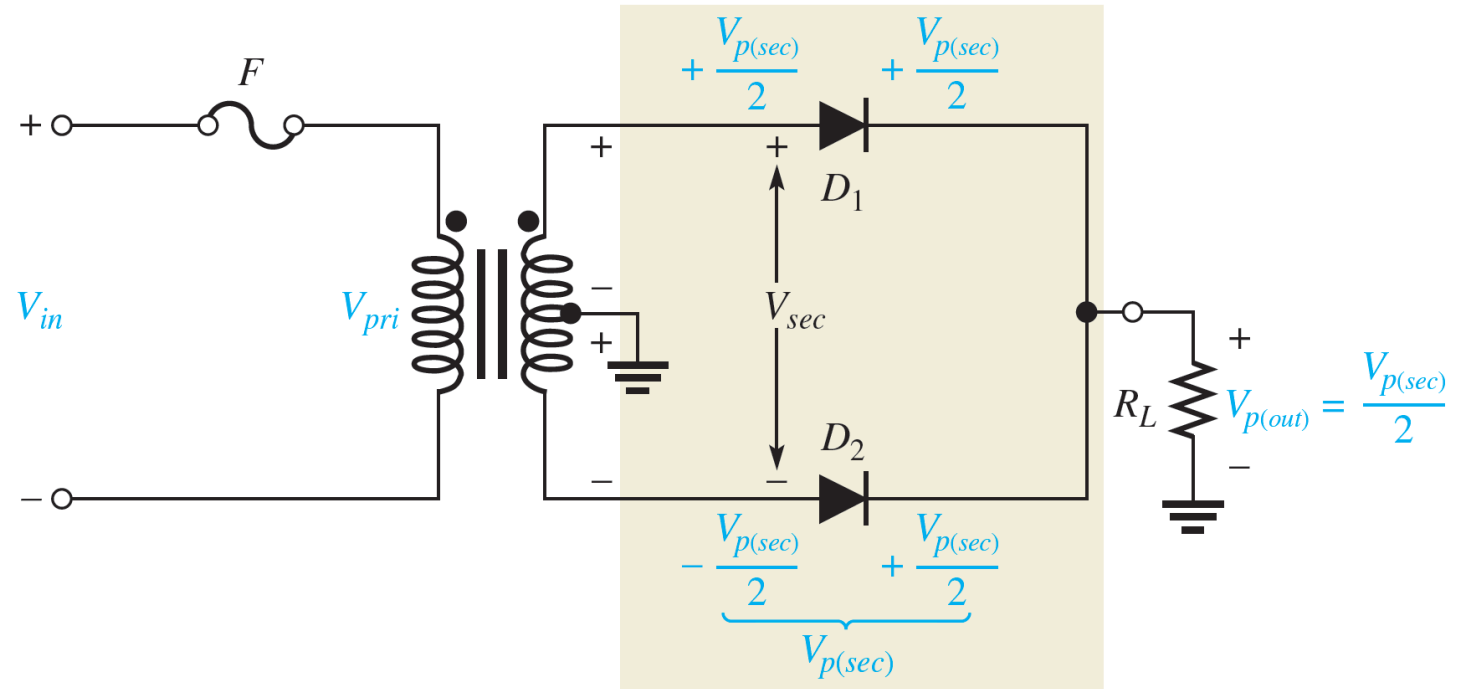


Fig. 17: Center-Tapped Full-Wave Rectifier showing the Peak Inverse Voltage PIV

Center-Tapped Full-Wave Rectifier

Example 4:

- For **ideal diodes**, show the voltage waveforms across the secondary winding and R_L when a 120 V_{rms} sine wave is applied to the primary winding in Fig. 18.
- What minimum PIV rating must the diodes have?

Solution:

$$a) V_{p(pri)} = \frac{V_{rms}}{0.707} = 169.7\text{ V}$$

$$V_{p(sec)} = nV_{p(pri)}$$

$$V_{p(sec)} = 2V_{p(pri)} = 2 \times 169.7$$

$$= 339.4\text{ V}$$

$$V_{p(RL)} = \frac{V_{p(sec)}}{2} = \frac{339.4}{2} = 169.7\text{ V}$$


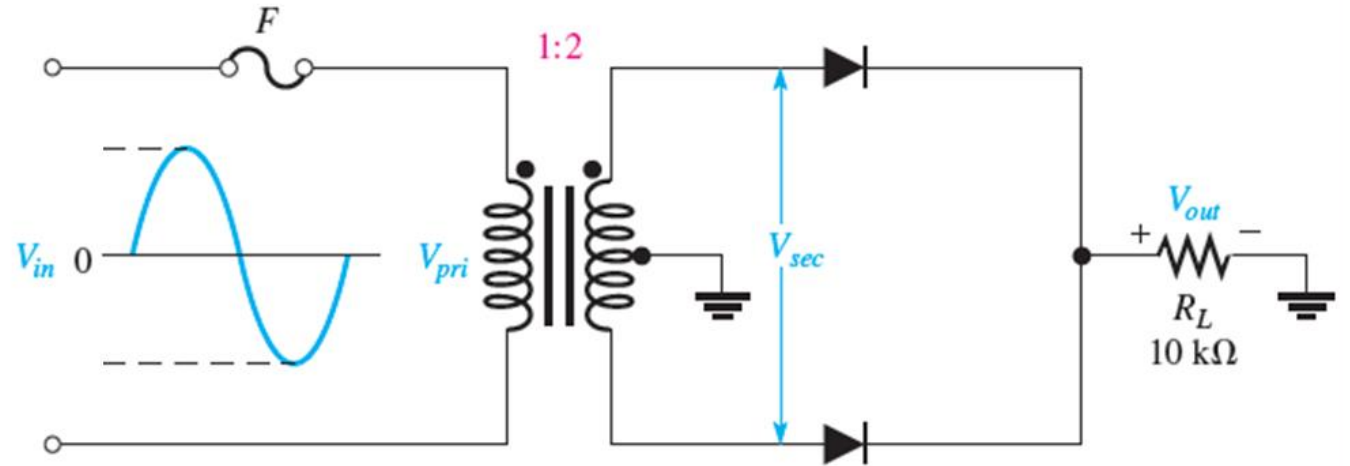



Fig. 18: Center-Tapped Full-Wave Rectifier

Center-Tapped Full-Wave Rectifier

Complement example 4:

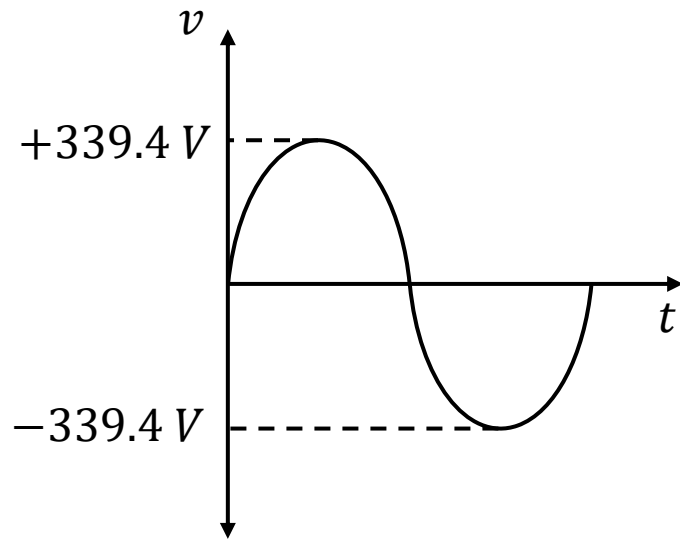

Waveforms across the secondary winding

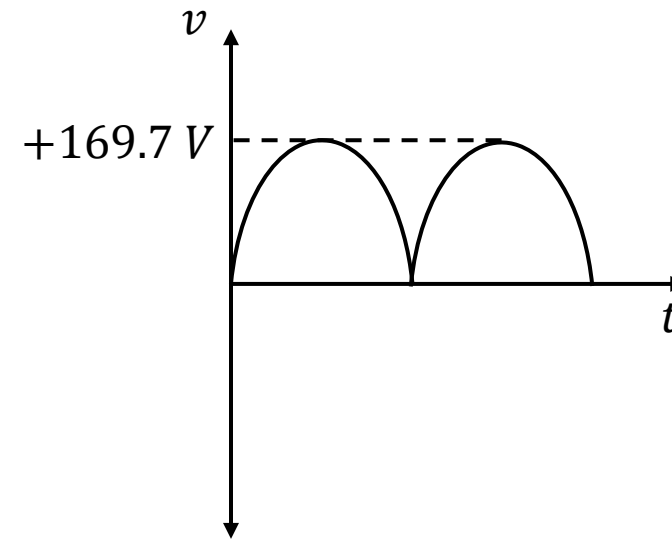

Waveforms across the R_L

$$b) PIV = V_{p(sec)} = 339.4 V$$

Center-Tapped Full-Wave Rectifier

Example 5:

- For the **diodes**, show the voltage waveforms across the secondary winding and R_L when a 120 V_{rms} sine wave is applied to the primary winding in Fig. 18.
- What minimum PIV rating must the diodes have?

Exercises

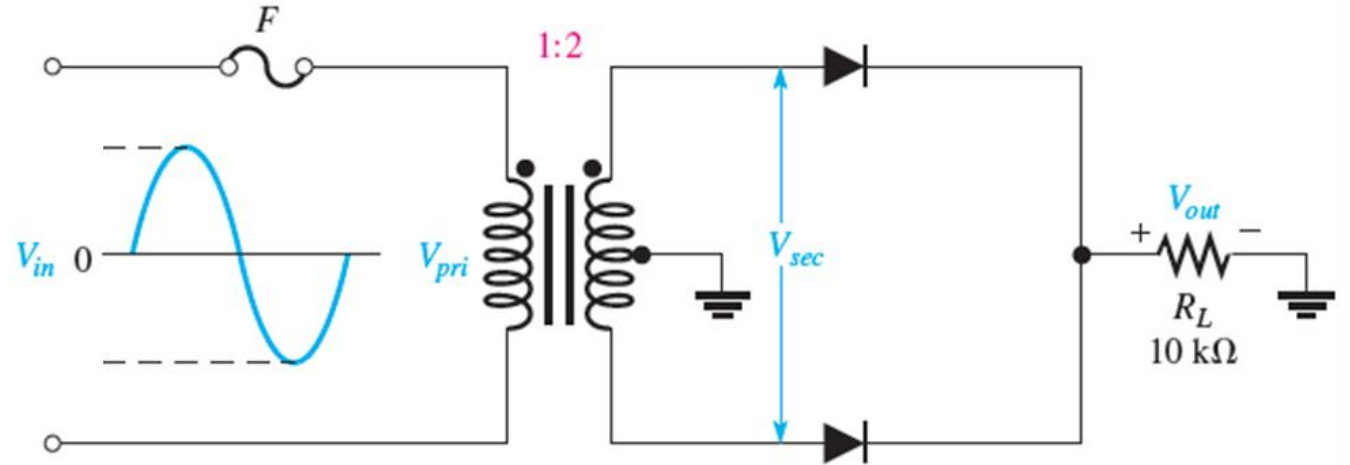


Fig. 18: Center-Tapped Full-Wave Rectifier