



# LECTURE 6

## Full-Wave Rectifier (FWR)

**Analog Electronics**

**07.11.2022**

*By*

*Dr. Basim Al-Qargholi*

# Outline and Aim

---

**After completing this lecture, you should be able to:**

- Analyze the operation of a Full-Wave Bridge Rectifier
- Describe how the diodes function in a Full-Wave Bridge Rectifier
- Determine the average value of a Full-Wave Bridge Rectifier
- Determine the peak inverse voltage (PIV)
- Compare between (HWR), Centre-tapped (FWR) & Bridge (FWR)

# Full-Wave Bridge Rectifier

The full-wave **bridge rectifier** uses four diodes, as shown in Fig. 1.

- a) When the input cycle is positive, as in Fig. 1, a), diodes  $D_1$  and  $D_2$  are forward-biased and conduct current in the direction shown. A voltage is developed across  $R_L$  that looks like the positive half of the input cycle. During this time, diodes  $D_3$  and  $D_4$  are reverse-biased.

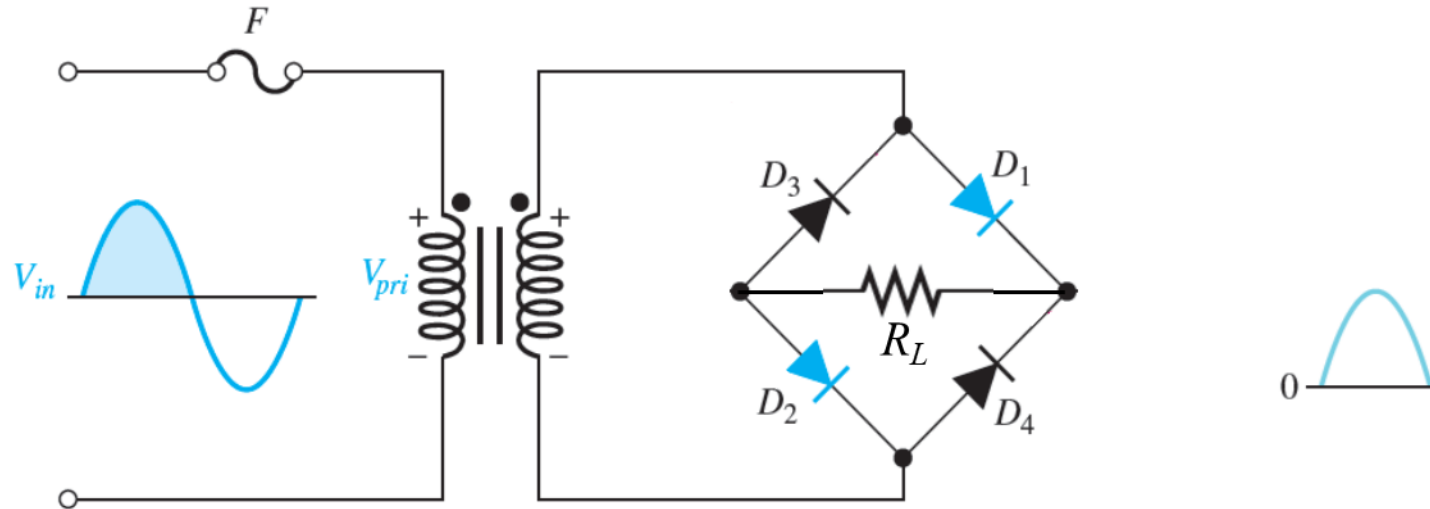


Fig. 1, a): During positive half-cycle of the input,  $D_1$  and  $D_2$  are forward-biased and conduct current.  $D_3$  and  $D_4$  are reverse-biased

# Full-Wave Bridge Rectifier

The full-wave **bridge rectifier** uses four diodes, as shown in Fig. 1.

- b) When the input cycle is negative, as in Fig. 1, b), diodes  $D_3$  and  $D_4$  are forward-biased and conduct current in the same direction through as during the positive half-cycle. During the negative half-cycle,  $D_1$  and  $D_2$  are reverse-biased. A full-wave rectified output voltage appears across  $R_L$  as a result of this action.

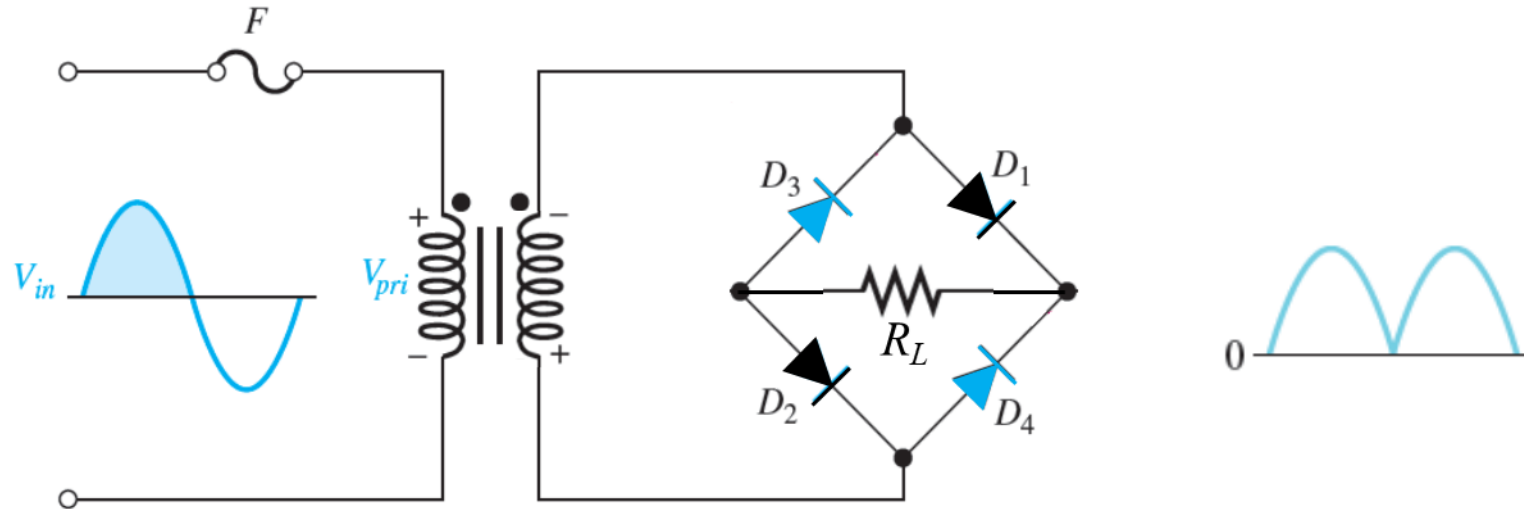


Fig. 1, b): During positive half-cycle of the input,  $D_3$  and  $D_4$  are forward-biased and conduct current.  $D_1$  and  $D_2$  are reverse-biased

# Full-Wave Bridge Rectifier

## The bridge output voltage from the transformer:

The secondary voltage is equal to the primary voltage times the turns ratio as stated by the equation:

$$V_{p(sec)} = V_{p(out)}$$

$$V_{p(sec)} = V_{p(out)} = nV_{p(pri)}$$

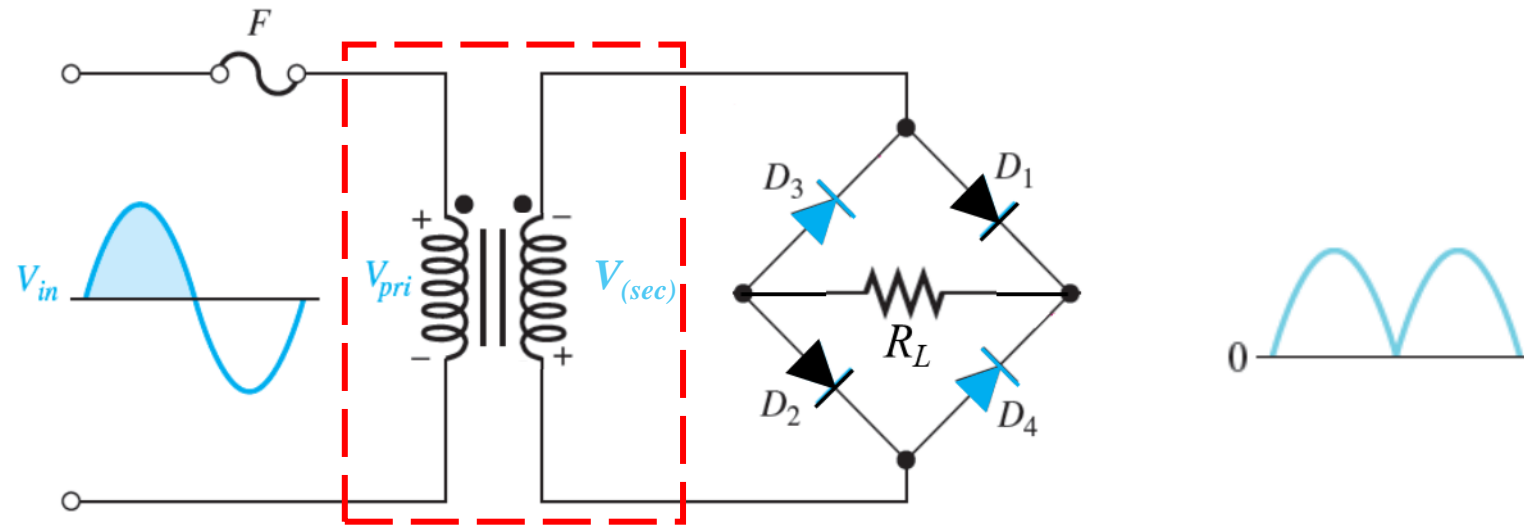


Fig. 2: The bridge output voltage from the transformer

# Full-Wave Bridge Rectifier

## Peak Inverse Voltage (PIV)

Let's assume that the input is in its positive half-cycle Then:

- $D_1$  and  $D_2$  are forward-Biased
- $D_3$  and  $D_4$  are reversed-Biased
- In Fig.1, a), PIV is equal to the  $V_{p(sec)}$  which is equal to the  $V_{p(out)}$

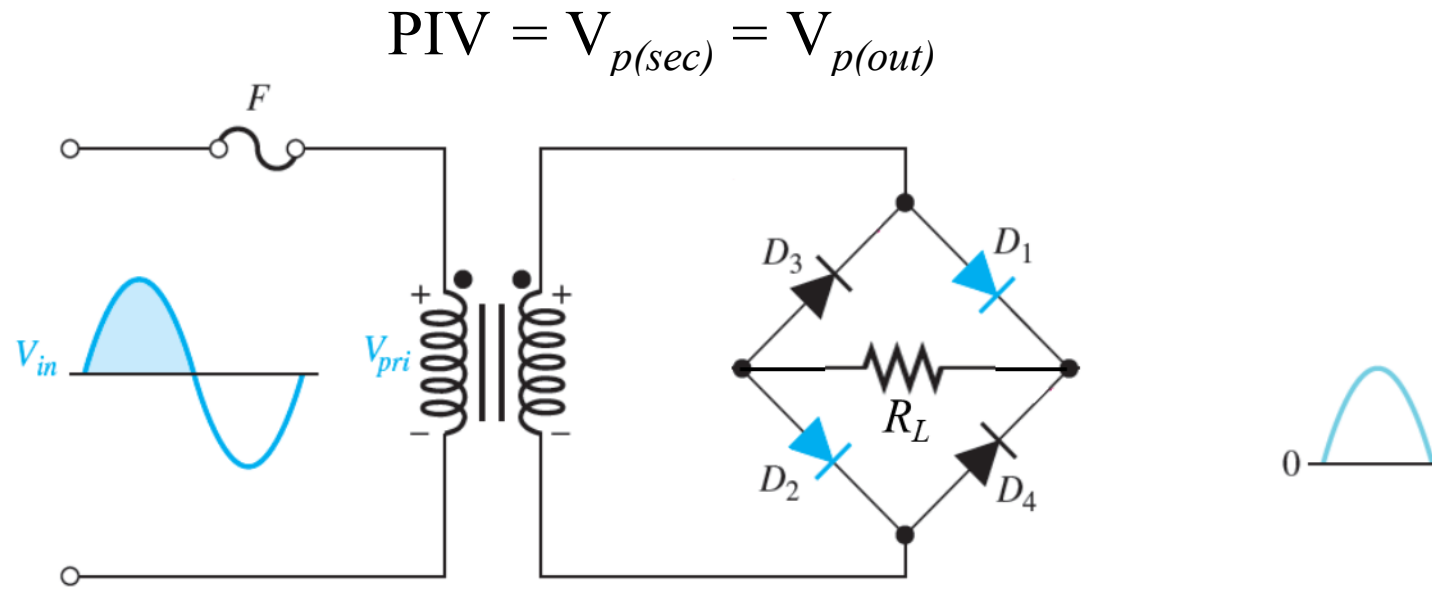


Fig. 1, a): During positive half-cycle of the input,  $D_1$  and  $D_2$  are forward-biased and conduct current.  $D_3$  and  $D_4$  are reverse-biased

# Full-Wave Bridge Rectifier

## Peak Inverse Voltage (PIV)

The PIV rating of the **bridge diodes** is **half** that required for the **center-tapped rectifier** for the same output voltage.

$$\text{PIV} = V_{p(sec)} = V_{p(out)}$$

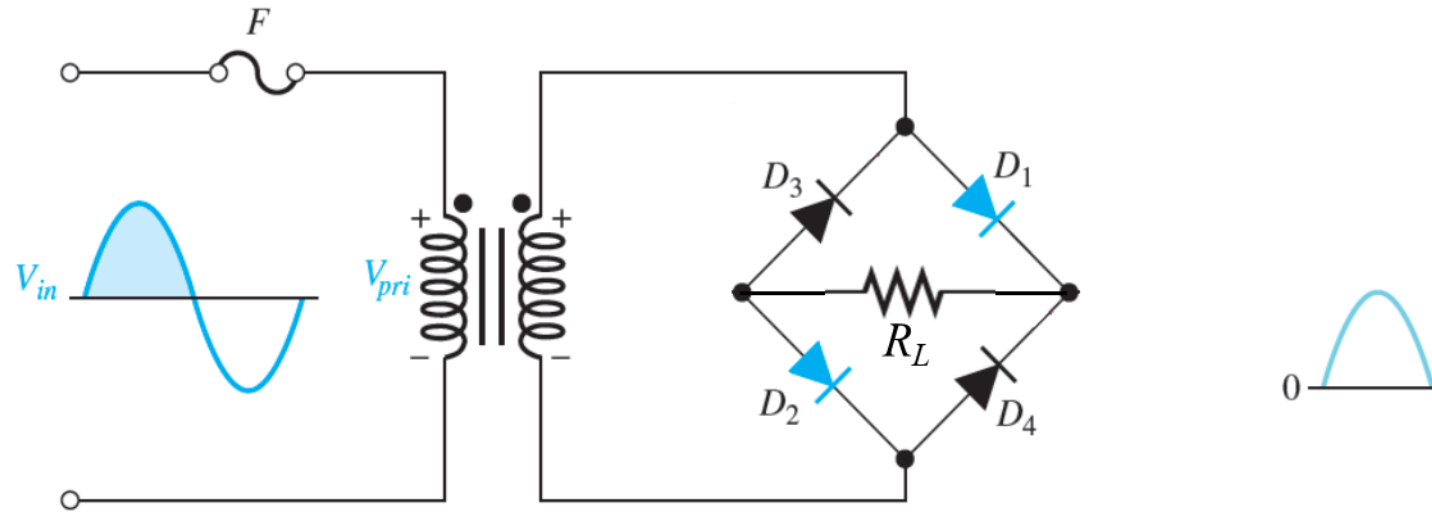


Fig. 1, a): During positive half-cycle of the input,  $D_1$  and  $D_2$  are forward-biased and conduct current.  $D_3$  and  $D_4$  are reverse-biased

# Full-Wave Bridge Rectifier

## Example 1:

- Determine the peak output voltage  $V_{p(out)}$ ,  $V_{p(RL)}$  and  $V_{AVG}$  for the bridge rectifier in Fig. 3.
- What is the minimum PIV rating required for the diodes?

## Solution:

$$a) V_{p(out)} = V_{p(sec)} = nV_{p(in)} = (1)25 V = 25 V$$

$$V_{p(RL)} = V_{p(out)} - 2(V_B) = 23.6 V$$

$$V_{AVG} = \frac{2V_{p(RL)}}{\pi} = \frac{47.2}{3.14} = 15 V$$

$$b) PIV = V_{p(sec)} = V_{p(out)} = 25 V$$

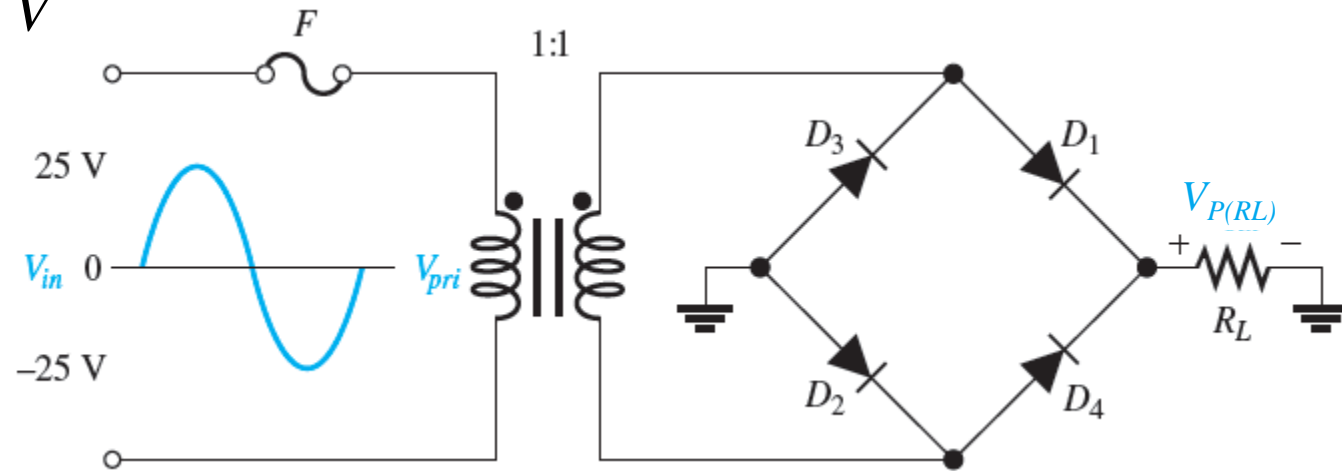





Fig. 3: Full-Wave Bridge Rectifier





## Compression between (HWR), Centre-tapped (FWR) & Bridge (FWR)

	<b>HWR</b>	<b>Center-tapped FWR</b>	<b>Bridge FWR</b>
<b>Allows</b>	Allows only one-half	Allows unidirectional half	Allows unidirectional half
<b>Output wave</b>			
<b>Transformer type</b>	Standard	Center-Tapped	Standard
<b>Number of diodes</b>	1	2	4
$V_{AVG}$	$= \frac{V_{p(out)}}{\pi}$	$V_{AVG} = \frac{2V_{p(out)}}{\pi}$	$V_{AVG} = \frac{2V_{p(out)}}{\pi}$
$V_{p(RL)}$	$= V_{p(out)} - 0.7 V$ $= V_{p(sec)} - 0.7 V$	$= V_{p(out)} - 0.7 V$ $= \frac{V_{p(sec)}}{2} - 0.7 V$	$= V_{p(out)} - 2 \times 0.7 V$ $= V_{p(sec)} - 2 \times 0.7 V$
<b>PIV</b>	$= V_{p(sec)}$	$= V_{p(sec)} = 2V_{p(out)}$	$= V_{p(sec)}$
<b>Frequency</b>	Equal	Double	Double