



# Lecture No. 11,12

## “Star-delta


# transformation

”



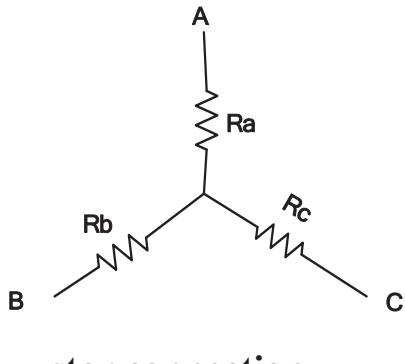
## Star delta transformation :

In solving complicated networks , it is necessary to transform from star to delta or from delta to star as shown below .



star connection

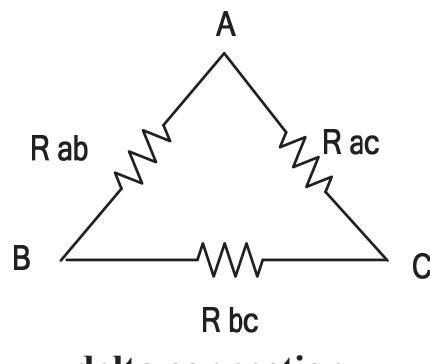

delta connection

### 1. Convert from star to delta :

$$R_{ab} = R_a + \frac{R_a \times R_b}{R_c}$$

$$R_{ac} = R_a + \frac{R_a \times R_c}{R_b}$$

$$R_{bc} = R_b + \frac{R_b \times R_c}{R_a}$$



## 2. Convert from delta to star :



$$R_a = \frac{R_{ab} \times R_{ac}}{R_{ab} + R_{ac} + R_{bc}}$$

$$R_b = \frac{R_{ab} \times R_{bc}}{R_{ab} + R_{ac} + R_{bc}}$$

$$R_c = \frac{R_{ac} \times R_{bc}}{R_{ab} + R_{ac} + R_{bc}}$$



**Example : For the circuit shown in fig. 1 , find the total resistance**

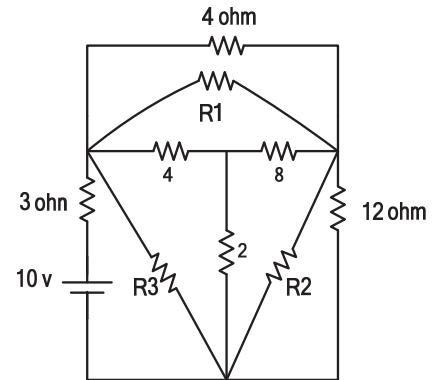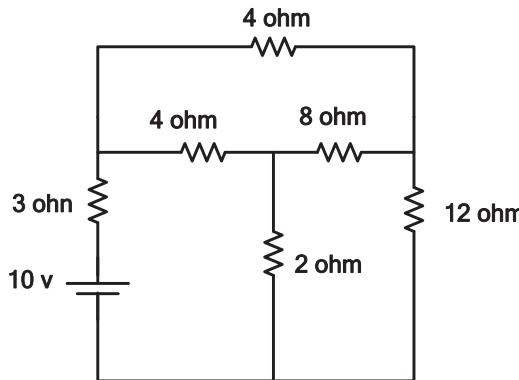


**Fig. 1**

**Convert star to delta**

$$R_1 = 4 + \frac{8}{2} = 28 \Omega$$


$$R_2 = 2 + \frac{8}{4} = 14 \Omega$$

$$R_3 = 2 + \frac{4}{8} = 7 \Omega$$

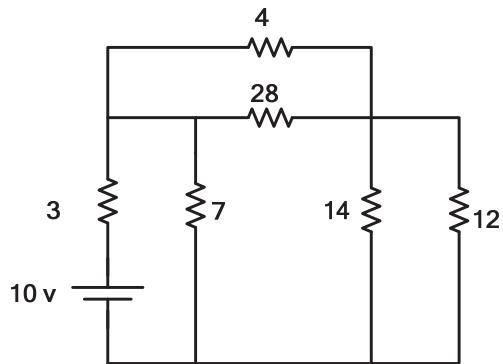


$$4 \Omega // 28 \Omega , \quad \frac{4 \times 28}{14 \times 12} = 3.5 \Omega$$
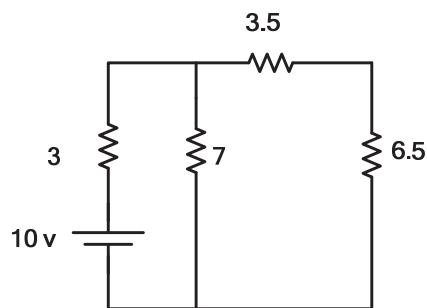
$$14 \Omega // 12 \Omega , \quad \frac{14 \times 12}{14 + 12} = 6.5 \Omega$$



$$3.5 + 6.5 = 10 \Omega$$

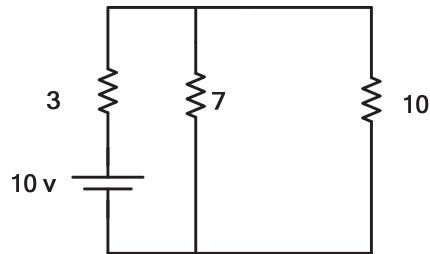

$$7 \Omega // 10 \Omega$$

$$\frac{7 \times 10}{7 + 10} = 4 \Omega$$

$$R_t = 3 + 4 = 7 \Omega$$