



Class: 1st
Subject: Electrical Technology
Lecturer: Omar A. Alkawak
E-mail: OmarAhmed@mustaqbal-college.edu.iq



Lecture No. 4,5

“Kirchhoffs laws”

Lecture Four, Five

Kirchhoffs laws:

1. kirchhoffs voltage law:

The algebraic sum of voltages in any closed loop is zero .

$$\sum V = 0$$

Now , from fig. 1 , there are three equation according to kirchhoffs voltage law .

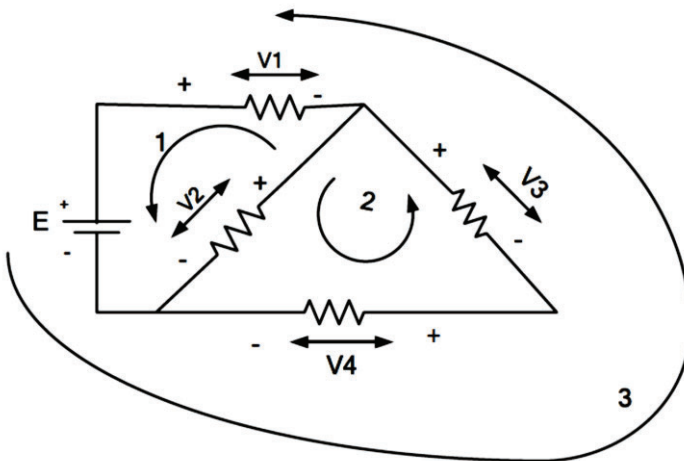


Fig. 1

Loop 1 :

$$E - V1 - V2 = 0$$

$$E = V1 + V2 \text{ ----- (1)}$$

Loop 2 :

$$V2 - V3 - V4 = 0$$

$$V2 = V3 + V4 \text{ ----- (2)}$$

Loop 3 :

$$E - V1 - V3 - V4 = 0$$

$$E = V1 + V3 + V4 \text{ ----- (3)}$$

Example : For the circuit shown in fig. 2 , using kirchhoffs voltage law ,find V1 and V2 .

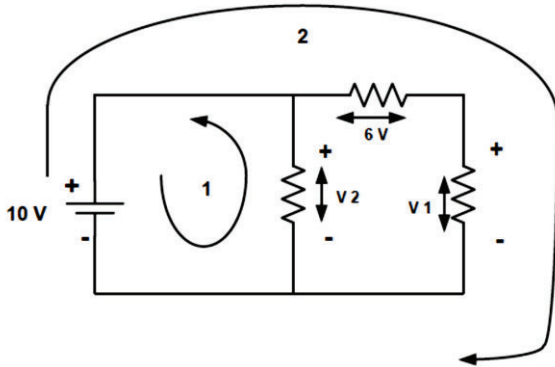


Fig. 2

Loop 1 :

$$10 - V2 = 0 \quad V2 = 10 \text{ v}$$

Loop 2 :

$$-10 + 6 + V1 = 0$$

$$V1 = 10 - 6 = 4 \text{ v}$$

2. kirchhoffs current law:

In any electrical network , the algebraic sum of currents meeting at a point (junction) is zero as shown in fig. 3 .

$$\sum I = 0$$

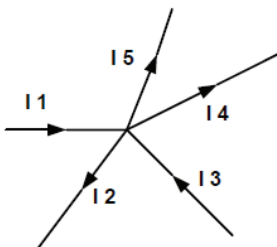


Fig. 3

$$I1 + I3 = I2 + I4 + I5$$

$$I1 + I3 - I2 - I4 - I5 = 0$$

Example : Using kirchhoffs current lae , find I 5 from fig. 4 .

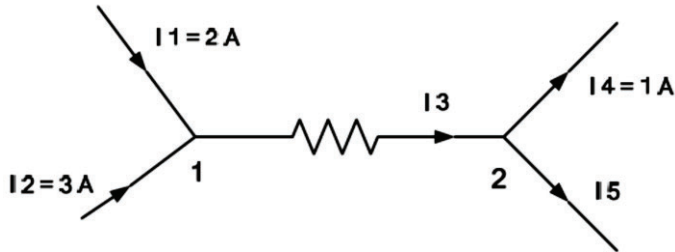


Fig. 4

At node 1 :

$$I_1 + I_2 = I_3$$

$$2 + 3 = 5 \text{ A} , \text{ therefore } I_3 = 3 \text{ A}$$

At node 2 :

$$I_3 = I_4 + I_5$$

$$3 = 1 + I_5$$

$$I_5 = 3 - 1 = 2 \text{ A}$$

Example : Using kirchhoffs law , find I 1 , I 2 and I 3 for the circuit shown in fig. 5 .

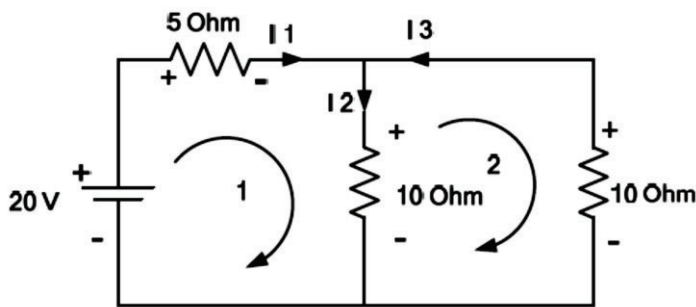


Fig. 5

$$I_1 = I_2 + I_3 \text{ ----- (1) Loop 1 :}$$

$$5 + 20 - I_1 + 10 I_2 = 0$$

$$5I_1 + 10 I_2 = 20$$

$$I_1 + 2 I_2 = 4 \text{ ----- (2)}$$

Loop 2 :



$$10 - I_2 + I_3 = 0$$

$$I_2 = I_3 \text{ ----- (3)}$$

From Equ . (2)

$$I_1 = 4 - 2 I_2 \text{ ----- (4)}$$

Sub. Equ. (3) and (4) in (1)

$$4 - 2 I_2 = I_2 + I_2$$

$$I_2 = 1 \text{ A}$$

From Equ . (4)

$$I_1 = 4 - (2 \times 1) = 2 \text{ A}$$

$$I_3 = I_2$$

$$I_3 = 1 \text{ A}$$

Maxwells Method :

In this method loop current is used instead of branch currents as in kirchhoffs laws . Here , the current in different meshes are assigned continuous paths so that they do not split at a junction into branch current . Basically , this method consists of writing loop voltage equation in terms of the unknown loop currents .

Example : Using maxwells method , calculate all currents for the circuit shown in fig. 6 .

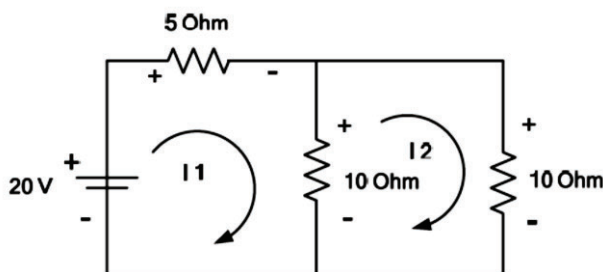


Fig. 6

Loop 1 :

$$- 20 + 5 I_1 + 10 (I_1 - I_2) + 10 I_1 - 10 I_2 = 20$$

$$3 I_1 - 2 I_2 = 4 \text{ ----- (1)}$$



Loop 2 :

$$10(I_2 - I_1) + 10I_2 = 0$$

$$10I_2 - 10I_1 + 10I_2 = 0$$

$$20I_2 = 10I_1$$

$$I_1 = 2I_2 \text{ ----- (2)}$$

Sub. Equ. (2) in (1)

$$3(2I_2) - 2I_2 = 4$$

$$6I_2 - 2I_2 = 4$$

$$I_2 = 1 \text{ A}$$

$$I_1 = 2I_2 \quad I_1 = 2 \text{ A}$$

Now , branch current will be calculated as follows :

The current through 5Ω resistor $I_{5\Omega} = I_1 = 2 \text{ A}$.

The current through 10Ω resistor $I_{10\Omega} = I_1 - I_2 = 2 - 1 = 1 \text{ A}$.

The current through 10Ω resistor $I_{10\Omega} = I_2 = 1 \text{ A}$.