



Ministry of Higher Education

and Scientific Research

Al-Mustaqbal University College

Department of Medical Instrumentation Techniques Engineering

Subject: Fundamentals of Electrical Engineering

First Class

Lecture 3

(Kirchhoff's law & their use in network)


By

Dr. Jaber Ghaib

قانون كيرشوف للجهود (Kirchhoff's Voltage Law (KVL))



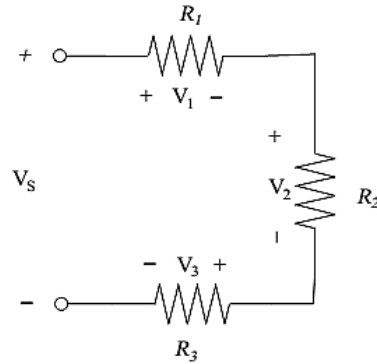ينص كيرشوف على " في اي مسار مغلق يكون المجموع الجبري للجهود مساوياً صفراً "



$$V_s = V_1 + V_2 + V_3$$


$$V_s - V_1 - V_2 - V_3 = 0$$

خطوات الحل بطريقة كير شوف:-

1- نترض اتجاه التيار في كل فرع (مسار مغلق)

2- كتابة معادلة الجهد لكل مسار مغلق

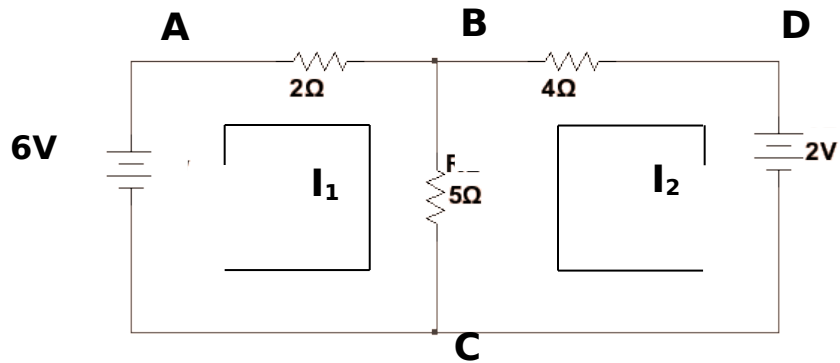Example 1: In the following circuit, calculate the current in each element of the circuit using Kirchhoff's Law



Sol:

In the first loop I_1 :



$$6 = 2 \times I_1 + 5 \times (I_1 + I_2)$$

In the second loop I_2 :

$$2 = 4 \times I_2 + 5 \times (I_1 + I_2)$$

Solving the two equations

$$\begin{aligned} 30 &= 35 \times I_1 + 25 \times I_2 \\ -14 &= -35 \times I_2 - 63 \times I_2 \end{aligned}$$

$$16 = 0 - 38 I_2$$

$$\therefore I_2 = \frac{16}{-38} = -0.421 \text{ A}$$

Sub. The value of I_2 in the second equation we get:

$$2 = 5 \times I_1 - 9 \times 0.421$$

$$I_1 = \frac{5.789}{5} = 1.16 \text{ A}$$

So the current flow in R_{BC} is:

$$I_3 = I_1 + I_2$$

$$= 1.16 + (-0.421) = 0.739 \text{ A}$$

قانون تقسيم الجهد (Voltage divider Rule)

بما ان التيار المار في مقاومات موصلة على التوالي يكون متساوياً فان هذا يؤدي الى ان هبوط الجهد على مقاومة حسب قانون اوم يعتمد على قيمة المقاومة.

فمن هذا البيان يتضح لنا, ان الجهد المطبق في الدائرة الموصلة على التوالي سوف يتسم على المقاومات حسب قيمة كل منها, فالاكبر يكون هبوط الجهد عليها كبيراً وهكذا.



Department of Medical Instrumentation Techniques
Engineering. : Fundamentals of Electrical
Engineering

ولحساب قيمة الجهد على مقاومة في الدائرة فاننا نطبق العلاقة التالية:

$$V_x = \left(\frac{R_x}{R_T} \right) V_s$$


حيث:

V_x : هبوط الجهد المجهول على المقاومة R_x .

R_T : المقاومة الكلية

V_s : جهد المصدر

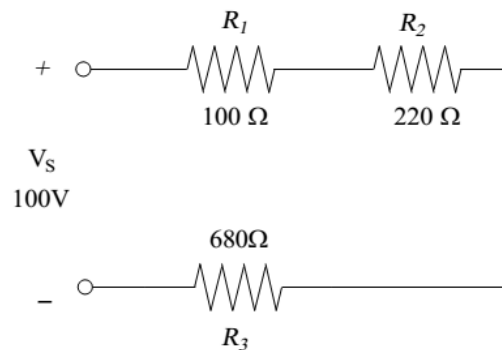Example 2: In the following circuit find the value of voltage drop through the resistance R_3



:Sol

$$V_{R3} = V_s \left(\frac{R_x}{R_T} \right)$$

$$R_T = R_1 + R_2 + R_3$$


$$R_T = 100\Omega + 220\Omega + 680\Omega = 1K\Omega$$

$$\frac{100 * 680}{1000} = 68 V$$



قانون كيرشوف للتيار (Kirchhoff's Current Law (KCL))

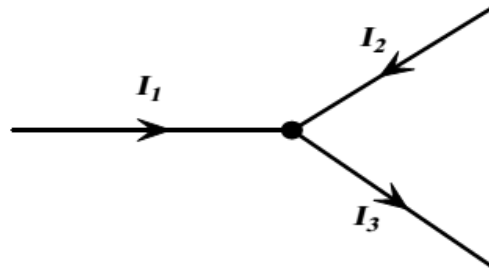
في اي نقطة في الدائرة فان المجموع الجبري للتيارات يساوي الصفر. اي ان مجموع التيارات الداخلة الى النقطة والخارجة من النقطة تساوي الصفر. ويتضح هذا من الشكل التالي:



ويمكن اعتبار ان اشارة التيار الداخل الي النقطة تكون سالبة و اشارة التيار الخارج من النقطة تكون موجبة و بالتالي:

$$I_3 - I_2 - I_1 = 0$$

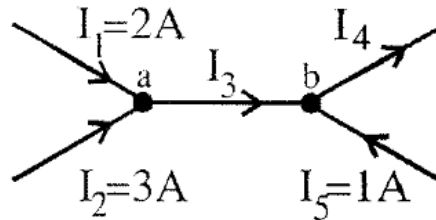Example 3: Find the value I_3 and I_4 using Kirchhoff's Current Law (KCL).



Sol:

At node (a)




$$I_3 = I_1 + I_2$$
$$I_3 = 2A + 3A = 5A$$

At node (b)

$$I_4 = I_3 + I_5$$

$$I_4 = 5A + 1A = 6A$$

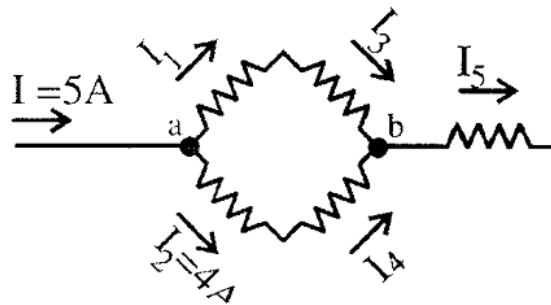Example 4: From the figure below find the value of I_1 , I_3 , I_4 , and I_5



Sol: at node (a)

$$I = I_1 + I_2$$

$$5A = I_1 + 4A$$

$$I_1 = 1A$$

At node (b)

$$I_3 + I_4 = I_5$$

Since I_1 is not divide so its equal to I_3

$$I_3 = I_1 = 1A$$




So that for $I_4 = I_2$

$$I_4 = I_2 = 4A$$


$$I_5 = I_3 + I_4 = 1A + 4A = 5A$$

قانون تجزئة التيار (Current Divider Rule(CDR))

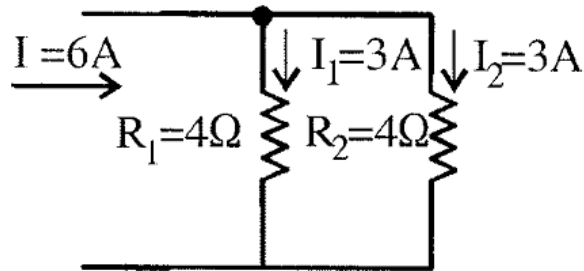
1- يتجزأ التيار المار في مقاومتين على التوازي, و يتجزأ قيمته بالتساوي على مقاومتين في حالة تساويهما في القيمة



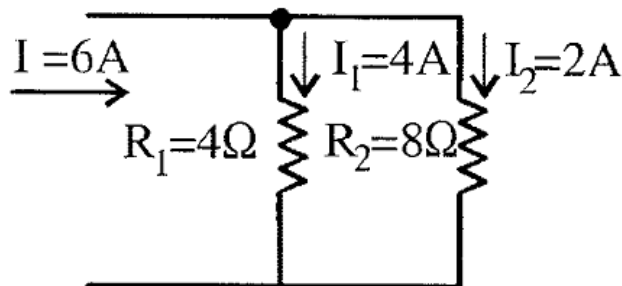2- اما التيار المار في مقاومتين مختلفتين فيتجزأ بحيث يكون للمقاومة الاصغر تيار أكبر, ويكون للمقاومة الاكبر قيمة تيار أصغر.



في حالة مقاومتين متصلتين على التوازي

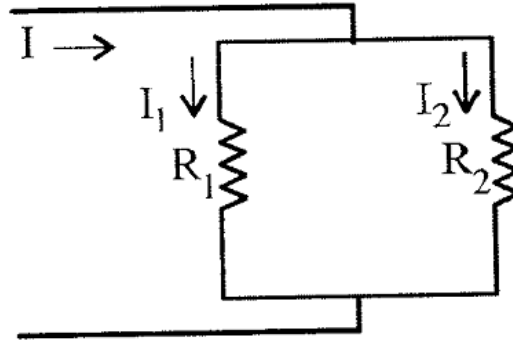

$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

$$I_1 = \frac{R_T}{R_1} I$$


$$\therefore = \frac{[(R_1 R_2) / (R_1 + R_2)]}{R_1} I$$

$$\therefore I_1 = \frac{R_2}{R_1 + R_2} I$$

وبنفس الكيفية تكون قيمة I_2

$$\therefore I_2 = \frac{R_1}{R_1 + R_2} I$$

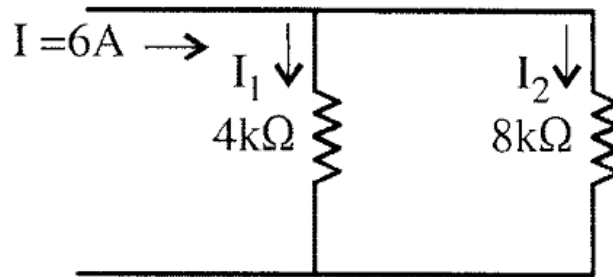Example 5: find the value of the current I_2 in the following circuit using (CDR):




Sol:

$$I_2 = \frac{R_1}{R_1 + R_2} I = \frac{(4k\Omega)(6A)}{4k\Omega + 8k\Omega}$$

$$I_2 = \frac{24}{12} = 2A$$

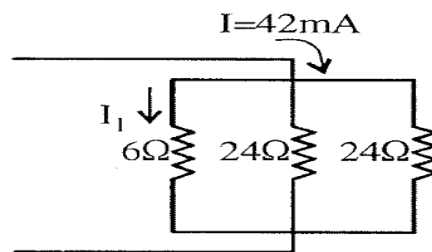Example 6: Find the value of the current I_1 in the circuit bellow.



Sol:

$$\begin{aligned} R_T &= 6\Omega // 24\Omega // 24\Omega \\ &= 6\Omega // 12\Omega \end{aligned}$$




$$= \frac{6 \times 12}{6 + 12} = \frac{72}{18}$$

$$R_T = 4\Omega$$

$$I_1 = \frac{R_T}{R_1} I \qquad I_1 = \frac{(4\Omega)(42 \times 10^{-3} A)}{6\Omega} = 28mA$$

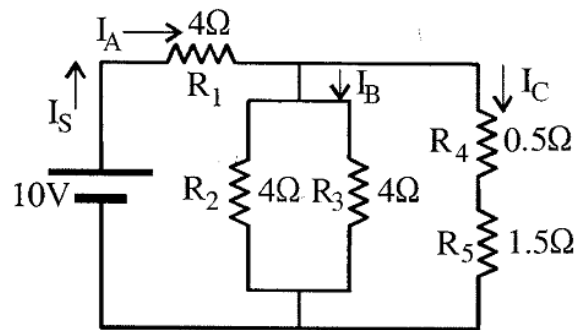Example 7: from the circuit in the following figure find the value of the current and voltage in each resistance.



Sol: by simplification the circuit we get


$$R_A = R_1 = 4\Omega$$

$$R_B = R_2 // R_3 = 4\Omega // 4\Omega$$

$$R_B = 2\Omega$$

$$R_C = R_4 + R_5 = 0.5 + 1.5$$

$$R_C = 2\Omega$$

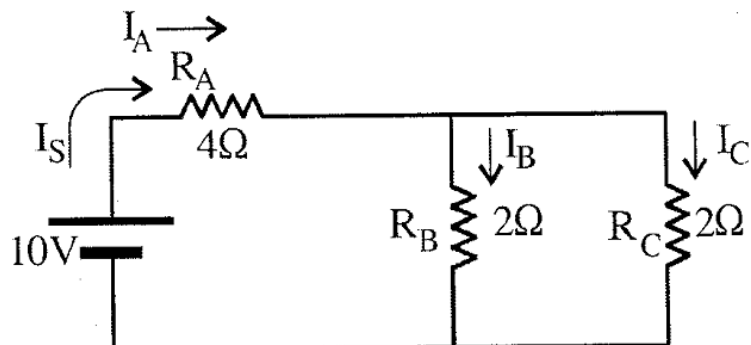



Department of Medical Instrumentation Techniques
Engineering. : Fundamentals of Electrical
Engineering

The resistance R_B and R_C are in parallel

$$\therefore R_{B//C} = \frac{R}{N} = \frac{2\Omega}{2} = 1\Omega$$

The total resistance is

$$R_T = R_A + R_{B//C}$$

$$R_T = 4\Omega + 1\Omega = 5\Omega \quad \longrightarrow \quad I_S = \frac{E}{R_T} = \frac{10V}{5\Omega} = 2A$$

We can find currents in the circuit I_A , I_B , I_C


$$I_A = I_S = 2A$$

Since R_B , R_C are equal, so the current will be divided between them

$$I_B = I_C = \frac{I_A}{2} = \frac{2A}{2} = 1A$$

By return to the original shape of the circuit, we can find the current following through the resistance R_2 , R_3
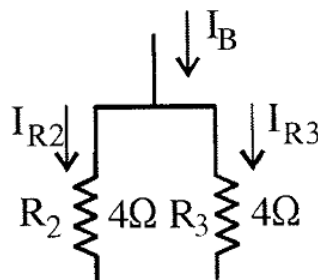
$$I_{R_2} = I_{R_3} = \frac{I_B}{2} = \frac{1A}{2} = 0.5A$$



The voltages V_A , V_B , V_C can be found as:



Department of Medical Instrumentation Techniques
Engineering. : Fundamentals of Electrical
Engineering

$$V_A = I_A R_A = (2A) (4\Omega) = 8V$$

$$V_B = I_B R_B = (1A) (2\Omega) = 2V$$

$$V_C = I_C R_C = (1A) (2\Omega) = 2V$$

By using KVL to prove the solution

$$\sum V = 0$$


$$E - V_A - V_B = 0$$

$$10 - 8 - 2 = 0$$

$$10 - 10 = 0$$

$$0 = 0$$

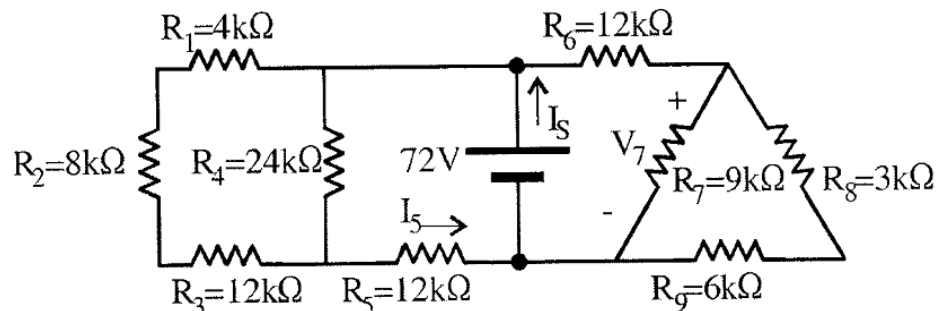Example 8: In the following circuit find the two currents I_s and I_5 and the voltage V_7 .




Sol:

The resistances R_1 , R_2 and R_3 are connected in series and its equivalent $24\text{ k}\Omega$. The resistance R_8 and R_9 are connected in series and their equivalent is $9\text{ k}\Omega$.

So the circuit can be drawn as



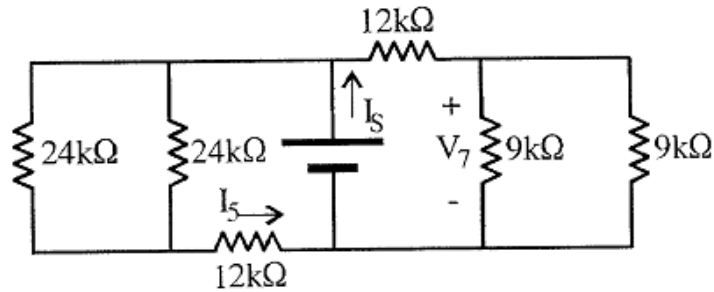Department of Medical Instrumentation Techniques
Engineering. : Fundamentals of Electrical
Engineering




$$12k\Omega \longleftarrow 24k\Omega // 24k\Omega$$

$$24k\Omega \longleftarrow 12k\Omega + 12k\Omega$$

$$4.5k\Omega \longleftarrow 9k\Omega // 9k\Omega$$

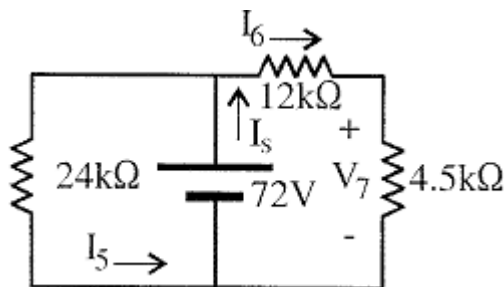The voltage of the 24 kΩ resistance equal to 72V in parallel with the voltage source



$$\therefore I_5 = \frac{72V}{24k\Omega} = 3mA$$


To calculate the value of V_7 we use Voltage Divided Rule

$$V_7 = \frac{(72V)(4.5k\Omega)}{4.5k\Omega + 12k\Omega} = \frac{324V}{16.5} = 19.6V$$

To find the current I_6

$$I_6 = \frac{19.6V}{4.5k\Omega} = 4.35mA$$

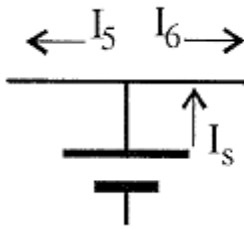To calculate the current I_s we use Kirchoff's Voltage Law(KVL)



$$I_s = I_5 + I_6$$
$$= 3\text{mA} + 4.35\text{mA} = 7.35\text{mA}$$

Example 2.19. A circuit consists of two parallel resistors, having resistance of $20\ \Omega$ and $30\ \Omega$ respectively, connected in series with $15\ \Omega$. If current through $15\ \Omega$ resistor is $3\ \text{A}$, find (i) the current through $20\ \Omega$ and $30\ \Omega$ resistors (ii) the voltage across the whole circuit and (iii) total power.

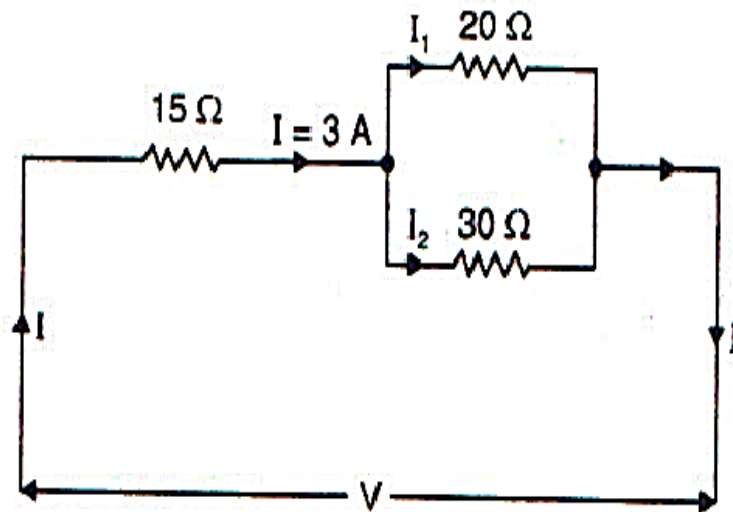


Fig. 2.25

Solution. Fig. 2.25 shows the circuit arrangement.

(i) The total current of $3\ \text{A}$ will divide between $20\ \Omega$ and $30\ \Omega$ as under :
Current through $20\ \Omega$,

$$I_1 = 3 \times \frac{30}{20+30} = 1.8\ \text{A}$$



Department of Medical Instrumentation Techniques
Engineering. : Fundamentals of Electrical
Engineering

Current through 30Ω , $I_2 = 3 \times \frac{20}{20 + 30} = 1.2 \text{ A}$


(ii) For parallel circuit, $R_p = \frac{20 \times 30}{20 + 30} = 12 \Omega$

Total circuit resistance = $15 + 12 = 27 \Omega$

\therefore Supply voltage, $V = 3 \times 27 = 81 \text{ V}$


(iii) Total power = $V I = 81 \times 3 = 243 \text{ watts}$

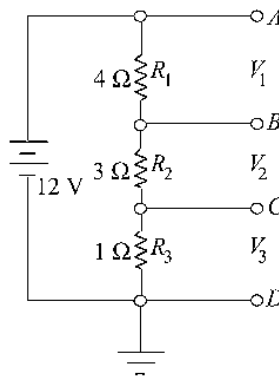Q1: find the value of different voltages that can be obtained from a 12-V battery (V_{AB} , V_{BC} , V_{CD} , V_{AC} , V_{AD}) with the help of voltage divider circuit shown below



Ans.[6 V, 4.5 V, 1.5 V, 10.5 V, 12 V]

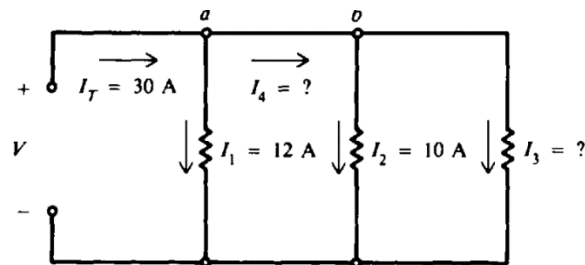Q2: Find the value of I_3 and I_4 using KCL



Ans.[8 A, 18 A]



Department of Medical Instrumentation Techniques
Engineering. : Fundamentals of Electrical
Engineering
