



AL- MUSTAQBAL UNIVERSITY COLLEGE
DEPARTMENT OF BIOMEDICAL ENGINEERING

Signals and Systems for BME

BME 322

Lecture 1

- Introduction -

Dr. Zaidoon AL-Shammari

Lecturer / Researcher


zaidoon.waleed@mustaqbal-college.edu.iq

www.uomus.edu.iq

What is a system ?



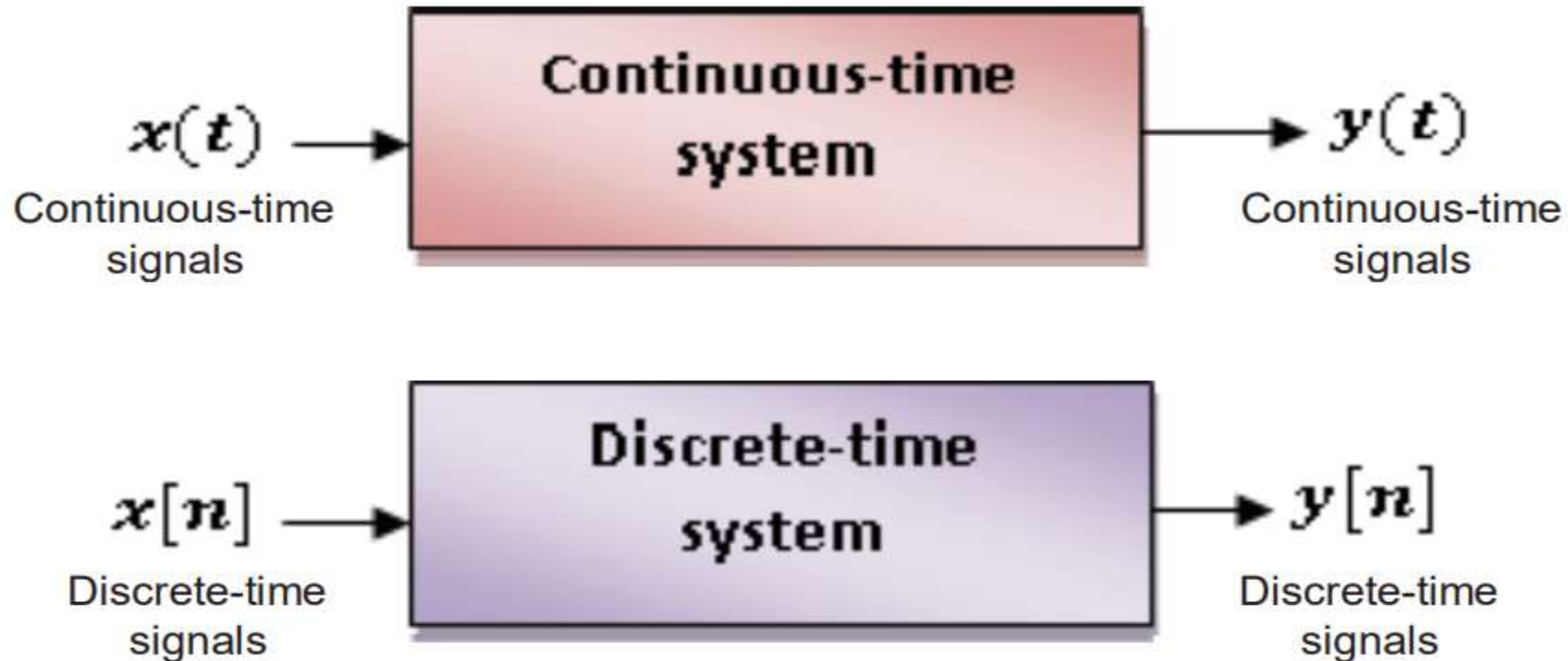
- A system S is any physical device, process or computer algorithm that transforms input signals into output signals.



A mathematical model of a system



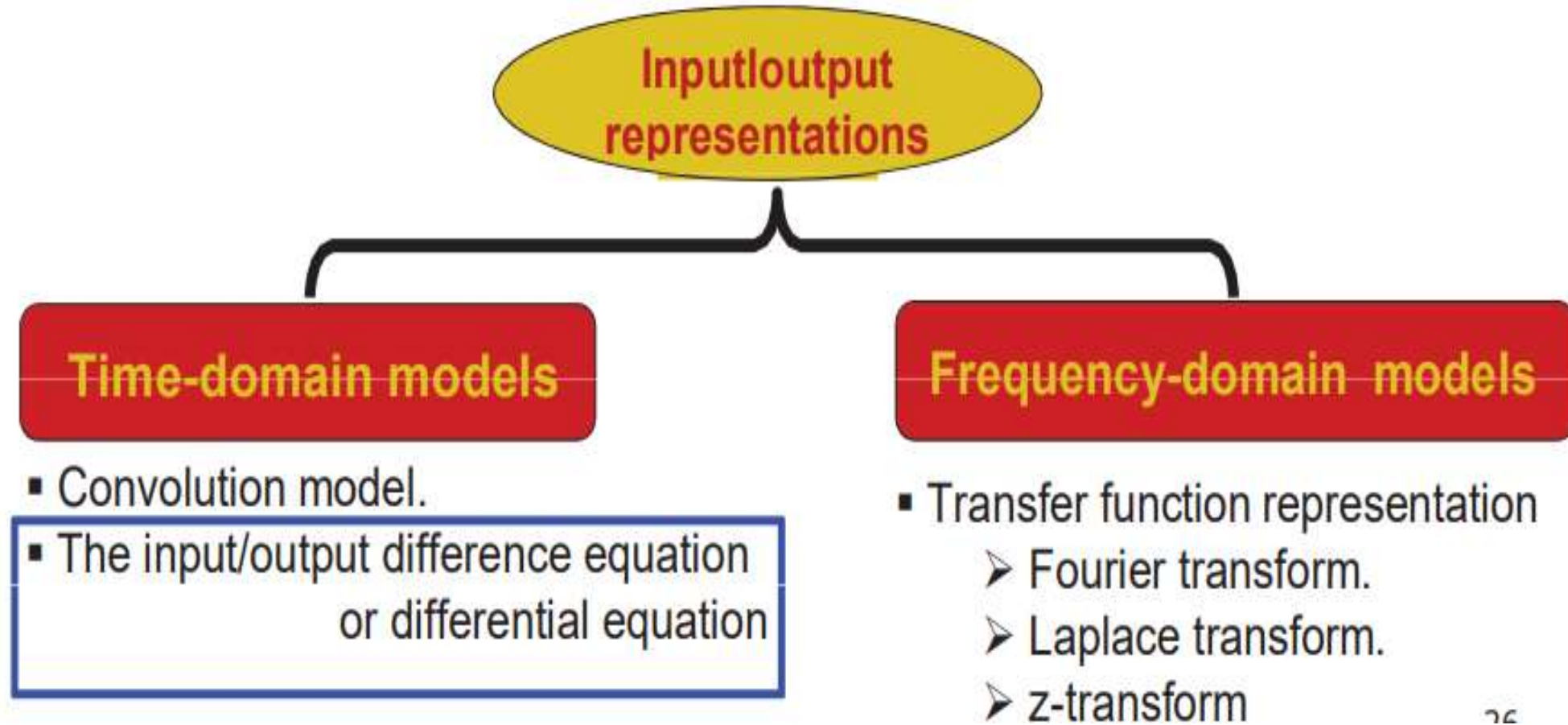- A mathematical model of a system consists of the equations that describe the relationships between all signals appearing in that system. This model allow an in-depth study of that system.
- The basic type of mathematical models is: input/output representations describing the relationship between the input and output signals of a system.





- Moving Average Filter (discrete-time system)

The N-point moving average (MA) filter is given by the input/output relationship:

$$y[n] = \sum_{k=0}^{N-1} \frac{1}{N} \cdot x[n - k] \quad ; \text{ where } N \text{ is a positive integer}$$

Where

- $x[n]$ is the input applied to the filter.
- $y[n]$ is the resulting output response.




$$y[n] = \frac{1}{N} [x[n] + x[n - 1] + x[n - 2] + \dots + x[n - N + 1]]$$

- The output $y[n]$ at time n of the N -point MA filter is the average of the N input values.
- MA filters are often used to reduce the magnitude of the noise that may be present in a signal.

Review: Kirchhoff's laws




Kirchhoff's voltage law (KVL):

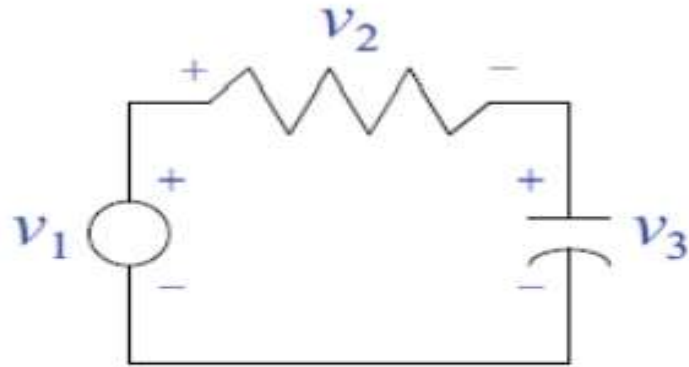

The sum of voltages in a loop is equal to zero:

$$-v_1 + v_2 + v_3 = 0$$

Kirchhoff's current law (KCL):

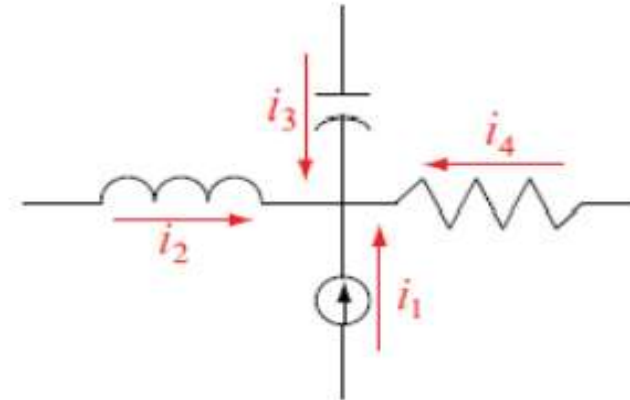


The sum of currents entering a node is equal to zero:

$$i_1 + i_2 + i_3 + i_4 = 0$$

Review: linear circuit elements




Resistor:

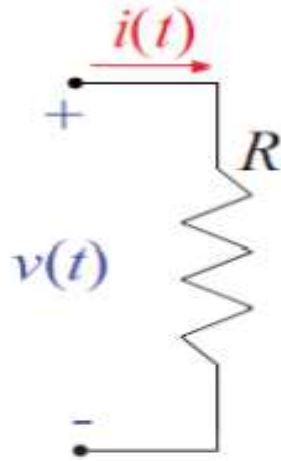

$$v(t) = Ri(t)$$

$$i(t) = \frac{v(t)}{R}$$


Inductor:

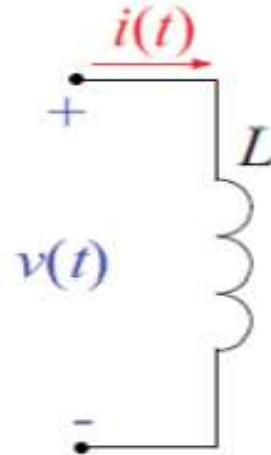

$$v(t) = L \frac{di(t)}{dt}$$

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau$$

Capacitor:

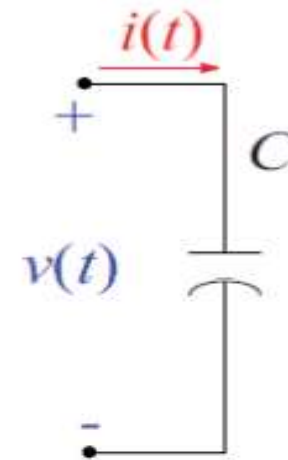


$$i(t) = C \frac{dv(t)}{dt}$$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$$



- RC Circuit (continuous-time systems)

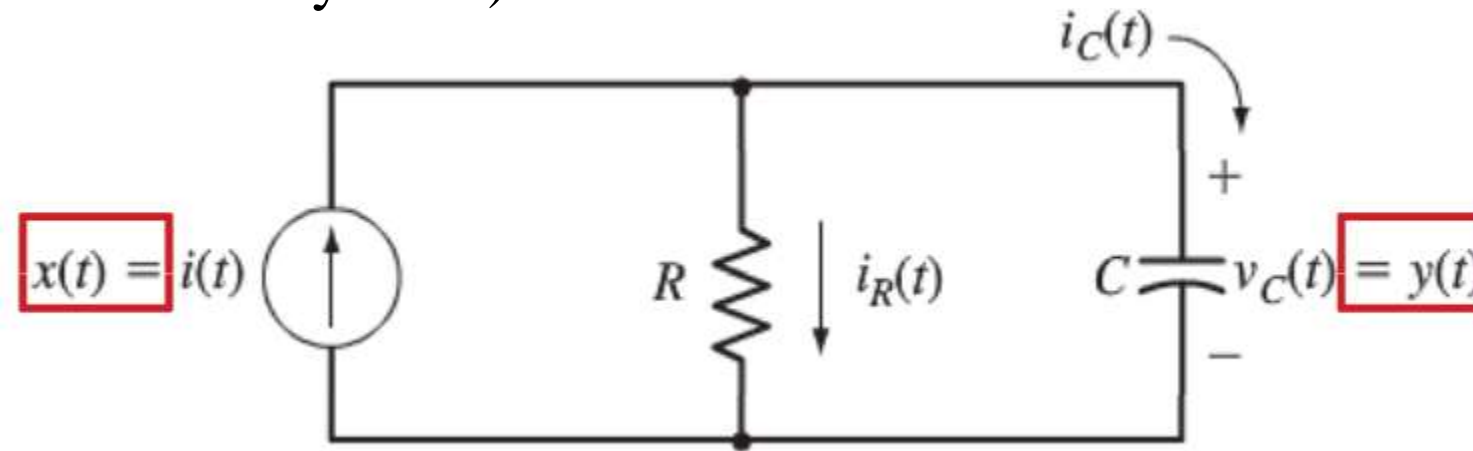

- Input/output differential equation of the circuit, that describe the relationship between the input $x(t)$ and the output $y(t)$.

$$C \frac{dy(t)}{dt} + \frac{1}{R} y(t) = x(t)$$

