



## Lecture Four

### Circuit Theorems

#### 4.1 Introduction

The growth in areas of application of electric circuits has led to an evolution from simple to complex circuits. To handle the complexity, engineers over the years have developed some theorems to simplify circuit analysis. Such theorems include Thevenin's and Norton's theorems. Since these theorems are applicable to **linear circuits**, we first discuss the concept of circuit linearity. In addition to circuit theorems, we discuss the concepts of **superposition**, **maximum power transfer**, **Millman's theorem**, **Substitution theorem**, and **Reciprocity theorem** in this lecture.

#### 4.2 Linearity Property

Linearity is the property of an element describing a linear relationship between cause and effect. The property is a combination of both the homogeneity property and the additivity property. The homogeneity property requires that if the input (also called the excitation) is multiplied by a constant, then the output (also called the response) is multiplied by the same constant. For a resistor, for example, Ohm's law relates the input  $\mathbf{i}$  to the output  $\mathbf{v}$ ,

$$\mathbf{v} = \mathbf{iR} \quad (4.1)$$

If the current is increased by a constant  $\mathbf{k}$ , then the voltage increases correspondingly by  $\mathbf{k}$ , that is,

$$\mathbf{kiR} = \mathbf{kv} \quad (4.2)$$

The additivity property requires that the response to a sum of inputs is the sum of the responses to each input applied separately. Using the relationship of a resistor, if

$$\mathbf{v}_1 = \mathbf{i}_1\mathbf{R} \quad \text{and} \quad \mathbf{v}_2 = \mathbf{i}_2\mathbf{R} \quad (4.3)$$

then applying  $(\mathbf{i}_1 + \mathbf{i}_2)$  gives

$$\mathbf{v} = (\mathbf{i}_1 + \mathbf{i}_2) \mathbf{R} = \mathbf{i}_1\mathbf{R} + \mathbf{i}_2\mathbf{R} = \mathbf{v}_1 + \mathbf{v}_2 \quad (4.4)$$

A linear circuit is one whose output is linearly related (or directly proportional) to its input.

**Example 4.1:** For the circuit in Fig. 4.1, find  $i_o$  when  $v_s = 12\text{ V}$  and  $v_s = 24\text{ V}$ .

**Solution:** Applying KVL to the two loops, we obtain

$$12i_1 - 4i_2 + v_s = 0 \tag{4.1.1}$$

$$-4i_1 + 16i_2 - 3v_x - v_s = 0 \tag{4.1.2}$$

But  $v_x = 2i_1$ . Equation (4.1.2) becomes

$$-10i_1 + 16i_2 - v_s = 0 \tag{4.1.3}$$

Adding Eqs. (4.1.1) and (4.1.3) yields

$$2i_1 + 12i_2 = 0 \Rightarrow i_1 = -6i_2$$

Substituting this in Eq. (4.1.1), we get

$$-76i_2 + v_s = 0 \Rightarrow i_2 = v_s/76$$

When  $v_s = 12\text{ V}$ ,  $i_o = i_2 = 12/76\text{ A}$

When  $v_s = 24\text{ V}$ ,  $i_o = i_2 = 24/76\text{ A}$

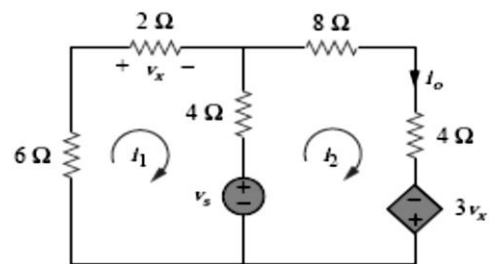


Fig. 4.1: For Example 4.1.

### 4.3 Superposition

The idea of superposition rests on the linearity property.

**The superposition principle states that the voltage across (or current through) an element in a linear circuit is the algebraic sum of the voltages across (or currents through) that element due to each independent source acting alone.**

However, to apply the superposition principle, we must keep two things in mind:

1. We consider one independent source at a time while all other independent sources are turned off. This implies that we replace every voltage source by 0 V (or a short circuit), and every current source by 0 A (or an open circuit).
2. Dependent sources are left intact because they are controlled by circuit variables. With these in mind, we apply the superposition principle in three steps:

**Steps to Apply Super position Principle:**

1. Turn off all independent sources except one source. Find the output (voltage or current) due to that active source using nodal or mesh analysis.
2. Repeat step 1 for each of the other independent sources.
3. Find the total contribution by adding algebraically all the contributions due to the independent sources.

Analyzing a circuit using superposition has one major disadvantage: it may very likely involve more work. Keep in mind that superposition is based on linearity.

**Example 4.2:** Use the superposition theorem to find  $v$  in the circuit in Fig. 4.2.

**Solution:**

Since there are two sources, let

$$v = v_1 + v_2$$

where  $v_1$  and  $v_2$  are the contributions due to the 6-V voltage source and the 3-A current source, respectively. To obtain  $v_1$ , we set the current source to zero, as shown in Fig. 4.3(a).

Applying KVL to the loop in Fig. 4.3(a) gives

$$12i_1 - 6 = 0 \Rightarrow i_1 = 0.5 \text{ A}$$

Thus,

$$v_1 = 4i_1 = 2 \text{ V}$$

We may also use voltage division to get  $v_1$  by writing

$$v_1 = \frac{4}{4+8}(6) = 2 \text{ V}$$

To get  $v_2$ , we set the voltage source to zero, as in Fig. 4.3(b).

Using current division,

$$i_3 = \frac{8}{4+8}(3) = 2 \text{ A}$$

Hence,  $v_2 = 4i_3 = 8 \text{ V}$

And we find  $v = v_1 + v_2 = 2 + 8 = 10 \text{ V}$

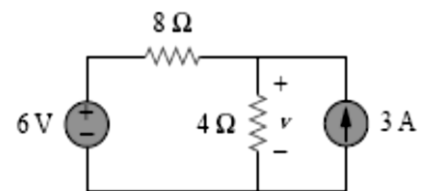


Fig. 4.2: For Example 4.2.

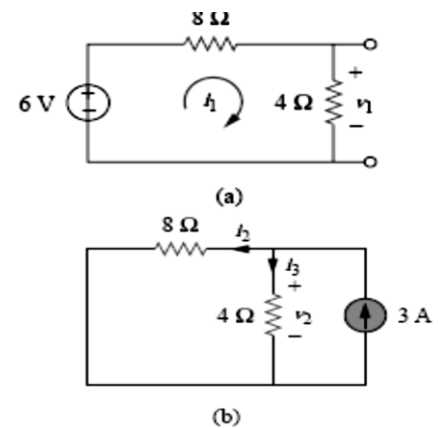


Fig. 4.3: For Example 4.2: (a) calculating  $v_1$ , (b) calculating  $v_2$ .

### 4.4 Source Transformation

We have noticed that series-parallel combination and wye-delta transformation help simplify circuits. Source transformation is another tool for simplifying circuits. We can substitute a voltage source in series with a resistor for a current source in parallel with a resistor, or vice versa, as shown in Fig. 4.4. Either substitution is known as a *source transformation*.

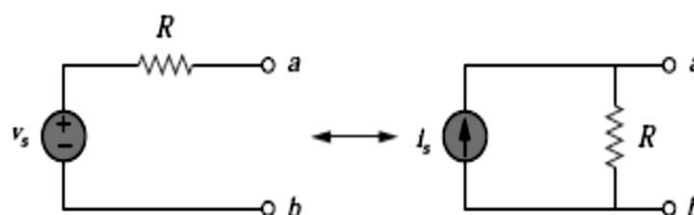


Fig. 4.4: Transformation of independent sources.

**Key Point:** A source transformation is the process of replacing a voltage source  $v_s$  in series with a resistor  $R$  by a current source  $i_s$  in parallel with a resistor  $R$ , or vice versa.

We need to find the relationship between  $v_s$  and  $i_s$  that guarantees the two configurations in **Fig. 4.4** are equivalent with respect to nodes **a, b**.

Suppose  $R_L$  is connected between nodes **a, b** in **Fig. 4.4(a)**. Using Ohms law, the current in  $R_L$  is.

$$i_L = \frac{v_s}{(R+R_L)} \quad \mathbf{R \text{ and } R_L \text{ in series}} \quad (4.5)$$

If it is to be replaced by a current source then load current must be  $\frac{v}{(R+R_L)}$


Now suppose the same resistor  $R_L$  is connected between nodes **a, b** in **Fig. 4.4 (b)**. Using current division, the current in  $R_L$  is

$$i_L = i_s \frac{R}{(R+R_L)} \quad (4.6)$$

If the two circuits in **Fig. 4.4** are equivalent, these resistor currents must be the same. Equating the right-hand sides of **Eqs.4.5** and **4.6** and simplifying

$$i_s = \frac{v_s}{R} \text{ or } v_s = i_s R \quad (4.7)$$

Source transformation also applies to dependent sources, provided we carefully handle the dependent variable. As shown in **Fig. 4.5**, a dependent voltage source in series with a resistor can be transformed to a dependent current source in parallel with the resistor or vice versa.

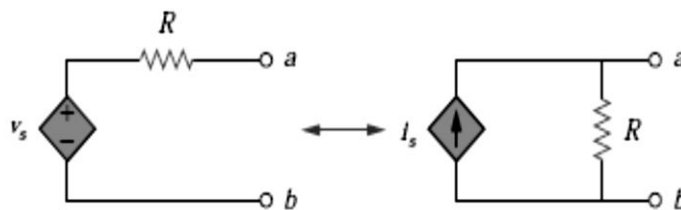

**Fig. 4.5:** Transformation of dependent sources.

However, we should keep the following points in mind when dealing with source transformation.

1. Note from **Fig. 4.4** (or **Fig. 4.5**) that the arrow of the current source is directed toward the positive terminal of the voltage source.

2. Note from Eq. (4.7) that source transformation is not possible when  $\mathbf{R} = \mathbf{0}$ , which is the case with an ideal voltage source. However, for a practical, nonideal voltage source,  $\mathbf{R} \neq \mathbf{0}$ . Similarly, an ideal current source with  $\mathbf{R} = \infty$  cannot be replaced by a finite voltage source.

**Example 4.3:** Use source transformation to find  $v_o$  in the circuit in Fig. 4.6.

**Solution:**

We first transform the current and voltage sources to obtain the circuit in Fig. 4.7(a). Combining the 4- $\Omega$  and 2- $\Omega$  resistors in series and transforming the 12-V voltage source gives us Fig. 4.7(b). We now combine the 3- $\Omega$  and 6- $\Omega$  resistors in parallel to get 2- $\Omega$ . We also combine the 2-A and 4-A current sources to get a 2-A source. Thus, by repeatedly applying source transformations, we obtain the circuit in Fig. 4.7(c).

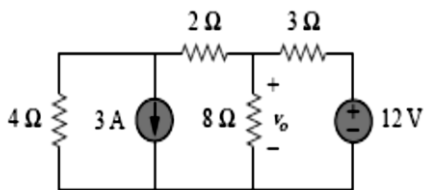


Fig. 4.6

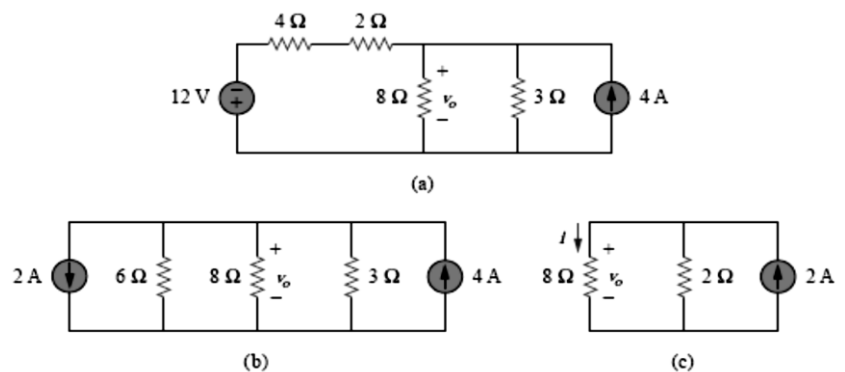


Fig. 4.7

Alternatively, since the 8- $\Omega$  and 2- $\Omega$  resistors in Fig. 4.7(c) are in parallel, they have the same voltage  $v_o$  across them. Hence,

$$v_o = (8||2)(2 \text{ A}) = \frac{8 \times 2}{10} (2) = 3.2 \text{ V}$$

## 4.5 Thevenin's Theorem


It often occurs in practice that a particular element in a circuit is variable (usually called the load) while other elements are fixed. As a typical example, a household outlet terminal may be connected to different appliances constituting a variable load. Each time the variable element is changed, the entire circuit has to be analyzed all over again. To avoid this problem, Thevenin's theorem provides a technique by which the fixed part of the circuit is replaced by an equivalent circuit.

According to Thevenin's theorem, the linear circuit in **Fig. 4.8(a)** can be replaced by that in **Fig. 4.8(b)** is known as the Thevenin equivalent circuit; it developed in 1883 by M. Leon Thevenin (1857–1926), French telegraph engineer.


Thevenin's theorem states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a voltage source  $V_{Th}$  in series with a resistor  $R_{Th}$ , where  $V_{Th}$  is the open-circuit voltage at the terminals and  $R_{Th}$  is the input or equivalent resistance at the terminals when the independent sources are turned off.

To find the Thevenin equivalent voltage  $V_{Th}$  and resistance  $R_{Th}$ , suppose the two circuits in **Fig. 4.8** are equivalent. the open-circuit voltage across the terminals a-b in **Fig. 4.8(a)** must be equal to the voltage source  $V_{Th}$  in **Fig. 4.8(b)**, since the two circuits are equivalent. Thus  $V_{Th}$  is the open-circuit voltage across the terminals as shown in **Fig. 4.9(a)**; that is,

$$V_{Th} = v_{oc} \tag{4.8}$$

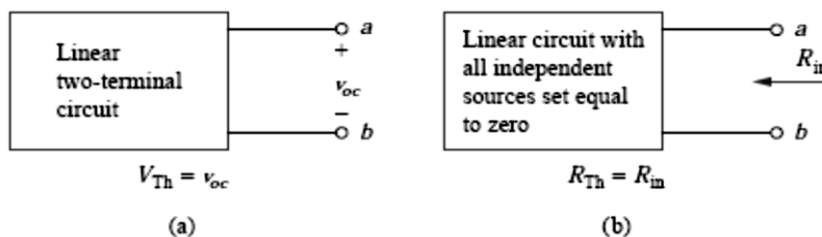

**Fig. 4.9: Finding  $V_{Th}$  and  $R_{Th}$ .**

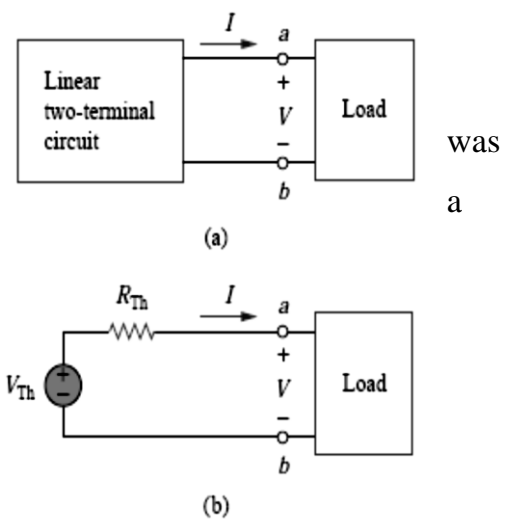

**Fig. 4.8: Replacing a linear two-terminal circuit by its Thevenin equivalent: (a) original circuit, (b) the Thevenin equivalent circuit.**

$R_{Th}$  is the input resistance at the terminals when the independent sources are turned off, as shown in **Fig. 4.9(b)**; that is,

$$R_{Th} = R_{in} \quad (4.9)$$

To apply this idea in finding the Thevenin resistance  $R_{Th}$ , we need to consider two cases.

**CASE 1:** If the network has no dependent sources, we turn off all independent sources.  $R_{Th}$  is the input resistance of the network looking between terminals **a** and **b**, as shown in **Fig. 4.9(b)**.

**CASE 2:** If the network has dependent sources, we turn off all independent sources. As with superposition, dependent sources are not to be turned off because they are controlled by circuit variables. We apply a voltage source  $v_o$  at terminals **a** and **b** and determine the resulting current  $i_o$ . Then  $R_{Th} = v_o/i_o$ , as shown in **Fig. 4.10(a)**. Alternatively, we may insert a current source  $i_o$  at terminals **a-b** as shown in **Fig. 4.10(b)** and find the terminal voltage  $v_o$ . Again  $R_{Th} = v_o/i_o$ .

Either of the two approaches will give the same result. In either approach we may assume any value of  $v_o$  and  $i_o$ . For example, we may use  $v_o = 1$  V or  $i_o = 1$  A, or even use unspecified values of  $v_o$  or  $i_o$ .


It often occurs that  $R_{Th}$  takes a negative value. In this case, the negative resistance ( $v = -iR$ ) implies that the circuit is supplying power. This is possible in a circuit with dependent sources.

The current  $I_L$  through the load and the voltage  $V_L$  across the load are easily determined once the Thevenin equivalent of the circuit at the load's terminals is obtained, as shown in **Fig. 4.11(b)**. From **Fig. 4.11(b)**, we obtain

$$I_L = \frac{V_{Th}}{R_{Th} + R_L} \quad (4.10a)$$

$$V_L = R_L I_L = \frac{R_L}{R_{Th} + R_L} V_{Th} \quad (4.10b)$$

Note from **Fig. 4.11(b)** that the Thevenin equivalent is a simple voltage divider, yielding  $V_L$  by mere inspection.

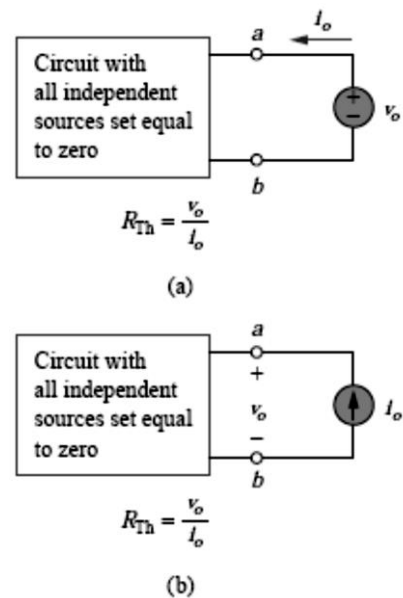

**Fig. 4.10:** Finding  $R_{Th}$  when circuit has dependent sources.

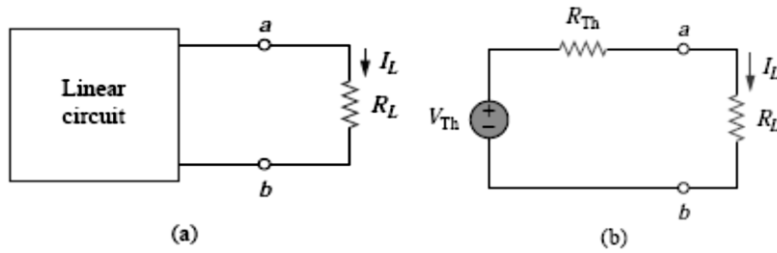


Fig. 4.11: A circuit with a load : (a) original circuit, (b) Thevenin equivalent.

**Example 4.4:** Find the Thevenin equivalent circuit of the circuit shown in Fig. 4.12, to the left of the terminals a-b. Then find the current through  $R_L = 6, 16, \text{ and } 36 \Omega$ .

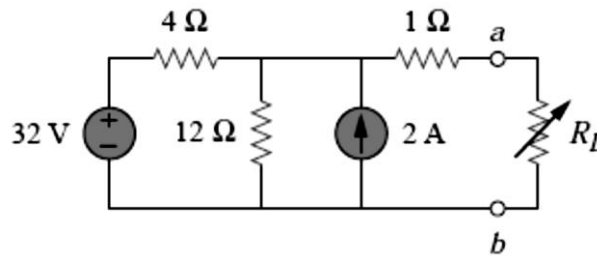


Fig. 4.12: For Example 4.4.

**Solution:**

We find  $R_{Th}$  by turning off the 32-V voltage source (replacing it with a short circuit) and the 2-A current source (replacing it with an open circuit). The circuit becomes what is shown in Fig. 4.13(a). Thus,

$$R_{Th} = 4 \parallel 12 + 1 = \frac{4 \times 12}{16} + 1 = 4 \Omega$$

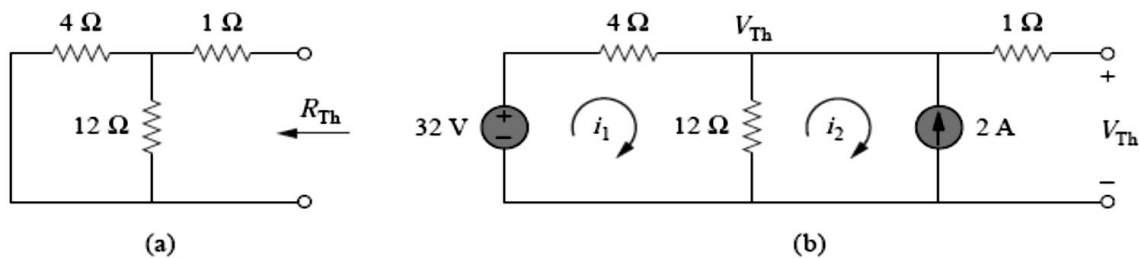


Fig. 4.13: For Example 4.4: (a) finding  $R_{Th}$ , (b) finding  $V_{Th}$ .

To find  $V_{Th}$ , consider the circuit in Fig. 4.13(b). Applying mesh analysis to the two loops, we obtain

$$-32 + 4i_1 + 12(i_1 - i_2) = 0, \quad i_2 = -2 \text{ A}$$

Solving for  $i_1$ , we get  $i_1 = 0.5 \text{ A}$ . Thus,

$$V_{Th} = 12(i_1 - i_2) = 12(0.5 + 2.0) = 30 \text{ V}$$




The Thevenin equivalent circuit is shown in **Fig. 4.14**. The current through  $R_L$  is

$$I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{30}{4 + R_L}$$

When  $R_L = 6$ ,  $I_L = \frac{30}{10} = 3 A$

When  $R_L = 16$ ,  $I_L = \frac{30}{20} = 1.5 A$

When  $R_L = 36$ ,  $I_L = \frac{30}{40} = 0.75 A$

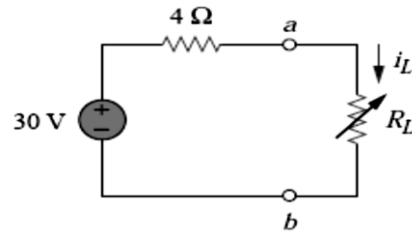


**Fig. 4.14:** The Thevenin equivalent circuit

### 4.6 Norton's Theorem

In 1926, about 43 years after Thevenin published his theorem, E. L. Norton, an American engineer at Bell Telephone Laboratories, proposed a similar theorem.

Norton's theorem states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a current source  $I_N$  in parallel with a resistor  $R_N$ , where  $I_N$  is the short-circuit current through the terminals and  $R_N$  is the input or equivalent resistance at the terminals when the independent sources are turned off.

Thus, the circuit in **Fig. 4.15(a)** can be replaced by the one in **Fig. 4.15(b)**.

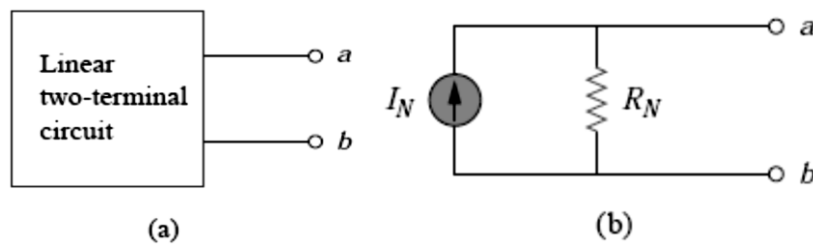

**Fig. 4.15:** (a) Original circuit, (b) Norton equivalent circuit.

We are mainly concerned with how to get  $R_N$  and  $I_N$ . We find  $R_N$  in the same way we find  $R_{Th}$ . In fact, the Thevenin and Norton resistances are equal; that is,

$$R_N = R_{Th} \tag{4.11}$$

To find the Norton current  $I_N$ , we determine the short-circuit current flowing from terminal a to b in both circuits in **Fig. 4.15**. It is evident that the short-circuit current in **Fig. 4.15(b)** is  $I_N$ . This must be the same short-circuit current from terminal a to b in **Fig. 4.15(a)**, since the two circuits are equivalent. Thus,

$$I_N = i_{sc} \tag{4.12}$$

Dependent and independent sources are treated the same way as in Thevenin's theorem. Observe the close relationship between Norton's and Thevenin's theorems:  $R_N = R_{Th}$  as in Eq. (4.11), and

$$I_N = \frac{V_{Th}}{R_{Th}} \quad (4.13)$$

This is essentially source transformation. For this reason, source transformation is often called Thevenin-Norton transformation.

We can calculate any two of the three using the method that takes the least effort and use them to get the third using Ohm's law. **Example 4.10** will illustrate this. Also, since

$$V_{Th} = v_{oc} \quad (4.14a)$$

$$I_N = i_{sc} \quad (4.14b)$$

$$R_{Th} = \frac{v_{oc}}{i_{sc}} = R_N \quad (4.14c)$$

the open-circuit and short-circuit tests are sufficient to find any Thevenin or Norton equivalent.

**Example 4.5** Find the Norton equivalent circuit of the circuit in Fig. 4.16.

**Solution:**

We find  $R_N$  in the same way we find  $R_{Th}$  in the Thevenin equivalent circuit. Set the independent sources equal to zero. This leads to the circuit in Fig. 4.17(a), from which we find  $R_N$ .

Thus,

$$R_N = 5 \parallel (8 + 4 + 8) = 5 \parallel 20 = \frac{20 \times 5}{25} = 4 \Omega$$

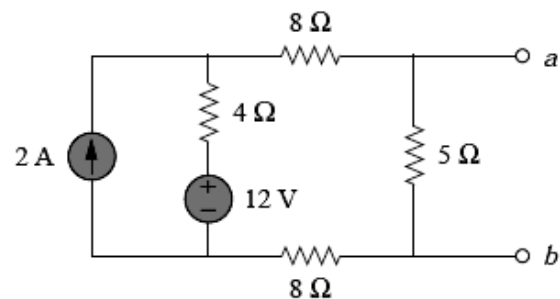


Fig. 4.16: For Example 4.5.

To find  $I_N$ , we short-circuit terminals a and b, as shown in Fig. 4.17(b). We ignore the 5-Ω resistor because it has been short-circuited. Applying mesh analysis, we obtain

$$i_1 = 2 \text{ A}, \quad 20i_2 - 4i_1 - 12 = 0$$

From these equations, we obtain

$$i_2 = 1 \text{ A} = i_{sc} = I_N$$

Alternatively, we may determine  $I_N$  from  $V_{Th}/R_{Th}$ . We obtain  $V_{Th}$  as the open-circuit voltage across terminals a and b in Fig. 4.17(c). Using mesh analysis, we obtain

$$i_3 = 2 \text{ A}$$

$$25i_4 - 4i_3 - 12 = 0 \Rightarrow i_4 = 0.8 \text{ A}$$

and

$$v_{oc} = V_{Th} = 5i_4 = 4 \text{ V}$$

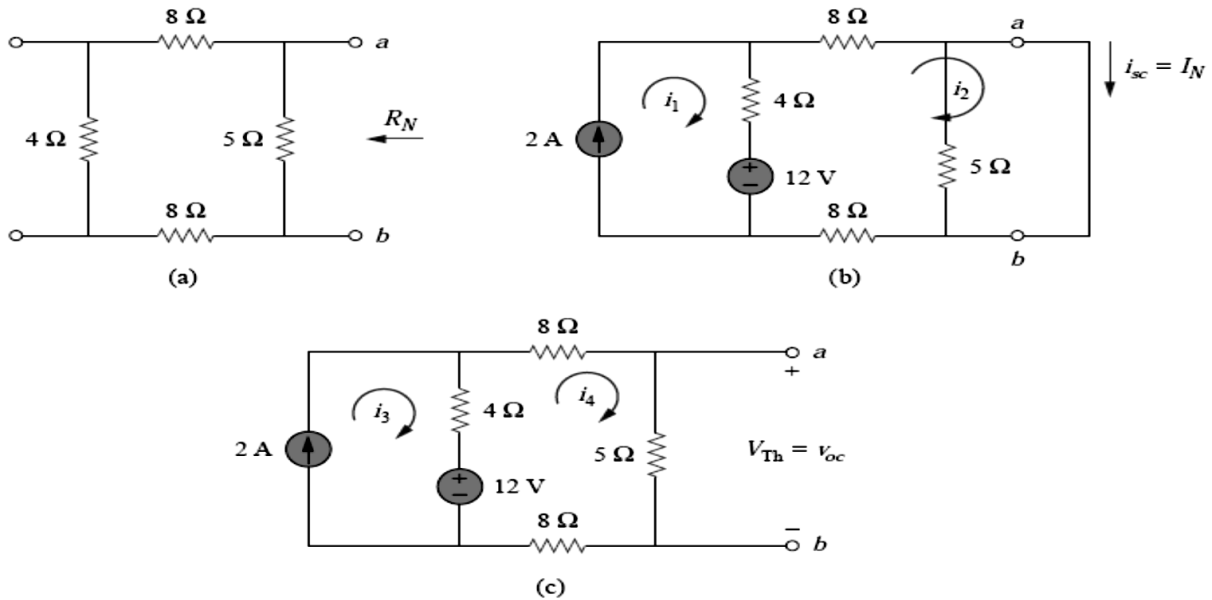


Fig. 4.17: For Example 4.5; finding: (a)  $R_N$ , (b)  $I_N = i_{sc}$ , (c)  $V_{Th} = v_{oc}$ .

Hence,

$$I_N = \frac{V_{Th}}{R_{Th}} = \frac{4}{4} = 1 \text{ A}$$

as obtained previously. This also serves to confirm Eq. that  $R_{Th} = v_{oc}/i_{sc} = 4/1 = 4 \Omega$ . Thus, the Norton equivalent circuit is as shown in Fig. 4.18.

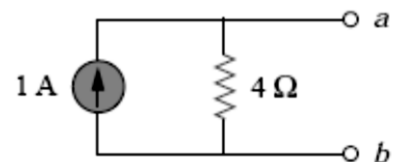
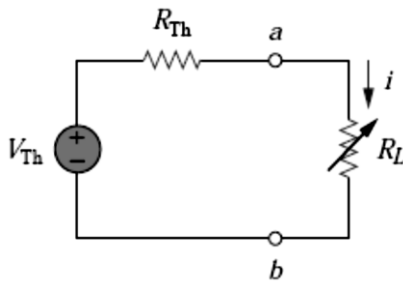


Fig. 4.18: Norton equivalent of the circuit in Fig. 4.16.

### 4.7 Maximum Power Transfer

In many practical situations, a circuit is designed to provide power to a load. While for electric utilities, minimizing power losses in the process of transmission and distribution is critical for efficiency and economic reasons, there are other applications in areas such as communications where it is desirable to maximize the power delivered to a load. We now address the problem of delivering the maximum power to a load when given a system with known internal losses.

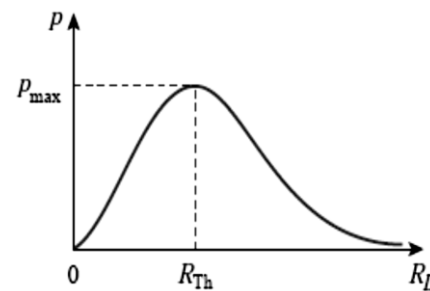


**Fig. 4.19:** The circuit used for maximum power transfer.

For a given circuit,  $V_{Th}$  and  $R_{Th}$  are fixed. By varying the load resistance  $R_L$ , the power delivered to the load varies as sketched in **Fig. 4.20**. We notice from **Fig. 4.20** that the power is small for small or large values of  $R_L$  but maximum for some value of  $R_L$  between  $0$  and  $\infty$ . We now want to show that this maximum power occurs when  $R_L$  is equal to  $R_{Th}$ . This is known as the maximum power theorem.

The Thevenin equivalent is useful in finding the maximum power a linear circuit can deliver to a load. We assume that we can adjust the load resistance  $R_L$ . If the entire circuit is replaced by its Thevenin equivalent except for the load, as shown in **Fig. 4.19**, the power delivered to the load is

$$p = i^2 R_L = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L \quad (4.15)$$



**Fig. 4.20:** Power delivered to the load as a function of  $R_L$ .

Maximum power is transferred to the load when the load resistance equals the Thevenin resistance as seen from the load ( $R_L = R_{Th}$ ).

To prove the maximum power transfer theorem, we differentiate  $p$  in **Eq. (4.15)** with respect to  $R_L$  and set the result equal to zero. We obtain

$$\frac{dp}{dR_L} = V_{Th}^2 \left[ \frac{(R_{Th} + R_L)^2 - 2R_L(R_{Th} + R_L)}{(R_{Th} + R_L)^4} \right] = V_{Th}^2 \left[ \frac{(R_{Th} + R_L - 2R_L)}{(R_{Th} + R_L)^3} \right] = 0$$

This implies that

$$0 = (R_{Th} + R_L - 2R_L) = (R_{Th} - R_L) \quad (4.16)$$

which yields

$$R_L = R_{Th} \quad (4.17)$$


showing that the maximum power transfer takes place when the load resistance  $R_L$  equals the Thevenin resistance  $R_{Th}$ . We can readily confirm that **Eq. (4.17)** gives the maximum power by showing that  $d^2p/dR_L^2 < 0$ .

The maximum power transferred is obtained by substituting **Eq. (4.17)** into **Eq. (4.15)**, for

$$p_{max} = \frac{V_{Th}^2}{4R_{Th}} \quad (4.18)$$

**Equation (4.18)** applies only when  $R_L = R_{Th}$ . When  $R_L \neq R_{Th}$ , we compute the power delivered to the load using **Eq. (4.15)**.

**Example 4.6:** Find the value of  $R_L$  for maximum power transfer in the circuit of **Fig. 4.21**. Find the maximum power.

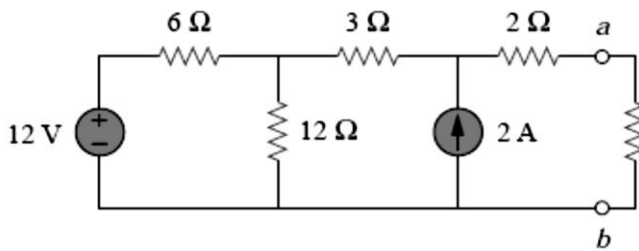


**Fig. 4.21:** For Example 4.6.

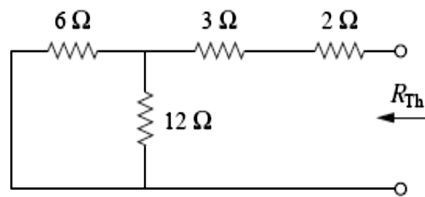
**Solution:**

We need to find the Thevenin resistance  $R_{Th}$  and the Thevenin voltage  $V_{Th}$  across the terminals a-b. To get  $R_{Th}$ , we use the circuit in **Fig. 4.22(a)** and obtain

$$R_{Th} = 2 + 3 + 6 \parallel 12 = 5 + \frac{6 \times 12}{18} = 9 \Omega$$



(a)

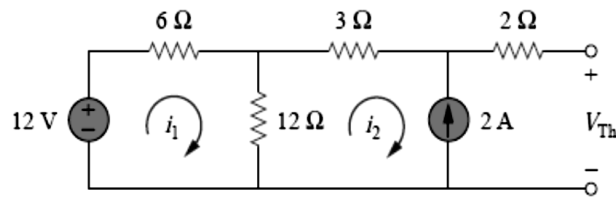

(b)

**Fig. 4.22:** For Example 4.6: (a) finding  $R_{Th}$ , (b) finding  $V_{Th}$ .

To get  $V_{Th}$ , we consider the circuit in **Fig. 4.22(b)**. Applying mesh analysis,

$$-12 + 18i_1 - 12i_2 = 0, \quad i_2 = -2 \text{ A}$$

Solving for  $i_1$ , we get  $i_1 = -2/3$ . Applying **KVL** around the outer loop to get  $V_{Th}$  across terminals a-b, we obtain

$$-12 + 6i_1 + 3i_2 + 2(0) + V_{Th} = 0 \Rightarrow V_{Th} = 22 \text{ V}$$

For maximum power transfer,


$$R_L = R_{Th} = 9 \Omega$$

and the maximum power is

$$P_{max} = \frac{V_{Th}^2}{4R_L} = \frac{22^2}{4 \times 9} = 13.44 \text{ W}$$

### 4.8 Millman's Theorem

Through the application of Millman's theorem, any number of parallel voltage sources can be reduced to one. In **Fig. 4.23**, for example, the three voltage sources can be reduced to one. This would permit finding the current through or voltage across  $R_L$  without having to apply a method such as mesh analysis, nodal analysis, superposition, and so on.

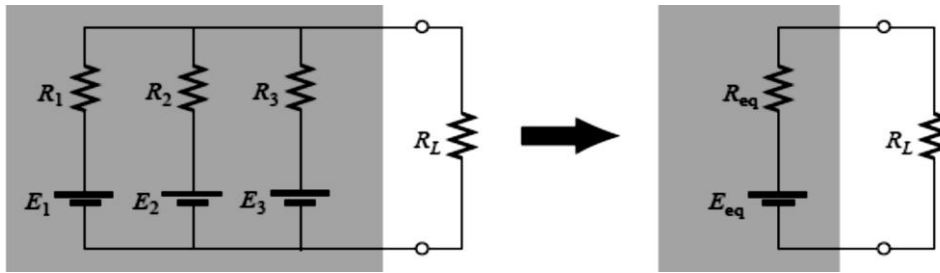

**Fig. 4.23: Demonstrating the effect of applying Millman's theorem.**

In general, Millman's theorem states that for any number of parallel voltage sources,

$$E_{eq} = \frac{\pm \frac{E_1}{R_1} \pm \frac{E_2}{R_2} \pm \frac{E_3}{R_3} \pm \dots \pm \frac{E_N}{R_N}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}} \quad (4.19)$$

and


$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}} \quad (4.20)$$

**Example 4.7:** Using Millman's theorem, find the current through and voltage across the resistor  $R_L$  of **Fig. 4.24**.

**Solution:** By Eq. (4.19),

$$E_{eq} = \frac{+\frac{E_1}{R_1} - \frac{E_2}{R_2} + \frac{E_3}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

The minus sign is used for  $E_2/R_2$  because that supply has the opposite polarity of the other two. The chosen reference direction is therefore that of  $E_1$  and  $E_3$ . The total conductance is unaffected by the direction,

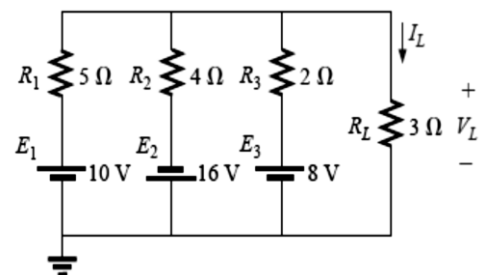


**Fig. 4.24: Example 4.7.**

And

$$E_{eq} = \frac{+\frac{10V}{5\Omega} - \frac{16V}{4\Omega} + \frac{8V}{2\Omega}}{\frac{1}{5\Omega} + \frac{1}{4\Omega} + \frac{1}{2\Omega}} = \frac{2A - 4A + 4A}{0.2 S + 0.25 S + 0.5 S}$$

$$= \frac{2 A}{0.95 S} = 2.105 V$$

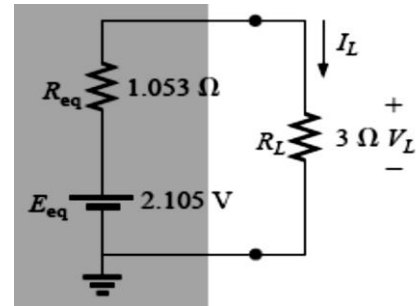

**Fig. 4.25:** The result of applying Millman's theorem to the network of Fig. 4.24.


with  $R_{eq} = \frac{1}{\frac{1}{5\Omega} + \frac{1}{4\Omega} + \frac{1}{2\Omega}} = \frac{1}{0.95 S} = 1.053 \Omega$

The resultant source is shown in **Fig. 4.25**, and

$$I_L = \frac{2.105V}{1.053\Omega + 3\Omega} = \frac{2.105 V}{4.053 \Omega} = 0.519 A$$

with  $V_L = I_L R_L = (0.519 A)(3 \Omega) = 1.557 V$

\*The dual of Millman's theorem appears in **Fig. 4.26**. It can be shown that  $I_{eq}$  and  $R_{eq}$ , as in **Fig. 4.26**, are given by

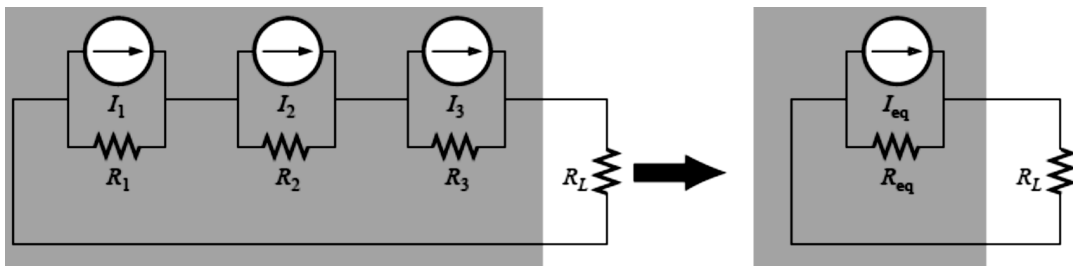

**Fig. 4.26:** The dual effect of Millman's theorem.

$$I_{eq} = \frac{\pm I_1 R_1 \pm I_2 R_2 \pm I_3 R_3}{R_1 + R_2 + R_3} \tag{4.21}$$

And  $R_{eq} = R_1 + R_2 + R_3 \tag{4.22}$


### 4.9 Substitution Theorem

The **substitution theorem** states the following:


**If the voltage across and the current through any branch of a dc bilateral network are known, this branch can be replaced by any combination of elements that will maintain the same voltage across and current through the chosen branch.**

More simply, the theorem states that for branch equivalence, the terminal voltage and current must be the same. Consider the


circuit of **Fig. 4.27**, in which the voltage across and current through the branch a-b are determined. Through the use of the substitution theorem, a number of equivalent a-b branches are shown in **Fig. 4.28**.

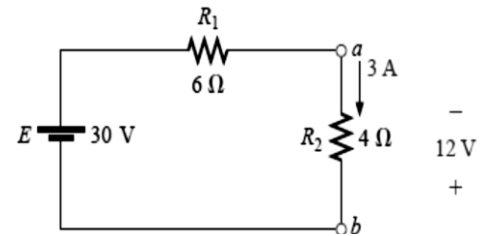

**Fig. 4.27: Demonstrating the effect of the substitution theorem.**

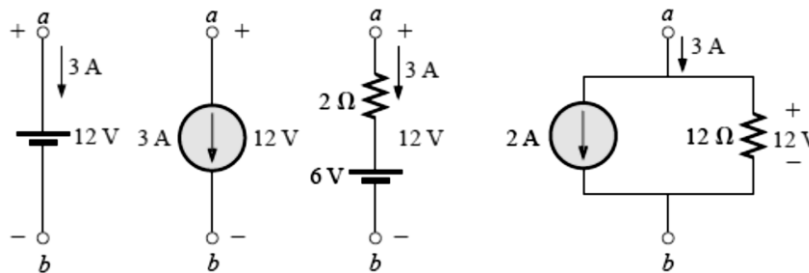

**Fig. 4.28: Equivalent branches for the branch a-b of Fig. 4.27.**

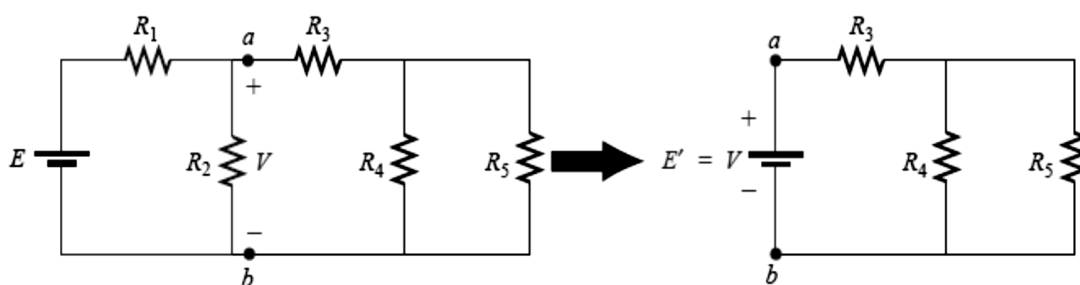


**Fig. 4.29: Demonstrating the effect of knowing a voltage at some point in a complex network.**

As demonstrated by the single-source equivalents of Fig. 4.28, a known potential difference and current in a network can be replaced by an ideal voltage source and current source, respectively. Understand that this theorem cannot be used to solve networks with two or more sources that are not in series or parallel. You will also recall from the discussion of bridge networks that  $V = 0$



and  $I = 0$  were replaced by a short circuit and an open circuit, respectively. This substitution is a very specific application of the substitution theorem.

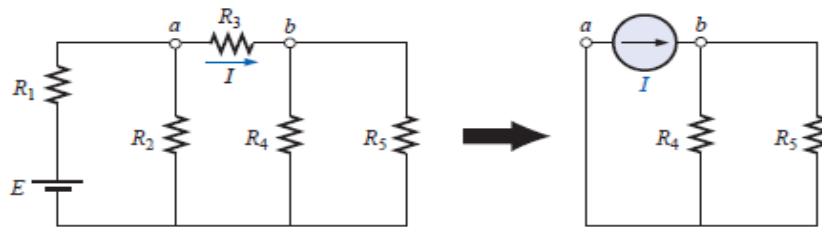

**Fig. 4.30: Demonstrating the effect of knowing a current at some point in a complex network.**


### 4.10 Reciprocity Theorem

The reciprocity theorem is applicable only to single-source networks. It is, therefore, not a theorem employed in the analysis of multisource networks described thus far. The theorem states the following:

***The current  $I$  in any branch of a network, due to a single voltage source  $E$  anywhere else in the network, will equal the current through the branch in which the source was originally located if the source is placed in the branch in which the current  $I$  was originally measured.***

In other words, the location of the voltage source and the resulting current may be interchanged without a change in current. The theorem requires that the polarity of the voltage source have the same correspondence with the direction of the branch current in each position. In the representative network of **Fig. 4.31(a)**, the current  $I$  due to the voltage source  $E$  was determined. If the position of each is interchanged as shown in **Fig.4.31 (b)**, the current  $I$  will be the same value as indicated. To demonstrate the validity of this statement and the theorem, consider the network of **Fig. 4.32**, in which values for the elements of **Fig. 4.31(a)** have been assigned.

The total resistance is

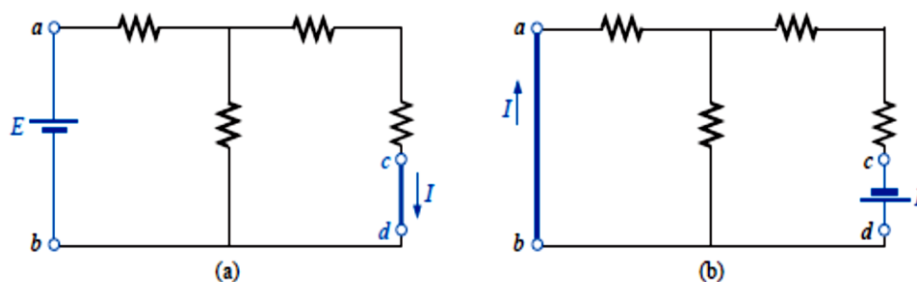


**Fig. 4.31: Demonstrating the impact of the reciprocity theorem.**

$$R_T = R_1 + R_2 \parallel (R_3 + R_4) = 12 \Omega + 6 \Omega \parallel (2 \Omega + 4 \Omega) = 15 \Omega$$

and  $I_S = E/R_T = 45/15 = 3 \text{ A}$

with  $I = 3 \text{ A}/2 = 1.5 \text{ A}$

For the network of **Fig. 4.33**, which corresponds to that of **Fig. 4.31(b)**, we find

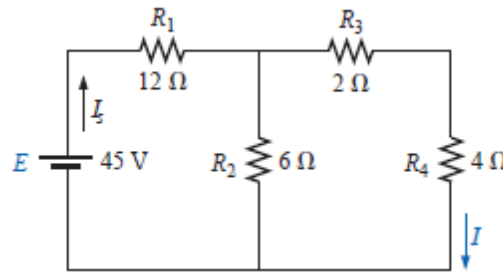

**Fig. 4.32** Finding the current **I** due to a source **E**.


$$R_T = R_4 + R_3 + (R_1 \parallel R_2)$$

$$= 4 + 2 + (12 \parallel 60) = 10 \Omega$$

and  $I_S = \frac{E}{R_T} = \frac{45}{10} = 4.5 \text{ A}$

so that  $I = \frac{4.5 \times 6}{12 + 6} = \frac{4.5}{3} = 1.5 \text{ A}$

which agrees with the above.

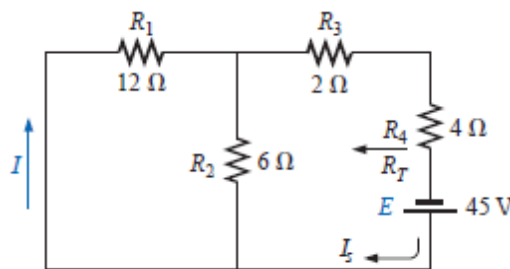

**Fig. 4.33:** Interchanging the location of **E** and **I** of **Fig. 4.31** to demonstrate the validity of the reciprocity theorem.