

***Biothermal physics***

***Ninth lecture***

***Bioelectricity***

***Part II***

***Dr. Nasma Adnan***

***Third Stage***

***Department of medical physics***

***Al-Mustaqbal University-College***


***2021- 2022***

- ✓ **Dielectrics** (i.e. electrical insulators) are materials that are not able to conduct charge.
- ✓ **A capacitance** is a circuit element able to store, and to release, electric charge.
- ✓ It is created by the combination of **conductors** and **dielectrics**. It consists of two conductive plates separated by a dielectric material.
- ✓ The amount of charge (Q) that to store is determined by its **dimensions** and by a **fundamental parameter of the dielectric**:
- ✓ **The permittivity** ( $\epsilon$ , units: C/V.m). Charge stored in the capacitance, at any time, is:

$$Q = CV$$

- ✓ where C is the capacitance value (units: farads, F), the value of the capacitance is:
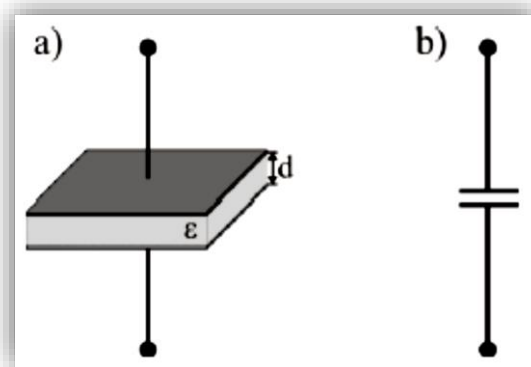
$$C = \epsilon \frac{A}{d} = \epsilon_r \epsilon_0 \frac{A}{d}$$



- ✓ Capacitance. a) simple implementation based on two conductive plates and a dielectric. b) Electrical symbol for a capacitance.
- ✓ where  $\epsilon_0$  is the permittivity of vacuum ( $= 8.9 \times 10^{-12}$  C/V.m),  $\epsilon_r$  is the relative permittivity of the material ( $\epsilon_r = \epsilon / \epsilon_0$ ), A is the area of the plates and d is the distance between the plates.

✓ **Displacement currents**


$$\frac{dQ}{dt} = C \frac{dV}{dt}$$
$$\Downarrow$$
$$I = C \frac{dV}{dt}$$

- ✓ the time derivative of the stored or released charge ( $I=dQ/dt$ ) depends on the time derivative of the voltage, a capacitance acts as a conducting element for fast changing currents.
- ✓ Actual charges do not flow through the capacitance but current appears to do so (i.e. *displacement currents*).
- ✓ **Alternating currents (AC)**, which are currents whose direction reverses cyclically with a specific frequency.
- ✓ For an alternating signal (voltage or current), it can be said that a capacitance behaves similarly to a resistance with a value that depends on the frequency of the signal. The “resistance” of a capacitance (actually its **impedance magnitude**


$$"R_{\text{CAPACITANCE}}" = |Z_C| = \frac{1}{2\pi fC}$$

- ✓ where C is the capacitance value, f is the frequency of the alternating signal and  $\pi$  is the mathematical constant.
- ✓ Note that for *high frequencies* a capacitance will act as a *short circuit* whereas for *low frequencies* it will act as an *open circuit*.
- ✓ capacitances are accompanied by resistances in *series*.
- ✓ Both AC and DC describe types of current flow in a circuit.
- ✓ **Direct Current (DC)**, the electric charge (current) only flows in one direction.
- ✓ **Alternating Current (AC)**, electric charge changes direction periodically.

### Direct Current (DC)

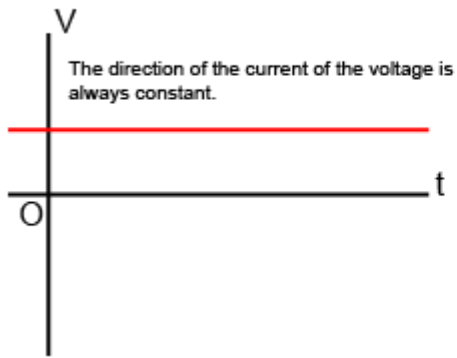

### Alternating Current (AC)

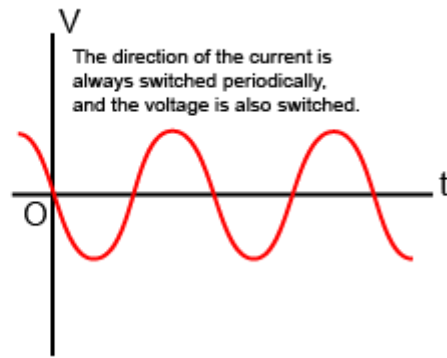

### Types of electric circuit

- ✓ Series Circuit.
- ✓ Parallel Circuit.
- ✓ Series-Parallel Circuits.
- ✓ Open circuit
- ✓ Closed-circuit
- ✓ Short circuit
- ✓ D. C. Circuit
- ✓ A. C. Circuit

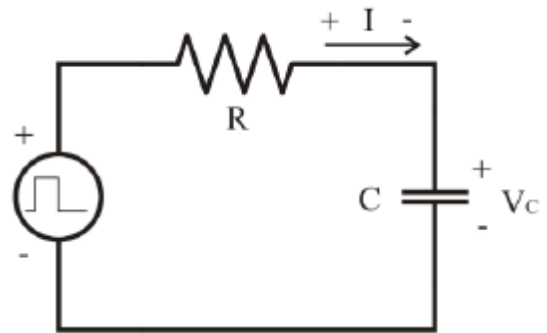


Figure shows what happens when a voltage pulse is applied to a circuit that consists of a resistance in series with a capacitance (*RC circuit*).