



جامعة المستقبل
AL MUSTAQBAL UNIVERSITY



Analogue Electronic

Prof. Dr. Ehssan Al-Bermamy

ihsan.zia@uomus.edu.iq

1st semester

Chapter 3

Special-Purpose Diodes

Lec. 6

The Zener Diode

A Zener diode **is a silicon pn junction device** designed for **operation in the reverse-breakdown region.**

When a diode **reaches reverse breakdown**, its **voltage remains almost constant even though the current changes drastically**, and this is **key** to the zener diode operation.


A major **application** for zener diodes is a **voltage regulator** for **providing stable reference voltages** for **power supplies, voltmeters**, and **other** instruments.

The symbol for a Zener diode is shown in Figure 1.

Cathode (K)



Anode (A)

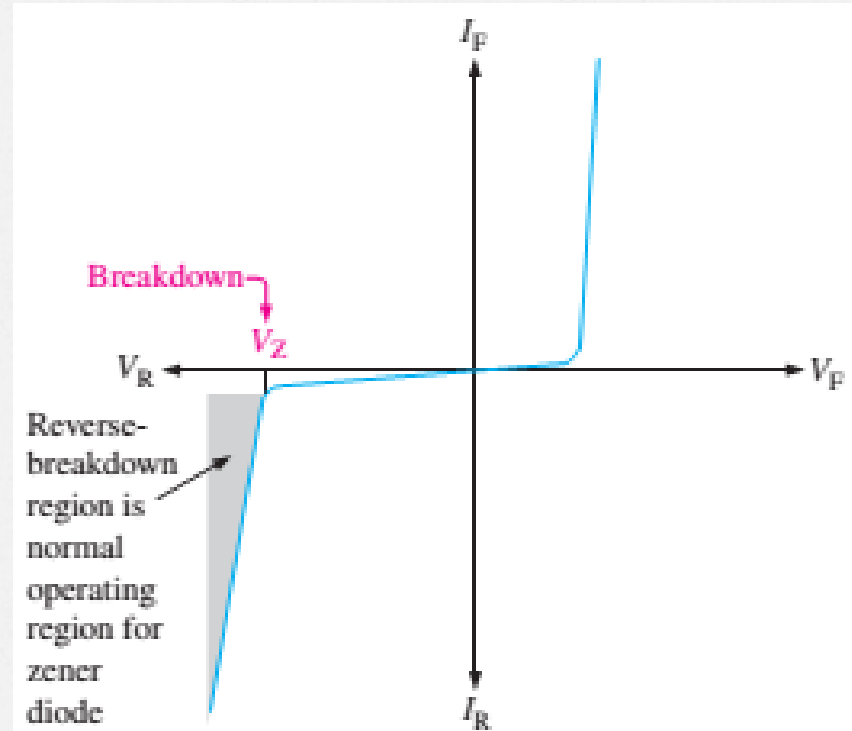

Forward Bias

Zener diodes with **breakdown voltages** of **less than approximately 5V operate** in zener breakdown.

Those with breakdown **voltages greater than approximately 5V** operate mostly in **avalanche breakdown**. Both types are called zener diodes.

Zener has **breakdown voltages** from **less than 1V to more than 250V**.

As the **reverse voltage (V_R)** increases, the **reverse current (I_R)** remains extremely **small up to the knee of the curve**.

Reverse current is also **called** zener current (I_Z).

At the **knee point**, the **breakdown effect begins**, and the **internal zener resistance (Z_Z)** decreases.

The **reverse current** increases **rapidly**. The **zener breakdown (V_Z)** **voltage remains** nearly **constant**.

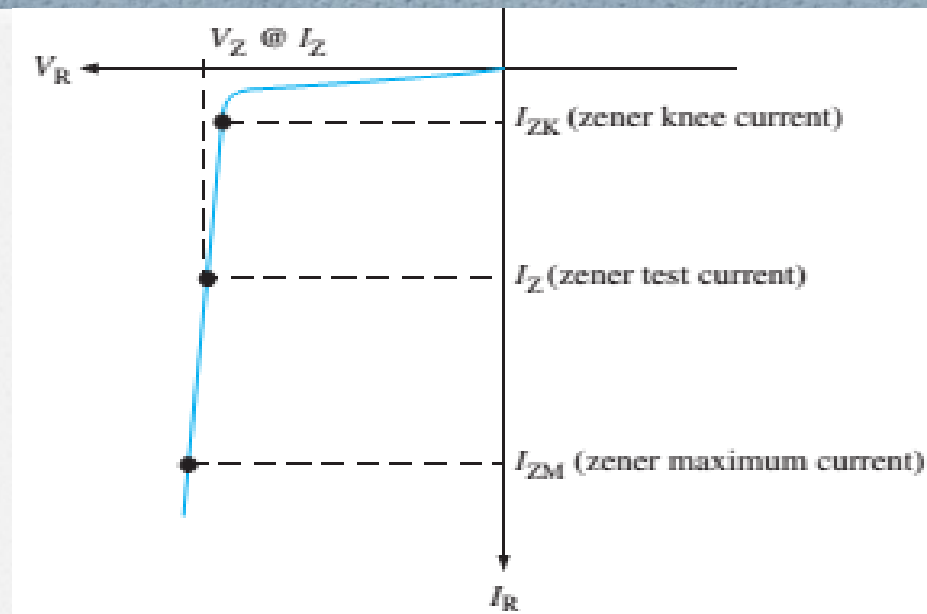



Figure 3: Reverse characteristic of a zener diode.

V_Z is usually specified at **a value of the zener current** known as **the test current**. The **zener impedance**, Z_Z , is the **ratio** of a **change in voltage** in the **breakdown region to the corresponding change in the current**:

$$Z_Z = \frac{\Delta V_Z}{\Delta I_Z}$$

The **zener impedance**, Z_Z , is the **ratio** of a **change in voltage** in the **breakdown region** to **the corresponding change in the current**:

$$Z_Z = \frac{\Delta V_Z}{\Delta I_Z}$$

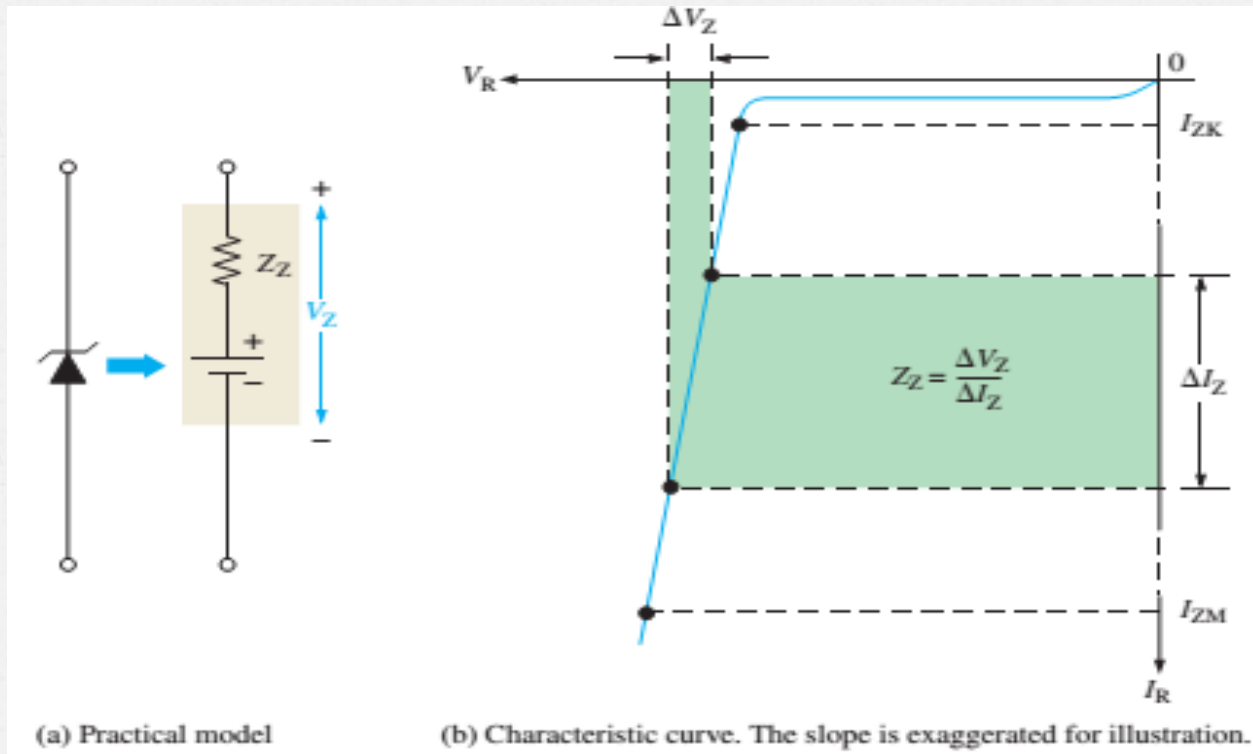

Example 1: What is the zener impedance if the zener diode voltage changes from 4.79 V to 4.94 V when the current changes from 5.00 mA to 10.0 mA? **HW**

Zener Diode Applications

Zener Regulation with a Variable Input Voltage


The zener diode can be used as a **voltage regulator for providing stable reference voltages**, as shown in Figure 5.

The **ability to keep reverse voltage constant across** its terminal is the **key feature of the zener diode**. It maintains **constant voltage** over a **range of reverse current values**.


A **minimum reverse current I_{ZK}** must be maintained to **keep the diode in regulation mode**.

Voltage decreases drastically **if the current is reduced below the knee of the curve**.

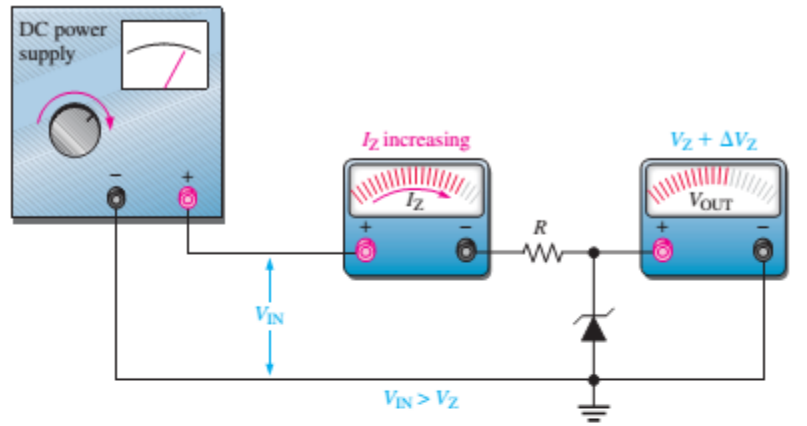Above I_{ZM} , max current, the zener may get damaged permanently.



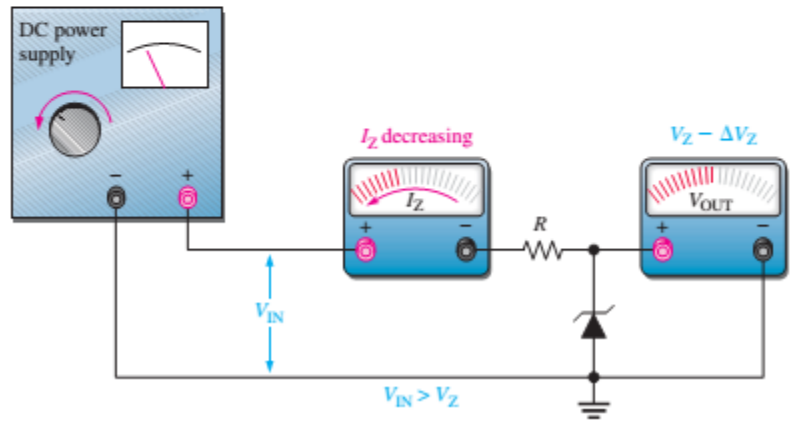(a) As the input voltage increases, the output voltage remains nearly constant ($I_{ZK} < I_Z < I_{ZM}$).




(b) As the input voltage decreases, the output voltage remains nearly constant ($I_{ZK} < I_Z < I_{ZM}$).

Figure 5: Zener regulation of a varying input voltage.

To illustrate **regulation**, let us use the **ideal model of the 1N4740A zener diode** (ignoring the zener resistance) in the circuit of Figure 6.

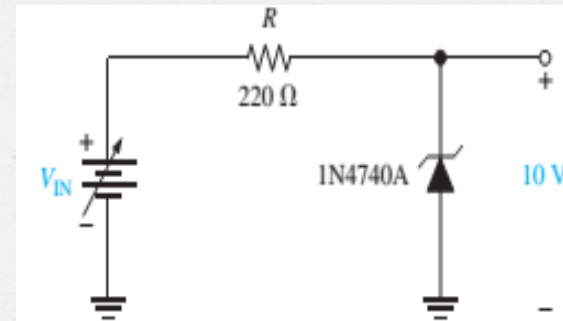- Ideal model of 1N4047A
- $I_{ZK} = 0.25\text{mA}$
- $V_Z = 10\text{V}$
- $P_D(\text{max}) = 1\text{W}$



For the minimum zener current, the voltage across the 220Ω resistor is

$$V_R = I_{ZK}R = (0.25\ \text{mA})(220\Omega) = 55\text{mV},$$

Since $V_{IN} = V_R + V_Z$,

$$V_{IN(\text{min})} = V_R + V_Z = 55\text{mV} + 10\text{V} = 10.055\text{V}$$

For the maximum zener current, the voltage across the 220Ω resistor is

$$V_R = I_{ZM}R = (100\ \text{mA})(220\Omega) = 22\text{V}$$

Therefore, $V_{IN(\text{max})} = 22\text{V} + 10\text{V} = 32\text{V}$

This shows that this **zener diode can ideally regulate an input voltage from 10.055 to 32V and maintain an approximate 10V output.**