



جامعة المستقبل  
AL MUSTAQBAL UNIVERSITY



# Analog Electronics

**Prof. Dr. Ehssan Al-Bermamy**

[ihsan.zia@uomus.edu.iq](mailto:ihsan.zia@uomus.edu.iq)

**1<sup>st</sup> semester**

# **Chapter 3**

# **Special-Purpose Diodes**

## **Lec. 7**

## Zener Regulation with variable load

Figure 1 shows a zener voltage regulator with a **variable load resistor across** the terminals.

The zener diode **maintains a nearly constant voltage across  $R_L$**  as long as the **zener current is greater than  $I_{ZK}$**  and **less than  $I_{ZM}$** .


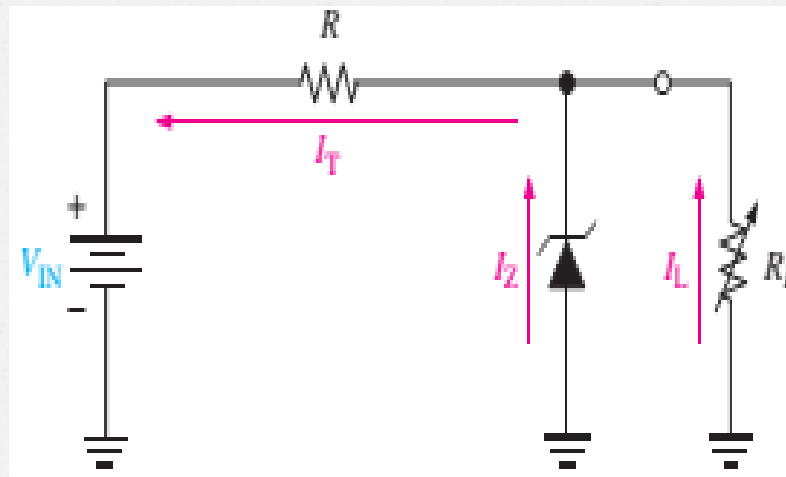


Figure 1: Zener regulation with a variable load.

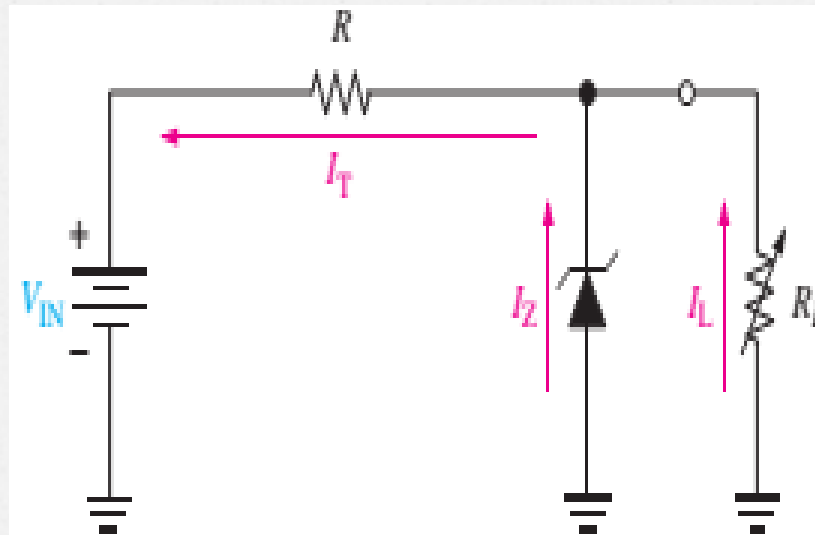



When  $R_L = \infty$  (open-cut), the **load current is zero**, and **all the current passes through the Zener diode**.

The **current is divided** between the **Zener diode and  $R_L$** , when  $R_L$  is connected. The **total current** through  $R$  remains constant **as long as** the Zener is regulated.

As  **$R_L$  decreases**,  **$I_L$  increases**, and  **$I_Z$  decreases**. The Zener continues to regulate the voltage **until  $I_Z$  reaches its minimum value**.

Now, the **load current is maximum**, and a **full-load condition exists**.

## Example:

Determine the **minimum** and the **maximum load currents** for the Zener diode in Figure 3 will maintain regulation. What is the **minimum value of  $R_L$**  that can be used?  $V_Z = 12\text{ V}$ ,  $I_{ZK} = 1\text{ mA}$  and  $I_{ZM} = 50\text{ mA}$ . Assume an ideal Zener diode where  $Z_Z = 0\ \Omega$  and  $V_Z$  remains a constant  $12\text{ V}$  over the range of current values.

### Solution

When  $I_L = 0$ , ( $R_L = \infty$ ),  $I_Z = I_{Z\max} = I_T$

$$I_{(Z(\max))} = I_T = (V_{IN} - V_Z) / R = (24 - 12) / 470 = 25.5\text{ mA}$$

**$R_L$  can be removed** without disturbing regulation if this value is less than  $50\text{ mA}$ .

$$I_{L(\min)} = 0\text{ A}$$


$I_{L(\max)}$  occurs when  $I_Z$  is minimum ( $I_Z = I_{ZK}$ )

$$I_{L(\max)} = I_T - I_{Z(\min)} = 25.5\text{ mA} - 1\text{ mA} = 24.5\text{ mA}$$

The minimum value of  $R_L$  is


$$\mathbf{R_{(L(\min))} = V_Z / I_{(L(\max))} = 12\text{ V} / 24.5\text{ mA} = 490\ \Omega}$$

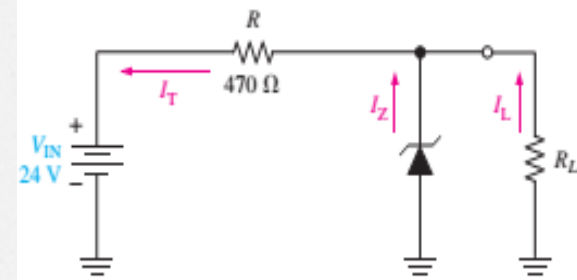Regulation is **maintained** for any value of  $R_L$  **between  $490\ \Omega$  and infinity**.


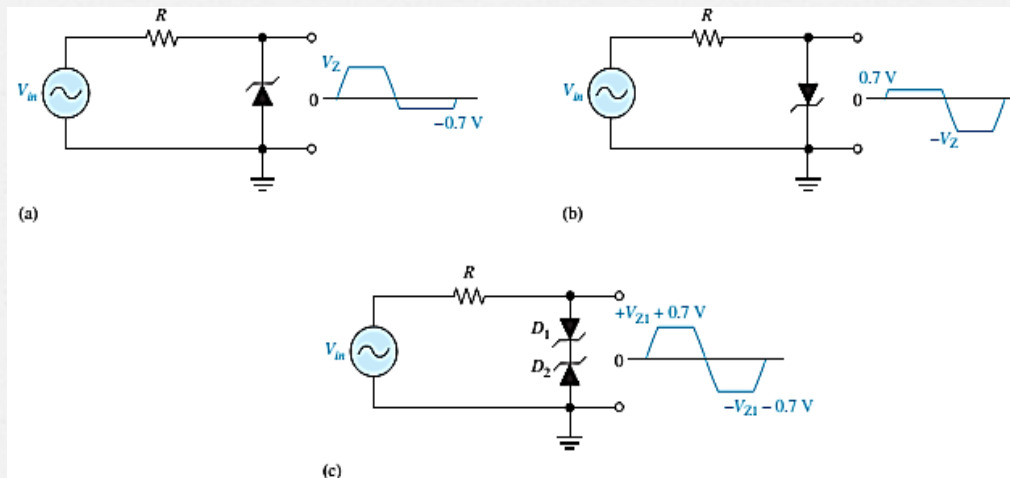
# Zener Limiter

- Zener diodes can be used as **limiters**. Figure 4 shows **three basic ways** the limiting action of a Zener diode can be used.
- During the negative alternation, the Zener acts as a **forward-biased diode and limits the negative voltage to 0.7V**, as in part (A).
- When the Zener is **turned around**, as in part (B), the **negative peak** is limited by Zener action, and the **positive voltage is limited to +0.7V**. **Two back-to-back Zeners limit both peaks to the Zener voltage  $\pm 0.7V$** , as shown in part (C).



- Figure 4: Basic Zener limiting action with a sinusoidal input voltage.




## Varactor Diode

A varactor diode is a special-purpose diode **operated** in **reverse bias** to **form a voltage-controlled capacitor** rather than traditional diodes.

The **applied voltage controls** the **capacitance** and hence the resonant **frequency**. The **width of the depletion region increases** with **reverse bias**.

These devices are commonly **used** in **communication systems**.

Varactor diodes are also referred to as **tuning diodes**.

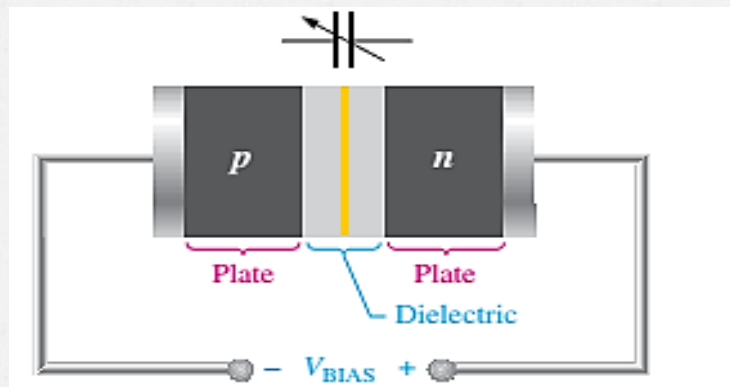

**Figure 5:** The reverse-biased varactor diode acts as a variable capacitor.

# Optical Diodes

This section introduces three types of optoelectronic devices: the light-emitting diode, quantum dots, and the photodiode.

## The Light-Emitting Diode (LED)

Light Emitting Diodes (LEDs), diodes can be **made** to **emit light electroluminescence** or **sense light**.

When the **device** is **forward-biased**, **electrons cross the pn junction from the n-type material and recombine** with **holes** in the **p-type material**.

The **free electrons** are **in the conduction band** and at a higher energy than the **holes in the valence band**.


The **difference in energy between the electrons** and the holes **corresponds to the energy of visible light**.

When **recombination** takes place, the **recombining electrons release energy in the form of photons**.




# Conduction Electrons and Holes

The emitted light tends to be monochromatic (**one color**) depending on the **band gap** (**and other factors**). A **large exposed surface area** on one layer of the semiconductive material **permits the photons to be emitted as visible light**. This process, called **electroluminescence**, is illustrated in Figure 6. LEDs vary widely in **size** and **brightness**—from **small** indicating lights and displays to **high-intensity** LEDs used in **traffic** signals, outdoor **signs**, and general **illumination**.

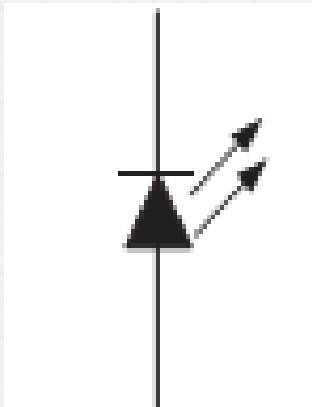

**Figure 6 A:** Symbol for an LED. When forward-biased, it emits light.

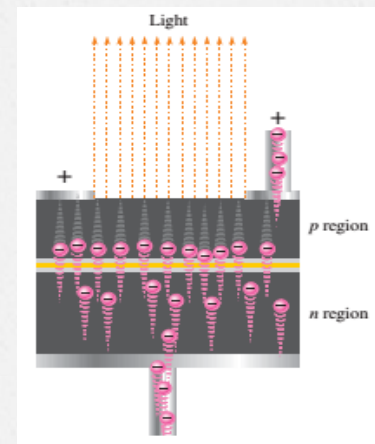

**Figure 6 B:** Electroluminescence in a forward-biased LED.

# The Photodiode

The **photodiode** is a device that **operates in reverse bias**, as shown in Figure 13,

where  $I_{\lambda}$  is the **reverse light current**.

The **photodiode** has a **small transparent window** that **allows light to strike the pn junction**.

A **photodiode** differs from a **rectifier diode** in that the **reverse current** increases with the **light intensity** when its pn junction is **exposed to light**. When **there is no incident light**, the **reverse current,  $I_{\lambda}$** , is almost **negligible** and is called the **dark current**.

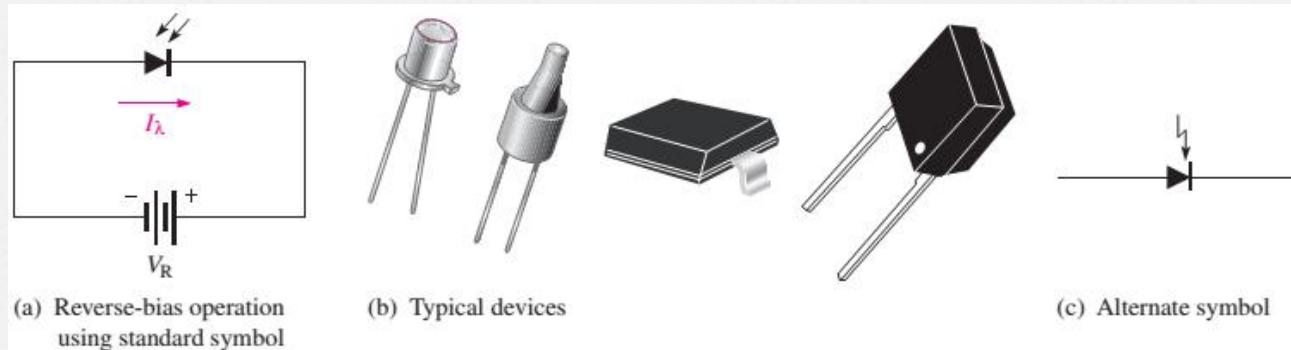


Figure 13:Photodiode.




You are less likely to encounter several types of diodes as a technician. Among these are the **laser diode**, the **Schottky diode**, the **pin diode**, the **step-recovery diode**, the **tunnel diode**, and the **current regulator diode**.

### The Laser Diode

Laser light is **monochromatic**, meaning it **consists of a single color, not** a mixture of colors, compared to incoherent light, which consists of a wide band of wavelengths.

The laser diode normally **emits coherent light**, whereas the **LED emits incoherent light**.

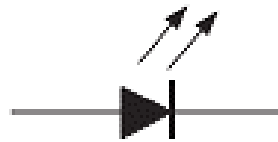

**Figure 14:** Symbol for a Laser Diode.