



جامعة المستقبل  
AL MUSTAQBAL UNIVERSITY



# Analog Electronics

**Prof. Dr. Ehssan Al-Bermamy**

[ihsan.zia@uomus.edu.iq](mailto:ihsan.zia@uomus.edu.iq)

**1<sup>st</sup> semester**

# **Chapter 4**

## **Transistor**

### **Lecture 9**

# Transistor Currents


The **conventional current flows** toward the **arrow** on the **emitter terminal**. The **emitter current** ( $I_E$ ) is the **sum** of the **collector current** ( $I_C$ ) and the **small base current** ( $I_B$ ).

That is,  $I_E = I_C + I_B$

$I_B$  is **very small** compared to  **$I_E$  or  $I_C$** . The capital-letter subscripts indicate DC values.

The **voltage drop** between the **base and emitter** is  $V_{BE}$ , whereas the voltage drop between the **collector and base** is called  $V_{CB}$ .

Figure:  
Transistor currents.

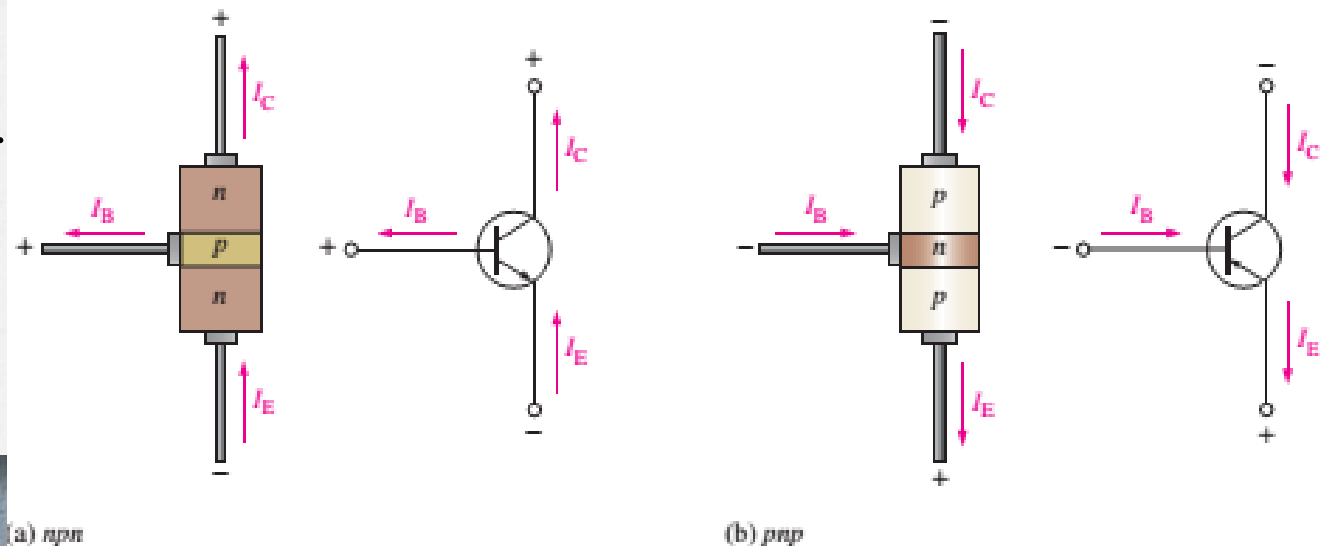




## BJT Characteristics and Parameters

Two important parameters,  $\beta_{DC}$  (DC current gain) and  $\alpha_{DC}$  are used to analyze a BJT circuit.


When a **transistor is connected to DC bias voltages**, as shown in **Figure below** for **both npn and pnp** types,

$V_{BB}$  forward-biases the base-emitter junction, and  $V_{CC}$  reverse-biases the base-collector junction.

Figures of transistor DC bias circuits.

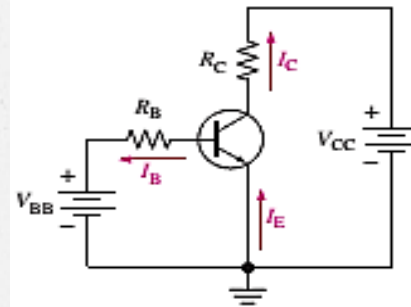

(a) npn

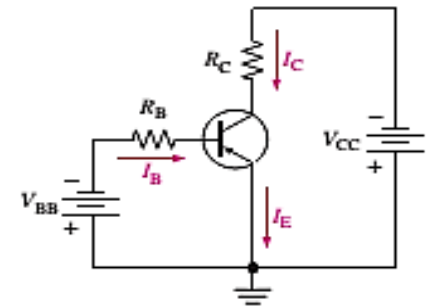

(b) pnp

The **collector current** is directly **proportional** to the **base current**.

$$I_C \propto I_B$$

The  $\beta_{DC}$  of a transistor is the **ratio** of the DC **collector current** ( $I_C$ ) to the **DC base current** ( $I_B$ ).

$$\beta_{DC} = \frac{I_C}{I_B}$$

This equation explains the amplification of current.

The ratio of the **DC collector current** ( $I_C$ ) to the **DC emitter current** ( $I_E$ ) is the ( $\alpha_{DC}$ ).

$\alpha_{DC}$  is always **less than 1**

$$\alpha_{DC} = \frac{I_C}{I_E}$$

## Example

Determine the dc current gain  $\beta_{DC}$  and the emitter current  $I_E$  for a transistor where  $I_B=50\mu\text{A}$  and  $I_C= 3.65 \text{ mA}$ .

### Solution

$$\beta_{DC} = \frac{I_C}{I_B} = \frac{3.65 \text{ mA}}{50 \mu\text{A}} = 73$$

$$I_E = I_C + I_B = 3.65 \text{ mA} + 50\mu\text{A} = 3.70 \text{ mA}$$

# BJT Circuit Analysis

Consider the basic transistor bias circuit configuration in the Figure below. Three transistor DC currents and three DC voltages can be identified.

**$I_B$ : DC base current**

**$I_E$ : DC emitter current**


**$I_C$ : DC collector current**

**$V_{BE}$ : DC voltage across the base-emitter junction**

**$V_{CE}$ : DC voltage across collector-emitter junction**

**$V_{CB}$ : DC voltage across collector-base junction**

**Figure 4: Transistor currents and voltages.**

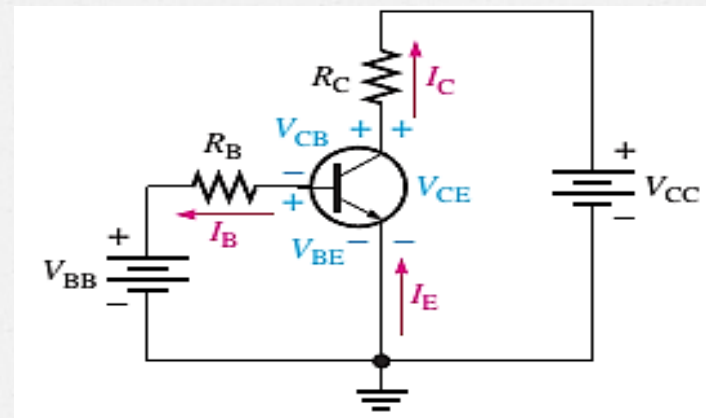



When the base-emitter junction is forward-biased,

It is like a forward-biased diode and has a forward voltage drop of  $V_{BE} \cong 0.7 \text{ V}$

The voltage at the **collector** concerning the grounded emitter is

$$V_{CE} = V_{CC} - I_C R_C \quad (I_C R_C = V_{RC})$$


The current across  $I_B$  is

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} \quad (I_B R_B = V_{RB})$$

The voltage across the **reverse-biased collector-base junction** is

$$V_{CB} = V_{CE} - V_{BE}$$

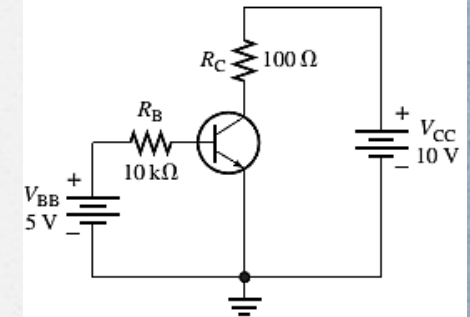**Example: Determine  $I_B$ ,  $I_C$ ,  $I_E$ ,  $V_{BE}$ ,  $V_{CE}$ , and  $V_{CB}$  in the circuit of the following Figure. The transistor has a  $\beta_{DC} = 150$ .**



**Solution:**

**$V_{BE} \cong 0.7$  V, Calculate the base, collector, and emitter currents as follows:**

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5\text{ V} - 0.7\text{ V}}{10\text{ k}\Omega} = 430\ \mu\text{A}$$

$$I_C = \beta_{DC} I_B = (150)(430\ \mu\text{A}) = 64.5\text{ mA}$$

$$I_E = I_C + I_B = 64.5\text{ mA} + 430\ \mu\text{A} = 64.9\text{ mA}$$

Solve for  $V_{CE}$  and  $V_{CB}$ .

$$V_{CE} = V_{CC} - I_C R_C = 10\text{ V} - (64.5\text{ mA})(100\ \Omega) = 10\text{ V} - 6.45\text{ V} = 3.55\text{ V}$$

$$V_{CB} = V_{CE} - V_{BE} = 3.55\text{ V} - 0.7\text{ V} = 2.85\text{ V}$$

**Since the collector is at a higher voltage than the base, the CB junction is reverse-biased.**




## Collector Characteristic Curves

The collector characteristic curves show **three modes** of operation of the transistor. The collector current  $I_C$  variation varies with the  $V_{CE}$  for a specified value of base current  $I_B$ .

Assume that  $V_{BB}$  is set to produce a certain value of  $I_B$ ,  $V_{CC}$  is zero, and  $V_{CE}$  is zero. As  $V_{CE}$  is increased,  $I_C$  increases until  $I_B$  becomes constant. When both BE, and BC junctions are forward biased, and **the transistor is in the saturation region.**

Figure : Collector characteristic curves.

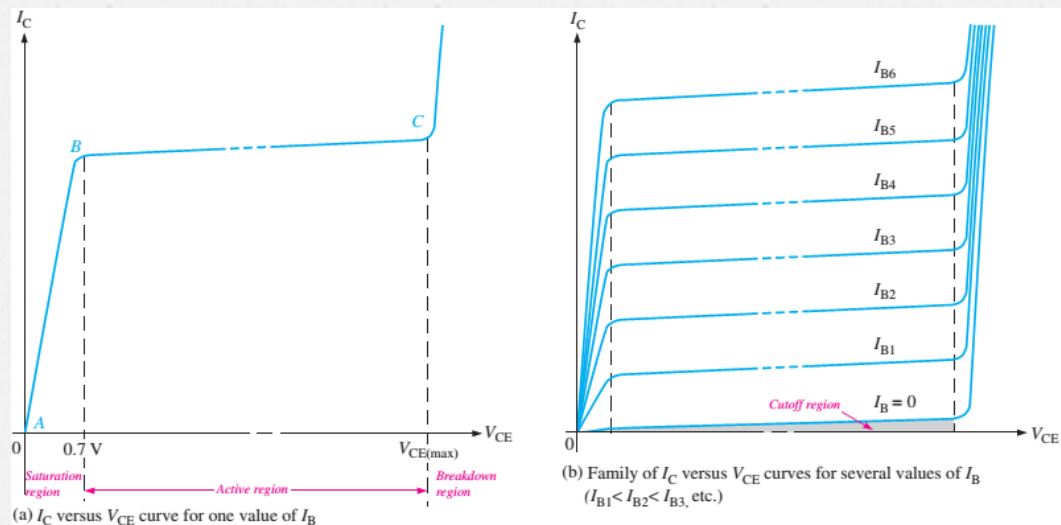

**In saturation**, an increase in **base current** does not affect **the collector current**, and the relation  $I_C = \beta_{DC} I_B$  is no longer valid.

$$I_{C(SAT)} = \frac{V_{CC} - V_{CE(SAT)}}{R_C}$$

The transistor current is maximum, and the voltage across the collector is minimum for a given load.

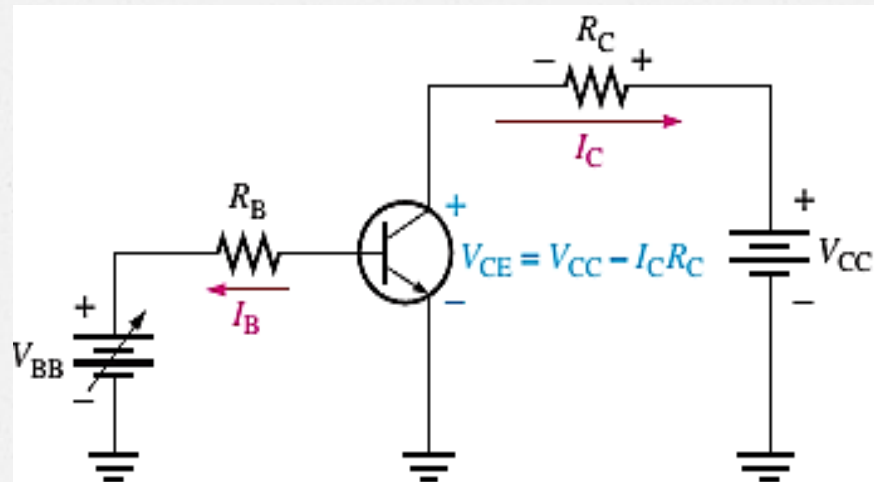


Figure : Base-emitter and base-collector junctions are forward-biased.



When  $V_{CE}$  is increased further and exceeds **0.7 V**, the **base-collector junction becomes reverse-biased**, and the **transistor goes into its operation's active, or linear, region**.

$I_C$  **levels off** and remains essentially **constant** for a given value of  $I_B$  as  $V_{CE}$  continues to increase. The value of  $I_C$  is determined only by the relationship expressed as  $I_C = \beta_{DC} I_B$ .

A family of collector characteristic curves is produced when  $I_C$  versus  $V_{CE}$  is plotted for several values of  $I_B$ , as illustrated in Figure below. It can be read from the curves. **The value of  $\beta_{DC}$  is nearly the same** wherever it is read in the active region. In a **BJT, the cutoff is the condition of no base current ( $I_B=0$ )**, which results in only an extremely small leakage current ( $I_{CEO}$ ) in the collector circuit.

The subscript CEO represents collector to emitter with the base open. For practical work, **this current is assumed to be zero**. In **cutoff**, **neither the BE junction nor the BC junction is forward-biased**.


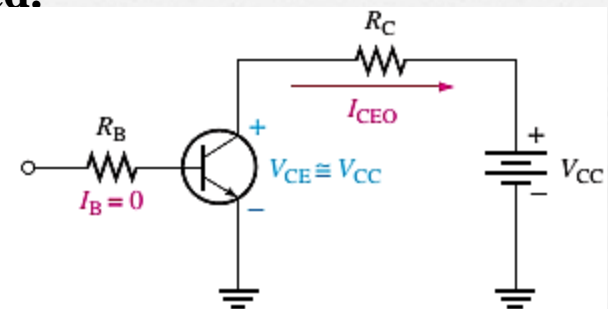


Figure: Cutoff: Base-emitter and base-collector junctions are reverse-biased.

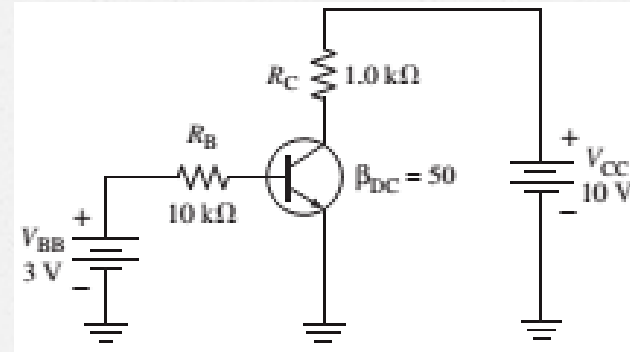

## Example:

Determine whether or not the transistor in the following figure is in saturation. Assume  $V_{CE(\text{sat})} = 0.2\text{V}$ .



### Solution:

First, determine  $I_{C(\text{sat})}$ .

$$I_{C(\text{sat})} = \frac{V_{CC} - V_{CE(\text{sat})}}{R_C} = \frac{10\text{V} - 0.2\text{V}}{1.0\text{k}\Omega} = \frac{9.8\text{V}}{1.0\text{k}\Omega} = 9.8\text{mA}$$

Now, see if  $I_B$  is large enough to produce  $I_{C(\text{sat})}$ .

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{3\text{V} - 0.7\text{V}}{10\text{k}\Omega} = \frac{2.3\text{V}}{10\text{k}\Omega} = 0.23\text{mA}$$

$$I_C = \beta_{DC} I_B = (50)(0.23\text{mA}) = 11.5\text{mA}$$

This shows that with the specified  $\beta_{DC}$ , this base current can produce an  $I_C$  greater than  $I_{C(\text{sat})}$ . Therefore, **the transistor is saturated.**

## The BJT as a Switch

A BJT can be used as a switching device in logic circuits to turn on or off the current to a load. As a switch, the transistor is normally in either cutoff (load is OFF) or saturation (load is ON).

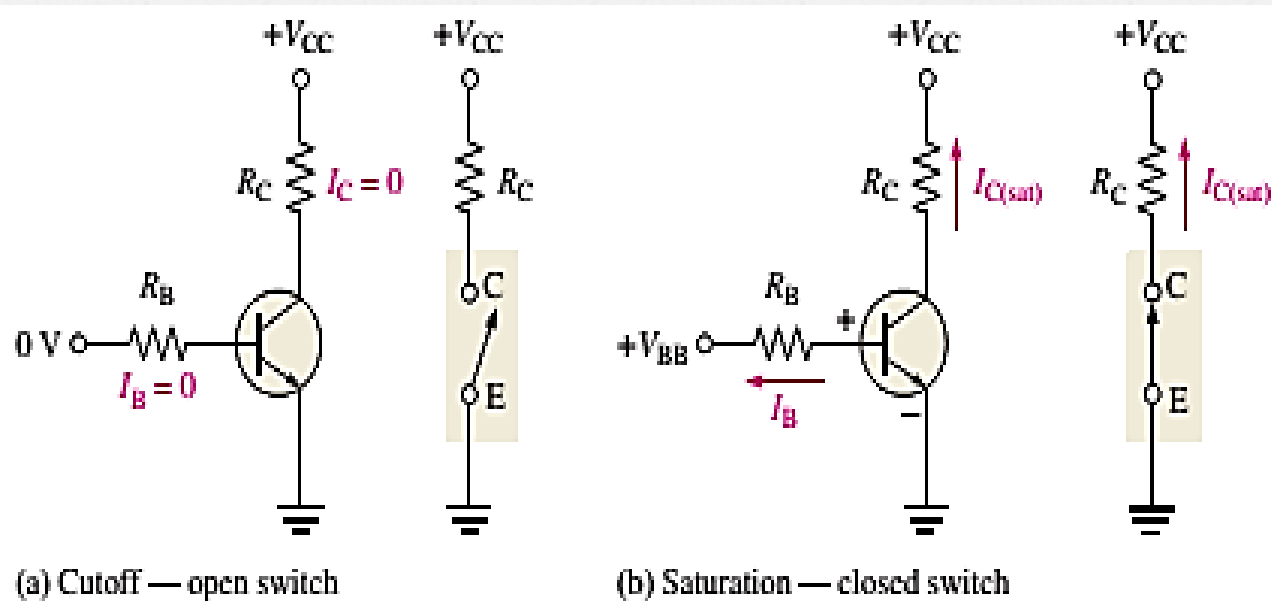


Figure: Switching action of an ideal transistor.