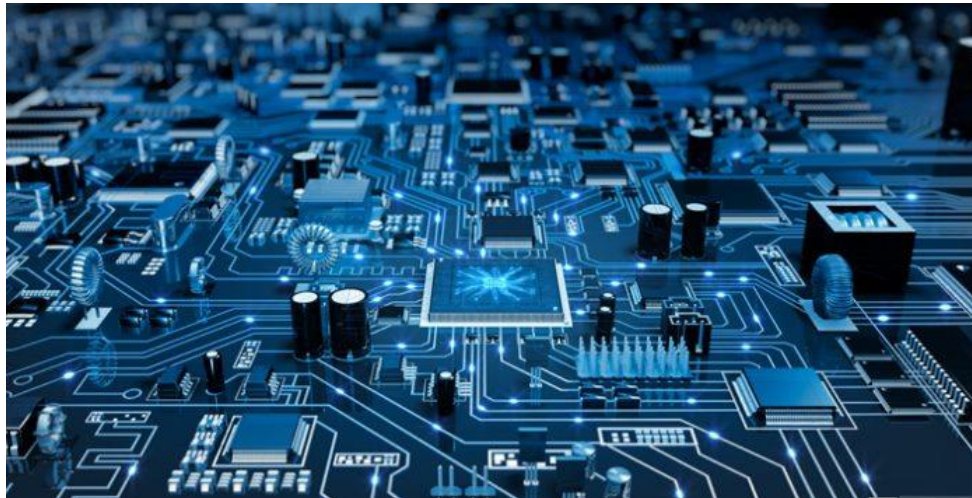


**Ministry of high Education and Scientific Research  
Middle Technical University  
Electrical Engineering Technical College  
Medical Instrumentation Techniques Engineering**

## **Module 4**

# **Regulated Power Supplies (Part 3)**

For  
Students of the Third Stage  
Department of Medical Instrumentation Techniques Engineering



**By**

Ali Abdulelah Al-Naji  
Dep. Medical Instrumentation  
Techniques Engineering

2024

## 1. Overview

### a. Target population:

This educational module is intended for third-class students enrolled in the Department of Medical Instrumentation Techniques Engineering at the Electrical Engineering Technical College, Middle Technical University in Baghdad, Iraq.

### b. Rationale:

The module aims to provide an in-depth understanding of Zener diodes and IC regulators as voltage regulators, a critical topic in the field of electrical engineering and medical instrumentation.

### c. Objectives:

Upon completion of the lecture, students will achieve the following learning outcomes:

- Explain the applications and significance of Zener diodes and IC regulator in medical instrumentation.
- Demonstrate the ability to calculate and select appropriate Zener diodes for specific voltage regulation tasks.


## 2. Introduction:

A **regulated power supply** converts unregulated AC (Alternating Current) to a constant DC (Direct Current). A regulated power supply is used to ensure that the output remains constant even if the input changes. The basic building blocks of a regulated DC power supply are as follows:

1. A step-down transformer.
2. A rectifier.
3. A DC filter.
4. A regulator.
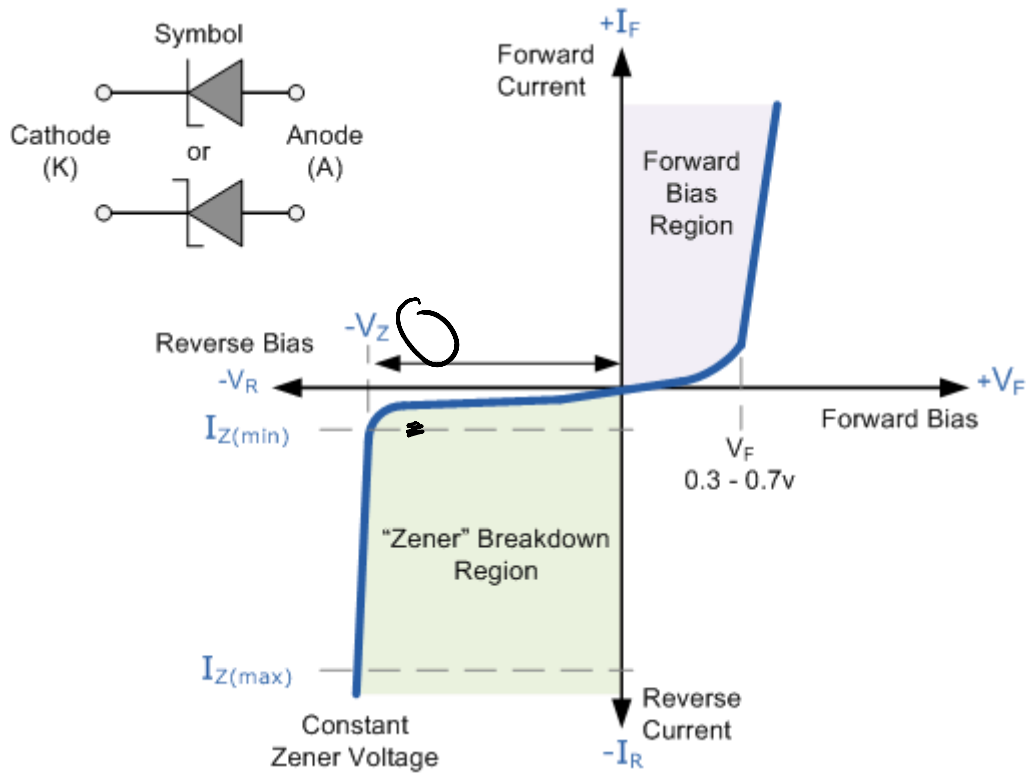
## Zener Diode Regulator

A **Zener diode** is a special type of diode designed to reliably allow current to flow "backwards" when a certain set reverse voltage, known as the Zener voltage, is reached.




The values of the individual Zener diodes can be chosen to suit the application while the silicon diode will always drop about 0.6 – 0.7V in the forward bias condition. The supply voltage,  $V_{in}$  must of course be higher than the largest output reference voltage and in our example above this is 19v.


A typical **Zener diode** for general electronic circuits is the 500mW, BZX55 series or the larger 1.3W, BZX85 series were the Zener voltage is given as, for example, C7V5 for a 7.5V diode giving a diode reference number of BZX55C7V5.

As well as producing a single stabilized voltage output, Zener diodes can also be connected together in series along with normal silicon signal diodes to produce a variety of different reference voltage output values as shown below.

### Zener Diodes Connected in Series

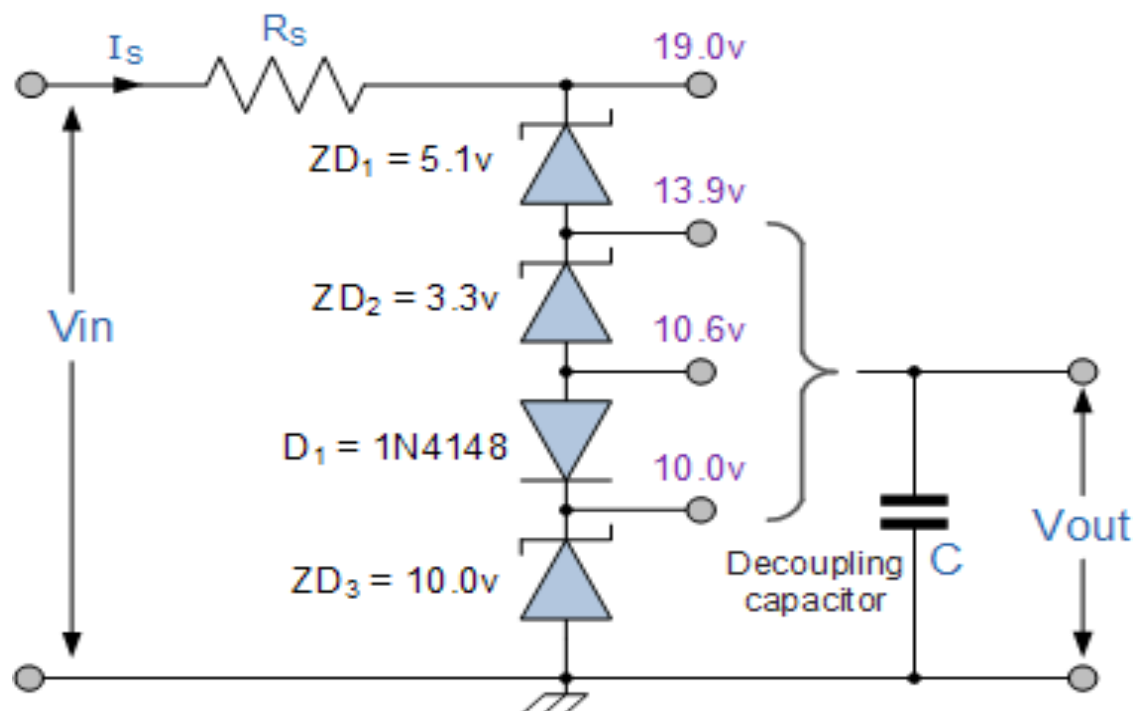

### Stage 1: Fixed $V_i$ and Fixed $R_L$

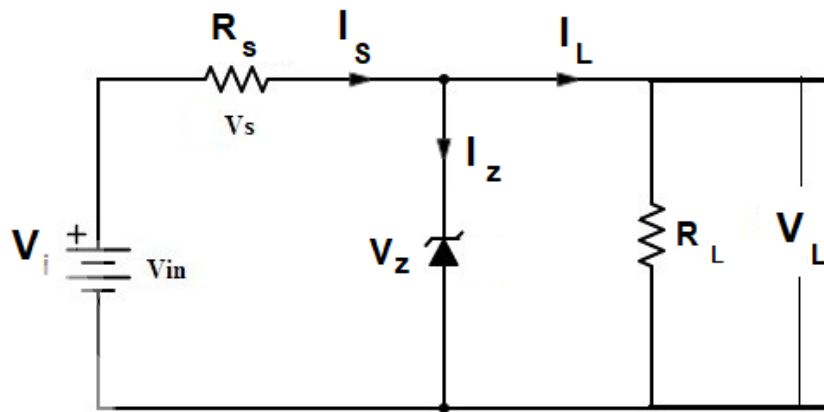

When  $V_z > V_L$  Zener is off

$$V_L = \frac{R_L}{R_L + R_s} V_i$$


$$I_L = \frac{V_L}{R_L}$$

$$V_i - V_s - V_L = 0$$

$$I_s = \frac{V_s}{R_s}$$

$$I_z = 0$$

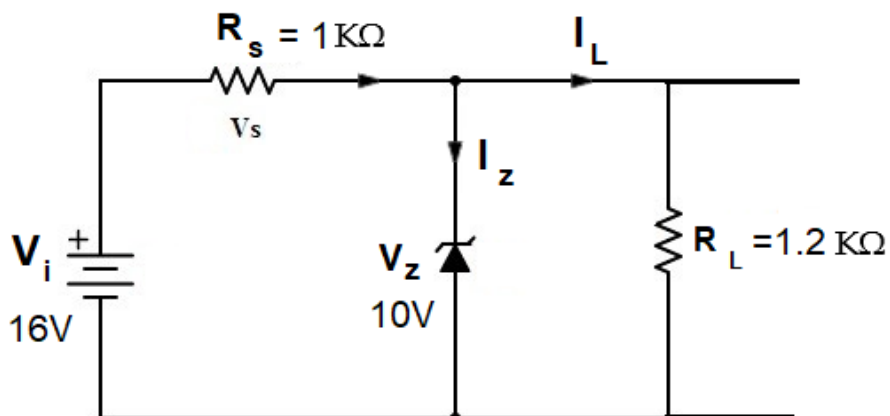**Ex1:** For the Zener circuit below, determine  $V_L, I_L, V_s, I_s$  and  $I_z$



Ans:

$$V_L = \frac{R_L}{R_L + R_S} V_i = \frac{1.2}{1.2 + 1} \times 16 = 8.72 \text{ V}$$

$\therefore V_Z (10 \text{ V}) > V_L (8.72 \text{ V}) \quad \therefore \text{Zener is off}$


$$I_L = \frac{V_L}{R_L} = \frac{8.72}{1.2 \times 10^3} = 7.27 \text{ mA}$$

$$\begin{aligned} V_i - V_S - V_L &= 0 \\ 16 - V_S - 8.72 &= 0 \\ V_S &= 7.27 \text{ V} \end{aligned}$$

$$I_S = \frac{V_S}{R_S} = \frac{7.27}{1K} = 7.27 \text{ mA}$$

$$I_Z = 0$$

Answer with MULTISIM

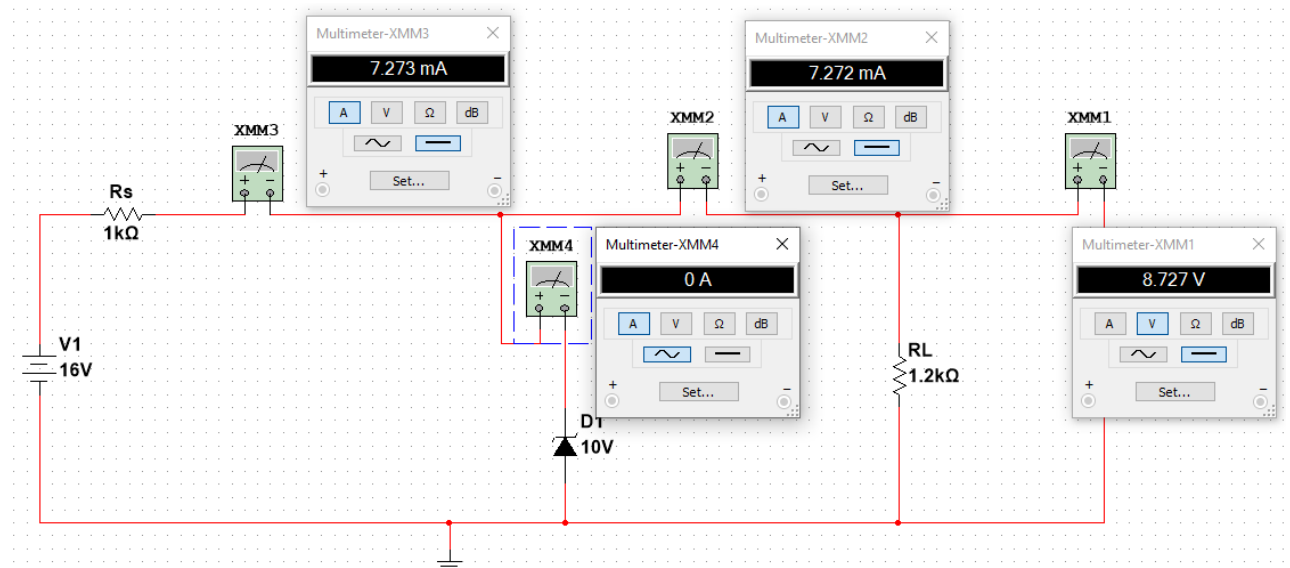

Repeat Ex.1 with  $R_L = 3\text{ K}\Omega$

Ans:

$$V_L = \frac{R_L}{R_L + R_S} V_i = \frac{3}{3 + 1} \times 16 = 12\text{ V}$$

$\therefore V_Z (10\text{ V}) < V_L (12\text{ V}) \quad \therefore \text{Zener is on}$

$$\therefore V_L = V_Z = 10\text{ V}$$

$$I_L = \frac{V_L}{R_L} = \frac{10}{3 \times 10^3} = 3.33\text{ mA}$$


$$\begin{aligned} V_i - V_S - V_Z &= 0 \\ 16 - V_S - 10 &= 0 \\ V_S &= 6\text{ V} \end{aligned}$$

$$I_S = \frac{V_S}{R_S} = \frac{6}{1\text{ K}} = 6\text{ mA}$$

$$I_S = I_Z + I_L$$

$$\therefore I_Z = I_S - I_L = 6 - 3.33 = 2.67\text{ mA}$$

Answer with MULTISIM

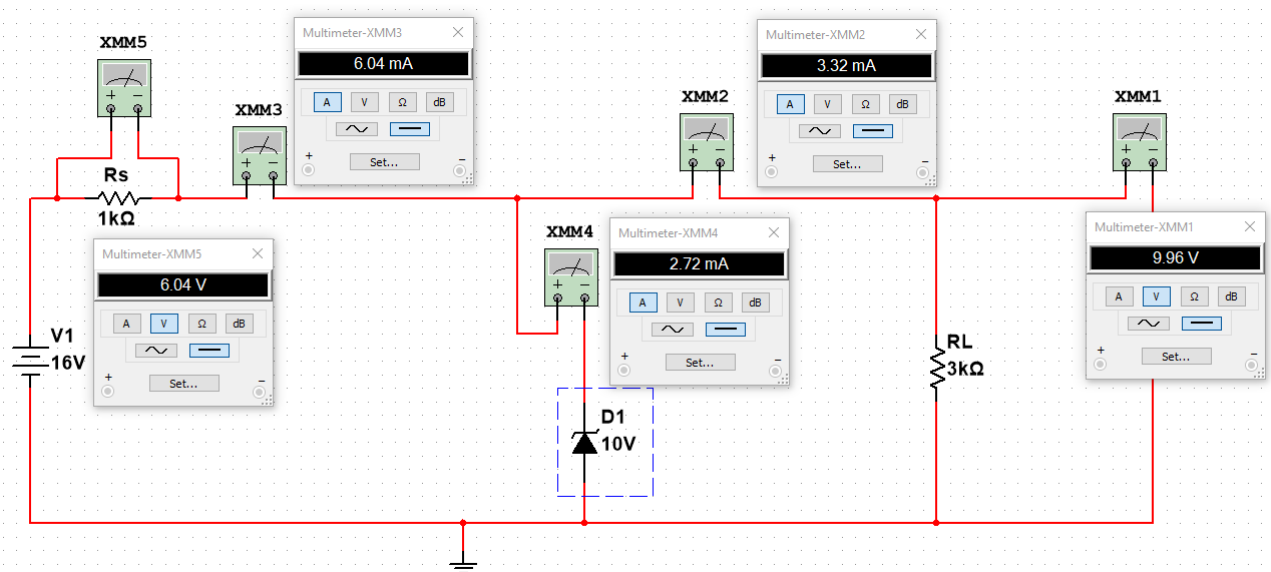

**Ex2:** A 5.0V stabilized power supply is required to be produced from a 12V DC power supply input source. The maximum power rating  $P_Z$  of the Zener diode is 2W. Using the Zener regulator circuit above calculate:

a). The maximum current flowing through the Zener diode.

$$\text{Maximum Current} = \frac{\text{Watts}}{\text{Voltage}} = \frac{2\text{w}}{5\text{v}} = 400\text{mA}$$

b). The minimum value of the series resistor,  $R_S$

$$R_S = \frac{V_S - V_Z}{I_Z} = \frac{12 - 5}{400\text{mA}} = 17.5\Omega$$


c). The load current  $I_L$  if a load resistor of  $1\text{k}\Omega$  is connected across the Zener diode.

$$I_L = \frac{V_Z}{R_L} = \frac{5\text{v}}{1000\Omega} = 5\text{mA}$$

d). The Zener current  $I_Z$  at full load.


$$I_Z = I_S - I_L = 400\text{mA} - 5\text{mA} = 395\text{mA}$$

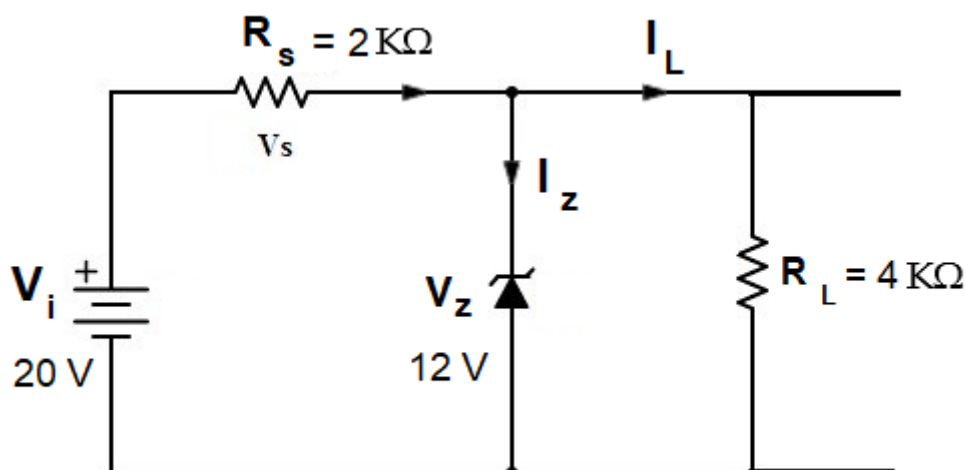**Ex3 (H.W):** For the Zener circuit below, determine  $V_L, I_L, V_S, I_S$  and  $I_Z$




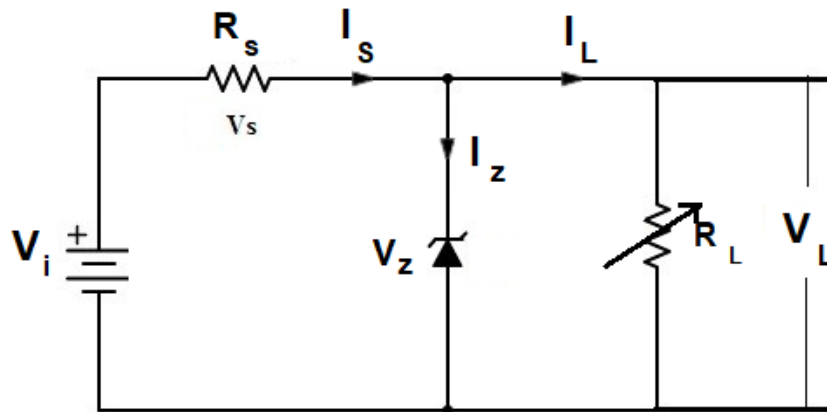
## Stage 2: Fixed $V_i$ and Variable $R_L$



$$R_{Lmin} = \frac{V_z}{V_i - V_z} R_s$$

$$V_L = V_z$$


$$I_{Lmax} = \frac{V_z}{R_{Lmin}}$$

$$I_z = I_s - I_L$$

$$I_{Lmin} = I_s - I_{zmax}$$

$$I_{Lmin} = \frac{V_z}{R_{Lmax}}$$

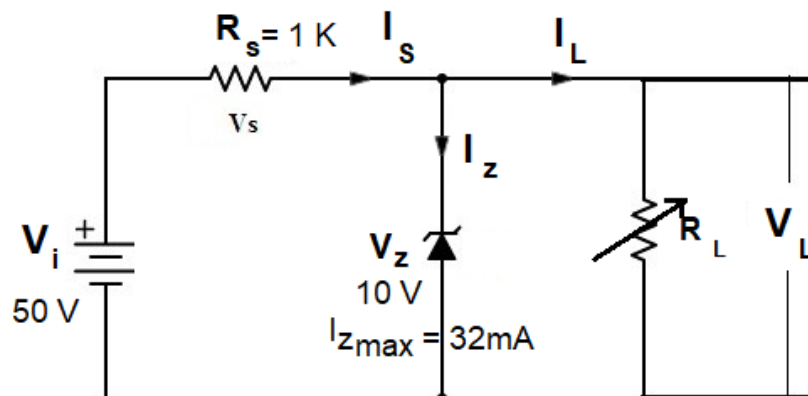**Ex4:** For the Zener circuit below, determine the range of  $R_L$  and  $I_L$



Ans:

$$R_{Lmin} = \frac{V_z}{V_i - V_z} R_s = \frac{10}{50 - 10} \times 1000 = 0.25 K\Omega$$

$$\begin{aligned} V_i - V_s - V_z &= 0 \\ 50 - V_s - 10 &= 0 \\ V_s &= 40 V \end{aligned}$$


$$I_s = \frac{V_s}{R_s} = \frac{40}{1K} = 40 mA$$


$$I_{Lmin} = I_s - I_{zmax} = 40 - 32 = 8 mA$$

$$R_{Lmin} = \frac{V_z}{I_{Lmax}} = \frac{10}{8m} = 1.25 K\Omega$$


$$I_{Lmax} = \frac{V_z}{R_{Lmin}} = \frac{10}{0.25K} = 40 mA$$

Answer with MULTISIM

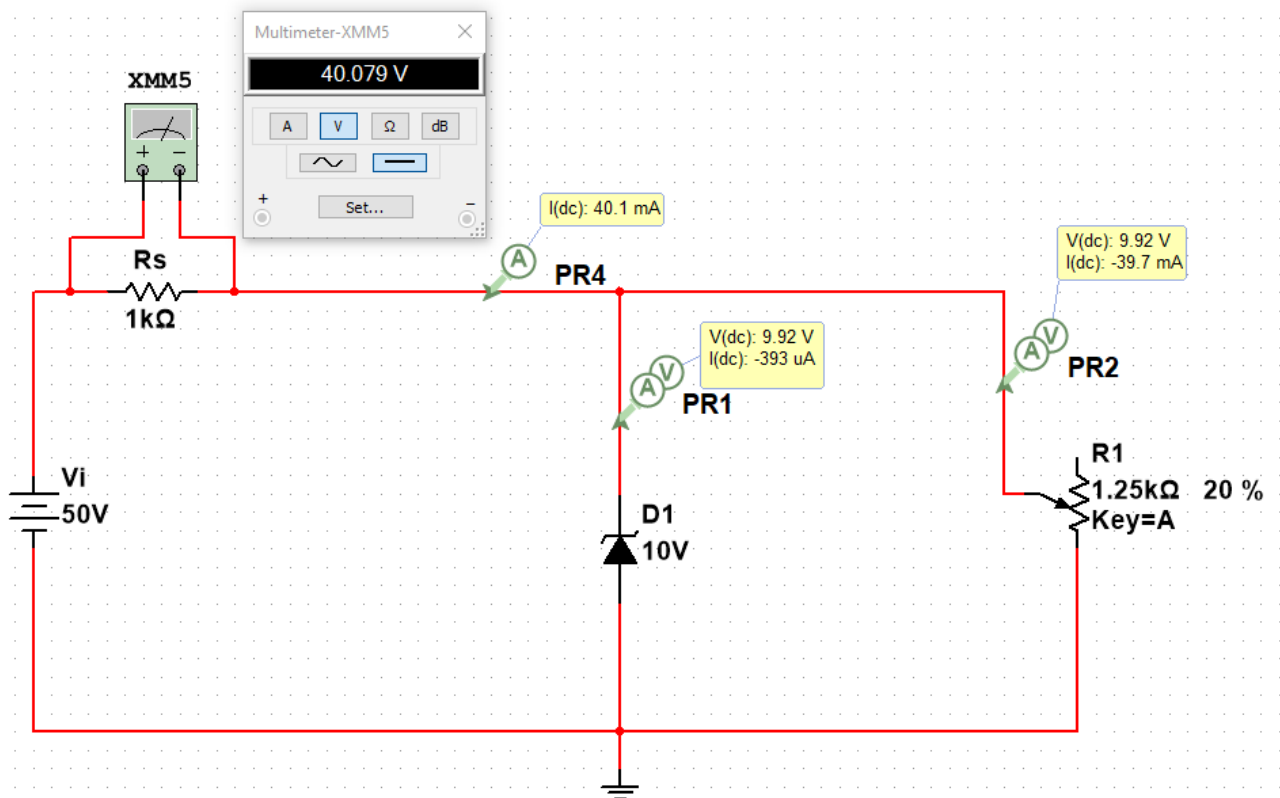


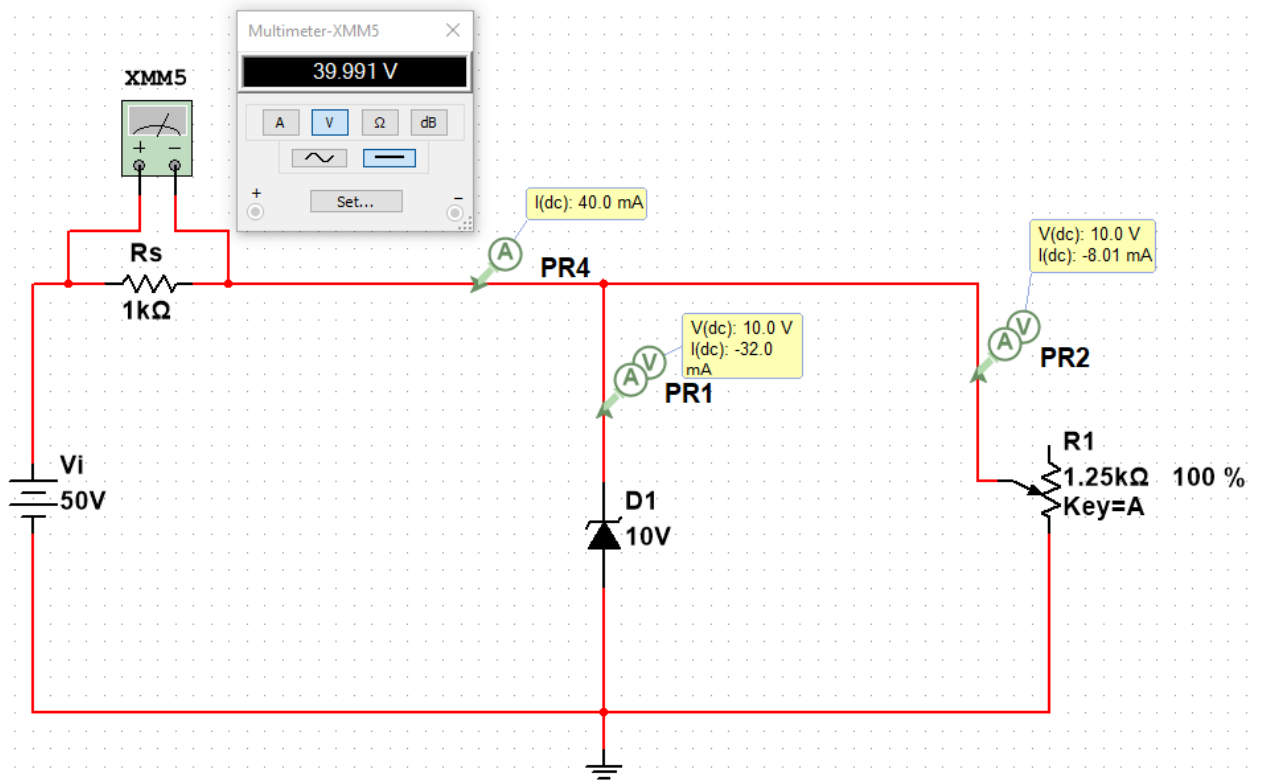

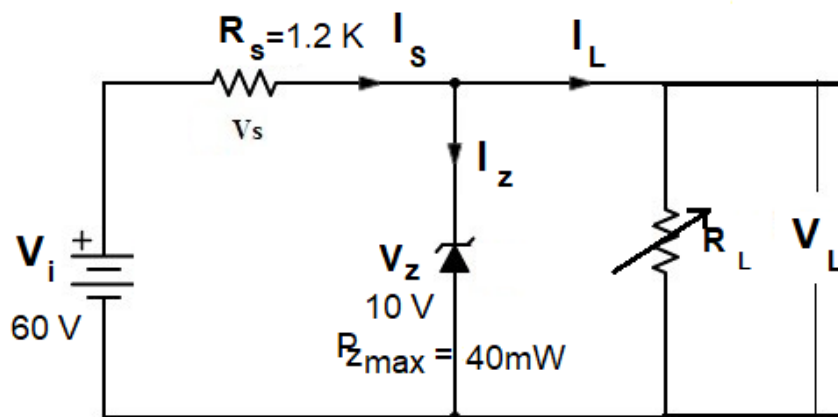Ex5 (H.W): For the Zener circuit below, determine the range of  $R_L$  and  $I_L$


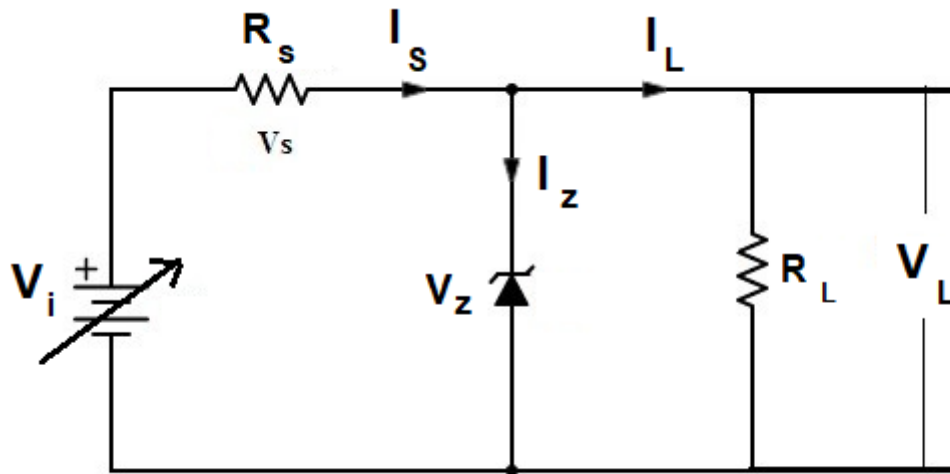
### Stage 3: Variable $V_i$ and Fixed $R_L$



$$V_{i \min} = \frac{R_L + R_s}{R_L} V_z$$


$$I_{s \max} = I_{z \max} + I_L$$

$$V_{i \max} = I_{s \max} \cdot R_s + V_z$$

$$V_{s \max} = I_{s \max} R_s$$

$$V_{s \min} = I_{s \min} R_s$$

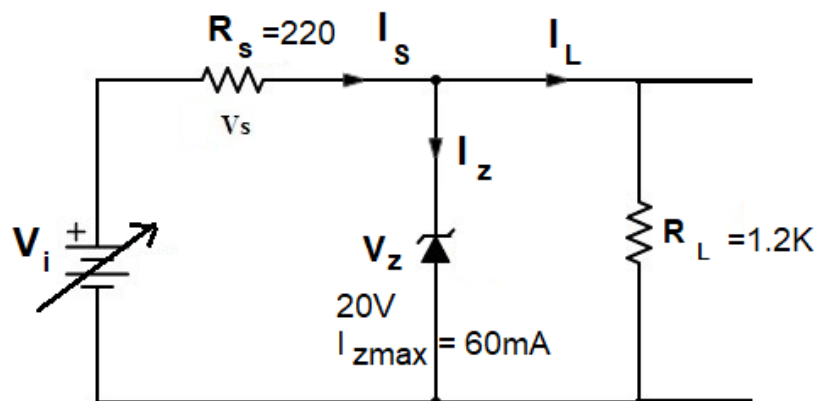**Ex6:** For the Following circuit, determine the range of the input voltage and  $V_s$ .



**Answer:**

$$V_{i \min} = \frac{R_L + R_S}{R_L} V_Z = \frac{1200 + 220}{1200} \times 20 = 23.67 \text{ V}$$


$$I_L = \frac{V_L}{R_L} = \frac{20}{1.2 \times 10^3} = 16.6 \text{ mA}$$


$$I_{S \max} = I_{Z \max} + I_L = 60 + 16.6 = 76.6 \text{ mA}$$

$$V_{i \max} = I_{S \max} \cdot R_S + V_Z = 76.6 \text{ m} \times 220 + 20 = 36.86 \text{ V}$$

$$V_{S \max} = I_{S \max} R_S = 76.6 \times 220 = 16.852 \text{ V}$$
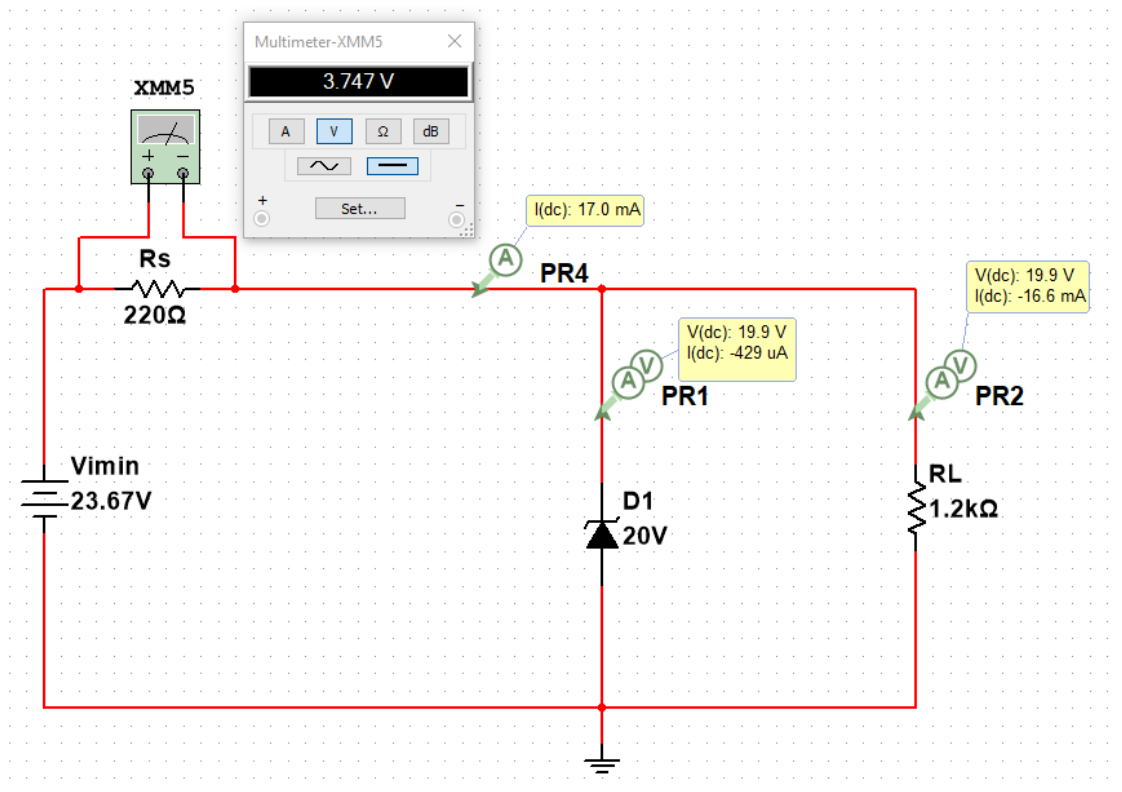
$$V_{S \min} = I_{S \min} R_S = 17.032 \times 220 = 3.747 \text{ V}$$




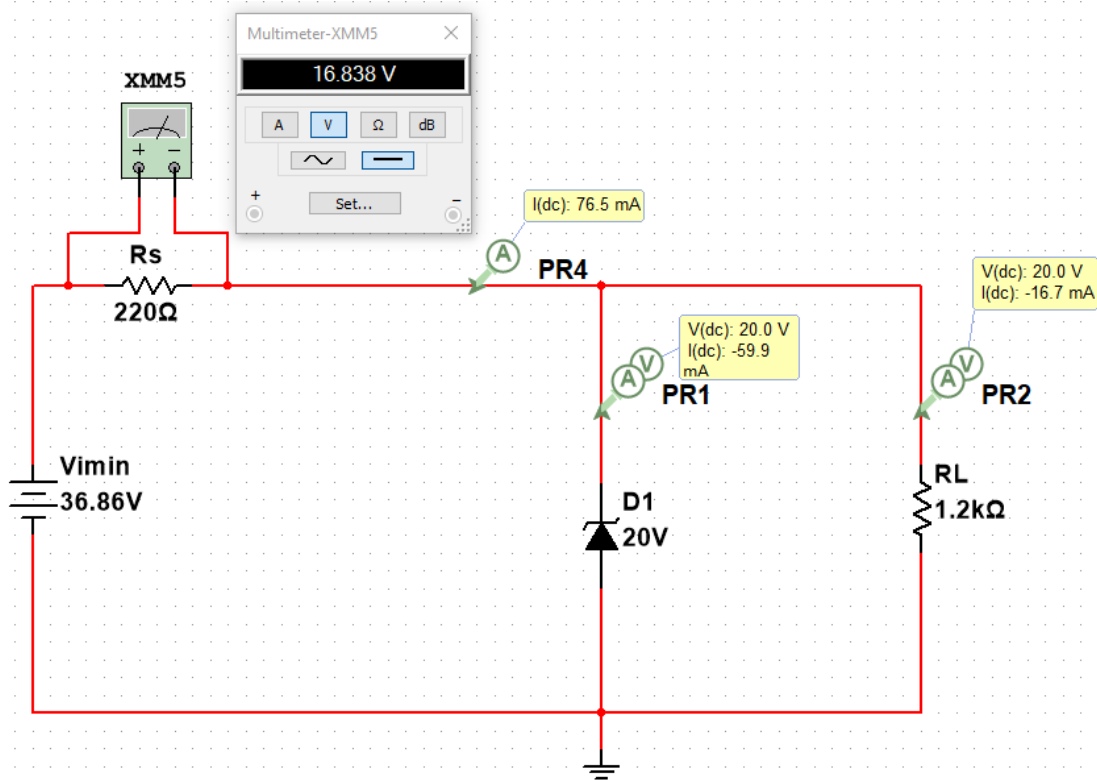


Ex7 (H.W): Repeat with  $R_s = 330$  and  $R_L = 2\text{ K}$  and  $V_z = 22\text{ V}$
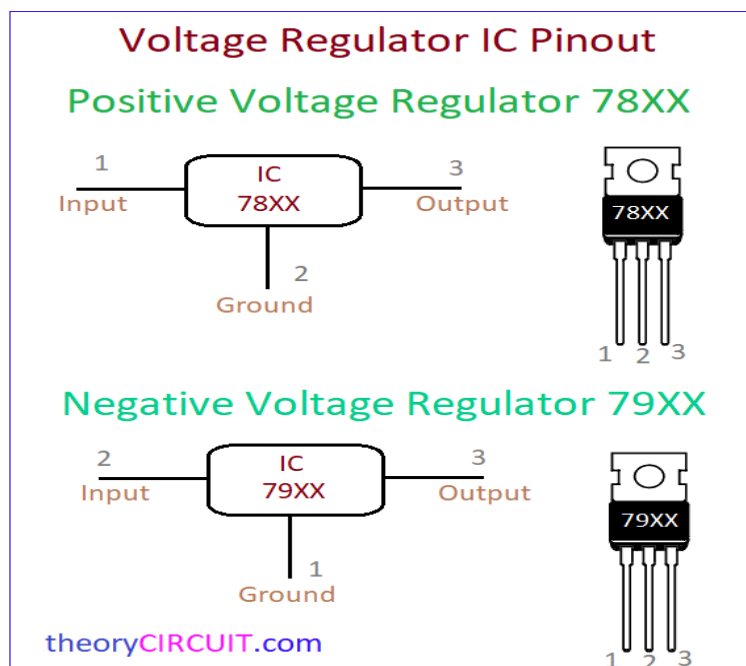
### IC Regulator

IC's like LM78XX and 79XX (such as the IC 7805) are used to obtain fixed values of voltages at the output.






## An example for LM7805 in Multisim

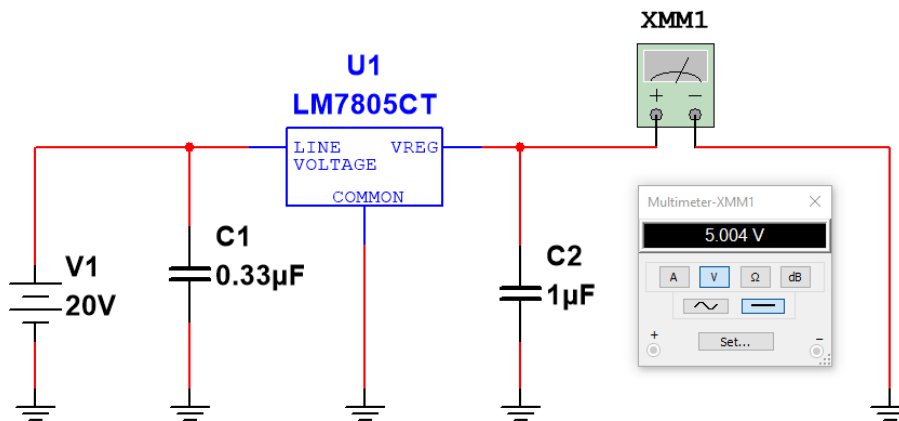

The adjustment of the output voltage to a required constant value can be achieved using ICs such as LM 317 and 723. The LM317 voltage regulator is depicted in the figure below. The adjustment of output voltage can be accomplished by modifying the resistances  $R_1$  and  $R_2$ . Typically, coupling capacitors with values ranging from  $0.01\mu\text{F}$  to  $10\mu\text{F}$  should be connected at both the output and input terminals to mitigate input noise and output transients. Ideally, the output voltage is determined by the following equation.
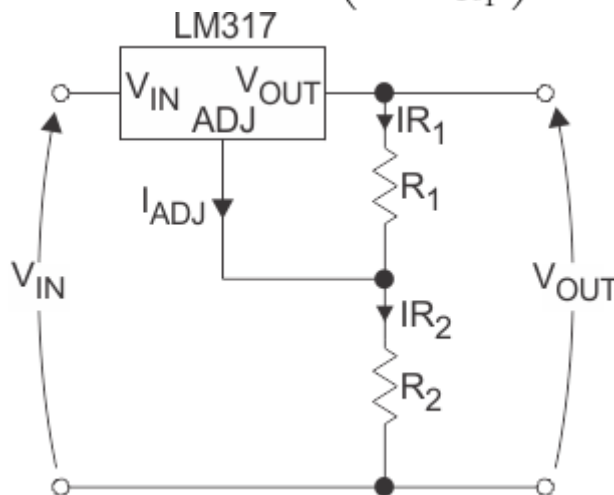
$$V_{OUT} = V_{REF} \left( 1 + \frac{R_2}{R_1} \right)$$




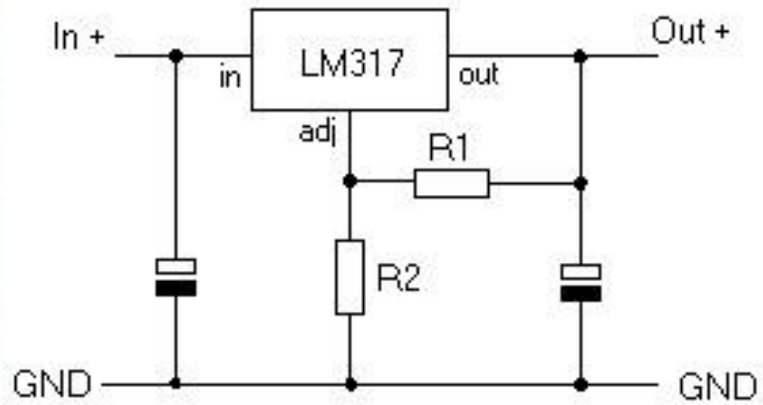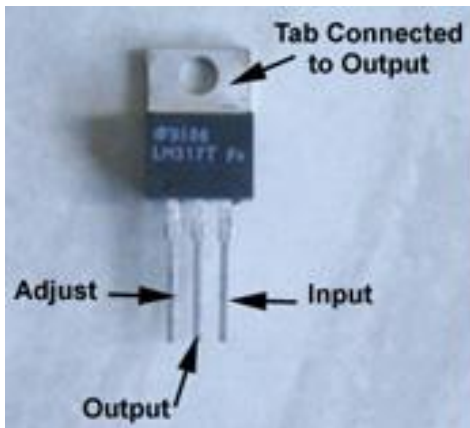

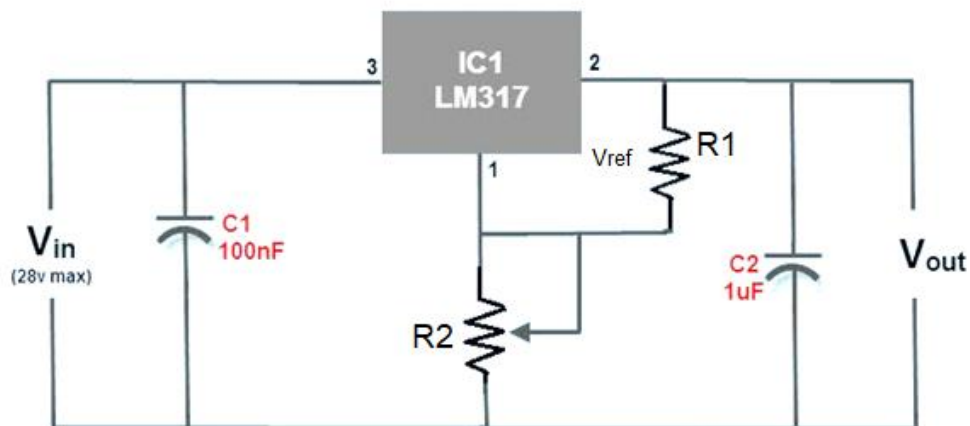**LM317 Voltage Regulator Circuit**

The LM317 features three terminals: an input pin, an output pin, and an adjustment pin. The circuit diagram for the LM317 voltage regulator, as illustrated in the figure below, represents a standard configuration, complete with decoupling capacitors. This LM317 circuit is capable of delivering a variable DC power supply with a maximum output of 1A, adjustable up to 30V. It includes a low-side resistor and a high-side resistor connected in series, forming a resistive voltage divider. This passive linear circuit generates an output voltage that is a fraction of its input voltage. Decoupling capacitors are implemented to prevent undesired coupling or interference between different sections of an electrical circuit. They serve to mitigate input noise and output transients, minimizing the impact of noise from specific circuit elements on the overall performance. Furthermore, to prevent excessive heat generation and component overheating resulting from high power dissipation, a heat sink is utilized in conjunction with the circuit.





LM317 Voltage Regulator Circuit

$C_1=C_{in}$  needed if regulator is located far from power supply filter.  
 $C_2=C_{out}$  improves transient response.

### Features of LM317 Voltage Regulator

There are some special features of LM317 regulator and a few are as follows:

- It is capable of providing excess current of 1.5A, hence it is conceptually considered as operational amplifier with an output voltage ranging from 1.2V to 37V.
- The LM317 voltage regulator circuit internally consists of [thermal overload protection](#) and short circuit current limiting constant with temperature.
- It is available in two packages as 3-Lead Transistor Package and surface mount D2PAK-3.
- Stocking of many fixed voltages can be eliminated.

## Working of Voltage Regulator LM317 Circuit (Adjustable Voltage Regulator)

The LM317 regulator can provide excess output current and hence with this capacity, it is conceptually considered as [an operational amplifier](#). The adjustment pin is the inverting input of the amplifier and to produce a stable reference voltage of 1.25V, an internal bandgap reference voltage is used to set the non-inverting input.

The output pin voltage can be continuously adjusted to a fixed amount using a resistive-voltage divider between the output and ground, which will configure the operational amplifier as a non-inverting amplifier.

A bandgap reference voltage is used to produce constant output voltage irrespective of the changes in supply power. It is also called as temperature independent reference voltage frequently used in integrated circuits.

The output voltage (ideally) of the LM317 voltage regulator circuit

$$V_{\text{out}} = V_{\text{ref}} * (1 + (R_2/R_1))$$

Where  $V_{\text{ref}}$  is 1.25V, an error term is added because some quiescent current flows from the adjustment pin of the device.

$$V_{\text{out}} = V_{\text{ref}} * (1 + (R_2/R_1)) + I_{\text{adj}} R_2$$

For achieving more stable output, the LM317 voltage regulator circuit diagram is designed such that to make the quiescent current less than or equal to 100 micro Amp. Thus, in all practical cases the error can be ignored.

If we replace the low-side resistor of the divider from the LM317 voltage regulator circuit diagram with the load, then the resulting configuration

of the LM317 regulator will regulate the current to a load. Hence, this LM317 circuit can be treated as LM317 Current Regulator Circuit.

The output current is the voltage drop of reference voltage across the resistance  $R_H$  and is given as

Output current in ideal case is

$$I_{out} = V_{ref}/R_1$$

Considering the quiescent current, the output current is given as


$$I_{out} = (V_{ref}/R_1) + I_{adj}$$

These linear voltage regulators LM317 and LM337 are frequently used in DC-DC converter applications. Linear regulators naturally draw much current as they supply. The power produced due to the multiplication of this current with the voltage difference between the input and output will be dissipated and wasted as heat.

Due to this, a heat is required to be considered for significant design and leads to inefficiency. If the voltage difference increases, then the power wasted will increase and sometimes this dissipated waste power will be more than the supplied power.

Even though this is insignificant, but as the linear voltage regulators with a few additional components is a simple way to obtain stable voltage, so, we must accept this trade-off. The switching voltage regulators are alternative for these linear regulators as these switching regulators are generally more efficient, but they require more number of components to design and thus need more space.

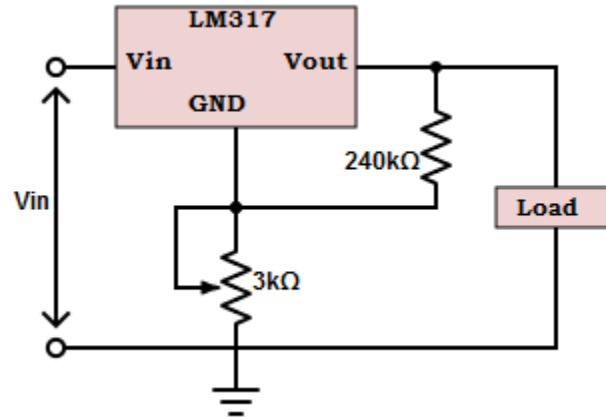**Ex 8:** Calculate the output voltage for LM317 regulator. The current  $I_{ADJ}$  is very small in the order of  $100\mu A$ . (Assume  $V_{REF}=1.25V$ )



**Answer:**

Explanation: The output voltage,  $V_{Out} = V_{REF}[1+(R_2/R_1)]+(I_{ADJ} \times R_2) = 1.25V \times [1+(3k\Omega/240\Omega)] + (100\mu A \times 3k\Omega) = 16.875 + 0.3$ .

$\Rightarrow V_{Out} = 17.17V$ .

**Ex9 (H.W):** Calculate the output voltage for an LM317 voltage regulator with  $R_2=1k\Omega$  and  $R_1=240\Omega$ , given a reference voltage  $V_{REF}$  of 1.25V and an adjustment pin current  $I_{ADJ}$  of  $100\mu A$ .

Answer:  $V_{Out} \approx 6.4585V$

**H.W:** Drive the following questions

$$V_{out} = V_{ref} \left(1 + \frac{R_2}{R_1}\right)$$


$$R_1 = R_2 \frac{1.25}{V_o - 1.25}$$

$$R_2 = R_1 \frac{V_o - 1.25}{1.25}$$

**Ex10 (H.W):** You are designing a power supply circuit using an LM317 voltage regulator. You have a reference voltage ( $V_{REF}$ ) of 1.25V and a resistor ( $R_1$ ) of  $240\Omega$ . The adjustment pin current ( $I_{ADJ}$ ) is  $100\mu A$ . If you desire an output voltage ( $V_{out}$ ) of 9V, what value of  $R_2$  should you choose to achieve this output voltage?

## Adjustable Current Regulator

### LM317 (adjustable current source)

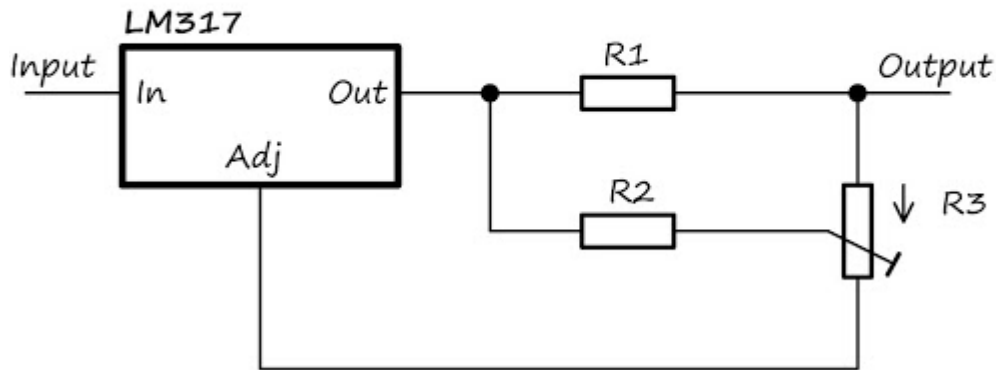


$$V_{R1} = 1.25 \left(1 + \frac{xR_3}{R_2}\right) \quad x = 0 \text{ to } 1$$

$$I_{R1} = \frac{V_{R1}}{R_1}$$

$$I_{min} = \frac{1.25}{R_1}$$

$$I_{max} = \frac{1.25}{R_1} \left(1 + \frac{R_3}{R_2}\right)$$

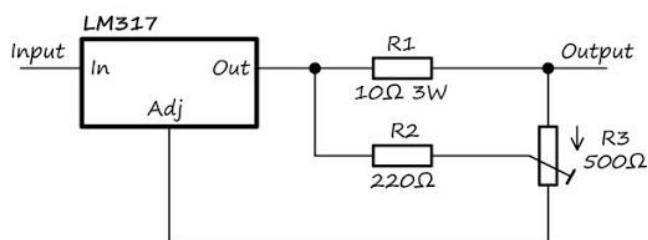Ex10 (H.W): Determine  $I_{min}$  and  $I_{max}$  of the following circuit.



LM317 adjustable current source  
approx. 125-400mA range

# Full Regulated Power Supply Using Multisim

