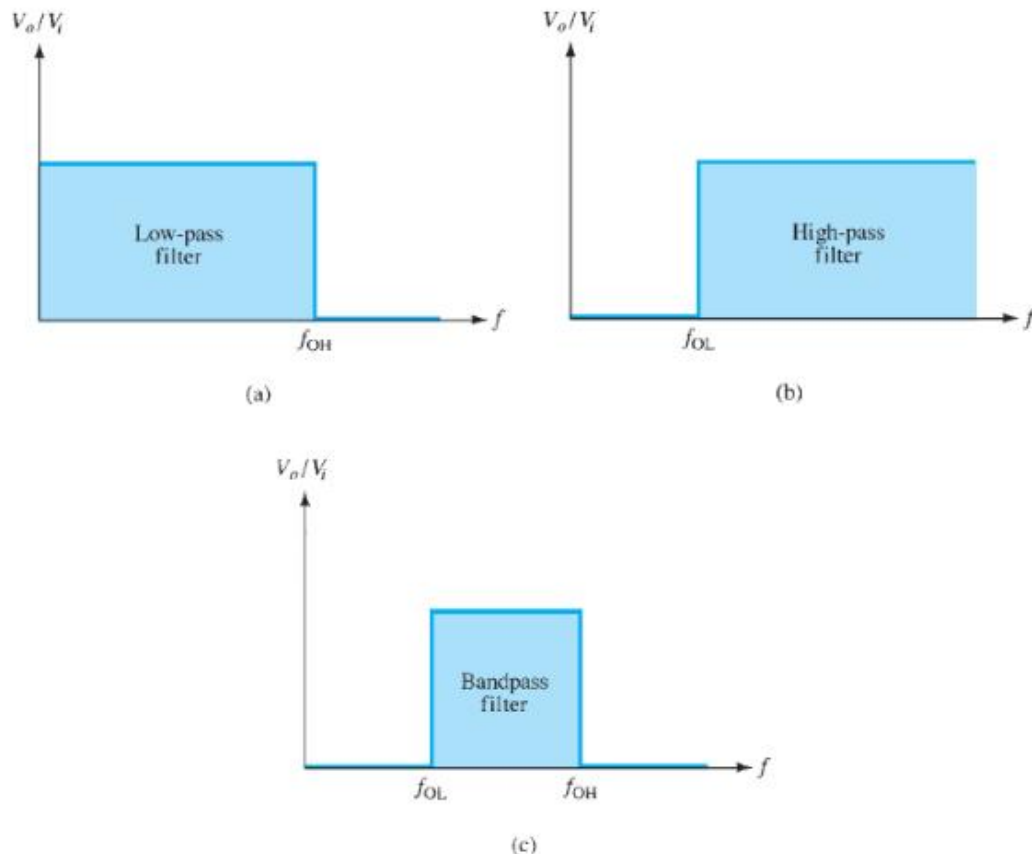




## ACTIVE FILTERS

A popular application uses op-amps to build active filter circuits. A filter circuit can be constructed using passive components: resistors and capacitors. An active filter additionally uses an amplifier to provide voltage amplification and signal isolation or buffering.

A filter that provides a constant output from dc up to a cutoff frequency  $f_{OH}$  and then passes no signal above that frequency is called an ideal low-pass filter. The ideal response of a low-pass filter is shown in Fig. a. A filter that provides or passes signals above a cutoff frequency  $f_{OL}$  is a high-pass filter, as idealized in Fig. b. When the filter circuit passes signals that are above one ideal cutoff frequency and below a second cutoff frequency, it is called a bandpass filter, as idealized in Fig. c.







## Low-Pass Filter

A first-order, low-pass filter using a single resistor and capacitor as in Fig. a has a practical slope of  $-20$  dB per decade, as shown in Fig. b (rather than the ideal response of Fig. a). The voltage gain below the cutoff frequency is constant at

$$A_v = 1 + \frac{R_F}{R_G}$$

at a cutoff frequency of

$$f_{OH} = \frac{1}{2\pi R_1 C_1}$$

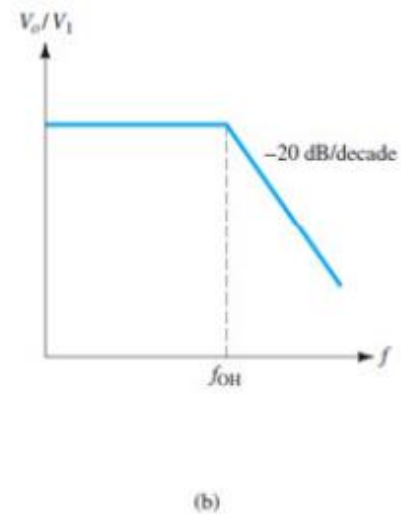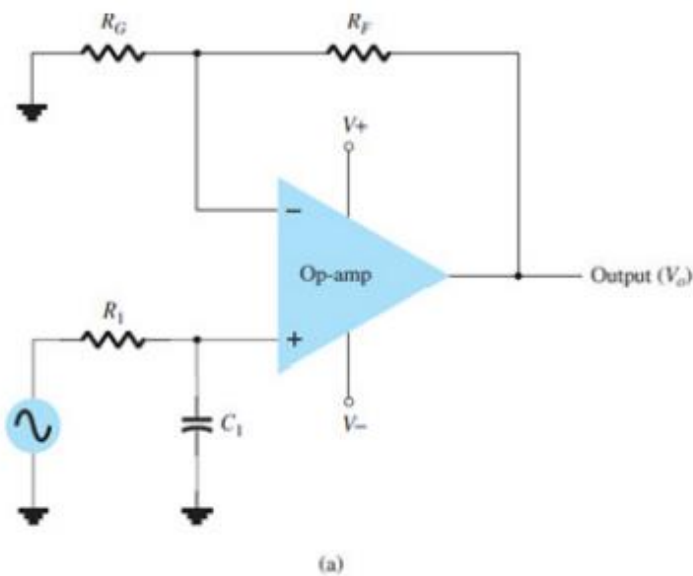


*First-order low-pass active filter.*



Al-Mustaqbal University College  
 Department of Medical Instrumentation Techniques Engineering  
 Class: Three  
 Subject: Medical electronic system  
 Lecturer: Dr. zahraa hashim kareem  
 Lecture-6: active filter

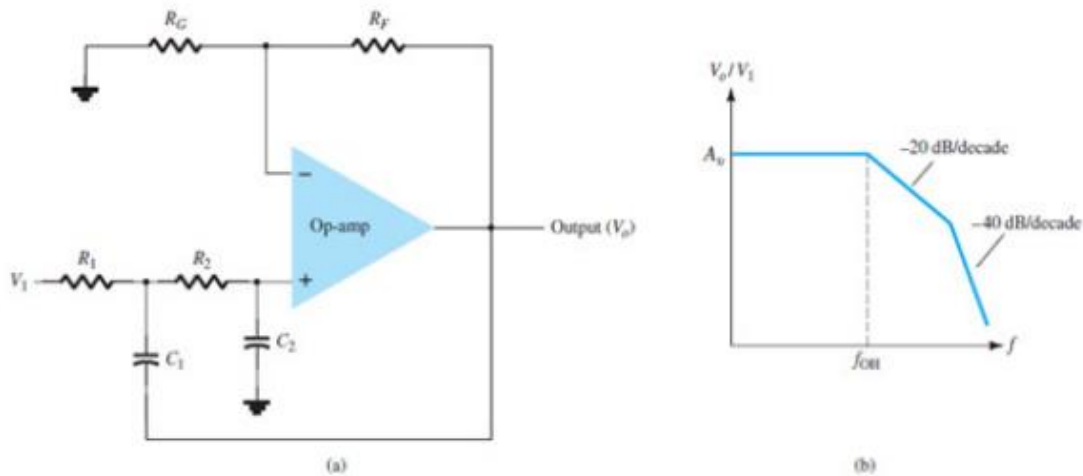Connecting two sections of filter as in Fig. results in a second-order low-pass filter with cutoff at  $-40$  dB per decade—closer to the ideal characteristic of Fig. The circuit voltage gain and the cutoff frequency are the same for the second-order circuit as for the first-order filter circuit, except that the filter response drops at a faster rate for a second-order filter circuit.



Second-order low-pass active filter.

**EXAMPLE** Calculate the cutoff frequency of a first-order low-pass filter for  $R_1 = 1.2 \text{ k}\Omega$  and  $C_1 = 0.02 \text{ }\mu\text{F}$ .

**Solution:**

$$f_{OH} = \frac{1}{2\pi R_1 C_1} = \frac{1}{2\pi(1.2 \times 10^3)(0.02 \times 10^{-6})} = 6.63 \text{ kHz}$$





### High-Pass Active Filter

First- and second-order high-pass active filters can be built as shown in Fig. . The amplifier gain is calculated using Eq. ( ). The amplifier cutoff frequency is

$$f_{OL} = \frac{1}{2\pi R_1 C_1}$$

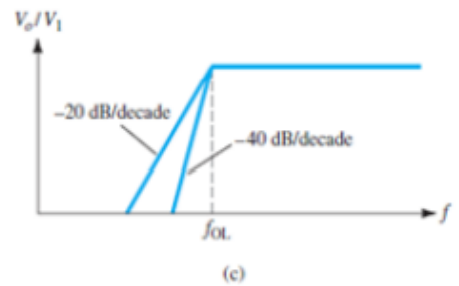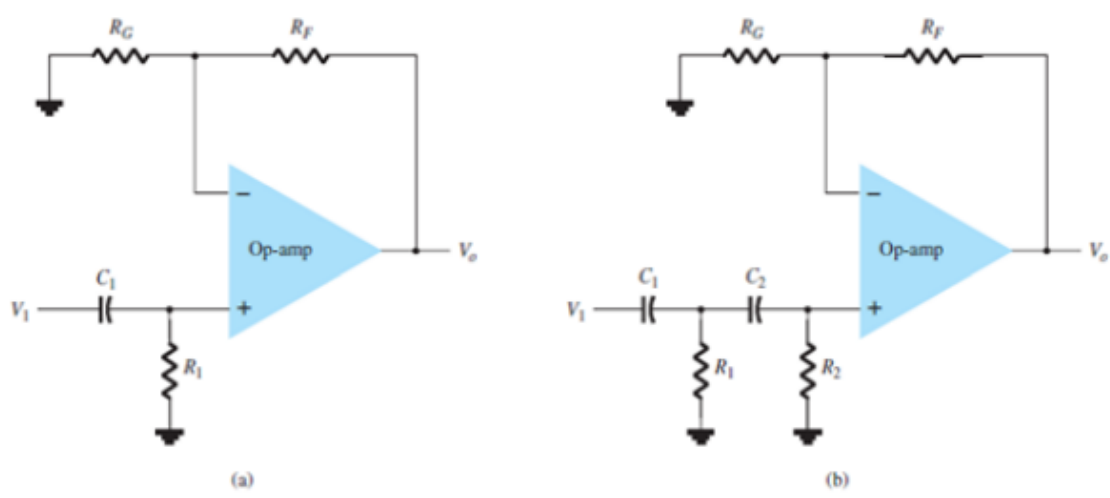with a second-order filter  $R_1 = R_2$ , and  $C_1 = C_2$  results in the same cutoff frequency as in Eq. ( ).



High-pass filter: (a) first order; (b) second order; (c) response plot.



Al-Mustaqbal University College  
Department of Medical Instrumentation Techniques Engineering  
Class: Three  
Subject: Medical electronic system  
Lecturer: Dr. zahraa hashim kareem  
Lecture-6: active filter

**EXAMPLE** Calculate the cutoff frequency of a second-order high-pass filter as in Fig. for  $R_1 = R_2 = 2.1 \text{ k}\Omega$ ,  $C_1 = C_2 = 0.05 \text{ }\mu\text{F}$ , and  $R_G = 10 \text{ k}\Omega$ ,  $R_F = 50 \text{ k}\Omega$ .

**Solution:**



$$A_v = 1 + \frac{R_F}{R_G} = 1 + \frac{50 \text{ k}\Omega}{10 \text{ k}\Omega} = 6$$

The cutoff frequency is then

$$f_{OL} = \frac{1}{2\pi R_1 C_1} = \frac{1}{2\pi(2.1 \times 10^3)(0.05 \times 10^{-6})} \approx 1.5 \text{ kHz}$$

### Bandpass Filter

Figure 11.34 shows a bandpass filter using two stages, the first a high-pass filter and the second a low-pass filter, the combined operation being the desired bandpass response.

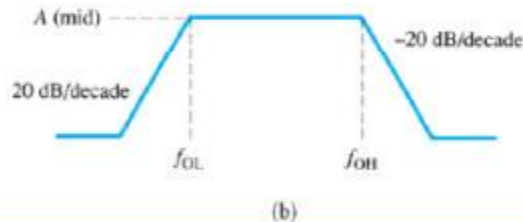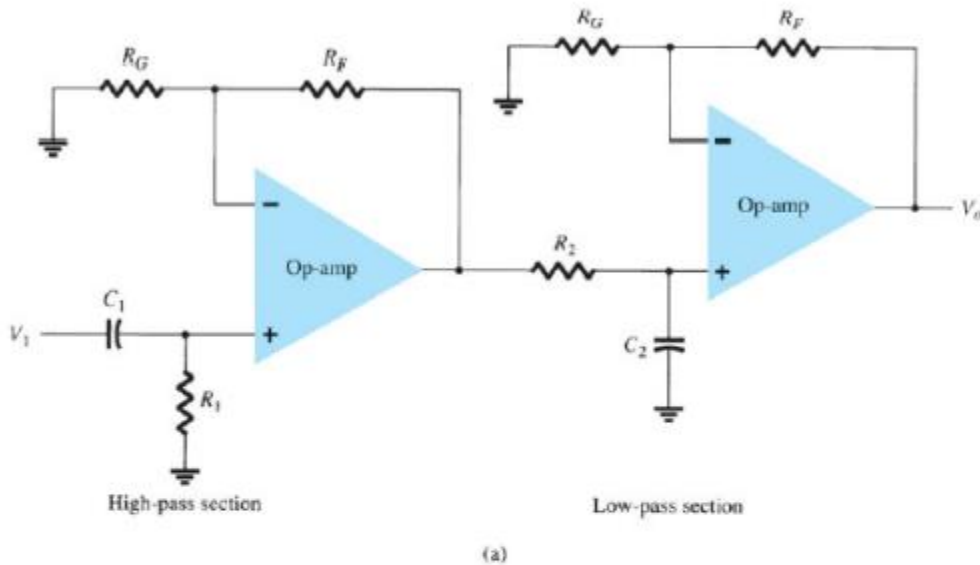

**EXAMPLE** Calculate the cutoff frequencies of the bandpass filter circuit of Fig. with  $R_1 = R_2 = 10\text{ k}\Omega$ ,  $C_1 = 0.1\text{ }\mu\text{F}$ , and  $C_2 = 0.002\text{ }\mu\text{F}$ .

**Solution:**

$$f_{OL} = \frac{1}{2\pi R_1 C_1} = \frac{1}{2\pi(10 \times 10^3)(0.1 \times 10^{-6})} = 159.15\text{ Hz}$$

$$f_{OH} = \frac{1}{2\pi R_2 C_2} = \frac{1}{2\pi(10 \times 10^3)(0.002 \times 10^{-6})} = 7.96\text{ kHz}$$