



Ministry of Higher Education

and Scientific Research

Al- Mustaqbal University College

Department of Medical Instrumentation Techniques Engineering

تكنولوجيا الكهرباء

Electrical Technology

Lecture 9

Lecture Name: TRANSFORMER

By

Dr. Jaber Ghaib Talib



## Example and Solution أمثلة وحلول

Exp:

A three-phase transformer bank is to handle (600 KVA) and have a (34.5/13.8 KV) voltage ratio. Find the rating of each individual transformer in bank (high voltage, low voltage, turns ratio, and apparent power) if the transformer bank is connected to (a) Y - Y (b)  $\Delta$  -  $\Delta$  (c)  $\Delta$  - Y (d) Y -  $\Delta$ ?

Solution:

For Y - Y connection

$$\text{Primary voltage} = \frac{34.5}{\sqrt{3}} = 19.9 \text{ KV} \quad , \text{Secondary voltage} = \frac{13.8}{\sqrt{3}} = 7.97 \text{ KV}$$

$$\text{Turns ratio} = \frac{19.9}{7.97} = 2.5$$

For  $\Delta$  -  $\Delta$  connection

$$\text{Primary voltage} = 34.5 \text{ KV} \quad , \text{Secondary voltage} = 13.8 \text{ KV}$$

$$\text{Turns ratio} = \frac{34.5}{13.8} = 2.5$$



For  $\Delta$  - Y connection

$$\text{Primary voltage} = 34.5 \text{ KV} \quad , \quad \text{Secondary voltage} = \frac{13.8}{\sqrt{3}} = 7.97 \text{ KV}$$

$$\text{Turns ratio} = \frac{34.5}{7.97} = 4.33$$

For Y - $\Delta$  connection

$$\text{Primary voltage} = \frac{34.5}{\sqrt{3}} = 19.9 \text{ KV} \quad , \quad \text{Secondary voltage} = 13.8 \text{ KV}$$

$$\text{Turns ratio} = \frac{19.9}{13.8} = 1.44$$

$$\text{Apparent power} = \frac{1}{3}(600) = 200 \text{ KVA}$$

Exp 2:

A three-phase transformer has 600 primary turns and 150 secondary turns. If the supply voltage is 1.5 kV determine the secondary line voltage on no-load when the windings are connected:

(a) delta-star, (b) star-delta.



(a) For a delta connection,  $V_L = V_P$

hence, primary phase voltage,  $V_{P_1} = 1.5 \text{ kV} = 1500 \text{ V}$

$$\text{Secondary phase voltage, } V_{P_2} = V_{P_1} \left( \frac{N_2}{N_1} \right) = (1500) \left( \frac{150}{600} \right) = 375 \text{ V}$$

For a star connection,  $V_L = \sqrt{3} V_P$

hence, **secondary line voltage** =  $\sqrt{3}(375) = \mathbf{649.5 \text{ V}}$

(b) For a star connection,  $V_L = \sqrt{3} V_P$  or  $V_P = \frac{V_L}{\sqrt{3}}$

$$\text{Primary phase voltage, } V_{P_1} = \frac{V_{L_1}}{\sqrt{3}} = \frac{1500}{\sqrt{3}} = 866.0 \text{ V}$$

For a delta connection,  $V_L = V_P$


$\frac{N_1}{N_2} = \frac{V_1}{V_2}$  from which, secondary phase voltage,

$$V_{P_2} = V_{P_1} \left( \frac{N_2}{N_1} \right) = (866.0) \left( \frac{150}{600} \right)$$

= **216.5 V = secondary line voltage**



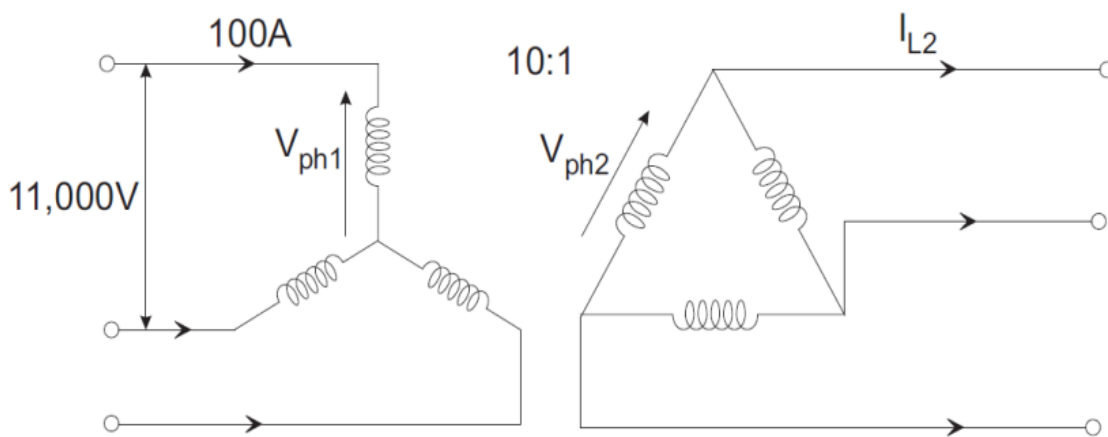Exp 3: A 3-phase transformer bank consisting of three single phase transformers is used to step-down the voltage of a 3-phase, 11000V transmission line. If the primary line current is 100A, calculate the secondary line voltage for Y/ $\Delta$  connection. The turns ratio is 10. Neglect losses. Solution



$$\text{Phase voltage on the primary side, } V_{ph1} = \frac{11,000}{\sqrt{3}} = 6.35kV$$

$$\text{Secondary side phase voltage, } V_{ph2} = \frac{6.35}{10} = 0.635kV$$

Secondary side line voltage = Secondary side phase voltage

$$\text{Secondary side line voltage, } V_{LL2} = \mathbf{0.635 kV}$$

Three single phase transformers of rating 50 kVA, 2000V/1000V are connected in  $\Delta / \Delta$ . Find the current in



Exp 4:

the primary windings of the transformer, when supplying a balanced three phase load of 40kW at 1000V and 0.8 power factor lagging?

Solution

$$\sqrt{3}V_L I_L \cos(\phi) = 40,000W$$

$$\sqrt{3} \times 1000 \times I_L \times 0.8 = 40,000W$$

$$I_L = \frac{40,000}{\sqrt{3} \times 1000 \times 0.8} = 28.86A$$

The current in the windings of the transformer secondary,  $I_{ph2} = \frac{28.86}{\sqrt{3}} = 16.66A$

Current in the primary windings of the transformer,  $I_{ph1} = 16.66 \times \frac{1000}{2000} = 8.33A$

Exp 5:

three phase step down transformer is connected to 3300V supply. The turns ratio per phase is 12 and it draws a current of 5 A from the mains. Calculate the



secondary line voltage and line current if transformer is deltastar connected. Solution

Delta-Star connection

$$\text{Secondary phase voltage} = \frac{3300}{12} = 275V$$

$$\begin{aligned} \therefore \text{Secondary line voltage} &= \text{Secondary phase voltage} \times \sqrt{3} \\ &= 476.31 V \end{aligned}$$

$\therefore$  Secondary line current = Secondary phase current (since, secondary is star)

Secondary phase current = (Primary phase current x 12)

$$\text{Primary phase current} = \frac{\text{Primary line current}}{\sqrt{3}}$$

$$\begin{aligned} \therefore \text{Secondary line current} &= \frac{5}{\sqrt{3}} \times 12 \\ &= 34.64 A \end{aligned}$$

Exp 6: three phase step down transformer is connected to 3300V supply. The turns ratio per phase is 12 and it draws a current of 5 A from the mains. Calculate the secondary line voltage and line current if transformer is stardelta connected. Solution

