



جامعة المستقبل
AL MUSTAQBAL UNIVERSITY



Analog Electronics

Prof. Dr. Ehssan Al-Bermamy

ihsan.zia@uomus.edu.iq

1st semester

Chapter 5

BJT Amplifiers

Lec. 11

The BJT as an Amplifier

- Amplification is the **process of increasing** the **power**, **voltage**, or **current** by **electronic** means it is one of the major properties of a transistor.
- As you learned, a **BJT** exhibits **current gain** (called β).
- When a **BJT** is biased in the active (or **linear**) region, the **BE junction** has a **low resistance due to forward bias** and the **BC junction** has a **high resistance due to reverse bias**.

The DC Operating Point

- Bias establishes a transistor amplifier's operating point (Q-point); the **AC signal moves above and below this point**.
- If an **amplifier is not biased** with **correct DC voltages** on the **input and output**, it can go into **saturation** or **cutoff** when an **input signal is applied**.
- **Improper biasing** can cause **distortion in the output signal**.

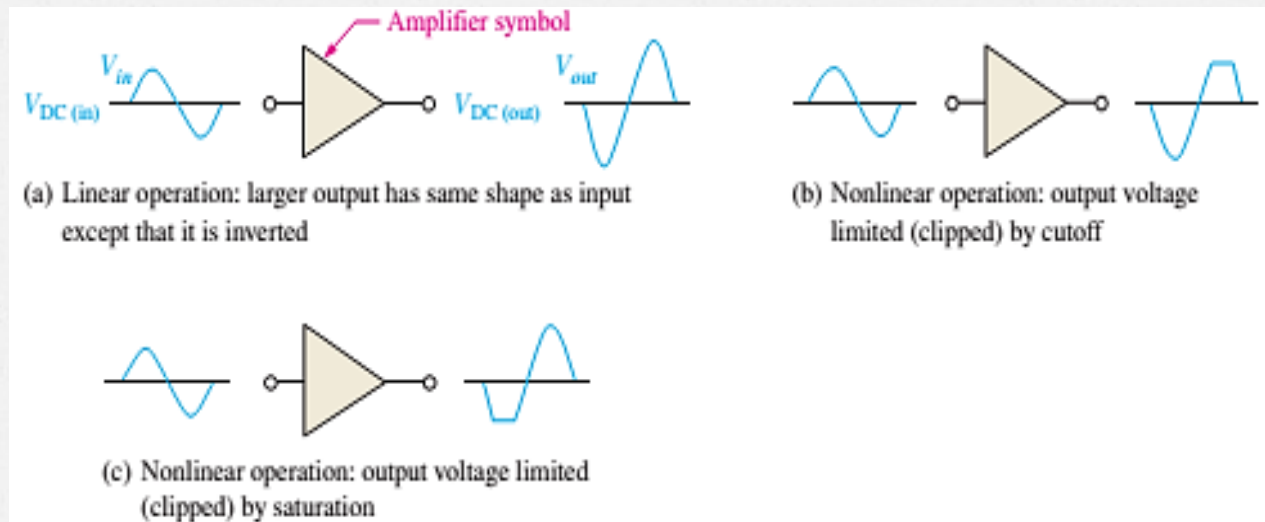


Figure: Examples of linear and nonlinear operation of an inverting amplifier.

- **Points A, Q, and B represent the Q-point for I_B 400 μ A, 300 μ A and 200 μ A, respectively.**
- **Assume sinusoidal voltage, V_{in} , is superimposed on V_{BB} varying between 100 μ A to 300 μ A. It makes the collector current varies between 10 mA and 30 mA.** As a result of the variation in I_C ,
- **the V_{CE} varies between 2.2V and 3.4V.**
- **Under certain input signal conditions, the location of the Q-point on the load line can cause one peak of the V_{ce} waveform to be limited or clipped, as shown in the Figure below. For example, the bias has established a low Q- Q-point. As a result, the signal will be clipped because it is too close to cutoff.**

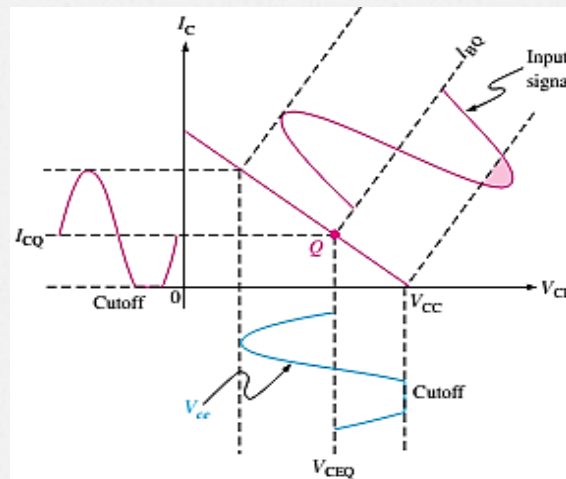


Figure: Graphical load line illustration of a transistor being driven into cutoff. 6

Voltage-Divider Bias

- A **practical** way to **establish a Q-point** is to form a **voltage-divider from V_{CC}** . This is the most widely used biasing method.
- A **DC bias voltage** at the base of the transistor can be developed by a resistive voltage divider that consists of R_1 and R_2 , as in Figure 16.
- R_1 and R_2 are selected to establish V_B .
- If the divider is **stiff**, I_B is **small compared** to I_2 .

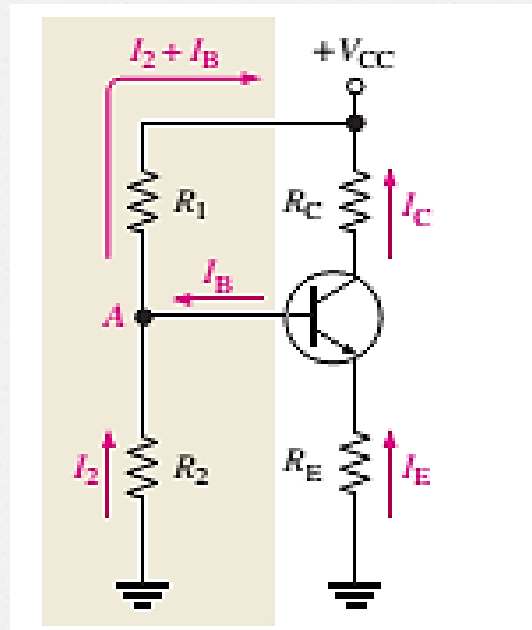


Figure 16: Voltage-divider bias.

- To **analyze a voltage-divider circuit** in which I_B is small compared to I_2 , **first** calculate the voltage on the base:

$$V_B \cong \left(\frac{R_2}{R_1 + R_2} \right) V_{CC}$$

Once you know the **base voltage**, you can find the **voltages** and **currents** in the circuit, as follows:

$$V_E = V_B - V_{BE}$$

And

$$I_C \cong I_E = \frac{V_E}{R_E}$$

Then

$$V_C = V_{CC} - I_C R_C$$

Once you know V_C and V_E , you can determine V_{CE} .

$$V_{CE} = V_C - V_E$$

A practical biasing technique that uses a single biasing source instead of separate V_{CC} and V_{BB} .

A dc bias voltage at the base of the transistor can be developed by a **resistive voltage divider** that consists of R_1 and R_2 .