



جامعة المستقبل
AL MUSTAQBAL UNIVERSITY



Analog Electronics

Prof. Dr. Ehssan Al-Bermamy

ihsan.zia@uomus.edu.iq

1st semester

Chapter 5

Amplifiers

Lec. 12

The Common-Emitter Amplifier

Three amplifier configurations are the **common-emitter**, the **common-base**, and the **common-collector**.

In the common-emitter (CE) amplifier, the **input signal** is applied to the **base** and the **inverted output** is **taken** from the **collector**. **The emitter is common to AC signals.**

Figure 4 shows a common-emitter amplifier with voltage-divider bias and coupling capacitors C_1 and C_3 on the input and output and a bypass capacitor, C_2 , from the emitter to the ground.

The input signal V_{in} is capacitive coupled to the base terminal, and the output signal **V_{out}** is capacitively coupled from the collector to the load.

The A_{CE} amplifier has **high voltage, current, and power gains** **but** a relatively **low input resistance**.

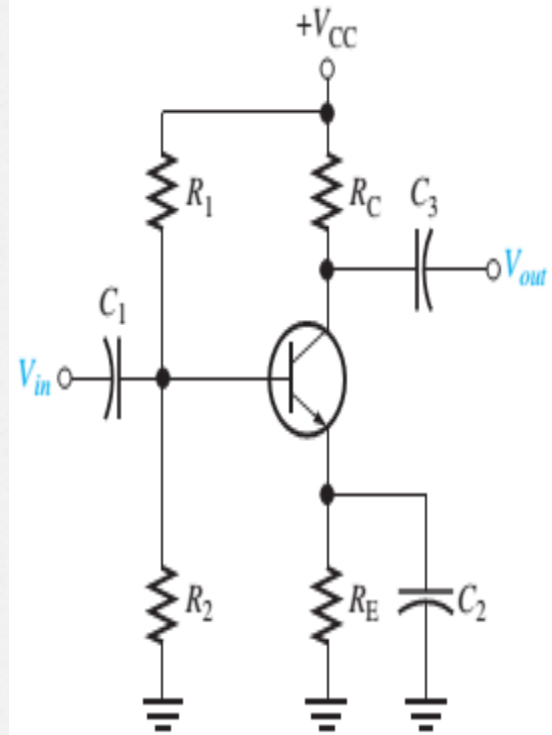


Figure 4: A common-emitter amplifier.

The Common-Base Amplifier

The common-base (CB) amplifier **provides high voltage gain** with a **maximum current gain of 1**. Since it has a low input resistance, the CB amplifier is the most appropriate type for certain applications where sources tend to have **very low-resistance outputs**.

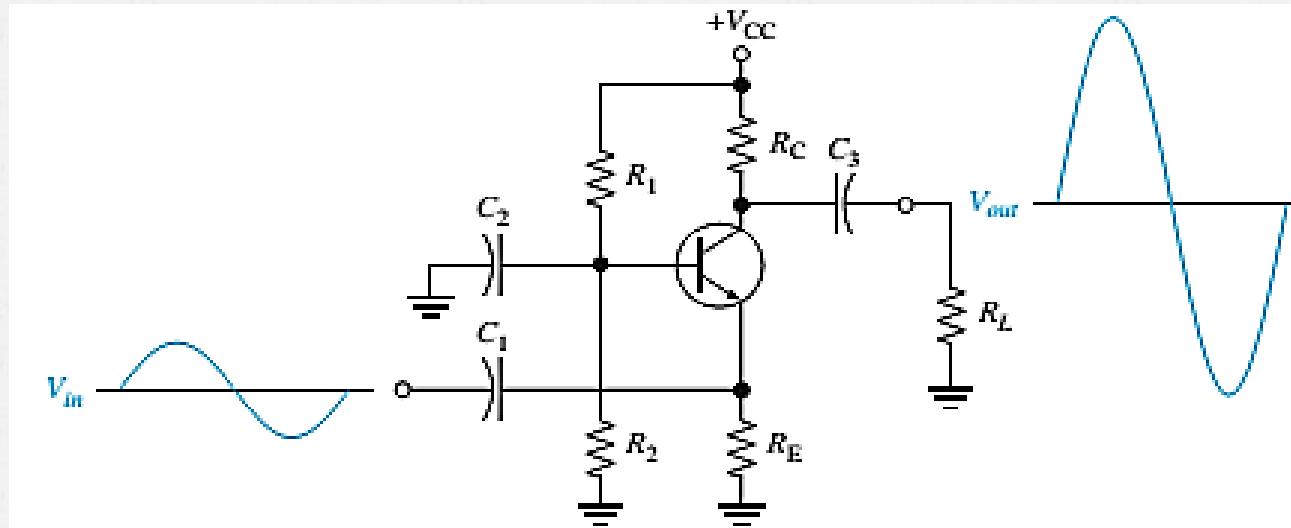


Figure 6: Common-base amplifier with voltage-divider bias.


Capacitors in Amplifier

Coupling capacitors are used to transmit an AC signal from one node to another. Coupling capacitors provide DC isolation between two nodes.

Bypass capacitor is used to short-circuit AC signals to the ground (while not affecting the DC operation of the circuit).

The **value** of the bypass capacitor **must** be **large enough** so that its reactance over the frequency range of the amplifier is very small (ideally) compared to R_E .

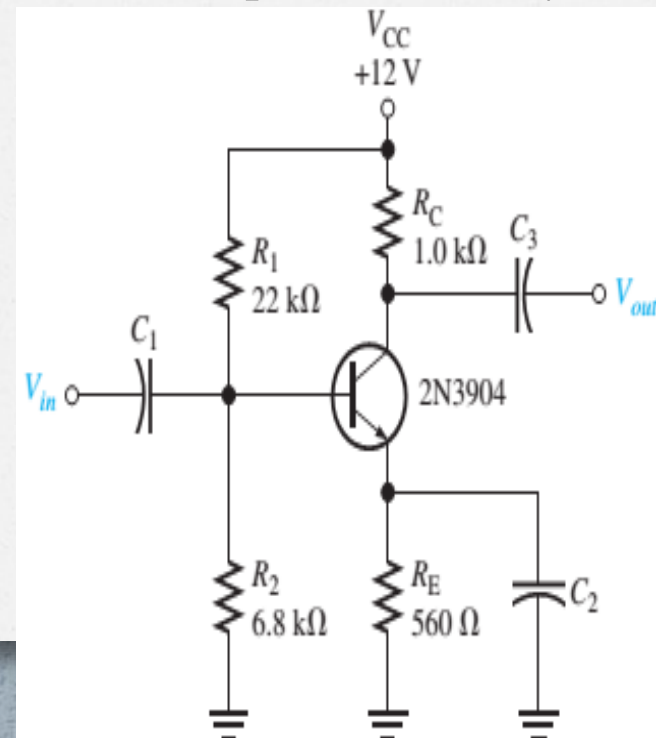The **capacitive reactance, X_C** , of the bypass capacitor should be **at least 10 times smaller than R_E** at the **minimum frequency** for which the amplifier must operate ($10X_C \leq R_E$).



Transistors as a Small Signal Amplifier

There are two analysis; **DC Analysis** and **AC Analysis**.

The **purpose** of DC analysis is to **determine the initial operating values** of **IC**, **IB** and **VCE** (Q-point).

The **goal** is to **set the Q-point** such that it **does not go into saturation or cutoff** when an **AC signal** is applied.

If the **Q-point** is in **active region**, the transistor can operate **as an amplifier**. The **purpose** of **AC analysis** is to **obtain the gain**.

An amplifier is a system that has a **gaining ability to amplify** where a **small** electrical signal will be converted into a strong one. Amplifiers are classified as **small** signal amplifiers (preamplifiers) and **strong** signal amplifiers (power amplifiers).

Amplifiers are able to amplify **current**, **voltage** and/or **power**. In other words, **only amplifiers** are able to produce **power gain** where as other devices such as **transformer** are **only** able to produce **voltage and current gain**.

Small signal amplification **causes small** current changes and **small** output voltage change surrounding operation point (Q-point from DC analysis). These small changes are **small enough** for us to disregard any influence it may have on the transistor's parameter values such as α and β .

There are 4 basic categories of small signal amplifiers:


- Voltage amplifier.
- Current Amplifier
- Trans-conductance Amplifier (converts voltage to current)
- Trans-resistance Amplifier (converts current to voltage)

Gain

The **gain of an amplifier** is the **ratio of an output parameter to an input parameter**.

An amplifier with a current gain of 100—during normal use, the output current is **a hundred times greater** than the input current. There are three types of gain:
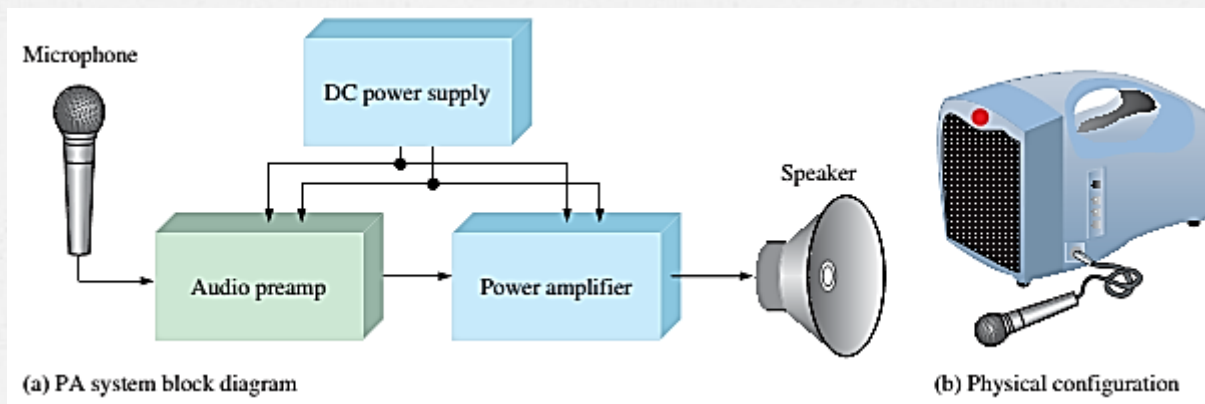
$$\begin{aligned} \text{Current gain} \quad A_i &= \frac{i_o}{i_i} \\ \text{Voltage gain} \quad A_v &= \frac{v_o}{v_i} \\ \text{Power gain} \quad A_p &= \frac{P_o}{P_i} = A_v A_i \end{aligned}$$



H.W

H.W.: Give examples of other amplifiers.