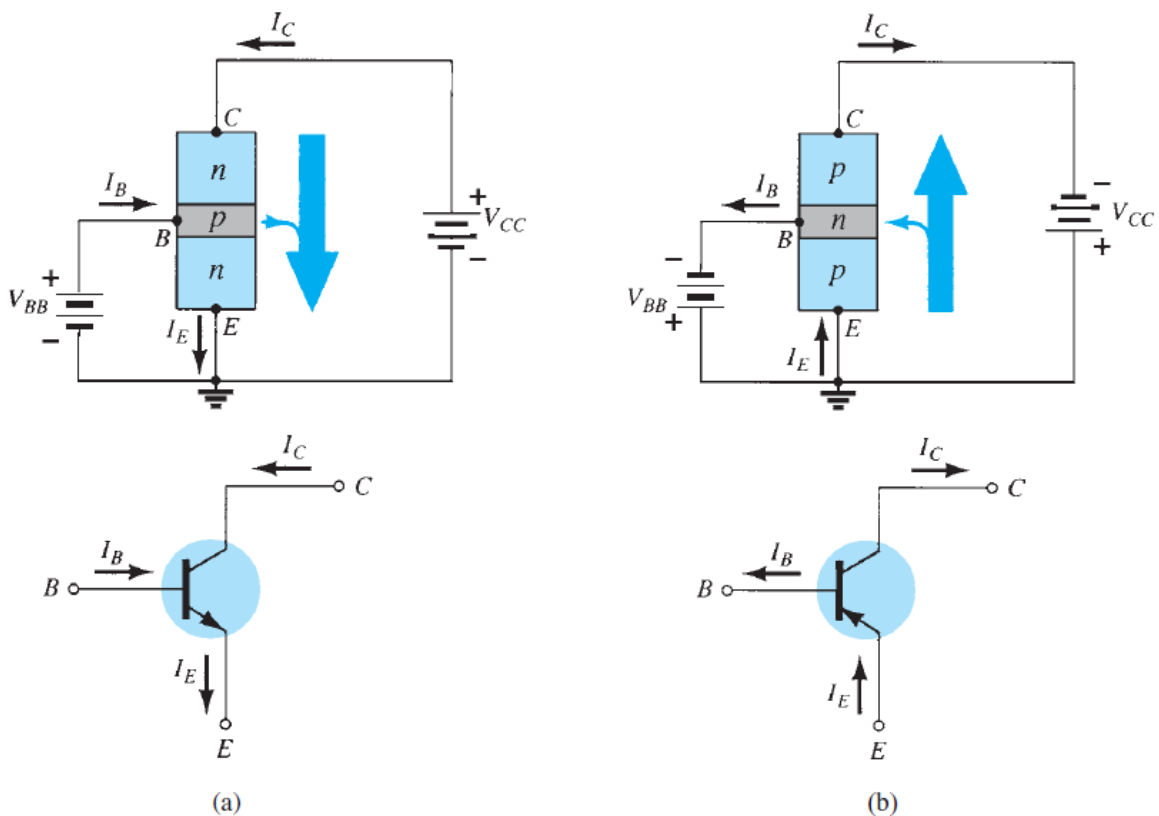


## Bipolar Junction Transistor(BJT)

### 3.5 COMMON-EMITTER CONFIGURATION

The most frequently encountered transistor configuration appears in Fig. 3.12 for the *npn* and *pnp* transistors. It is called the *common-emitter configuration* because the emitter is common to both the input and output terminals (in this case common to both the base and collector terminals). Two sets of characteristics are again necessary to describe fully the behavior of the common-emitter configuration: one for the *input* or *base-emitter* circuit and one for the *output* or *collector-emitter* circuit. Both are shown in Fig. 3.13.



**FIG. 3.12**

Notation and symbols used with the common-emitter configuration: (a) npn transistor;  
(b) pnp transistor.



## CHARACTERISTICS COMMON-EMITTER CONFIGURATION

For the common-emitter configuration the output characteristics are a plot of the output current ( $I_C$ ) versus ( output voltage ( $V_{CE}$ ) for a range of values of input current ( $I_B$ ). The input characteristics are a plot of the input current ( $I_B$ ) versus the input voltage ( $V_{BE}$ ) for a range of values of output voltage ( $V_{CE}$ ).


**Input characteristics:** it is the curve between  $I_B$  and  $V_{BE}$  at constant  $V_{CE}$  the magnitude of  $I_B$  is in microamperes, compared to milliamperes of  $I_C$

**$I_B$**  increases less rapidly with  $V_{BE}$

There for the input resistance of CE circuit is higher than that of CB

Circuit  $r_i = V_{BE}/I_B$

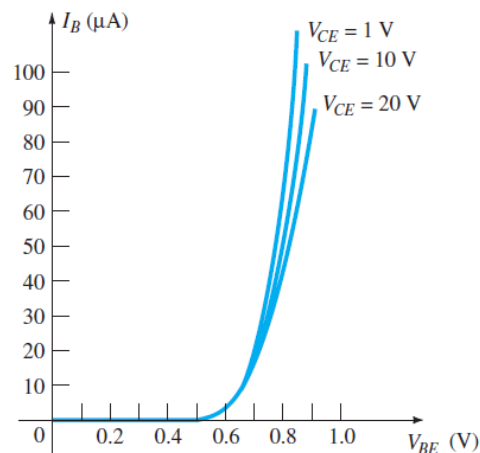,the input current  $I_E$  in CB circuit is higher than that of CB circuit  $I_B$



**Output characteristics;** it is the curve between  $I_C$  and  $V_{CE}$  for a range of values of input current ( $I_B$ ).


The output resistance is high  $r_o = V_{CE}/I_C$  Its value is of the order 500 K



In the active region of a common-emitter amplifier the collector-base junction is reverse-biased, while the base-emitter junction is forward-biased.

The active region of the common emitter configuration can be employed for voltage, current, or power amplification

**The active region;** for the common-emitter configuration is that portion of the upper-right quadrant that has the greatest linearity, that is, that region in which the curves for  $I_B$  are nearly straight and equally spaced. In Fig. 3.14a this region exists to the right of the vertical dashed line at  $V_{CEsat}$  and above the curve for  $I_B$  equal to zero. The region to the left of  $V_{CE sat}$  is called the saturation region In the active region of a common-emitter amplifier the collector-base junction is reversebiased, while the base-emitter junction is forward-biased.

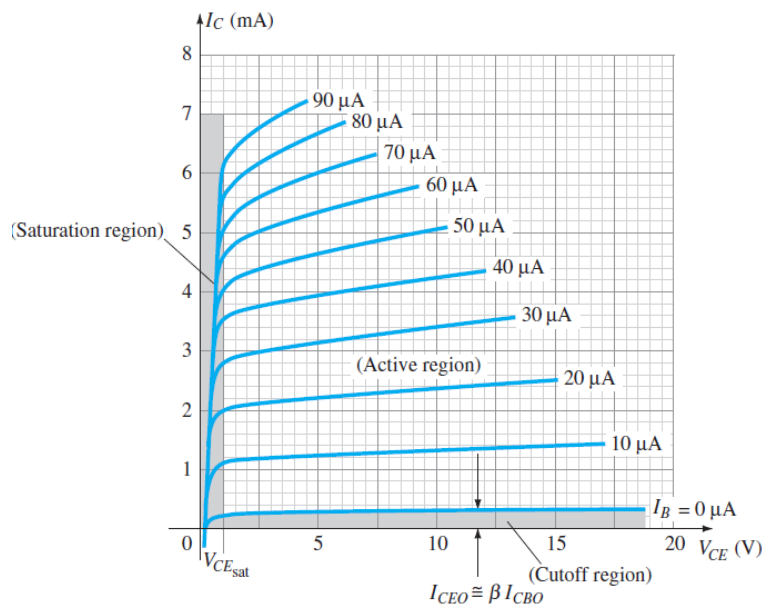

The collector current  $I_c$  varies with  $V_{ce}$  for  $V_{ce}$  between 0 and 1V only after this  $I_c$  becomes almost constant and independent of  $V_{ce}$



**The cutoff region** for the common-emitter configuration is not as well defined as for the common-base configuration. Note on the collector characteristics of Fig. 3.14 that  $I_C$  is not equal to zero when  $I_B$  is zero. For the common-base configuration, when the input current  $I_E$  was equal to zero, the collector current was equal only to the reverse saturation current  $I_{CO}$ , so that the curve  $I_E=0$ . and the voltage axis were, for all practical purposes, one Recall for the common-base configuration that the input set of characteristics was approximated by a straight-line equivalent that resulted in  $V_{BE} = 0.7$  V for any level of  $I_E$  greater than 0 mA..

### Beta ( $\beta$ )

**DC Mode** In the dc mode the levels of  $I_C$  and  $I_B$  are related by a quantity called *beta* and defined by the following equation:

$$\beta_{dc} = \frac{I_C}{I_B} \quad (3.10)$$

A relationship can be developed between  $\beta$  and  $\alpha$  using the basic relationships introduced thus far. Using  $\beta = I_C/I_B$ , we have  $I_B = I_C/\beta$ , and from  $\alpha = I_C/I_E$  we have  $I_E = I_C/\alpha$ . Substituting into

$$I_E = I_C + I_B$$

we have

$$\frac{I_C}{\alpha} = I_C + \frac{I_C}{\beta}$$

and dividing both sides of the equation by  $I_C$  results in

$$\frac{1}{\alpha} = 1 + \frac{1}{\beta}$$

or

$$\beta = \alpha\beta + \alpha = (\beta + 1)\alpha$$

so that


$$\alpha = \frac{\beta}{\beta + 1} \quad (3.12)$$

or

$$\beta = \frac{\alpha}{1 - \alpha} \quad (3.13)$$

## COMMON-COLLECTOR CONFIGURATION


The third and final transistor configuration is the common-collector configuration, shown in Fig. 3.20 with the proper current directions and voltage notation. The common-collector configuration is used primarily for impedance-matching purposes since it has a high input impedance and low output impedance, opposite to that of the common-base and common-emitter configurations.

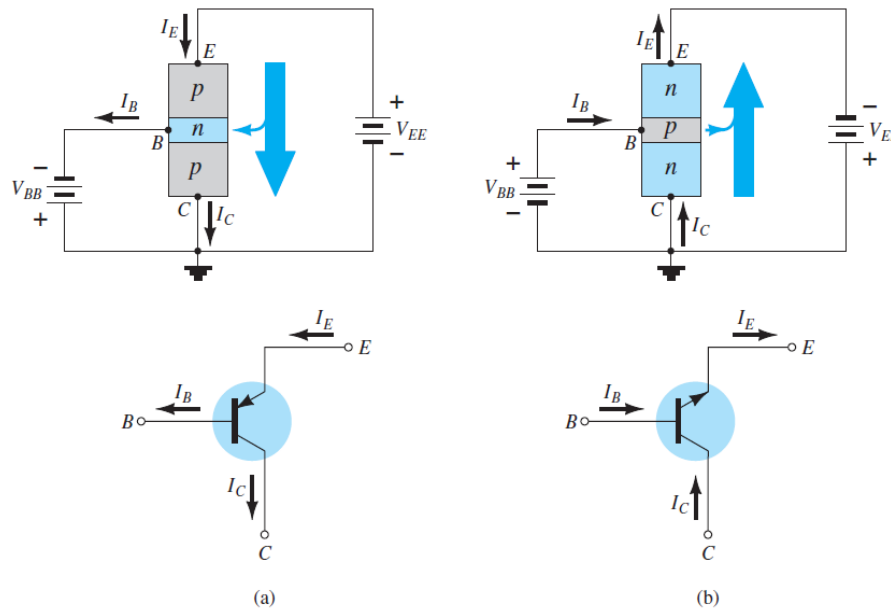

**FIG. 3.20**

*Notation and symbols used with the common-collector configuration: (a) pnp transistor; (b) npn transistor.*

A common-collector circuit configuration is provided in Fig. 3.21 with the load resistor connected from emitter to ground. Note that the collector is tied to ground even though the transistor is connected in a manner similar to the common-emitter configuration.

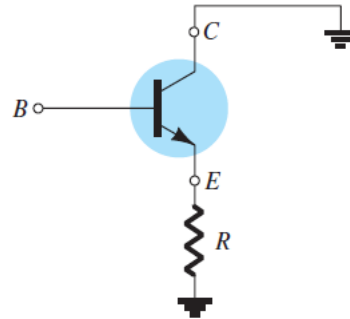

**FIG. 3.21**

*Common-collector configuration  
used for impedance-matching  
purposes.*

For all practical purposes, the output characteristics of the common-collector configuration are the same as for the common-emitter configuration. For the common-collector configuration the output characteristics are a plot of  $I_E$  versus  $V_{EC}$  for a range of values of  $I_B$ . The input current, therefore, is the same for both the common-emitter and common collector characteristics. The horizontal voltage axis for the common collector configuration is obtained by simply changing the sign of the collector-to-emitter voltage of the common-emitter characteristics. Finally, there is an almost unnoticeable change in the vertical scale of  $I_C$  of the common-emitter characteristics if  $I_C$  is replaced by  $I_E$  for the common collector characteristics. For the input circuit of the common-collector configuration the common-emitter base characteristics are sufficient for obtaining the required information.

## **LIMITS OF OPERATION**

For each transistor there is a region of operation on the characteristics which will ensure that the maximum ratings are not being exceeded and the output signal



exhibits minimum distortion . Such a region has been defined for the transistor characteristics of Fig. 3.22.

Some of the limits of operation are self-explanatory, such as maximum collector current (normally referred to on the specification sheet as continuous collector current) and maximum collector-to-emitter voltage (often abbreviated as  $V_{CE0}$  or  $V(BR)_{CE0}$  on the specification sheet). For the transistor of Fig. 3.22,  $I_{Cmax}$  was specified as 50 mA and  $V_{CE0}$  as 20 V. The vertical line on the characteristics defined as  $V_{CEsat}$  specifies

**At  $I_{Cmax}$**  At any point on the characteristics the product of  $V_{CE}$  and  $I_C$  must be equal to 300 mW. If we choose  $I_C$  to be the maximum value of 50 mA and substitute into the relationship above, we obtain

$$\begin{aligned}V_{CE}I_C &= 300 \text{ mW} \\V_{CE}(50 \text{ mA}) &= 300 \text{ mW} \\V_{CE} &= \frac{300 \text{ mW}}{50 \text{ mA}} = \mathbf{6 \text{ V}}\end{aligned}$$

**At  $V_{CEmax}$**  As a result we find that if  $I_C = 50 \text{ mA}$ , then  $V_{CE} = 6 \text{ V}$  on the power dissipation curve as indicated in Fig. 3.22. If we now choose  $V_{CE}$  to be its maximum value of 20 V, the level of  $I_C$  is the following:

$$\begin{aligned}(20 \text{ V})I_C &= 300 \text{ mW} \\I_C &= \frac{300 \text{ mW}}{20 \text{ V}} = \mathbf{15 \text{ mA}}\end{aligned}$$

defining a second point on the power curve.

**At  $I_C = \frac{1}{2}I_{Cmax}$**  If we now choose a level of  $I_C$  in the midrange such as 25 mA and solve for the resulting level of  $V_{CE}$ , we obtain

$$\begin{aligned}V_{CE}(25 \text{ mA}) &= 300 \text{ mW} \\ \text{and} \quad V_{CE} &= \frac{300 \text{ mW}}{25 \text{ mA}} = \mathbf{12 \text{ V}}\end{aligned}$$





## Important Conclusions and Concepts

1. Semiconductor devices have the following advantages over vacuum tubes: They are (1) of **smaller size**, (2) more **lightweight**, (3) more **rugged**, and (4) more **efficient**. In addition, they have (1) **no warm-up period**, (2) **no heater requirement**, and (3) **lower operating voltages**.
2. Transistors are **three-terminal devices** of three semiconductor layers having a base or center layer a great deal **thinner** than the other two layers. The outer two layers are both of either *n*- or *p*-type materials, with the sandwiched layer the opposite type.
3. One *p*-*n* junction of a transistor is **forward-biased**, whereas the other is **reverse-biased**.
4. The dc emitter current is always the **largest current** of a transistor, whereas the base current is always the **smallest**. The emitter current is always the **sum** of the other two.
5. The collector current is made up of **two components**: the **majority component** and the **minority current** (also called the *leakage current*).
6. The arrow in the transistor symbol defines the direction of **conventional current flow for the emitter current** and thereby defines the direction for the other currents of the device.
7. A three-terminal device needs **two sets of characteristics** to completely define its characteristics.
8. In the active region of a transistor, the base-emitter junction is **forward-biased**, whereas the collector-base junction is **reverse-biased**.
9. In the cutoff region the base-emitter and collector-base junctions of a transistor are **both reverse-biased**.
10. In the saturation region the base-emitter and collector-base junctions are **forward-biased**.
11. On an average basis, as a first approximation, the base-to-emitter voltage of an operating transistor can be assumed to be **0.7 V**.
12. The quantity alpha ( $\alpha$ ) relates the collector and emitter currents and is always close to **one**.





Al-Mustaqbal University  
 College of Engineering and Technologies  
 Medical Instrumentation Technique Engineering Department  
 Class: 2<sup>nd</sup>  
 Subject: Electronic Circuits  
 Lecturer: Dr. Rami Qays Malik  
 Lecture: 8- Bipolar Junction Transistor 2



13. The impedance between terminals of a forward-biased junction is always relatively **small**, whereas the impedance between terminals of a reverse-biased junction is usually **quite large**.
14. The arrow in the symbol of an *npn* transistor points out of the device (**not pointing in**), whereas the arrow points in to the center of the symbol for a *pnp* transistor (**pointing in**).
15. For linear amplification purposes, cutoff for the common-emitter configuration will be defined by  $I_C = I_{CEO}$ .
16. The quantity beta ( $\beta$ ) provides an important relationship between the base and collector currents, and is usually between **50 and 400**.
17. The dc beta is defined by a simple **ratio of dc currents at an operating point**, whereas the ac beta is **sensitive to the characteristics** in the region of interest. For most applications, however, the two are considered equivalent as a first approximation.
18. To ensure that a transistor is operating within its maximum power level rating, simply find the **product of the collector-to-emitter voltage and the collector current**, and compare it to the rated value.