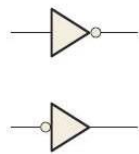


اسم المادة : تقنيات رقمية  
اسم التدريسي : م.م. علياء محمد جواد  
المرحلة : الثانية  
السنة الدراسية : 2023\_2024  
عنوان المحاضرة: Logic Gates


1

## Logic Gates

- The inverter (NOT circuit) performs the operation called *inversion or complementation*.
- The inverter changes one logic level to the opposite level. In terms of bits, it changes a 1 to a 0 and a 0 to a 1.
- Standard logic symbols for the **inverter** are shown below:



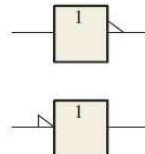(a) Distinctive shape symbols with negation indicators



(b) Rectangular outline symbols with polarity indicators

- The “bubble” indicates negation (**inversion or complementation**) when it appears on the input or output of any logic element.

2

## Logic Gates

### The inverter (NOT circuit)


- Inverter Truth Table

Inverter truth table.

Input	Output
LOW (0)	HIGH (1)
HIGH (1)	LOW (0)

- A **truth table** shows the output for each possible input in terms of levels and corresponding bits.

- Inverter Operation

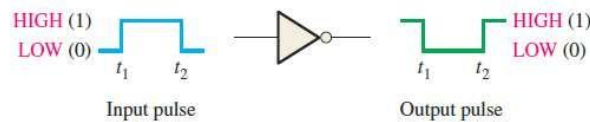

3


## Logic Gates

### The inverter (NOT circuit)

- Logic Expression for an Inverter

- In **Boolean algebra**, which is the mathematics of logic circuits, a variable is generally designated by one or two letters although there can be more.
- The **complement** of a variable is designated by a bar over the letter.
- The operation of an inverter (NOT circuit) can be expressed as follows: If the input variable is called  $A$  and the output variable is called  $X$ , then


$$X = \bar{A}$$

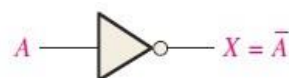

4
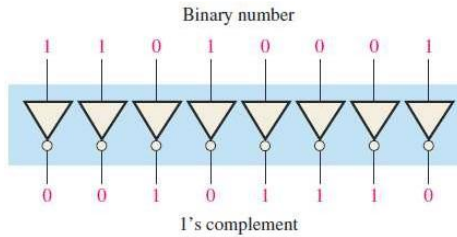
## The inverter (NOT circuit) An Application

- The figure below shows a circuit for producing the 1's complement of an 8-bit binary number.




- The bits of the binary number are applied to the inverter inputs and the 1's complement of the number appears on the outputs.


5
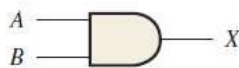
## The AND Gate

- The term *gate* is used to describe a circuit that performs a basic logic operation.
- The **AND gate** is one of the basic gates that can be combined to form any logic function.
- An **AND gate** can have two or more inputs and performs what is known as **logical multiplication**.



(a) Distinctive shape

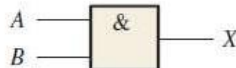

(b) Rectangular outline with the AND (&) qualifying symbol

Truth table for a 2-input AND gate.

Inputs		Output
A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

1 = HIGH, 0 = LOW

6

## Logic Gates

- The total number of **possible combinations of binary inputs to a gate** is determined by the following formula:

$$N = 2^n$$

where  $N$  is the **number of possible input combinations** and  $n$  is the **number of input variables**.

**Example: Develop the truth table for a 3-input AND gate**

**Solution:**

Inputs			Output
A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1




7

## AND Gate

- Logic Expressions for an AND Gate**
- The logical AND function of two variables is represented mathematically either by placing a dot between the two variables, as  $A \cdot B$ , or by simply writing the adjacent letters without the dot, as  $AB$ .
- Boolean multiplication** follows the same basic rules governing binary multiplication, and are as follows:

$$\begin{aligned} 0 \cdot 0 &= 0 \\ 0 \cdot 1 &= 0 \\ 1 \cdot 0 &= 0 \\ 1 \cdot 1 &= 1 \end{aligned}$$

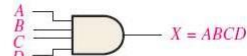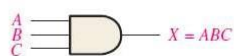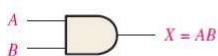**Boolean multiplication is the same as the AND function.**




Boolean expressions for AND gates with two, three, and four inputs.


8
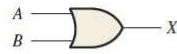
## The OR Gate

- An **OR gate** performs what is known as **logical addition**.
- An **OR gate** can have two or more inputs and one output.



(a) Distinctive shape

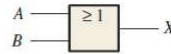

(b) Rectangular outline with the OR ( $\geq 1$ ) qualifying symbol

### OR Gate Truth Table

Truth table for a 2-input OR gate.

Inputs		Output
A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

9

## OR Gate

- **Logic Expressions for an OR Gate**
- The logical OR function of two variables is represented mathematically by a **+** between the two variables, e.g.,  $X = A + B$ . The plus sign is read as "OR."
- The basic rules for **Boolean addition** are as follows:


$$\begin{array}{l} 0 + 0 = 0 \\ 0 + 1 = 1 \\ 1 + 0 = 1 \\ 1 + 1 = 1 \end{array}$$

- **Boolean addition is the same as the OR function.**

10
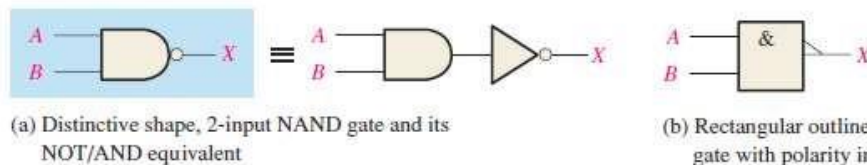
## NAND Gate

- The **NAND gate** is a popular logic element because it can be used as a universal gate such that NAND gates can be used in combination to perform the **AND, OR, and inverter** operations.
- The **NAND gate** is the same as the AND gate except the output is inverted.



11

## NAND Gate

- A **NAND gate** produces a LOW output only when all the inputs are HIGH. When any of the inputs is LOW, the output will be HIGH.
- The table below is for the specific case of a 2-input **NAND gate**

Truth table for a 2-input NAND gate.


Inputs		Output
A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

1 = HIGH, 0 = LOW.

12
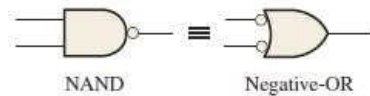
## NAND Gate

- **Negative-OR Equivalent Operation of a NAND Gate**
- For a 2-input NAND gate performing a negative-OR operation, output  $X$  is HIGH when either input  $A$  or input  $B$  is LOW, or when both  $A$  and  $B$  are LOW.





$A$	$B$	$\overline{AB} = X$
0	0	$\overline{0 \cdot 0} = \overline{0} = 1$
0	1	$\overline{0 \cdot 1} = \overline{0} = 1$
1	0	$\overline{1 \cdot 0} = \overline{0} = 1$
1	1	$\overline{1 \cdot 1} = \overline{1} = 0$

- **Logic Expressions for a NAND Gate**
- The Boolean expression for the output of a 2-input NAND gate is  $X = \overline{AB}$  where a bar over a variable or variables indicates an inversion.

13
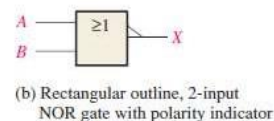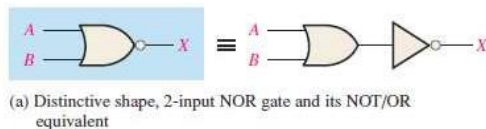
## The NOR Gate

- The **NOR gate**, like the NAND gate, is a useful logic element because it can also be used as a universal gate.
- The NOR is the same as the **OR** except the output is inverted.



- **Operation of a NOR Gate**

Truth table for a 2-input NOR gate.


Inputs		Output
$A$	$B$	$X$
0	0	1
0	1	0
1	0	0
1	1	0

1 = HIGH, 0 = LOW.

14
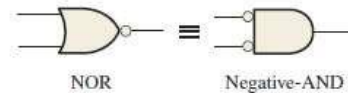
## The NOR Gate

- **Negative-AND Equivalent Operation of the NOR Gate**
- For a 2-input NOR gate performing a negative-AND operation, output  $X$  is HIGH only when both inputs  $A$  and  $B$  are LOW.



- **Logic Expressions for a NOR Gate**

The Boolean expression for the output of a 2-input NOR gate can be written as

$$X = A + B$$

$A$	$B$	$\overline{A + B} = X$
0	0	$\overline{0 + 0} = \overline{0} = 1$
0	1	$\overline{0 + 1} = \overline{1} = 0$
1	0	$\overline{1 + 0} = \overline{1} = 0$
1	1	$\overline{1 + 1} = \overline{1} = 0$


15

## The Exclusive-OR Gate


- The output of an exclusive-OR gate is HIGH *only* when the two inputs are at opposite logic levels.

Truth table for an exclusive-OR gate.

Inputs		Output
$A$	$B$	$X$
0	0	0
0	1	1
1	0	1
1	1	0

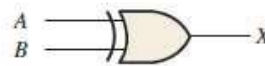

(a) Distinctive shape

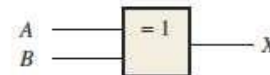

(b) Rectangular outline

16




## The Exclusive-NOR Gate


- For an **exclusive-NOR gate**, output  $X$  is LOW when input  $A$  is LOW and input  $B$  is HIGH, or when  $A$  is HIGH and  $B$  is LOW;  $X$  is HIGH when  $A$  and  $B$  are both HIGH or both LOW.

Truth table for an exclusive-NOR gate.

Inputs		Output
$A$	$B$	$X$
0	0	1
0	1	0
1	0	0
1	1	1

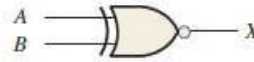

(a) Distinctive shape

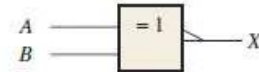


(b) Rectangular outline


17
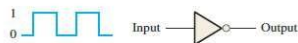
## Timing Diagrams

- a **timing diagram** is basically a graph that accurately displays the relationship of two or more waveforms with respect to each other on a time basis.
- Example:**
- A waveform is applied to an inverter in the figure below.



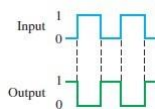- Determine the output waveform corresponding to the input and show the timing diagram.
- Solution:**
- The output waveform is exactly opposite to the input (inverted).



18



## Boolean Algebra and Logic Simplification

- Boolean algebra is the mathematics of digital logic.
- A **variable** is a symbol (usually an italic uppercase letter or word) used to represent an action, a condition, or data. In Boolean algebra, any single variable can have only a 1 or a 0 value.
- The **complement** is the inverse of a variable and it is indicated by a bar over the variable (overbar). For example, the complement of the variable  $A$  is  $\bar{A}$ . If  $A = 1$ , then  $\bar{A} = 0$ . If  $A = 0$ , then  $\bar{A} = 1$ .
- The **complement** of the variable  $A$  is read as “not  $A$ ” or “ $A$  bar.” Sometimes a prime symbol rather than an overbar is used to denote the complement of a variable; for example,  $A'$  indicates a complement of  $A$ .
- A **literal** is a variable or the complement of a variable.

19

## Boolean Addition

- The **Boolean addition** is equivalent to the **OR** operation.
- In Boolean algebra, a **sum term** is a sum of literals.
- Some examples of sum terms are  $A + B$ ,  $A + \bar{B}$ ,  $A + B + \bar{C}$ , and  $\bar{A} + B + C + D$ .
- A **sum term** is equal to 1 when one or more of the literals in the term are 1. A **sum term** is equal to 0 only if each of the literals is 0.
- **Example:** Determine the values of  $A$ ,  $B$ ,  $C$ , and  $D$  that make the sum term  $A + \bar{B} + C + \bar{D}$  equal to 0.
- **Solution:**
- For the sum term to be 0, each of the literals in the term must be 0. Therefore,  $A = 0$ ,  $B = 1$  so that  $\bar{B} = 0$ ,  $C = 0$ , and  $D = 1$  so that  $\bar{D} = 0$ .
- $A + \bar{B} + C + \bar{D} = 0 + 1 + 0 + 1 = 0 + 0 + 0 + 0 = 0$

20


## Boolean Multiplication

- **Boolean multiplication** is equivalent to the **AND** operation.
- In Boolean algebra, a **product term** is the product of literals.
- Some examples of product terms are  $A\bar{B}$ ,  $AB$ ,  $ABC$ , and  $A\bar{B}C\bar{D}$ .
- A **product term** is equal to **1** only if **each** of the **literals** in the term is **1**. A **product term** is equal to **0** when **one or more** of the literals are **0**.
- **Example:** Determine the values of  $A$ ,  $B$ ,  $C$ , and  $D$  that make the product term  $ABCD$  equal to 1.
- **Solution:**
  - For the product term to be 1, each of the literals in the term must be 1. Therefore,  $A = 1$ ,  $B = 0$  so that  $B = 1$ ,  $C = 1$ , and  $D = 0$  so that  $D = 1$ .
  - $ABCD = 1 \cdot 0 \cdot 1 \cdot 0 = 1 \cdot 1 \cdot 1 \cdot 1 = 1$

21
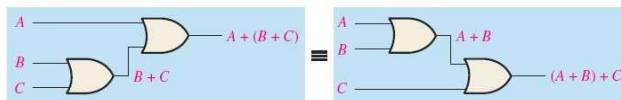
## Laws and Rules of Boolean Algebra

- The **commutative law of addition** for two variables is written as:  
 **$A+B = B+A$**
- The **commutative law of multiplication** for two variables is:  
 **$AB = BA$**
- The **associative law of addition** is written as follows for three variables:  
 **$A+(B+C) = (A+B)+C$**



The **associative law of multiplication** is written as follows for three variables:

$$A(BC) = (AB)C$$


22

## Laws and Rules of Boolean Algebra

- **Distributive Law**

- The distributive law is written for three variables as follows:

$$A(B+C)=AB+AC$$

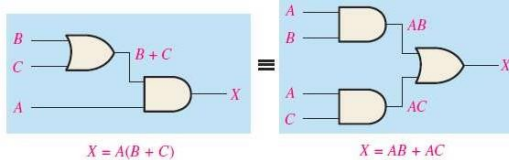

### Basic rules of Boolean algebra

- |                      |                               |
|----------------------|-------------------------------|
| 1. $A + 0 = A$       | 7. $A \cdot A = A$            |
| 2. $A + 1 = 1$       | 8. $A \cdot \bar{A} = 0$      |
| 3. $A \cdot 0 = 0$   | 9. $\bar{\bar{A}} = A$        |
| 4. $A \cdot 1 = A$   | 10. $A + \bar{A}B = A + B$    |
| 5. $A + A = A$       | 11. $A + \bar{A}B = A + B$    |
| 6. $A + \bar{A} = 1$ | 12. $(A + B)(A + C) = A + BC$ |

$A$ ,  $B$ , or  $C$  can represent a single variable or a combination of variables.

23

## Rules of Boolean Algebra

- **Rule 1:**  $A + 0 = A$ . A variable OR with 0 is always equal to the variable.
- **Rule 2:**  $A + 1 = 1$ . A variable OR with 1 is always equal to 1.
- **Rule 3:**  $A \cdot 0 = 0$ . A variable AND with 0 is always equal to 0.
- **Rule 4:**  $A \cdot 1 = A$ . A variable AND with 1 is always equal to the variable.
- **Rule 5:**  $A + A = A$ . A variable OR with itself is always equal to the variable.
- **Rule 6:**  $A + \bar{A} = 1$ . A variable OR with its complement is always equal to 1.
- **Rule 7:**  $A \cdot A = A$ . A variable AND with itself is always equal to the variable.
- **Rule 8:**  $A \cdot \bar{A} = 0$ . A variable AND with its complement is always equal to 0.
- **Rule 9:**  $\bar{\bar{A}} = A$ . The double complement of a variable is always equal to the variable.


24

## Rules of Boolean Algebra

- **Rule 10:**  $A + AB = A$ . This rule can be proved by applying the distributive law, rule 2, and rule 4 as follows:

$$\begin{aligned}
 A + AB &= A \cdot 1 + AB = A(1 + B) && \text{Factoring (distributive law)} \\
 &= A \cdot 1 && \text{Rule 2: } (1 + B) = 1 \\
 &= A && \text{Rule 4: } A \cdot 1 = A
 \end{aligned}$$

A	B	AB	A + AB
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

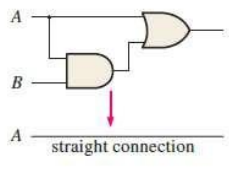


25

## Rules of Boolean Algebra

- **Rule 11:**  $A + \overline{AB} = A + B$ . This rule can be proved as follows:

$$\begin{aligned}
 A + \overline{AB} &= (A + AB) + \overline{AB} && \text{Rule 10: } A = A + AB \\
 &= (AA + AB) + \overline{AB} && \text{Rule 7: } A = AA \\
 &= AA + AB + A\overline{A} + \overline{AB} && \text{Rule 8: adding } A\overline{A} = 0 \\
 &= (A + \overline{A})(A + B) && \text{Factoring} \\
 &= 1 \cdot (A + B) && \text{Rule 6: } A + \overline{A} = 1 \\
 &= A + B && \text{Rule 4: drop the 1}
 \end{aligned}$$

A	B	$\overline{AB}$	$A + \overline{AB}$	$A + B$
0	0	0	0	0
0	1	1	1	1
1	0	0	1	1
1	1	0	1	1

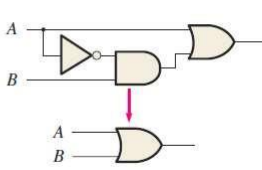


26

## Rules of Boolean Algebra

- **Rule 12:**  $(A + B)(A + C) = A + BC$ . This rule can be proved as follows:

$$\begin{aligned}
 (A + B)(A + C) &= AA + AC + AB + BC && \text{Distributive law} \\
 &= A + AC + AB + BC && \text{Rule 7: } AA = A \\
 &= A(1 + C) + AB + BC && \text{Factoring (distributive law)} \\
 &= A \cdot 1 + AB + BC && \text{Rule 2: } 1 + C = 1 \\
 &= A(1 + B) + BC && \text{Factoring (distributive law)} \\
 &= A \cdot 1 + BC && \text{Rule 2: } 1 + B = 1 \\
 &= A + BC && \text{Rule 4: } A \cdot 1 = A
 \end{aligned}$$

A	B	C	A + B	A + C	(A + B)(A + C)	BC	A + BC
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

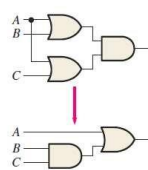

27

## DeMorgan's Theorems

- **DeMorgan's first theorem** is stated as follows:
- **The complement of a product of variables is equal to the sum of the complements of the variables.**

The formula for expressing this theorem for two variables is

$$\overline{XY} = \overline{X} + \overline{Y}$$

**DeMorgan's second theorem** is stated as follows:

- **The complement of a sum of variables is equal to the product of the complements of the variables.**

The formula for expressing this theorem for two variables is

$$\overline{X + Y} = \overline{X} \overline{Y}$$

28



## Applying DeMorgan's Theorems

- The following procedure illustrates the application of DeMorgan's theorems and Boolean algebra to the specific expression

$$\overline{\overline{A + BC} + D(E + F)}$$

**Step 1:** Identify the terms to which you can apply DeMorgan's theorems, and think of each term as a single variable. Let  $A + BC = X$  and  $D(E + F) = Y$ .

**Step 2:** Since  $\overline{X + Y} = \overline{X}\overline{Y}$ ,

$$\overline{(A + BC) + (D(E + F))} = \overline{(A + BC)}\overline{(D(E + F))}$$

**Step 3:** Use rule 9 ( $\overline{\overline{A}} = A$ ) to cancel the double bars over the left term (this is not part of DeMorgan's theorem).

$$(A + BC)\overline{(D(E + F))} = (A + BC)\overline{(D(E + F))}$$

**Step 4:** Apply DeMorgan's theorem to the second term.

$$(A + BC)\overline{(D(E + F))} = (A + BC)(\overline{D} + \overline{(E + F)})$$

**Step 5:** Use rule 9 ( $\overline{\overline{A}} = A$ ) to cancel the double bars over the  $E + F$  part of the term.

$$(A + BC)(\overline{D} + \overline{E + F}) = (A + BC)(\overline{D} + \overline{E} + \overline{F})$$

29

## Applying DeMorgan's Theorems

- Example:** Apply DeMorgan's theorems to the following expression:

$$\overline{(A + B + C)D}$$

- Solution:**

Let  $A + B + C = X$  and  $D = Y$ . The expression  $\overline{(A + B + C)D}$  is of the form  $\overline{XY} = \overline{X} + \overline{Y}$  and can be rewritten as

$$\overline{(A + B + C)D} = \overline{A + B + C} + \overline{D}$$

Next, apply DeMorgan's theorem to the term  $\overline{A + B + C}$ .

$$\overline{A + B + C} + \overline{D} = \overline{A} \overline{B} \overline{C} + \overline{D}$$

30



## Applying DeMorgan's Theorems

- Example: Apply DeMorgan's theorems to the following expression:

$$\overline{ABC + DEF}$$

### Solution

Let  $ABC = X$  and  $DEF = Y$ . The expression  $\overline{ABC + DEF}$  is of the form  $\overline{X + Y} = \overline{XY}$  and can be rewritten as

$$\overline{ABC + DEF} = (\overline{ABC})(\overline{DEF})$$

Next, apply DeMorgan's theorem to each of the terms  $\overline{ABC}$  and  $\overline{DEF}$ .

$$(\overline{ABC})(\overline{DEF}) = (\overline{A + B + C})(\overline{D + E + F})$$

31

## Applying DeMorgan's Theorems

- Example: Apply DeMorgan's theorems to the following expression:

$$\overline{\overline{AB} + \overline{CD} + EF}$$

- Solution:

Let  $\overline{AB} = X$ ,  $\overline{CD} = Y$ , and  $EF = Z$ . The expression  $\overline{\overline{AB} + \overline{CD} + EF}$  is of the form  $\overline{X + Y + Z} = \overline{XYZ}$  and can be rewritten as

$$\overline{\overline{AB} + \overline{CD} + EF} = (\overline{\overline{AB}})(\overline{\overline{CD}})(\overline{EF})$$

Next, apply DeMorgan's theorem to each of the terms  $\overline{\overline{AB}}$ ,  $\overline{\overline{CD}}$ , and  $\overline{EF}$ .

$$(\overline{\overline{AB}})(\overline{\overline{CD}})(\overline{EF}) = (\overline{A + B})(\overline{C + D})(\overline{E + F})$$

32





## Applying DeMorgan's Theorems

- Example: Apply DeMorgan's theorems to each of the following expressions:

(a)  $\overline{\overline{(A + B)} + \overline{C}}$

(b)  $\overline{(\overline{A} + B) + CD}$

(c)  $\overline{(A + B)\overline{CD} + E + \overline{F}}$

- Solution

(a)  $\overline{\overline{(A + B)} + \overline{C}} = \overline{(\overline{A + B})\overline{C}} = (A + B)C$

(b)  $\overline{(\overline{A} + B) + CD} = \overline{(\overline{A} + B)\overline{CD}} = (\overline{\overline{A}B})(\overline{C + D}) = \overline{A}\overline{B}(\overline{C + D})$

(c)  $\overline{(A + B)\overline{CD} + E + \overline{F}} = \overline{((A + B)\overline{CD})(E + \overline{F})} = \overline{(\overline{A}\overline{B} + C + D)EF}$

33

## Applying DeMorgan's Theorem

- Example:

- The Boolean expression for an exclusive-OR gate is  $\overline{A}B + A\overline{B}$ . With this as a starting point, use DeMorgan's theorems and any other rules or laws that are applicable to develop an expression for the exclusive-NOR gate.

- Solution:

Start by complementing the exclusive-OR expression and then applying DeMorgan's theorems as follows:

$$\overline{\overline{A}B + A\overline{B}} = \overline{(\overline{A}B)(A\overline{B})} = \overline{(\overline{A} + \overline{B})(\overline{A} + \overline{B})} = \overline{(\overline{A} + B)(A + \overline{B})}$$

Next, apply the distributive law and rule 8 ( $A \cdot \overline{A} = 0$ ).

$$\overline{(\overline{A} + B)(A + \overline{B})} = \overline{\overline{A}A + \overline{A}\overline{B} + AB + B\overline{B}} = \overline{\overline{A}\overline{B} + AB}$$

The final expression for the XNOR is  $\overline{\overline{A}\overline{B} + AB}$ . Note that this expression equals 1 any time both variables are 0s or both variables are 1s.

34

