

BJT Small-Signal Analysis

Common-Emitter Configuration:

The voltage divider circuit of Fig. 13-1 includes an emitter resistor (R_E) that may or may not be bypassed by an emitter capacitor (C_E) in the ac domain.

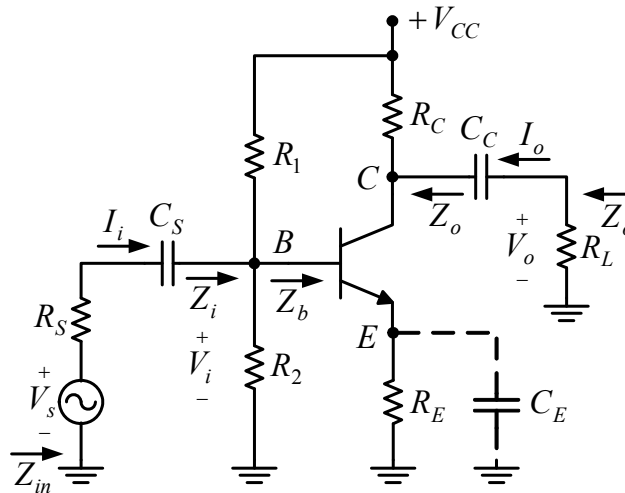


Fig. 13-1

Bypassed (absence of R_E):

For the ac equivalent circuit of Fig. 13-2,

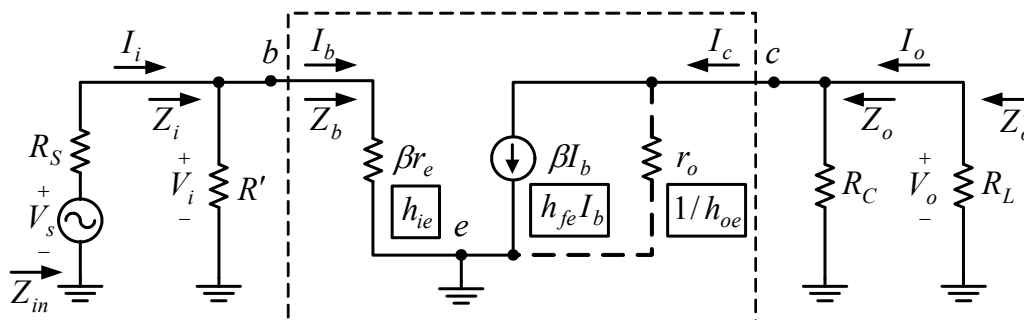


Fig. 13-2

Using r_e equivalent model:

Input impedance:

$$R' = R_1 \parallel R_2$$

$$Z_b = \beta r_e$$

$$Z_i = R' \parallel Z_b = R' \parallel \beta r_e$$

$$Z_{in} = R_S + Z_i = R_S + (R' \parallel \beta r_e)$$

Output impedance:

Approximate (neglecting r_o);
 $Z_o = R_C$
 $Z'_o = R_L \parallel Z_o = R_L \parallel R_C$

Exact (including r_o);
 $Z_o = R_C \parallel r_o$
 $Z'_o = R_L \parallel R_C \parallel r_o$

Voltage gain:

Approximate (neglecting r_o);
 $V_o = -I_c Z'_o = -\beta I_b (R_L \parallel R_C)$

Exact (including r_o);
 $A_v = -\frac{R_L \parallel R_C \parallel r_o}{r_e}$

$$I_b = \frac{V_i}{Z_b} = \frac{V_i}{\beta r_e}$$

$$A_v = \frac{V_o}{V_i} = -\frac{R_L \parallel R_C}{r_e}$$

$$A_{v_s} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \cdot \frac{V_i}{V_s} = A_v \cdot \frac{Z_i}{Z_i + R_S}$$

Current gain:

Approximate (neglecting r_o);
 $A_i = \frac{I_o}{I_i} = \frac{I_o}{I_c} \cdot \frac{I_c}{I_b} \cdot \frac{I_b}{I_i}$

Exact (including r_o);

$$A_i = \frac{\beta r_o R_C R'}{[r_o + (R_C \parallel R_L)](R_C + R_L)(R' + \beta r_e)}$$

$$= \frac{R_C}{R_C + R_L} \cdot \beta \cdot \frac{R'}{R' + Z_b}$$

$$= \frac{\beta R_C R'}{(R_C + R_L)(R' + \beta r_e)}$$

$$A_{i_s} = \frac{I_o}{I_s} = \frac{I_o}{I_i} \cdot \frac{I_i}{I_s} = A_i \cdot \frac{R_S}{R_S + Z_i}$$

As an option:

$$A_v = \frac{V_o}{V_i} = \frac{-I_o R_L}{I_i Z_i} = -\frac{I_o}{I_i} \cdot \frac{R_L}{Z_i} = -A_i \cdot \frac{R_L}{Z_i}$$

$$A_i = \frac{I_o}{I_i} = \frac{-V_o / R_L}{V_i / Z_i} = -\frac{V_o}{V_i} \cdot \frac{Z_i}{R_L} = -A_v \cdot \frac{Z_i}{R_L}$$

Phase relationship:

The negative sign in the resulting equation for A_v reveals that a 180° phase shift occurs between the input and output voltage signals.

Using hybrid equivalent model:

Approximate (neglecting h_{oe});

$$Z_b = h_{ie}$$

$$A_v = -\frac{h_{fe}(R_L \parallel R_C)}{h_{ie}}$$

$$A_i = \frac{h_{fe}R_C R'}{(R_C + R_L)(R' + h_{ie})}$$

Exact (including h_{oe});

$$A_v = -\frac{h_{fe}(R_L \parallel R_C \parallel 1/h_{oe})}{h_{ie}}$$

$$A_i = \frac{h_{fe}R_C R' / h_{oe}}{[1/h_{oe} + (R_C \parallel R_L)](R_C + R_L)(R' + h_{ie})}$$

Unbypassed (include of R_E):

For the approximate ac equivalent circuit ($r_o = 1/h_{oe} \approx \infty \Omega$) of Fig. 13-3,

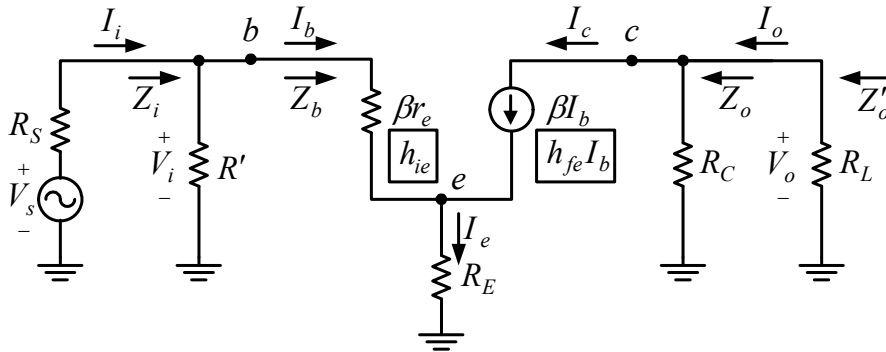


Fig. 13-3

Using r_e equivalent model:

Input impedance:

$$V_i = I_b \beta r_e + I_e R_E = I_b [\beta r_e + (\beta + 1) R_E]$$

$$Z_b = \frac{V_i}{I_b} = \beta r_e + (\beta + 1) R_E \approx \beta (r_e + R_E) \approx \beta R_E$$

$$Z_i = R' \parallel Z_b = R' \parallel [\beta r_e + (\beta + 1) R_E] \approx R' \parallel \beta (r_e + R_E) \approx R' \parallel \beta R_E$$

Output impedance:

$$Z_o = R_C$$

$$Z'_o = R_L \parallel Z_o = R_L \parallel R_C$$

Voltage gain:

$$V_o = -I_c Z'_o = -\beta I_b (R_L \parallel R_C)$$

$$I_b = \frac{V_i}{Z_b} = \frac{V_i}{\beta (r_e + R_E)}$$

$$A_v = \frac{V_o}{V_i} = -\frac{R_L \parallel R_C}{r_e + R_E} \approx -\frac{R_L \parallel R_C}{R_E}$$

Current gain:

$$\begin{aligned} A_i &= \frac{I_o}{I_i} = \frac{I_o}{I_c} \cdot \frac{I_c}{I_b} \cdot \frac{I_b}{I_i} \\ &= \frac{R_C}{R_C + R_L} \cdot \beta \cdot \frac{R'}{R' + Z_b} \\ &= \frac{\beta R_C R'}{(R_C + R_L)[R' + \beta(r_e + R_E)]} \approx \frac{\beta R_C R'}{(R_C + R_L)(R' + \beta R_E)} \end{aligned}$$

Phase relationship:

V_o and V_i are out-of-phase by 180° .

Using hybrid equivalent model:

$$Z_b = h_{ie} + (h_{fe} + 1)R_E \approx h_{ie} + h_{fe}R_E \approx h_{fe}R_E$$

$$A_v = -\frac{h_{fe}(R_L \parallel R_C)}{h_{ie} + h_{fe}R_E} \approx -\frac{R_L \parallel R_C}{R_E}$$

$$A_i = \frac{h_{fe}R_C R'}{(R_C + R_L)(R' + h_{ie} + h_{fe}R_E)} \approx \frac{h_{fe}R_C R'}{(R_C + R_L)(R' + h_{fe}R_E)}$$

Common-Base Configuration:

The common-base configuration of Fig. 13-4 is characterized as having a relatively low input and a high output impedance and a current gain less than 1. The voltage gain, however, can be quite large.

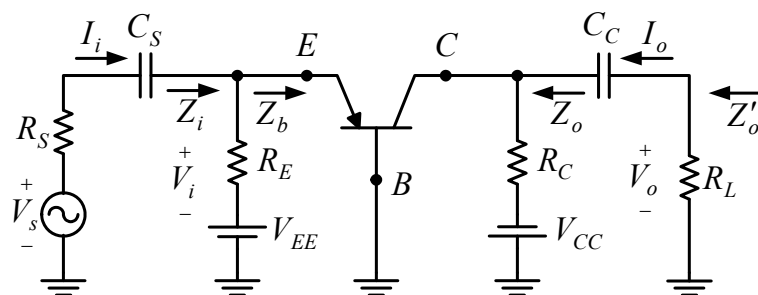


Fig. 13-4

Using r_e equivalent model:

For the approximate ac equivalent circuit ($r_o \approx \infty\Omega$) of Fig. 13-5,

Input impedance:

$$Z_b = r_e$$

$$Z_i = R_E \parallel r_e \quad [\text{low}]$$

Output impedance:

$$Z_o = R_C \quad [\text{high}]$$

$$Z'_o = R_L \parallel R_C$$

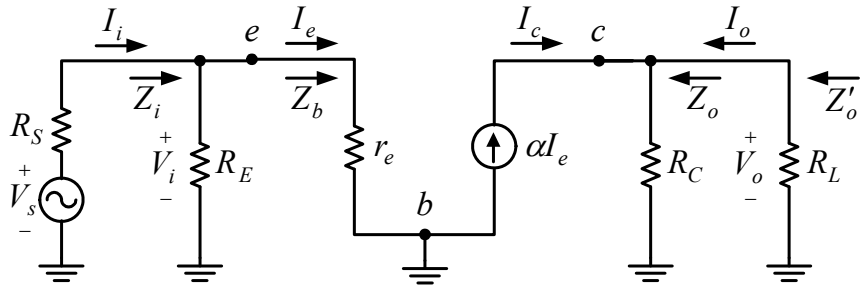


Fig. 13-5

Voltage gain:

$$V_o = I_c Z'_o = \alpha I_e (R_L \parallel R_C)$$

$$I_e = V_i / r_e$$

$$A_v = \frac{\alpha (R_L \parallel R_C)}{r_e} \cong \frac{R_L \parallel R_C}{r_e} \quad [\text{high}]$$

Current gain:

$$A_i = \frac{I_o}{I_i} = \frac{I_o}{I_c} \cdot \frac{I_c}{I_e} \cdot \frac{I_e}{I_i} = -\frac{R_C}{R_C + R_L} \cdot \alpha \cdot \frac{R_E}{R_E + r_e}$$

$$= -\frac{\alpha R_C R_E}{(R_C + R_L)(R_E + r_e)} \quad [\text{less than } 1]$$

Phase relationship:

V_o and V_i are in-phase.

Using hybrid equivalent model:

For the approximate ac equivalent circuit ($1/h_{ob} \approx \infty\Omega$) of Fig. 13-6,

$$Z_b = h_{ib}$$

$$Z_i = R_E \parallel h_{ib}$$

$$A_v = -\frac{h_{fb}(R_L \parallel R_C)}{h_{ib}}$$

$$A_i = \frac{h_{fb} R_C R_E}{(R_C + R_L)(R_E + h_{ib})}$$

[h_{fb} : -ve quantity]

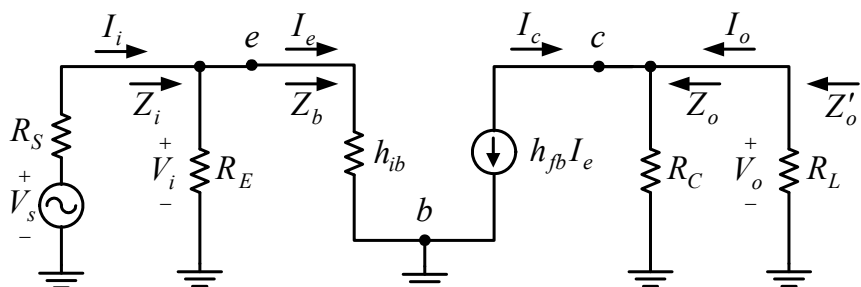


Fig. 13-6

Common-Collector (Emitter-Follower] Configuration:

When the output is taken from the emitter terminal of the transistor, an amplifier circuit is referred to as emitter-follower as shown in Fig. 13-7. The emitter-follower configuration is frequently used for impedance-matching purposes. It presents a high impedance at the input and a low impedance at the output. Also, the output voltage is always slightly less than the input signal with an in-phase relationship between them.

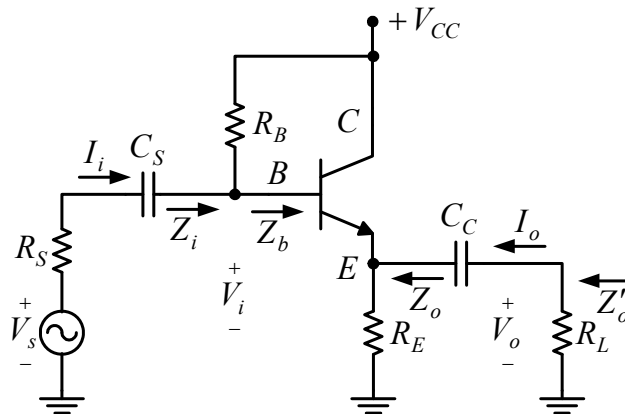


Fig. 13-7

Using r_e equivalent model:

For the ac equivalent circuit of Fig. 13-8,

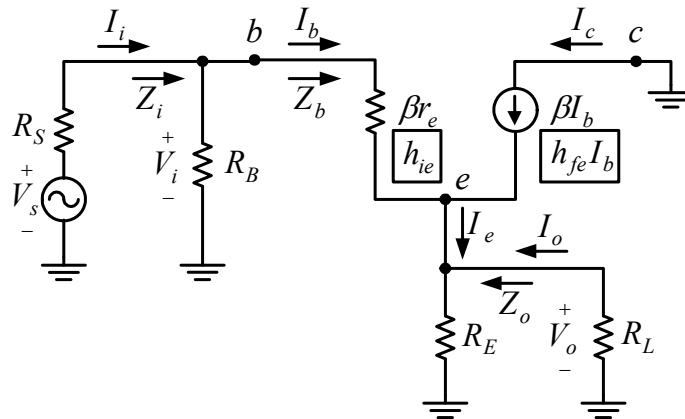


Fig. 13-8

Input impedance:

$$R' = R_L \parallel R_E$$

$$V_i = I_b \beta r_e + I_e R' = I_b [\beta r_e + (\beta + 1) R']$$

$$Z_b = V_i / I_b = \beta r_e + (\beta + 1) R'$$

$$\approx \beta (r_e + R') \approx \beta R' \quad [high]$$

$$Z_i = R_B \parallel Z_b$$

Output impedance:

$$V_s - I_i R_S - I_b \beta r_e - I_e R' = 0 \quad [\text{KVL}]$$

For the circuit of Fig. 13-9a,

$$R_{Th} = R_S \parallel R_B, \text{ and } E_{Th} = \frac{V_s R_B}{R_S + R_B}$$

where $R_B \gg R_S \Rightarrow$

$$R_{Th} \approx R_S, \quad E_{Th} \approx V_s, \quad \text{and } I_i \approx I_b$$

$$V_s - I_b R_S - I_b \beta r_e - I_b (\beta + 1) R' = 0$$

$$I_b = \frac{V_s}{R_S + \beta r_e + (\beta + 1) R'}$$

$$I_e = (\beta + 1) I_b = \frac{(\beta + 1) V_s}{R_S + \beta r_e + (\beta + 1) R'}$$

$$\approx \frac{V_s}{R_S / \beta + r_e + R'}$$

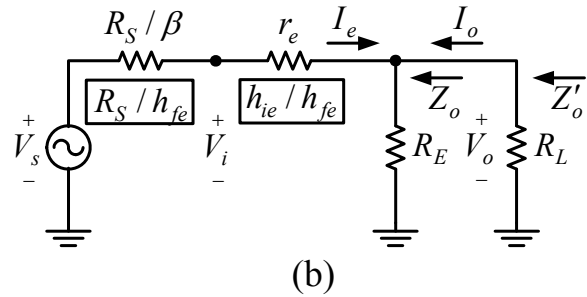
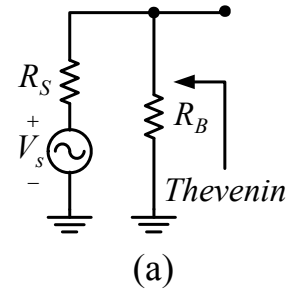


Fig. 13-9

Drawing the circuit to "fit" the above last equation will result in the configuration of Fig. 13-9b. Thus

$$Z_o = R_E \parallel (R_S / \beta + r_e) \quad [\text{low}]$$

$$Z'_o = R_L \parallel Z_o$$

Voltage gain:

$$A_v = \frac{V_o}{V_i} = \frac{I_e R'}{I_e (R' + r_e)} = \frac{R'}{R' + r_e} \quad [\text{less than } 1]$$

$$A_{v_s} = \frac{V_o}{V_s} = \frac{R'}{R' + R_S / \beta + r_e}$$

Current gain:

$$A_i = \frac{I_o}{I_i} = \frac{I_o}{I_e} \cdot \frac{I_e}{I_b} \cdot \frac{I_b}{I_i} = -\frac{R_E}{R_E + R_L} \cdot (\beta + 1) \cdot \frac{R_B}{R_B + Z_b}$$

$$\approx -\frac{\beta R_E R_B}{(R_E + R_L)(R_B + \beta R')} \quad [\text{high}]$$

Phase relationship:

V_o and V_i are in-phase.

Using *hybrid* equivalent model:

$$Z_b = h_{ie} + (h_{fe} + 1)R' \approx h_{fe}R'$$

$$Z_o = R_E \parallel (R_S + h_{ie}) / h_{fe}$$

$$A_v = \frac{R'}{R' + h_{ie} / h_{fe}}$$

$$A_{v_s} = \frac{R'}{R' + (R_s + h_{ie}) / h_{fe}}$$

$$A_i = -\frac{h_{fe}R_ER_B}{(R_E + R_L)(R_B + h_{fe}R')}$$

Example 13-1:

For the BJT amplifier circuit of Fig. 13-10 with the following parameters:

$V_{BE} = 0.7 \text{ V}$, $\beta = h_{fe} \approx 250$, and $r_o = 1/h_{oe} \approx \infty \Omega$, determine:

- (a) r_e , and dc output voltage (V_C).
- (b) h_{ie} , Z_b , Z_i , Z_o , and Z'_o .
- (c) $A_v = V_o/V_i$, and $A_i = I_o/I_i$.
- (d) $A_{v_s} = V_o/V_s$, and ac output voltage (V_o).

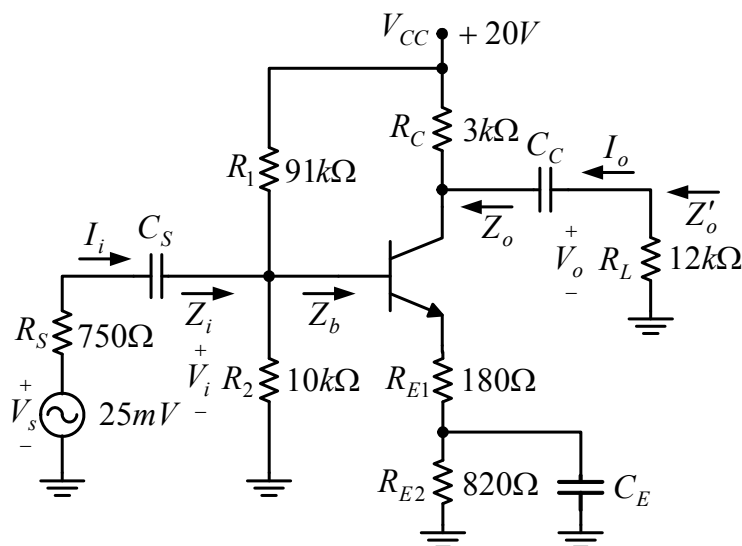


Fig. 13-10

Solution:

Testing: $\beta R_E \geq 10R_2$, $R_E = R_{E1} + R_{E2} = 0.18k + 0.82k = 1k\Omega$,
 $250(1k) \geq 10(10k)$, $250k > 100k$ Satisfied,

$$V_B = \frac{V_{CC} \cdot R_2}{R_1 + R_2} = \frac{20(10k)}{10k + 91k} = 1.98V, \quad I_E = \frac{V_B - V_{BE}}{R_E} = \frac{1.98 - 0.7}{1k} = 1.28mA,$$

$$r_e = \frac{26mV}{I_E} = \frac{26m}{1.28m} = 20.3\Omega, \quad I_C \approx I_E = 1.28mA, \text{ and}$$

$$V_C = V_{CC} - I_C R_C = 20 - 1.28m(3k) = 16.16V.$$

$$h_{ie} = \beta r_e = 250(20.3) = 5.075k\Omega,$$

$$Z_b = h_{ie} + (h_{fe} + 1)R_{E1} = 5.075k + 251(0.18k) = 50.26k\Omega,$$

$$R' = R_1 \parallel R_2 = 91k \parallel 10k = 9.01k\Omega, \quad Z_i = R' \parallel Z_b = 9.01k \parallel 50.26k = 7.64k\Omega,$$

$$Z_o = R_C = 3k\Omega, \text{ and } Z'_o = R_L \parallel R_C = 12k \parallel 3k = 2.4k\Omega.$$

$$A_v = -\frac{h_{fe} Z'_o}{Z_b} = -\frac{250(2.4k)}{50.26k} = -11.94, \text{ and } A_i = -A_v \frac{Z_i}{R_L} = \frac{11.94(7.64k)}{12k} = 7.6.$$

$$A_{v_s} = A_v \frac{V_i}{V_s} = A_v \frac{Z_i}{Z_i + R_S} = \frac{-11.94(7.64k)}{7.64k + 0.75k} = -10.87, \text{ and}$$

$$V_o = A_{v_s} \cdot V_s = -10.87(25m) = -271.75mV.$$

Example 13-2:

Design the BJT amplifier circuit shown in Fig. 13-11 to have a voltage gain magnitude of 4, $Z_i = 3.37 \text{ k}\Omega$, $Z_o = 3 \text{ k}\Omega$, and $Z'_o = 2 \text{ k}\Omega$. Assume that the transistor is silicon with $\beta = 100$, $h_{ie} = 1 \text{ k}\Omega$, $r_o = 1/h_{oe} \approx \infty \Omega$, and $\beta R_E > 10R_2$.

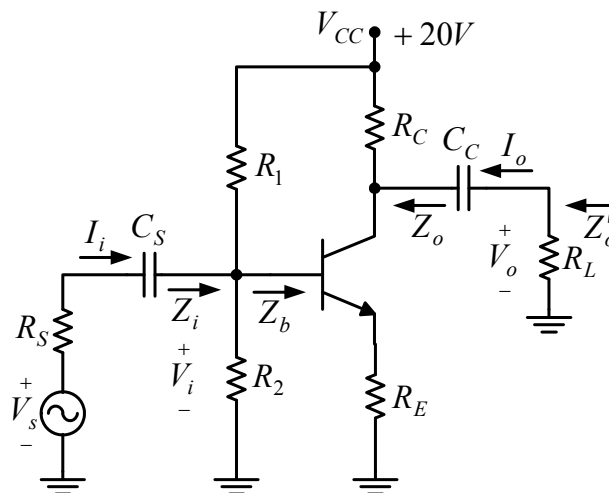


Fig. 13-11

Solution:

$$R_C = Z_o = 3k\Omega, \quad Z'_o = R_L \parallel R_C \Rightarrow 2k = R_L \parallel 3k \Rightarrow R_L = 6k\Omega.$$

$$A_v \approx \frac{Z'_o}{R_E} \Rightarrow 4 \approx \frac{2}{R_E} \Rightarrow R_E \approx 0.5k\Omega.$$

$$h_{ie} = \beta r_e \Rightarrow 1k = 100r_e \Rightarrow r_e = 10\Omega, \quad r_e = \frac{26mV}{I_E} \Rightarrow 10 = \frac{26m}{I_E} \Rightarrow I_E = 2.6mA.$$

$$V_E = I_E R_E = 2.6m(0.5k) = 1.3V, \quad V_B = V_E + V_{BE} = 1.3 + 0.7 = 2V.$$

$$\because \beta R_E > 10R_2 \Rightarrow \frac{V_B}{V_{CC}} = \frac{R_2}{R_1 + R_2} \Rightarrow \frac{2}{20} = \frac{R_2}{R_1 + R_2} \Rightarrow \frac{R_2}{R_1 + R_2} = 0.1 \text{ ----- [a]}$$

$$Z_b = h_{ie} + (\beta + 1)R_E = 1k + 101(0.5k) = 51.5k\Omega.$$

$$Z_i = R' \parallel Z_b \Rightarrow 3.37k = R' \parallel 51.5k \Rightarrow R' = 3.6k\Omega.$$

$$R' = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} \Rightarrow \frac{3.6k}{R_1} = \frac{R_2}{R_1 + R_2} \text{ ----- [b]}$$

$$\text{From Eqs. [a] and [b]: } \frac{3.6k}{R_1} = 0.1 \Rightarrow R_1 = 36k\Omega.$$

$$\text{From Eq. [a]: } \frac{R_2}{36k + R_2} = 0.1 \Rightarrow R_2 = 4k\Omega.$$

Example 13-3:

Complete the design of the BJT amplifier circuit shown in Fig. 13-12 for a voltage gain of 125, $Z_o = 2.4 k\Omega$, $Z'_o = 2 k\Omega$. Assume that $\alpha = 0.985$, $|V_{BE}| = 0.7 V$, and $r_o = 1/h_{ob} \approx \infty \Omega$. Calculate A_v , and V_o .

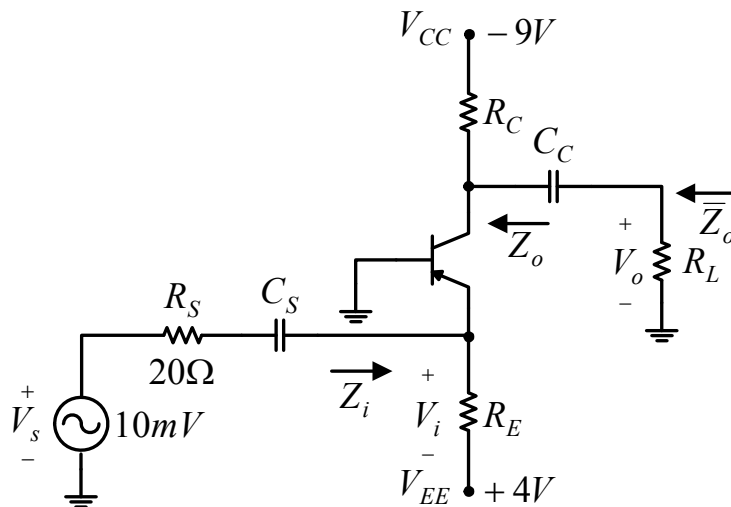


Fig. 13-12

Solution:

$$R_C = Z_o = 2.4k\Omega.$$

$$Z'_o = R_L \parallel R_C \Rightarrow 2k = R_L \parallel 2.4k \Rightarrow R_L = 12k\Omega.$$

$$A_v = \frac{\alpha Z'_o}{r_e} \Rightarrow 125 = \frac{0.985(2k)}{r_e} \Rightarrow r_e = 15.76\Omega.$$

$$r_e = \frac{26mV}{I_E} \Rightarrow 15.76 = \frac{26m}{I_E} \Rightarrow I_E = 1.65mA.$$

$$R_E = \frac{V_{EE} - V_{BE}}{I_E} = \frac{4 - 0.7}{1.65m} = 2k\Omega.$$

$$Z_i = r_e \parallel R_E = 15.76 \parallel 2k = 15.64\Omega.$$

$$A_{v_s} = A_v \frac{Z_i}{Z_i + R_s} = \frac{125(15.64)}{15.64 + 20} = 55.$$

$$V_o = A_{v_s} \cdot V_s = 55(10m) = 550mV.$$

Exercises:

1. For each one of the circuits shown in Fig. 13-13, write a mathematical expression to determine each of the following parameters by using *hybrid* or *r_e* equivalent model.

- (a) Z_b and Z_i . (b) Z_o and Z'_o . (c) A_i and A_v .

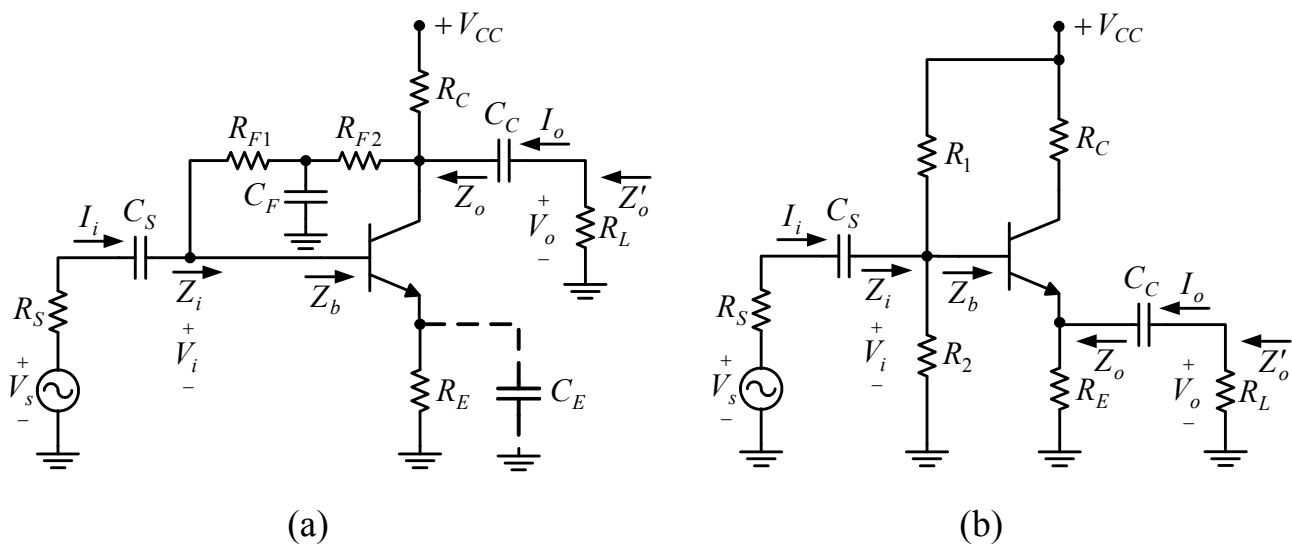


Fig. 13-13

2. For the common-base amplifier of Fig. 13-14, determine the following parameters using the complete hybrid equivalent model and compare the results to those obtained using the approximate model.
- (a) Z_b and Z_i . (b) Z_o and Z'_o . (c) A_i and A_{v_s} . (d) A_i and A_{i_s} .

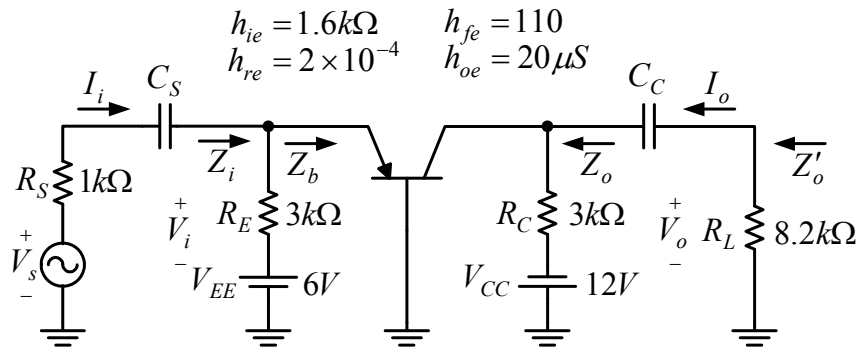


Fig. 13-14

3. Complete the design of the BJT amplifier circuit shown in Fig. 13-15 for a voltage gain magnitude of 205, $Z_i = 1.5k\ \Omega$, and $Z'_o = 3.2\ k\Omega$. Assume that $\beta = 100$, $V_{BE} = 0.7\ V$, $R_{F1}/R_{F2} = 1.95$, and $r_o = 1/h_{oe} \approx \infty\ \Omega$. Sketch V_o to the same time scale as V_s .

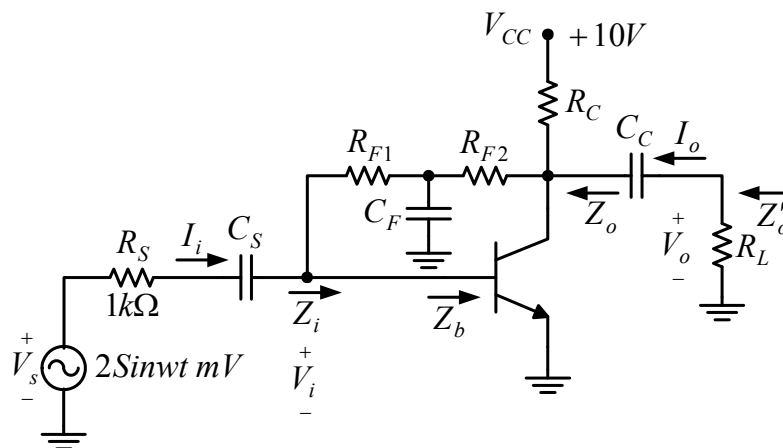


Fig. 13-15