

JFET Small-Signal Analysis

Common-Source Configuration:

The common-source configuration circuit of Fig. 17-1 includes a source resistor (R_S) that may or may not be bypassed by a source capacitor (C_S) in the ac domain.

 


Fig. 17-1

Bypassed (absence of R_S):

For the ac equivalent circuit of Fig. 17-2,

 


Fig. 17-2

Input impedance:

$$Z_i = R_G$$

Output impedance:

Approximate (neglecting r_d);

$$Z_o = R_D \quad (\text{for } r_d \geq 10R_D)$$

$$Z'_o = R_L \| R_D$$

Exact (including r_d);

$$Z_o = R_D \| r_d$$

$$Z'_o = R_L \| Z_o = R_L \| R_D \| r_d$$

Voltage gain:

Approximate (neglecting r_d);

$$V_o = -g_m V_{gs} (R_L \parallel R_D),$$

$$V_{gs} = V_i,$$

$$A_v = \frac{V_o}{V_i} = -g_m (R_L \parallel R_D)$$

$$A_{v_s} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \cdot \frac{V_i}{V_s} = A_v \cdot \frac{Z_i}{Z_i + R_{sig}}$$

Exact (including r_d);

$$A_v = -g_m (R_L \parallel R_D \parallel r_d)$$

Current gain:

$$A_i = \frac{I_o}{I_i} = -A_v \cdot \frac{Z_i}{R_L}$$

Phase relationship:

The negative sign in the resulting equation for A_v reveals that a 180° phase shift occurs between the input and output signals.

Unbypassed (include of R_s):

For the approximate ac equivalent circuit ($r_d \approx \infty \Omega$) of Fig. 17-3,

 


Fig. 17-3

Output impedance:

For $V_i = 0V$, $I_o + I_{R_D} = g_m V_{gs}$, with $V_{gs} = -V_{R_S} \Big|_{V_i=0V} = -(I_o + I_{R_D})R_S$,

so that $I_o + I_{R_D} = -g_m(I_o + I_{R_D})R_S$, or $I_o(1 + g_m R_S) = -I_{R_D}(1 + g_m R_S)$,

and $I_o = -I_{R_D}$.

Since $V_o = -I_{R_D} R_D$, Then $V_o = -(-I_o)R_D = I_o R_D$, and

$$Z_o = \frac{V_o}{I_o} = R_D$$

Voltage gain:

$$V_o = -g_m V_{gs} (R_L \| R_D)$$

$$V_{gs} = V_g - V_s = V_i - g_m V_{gs} R_S \Rightarrow V_i = (1 + g_m R_S) V_{gs}$$

$$A_v = \frac{V_o}{V_i} = -\frac{g_m (R_L \| R_D)}{1 + g_m R_S}$$

Common-Drain (Source-Follower) Configuration:

The common-drain (source-follower) configuration circuit is shown in Fig. 17-4.

 


Fig. 17-4

For the ac equivalent circuit of Fig. 17-5,

 


Fig. 17-5

Input impedance:

$$Z_i = R_G \quad [\text{high}]$$

Output impedance:

$$\text{For } V_i = 0V, I_o + g_m V_{gs} = I_{r_d} + I_{R_S} = V_o / r_d + V_o / R_S \Rightarrow$$

$$I_o = V_o (1/r_d + 1/R_S) - g_m V_{gs}, \text{ with } V_{gs} = -V_o |_{V_i=0V} \Rightarrow I_o = V_o (1/r_d + 1/R_S + g_m),$$

and $Z_o = V_o/I_o = 1/[1/r_d + 1/R_S + 1/(1/g_m)] \Rightarrow$

$$Z_o = r_d \| R_S \| 1/g_m \quad [\text{low}]$$

$$Z_o = R_S \| 1/g_m = \frac{R_S}{1 + g_m R_S} \quad (\text{for } r_d \geq 10R_S)$$

Voltage gain:

$$V_o = g_m V_{gs} (R_L \| R_S \| r_d),$$

$$V_{gs} = V_g - V_s = V_i - V_o = V_i - g_m V_{gs} (R_L \| R_S \| r_d) \Rightarrow V_i = [1 + g_m (R_L \| R_S \| r_d)] V_{gs},$$

$$A_v = \frac{V_o}{V_i} = \frac{g_m (R_L \| R_S \| r_d)}{1 + g_m (R_L \| R_S \| r_d)} \quad [\text{less than 1}]$$

$$A_v = \frac{g_m (R_L \| R_S)}{1 + g_m (R_L \| R_S)} \quad (\text{for } r_d \geq 10R_S)$$

Phase Relationship:

V_o and V_i are in-phase.

Common-Gate Configuration:

The common-gate configuration circuit is shown in Fig. 17-6.

 


Fig. 17-6

For the approximate ac equivalent circuit ($r_d \approx \infty \Omega$) of Fig. 17-7,

 


Fig. 17-7

Input impedance:

$$Z_i = R_S \| 1/g_m = \frac{R_S}{1 + g_m R_S} \quad [\text{low}] \quad (\text{Derive})$$

Output impedance:

$$Z_o = R_D$$

Voltage gain:

$$V_o = -g_m V_{gs} (R_L \| R_D), \text{ and } V_{gs} = -V_i \Rightarrow$$

$$A_v = \frac{V_o}{V_i} = g_m (R_L \| R_D)$$

Phase Relationship:

V_o and V_i are in-phase.

Example 17-1 (Analysis):

For the JFET amplifier circuit of Fig. 17-8 with parameter $g_m = 2.2 \text{ mS}$, determine: Z_i , Z_o , Z'_o , $A_v = V_o/V_i$, $A_i = I_o/I_i$, $A_{v_s} = V_o/V_s$ and V_o . Assume $r_d > 10R_D$.

 


Fig. 17-8

Solution:

$$Z_i = R_1 \| R_2 = 2.1M \| 0.27M = 239k\Omega.$$

$$Z_o = R_D = 2.4k\Omega, \quad Z'_o = R_L \| R_D = 4.7k \| 2.4k = 1.59k\Omega.$$

$$A_v = -\frac{g_m (R_L \| R_D)}{1 + g_m R_{S1}} = -\frac{(2.2m)(1.59k)}{1 + (2.2m)(0.3k)} = -2.11.$$

$$A_i = -A_v \frac{Z_i}{R_L} = -\frac{(-2.11)(239k)}{4.7k} = 107.$$

$$A_{v_s} = A_v \frac{Z_i}{Z_i + R_{sig}} = \frac{(-2.11)(239k)}{239k + 1k} = -2.10 \approx A_v.$$

$$V_o = A_{v_s} V_s = -2.10(200m) = 420mV.$$

Example 17-2 (Design):

Complete the design of the JFET amplifier circuit shown in Fig. 17-9 to have a voltage gain magnitude of 17.5 dB, using a relatively high level of g_m for this device defined at $V_{GSQ} = V_P/4$. Assume $r_d > 10R_D$.

 


Fig. 17-9

Solution:

$$V_{GSQ} = V_P / 4 = -4 / 4 = -1V,$$

$$g_m = \frac{2I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P} \right) = \frac{2(10m)}{4} \left(1 - \frac{-1}{-4} \right) = 3.75mS,$$

$$G(dB) = 20 \log_{10} |A_v| \Rightarrow 17.5 = 20 \log_{10} |A_v| \Rightarrow |A_v| = 7.5,$$


$$|A_v| = g_m (R_L \| R_D) \Rightarrow 7.5 = 3.75m(6k \| R_D) \Rightarrow R_D = 3k\Omega.$$

$$I_{DQ} = I_{DSS} \left(1 - \frac{V_{GSQ}}{V_P} \right)^2 = 10m \left(1 - \frac{-1}{-4} \right)^2 = 5.625mA,$$


$$V_{GSQ} = -I_{DQ} R_S \Rightarrow -1 = -5.625m(R_S) \Rightarrow R_S = 178\Omega.$$

 Exercises:

- For each one of the circuits shown in Fig. 17-10, determine:
 (a) V_{GS} , and g_m . (b) Z_i , and Z_o . (c) $A_v = V_o / V_i$, and $A_i = I_o / I_i$.



(a)

 

(b)

Fig. 17-10

- Choose the values of R_D , R_S , and R_L for the JFET amplifier circuit of Fig. 17-11 that will result in a gain of 18.062 dB. Assume that $I_{DSS} = 8 \text{ mA}$, $V_P = -4 \text{ V}$, $r_d \approx \infty \Omega$, $V_{DQ}/V_{DD} = 0.375$, and $I_{DQ}/I_{DSS} = 0.25$. Calculate $A_{v_s} = V_o / V_s$, and sketch V_o .

 


Fig. 17-11