



Half Subtractor:

H.S is used to subtract two bit numbers.



A	B	D	Br
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$D = A \oplus B$$

$$Br = \overline{AB}$$

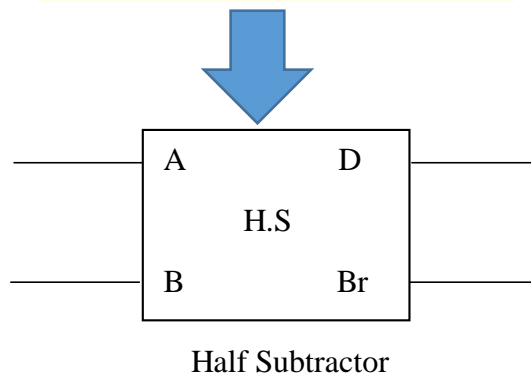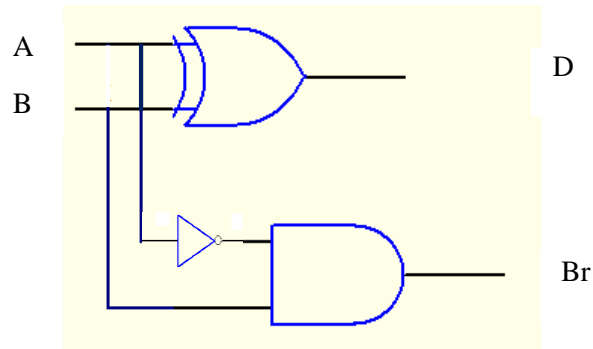

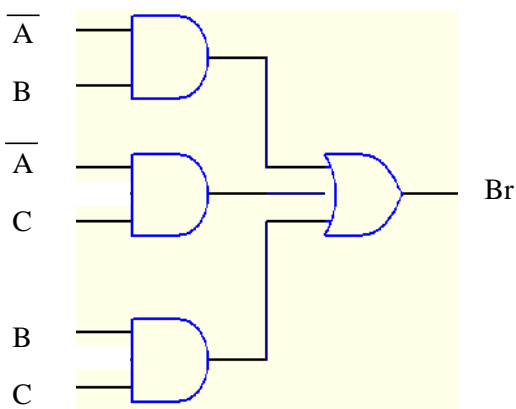
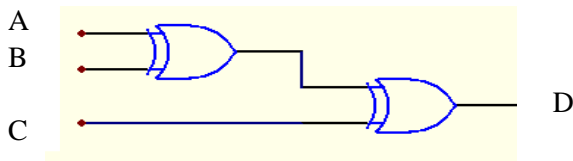
Full subtractor: Full Subtractor is used to subtract three bits.



A	B	C	D	Br
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


$$D = A \oplus B \oplus C$$
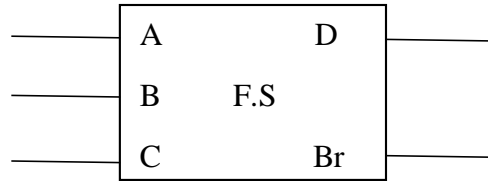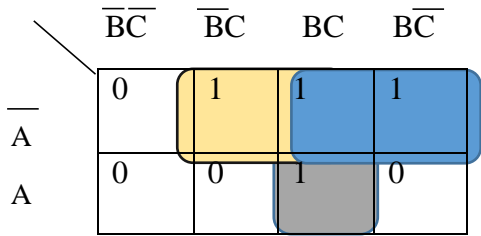
$$Br = \overline{A}B + \overline{A}C + BC$$




Full Subtractor


Ex1: Designing F.S using H.S's and OR gate

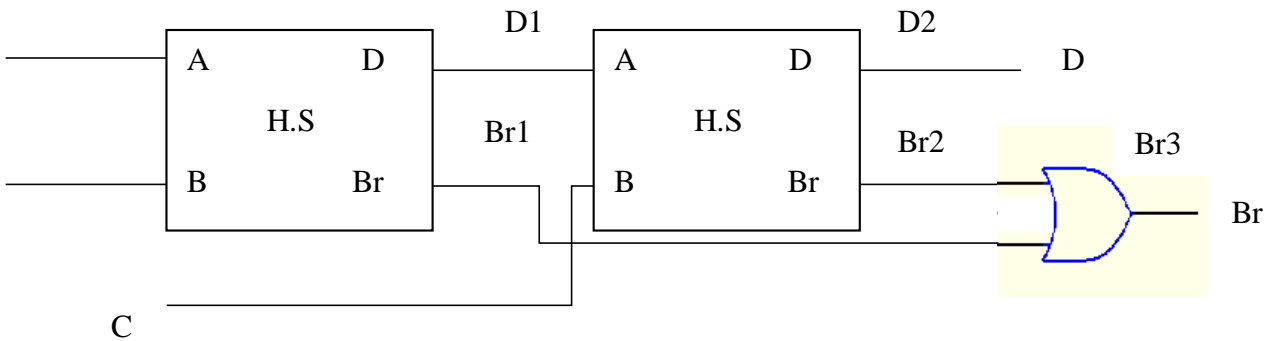

Ex2:


Design a logic circuit to subtract two 2-bit numbers using subtractions:

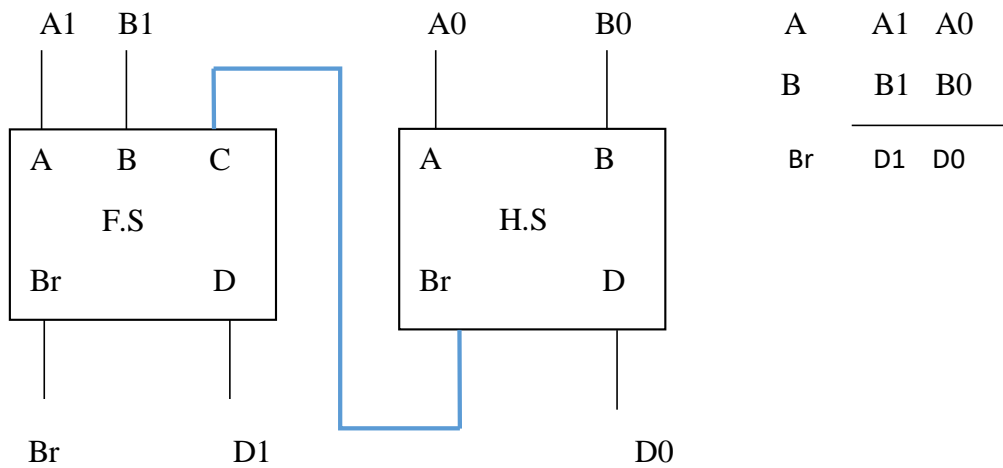

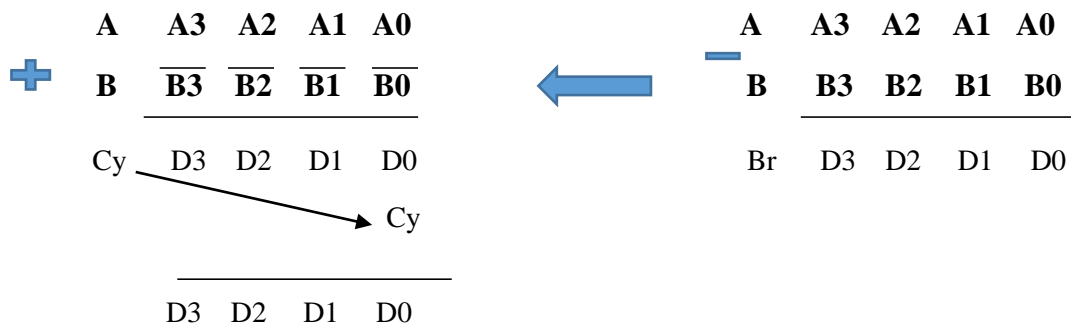


Ex5:

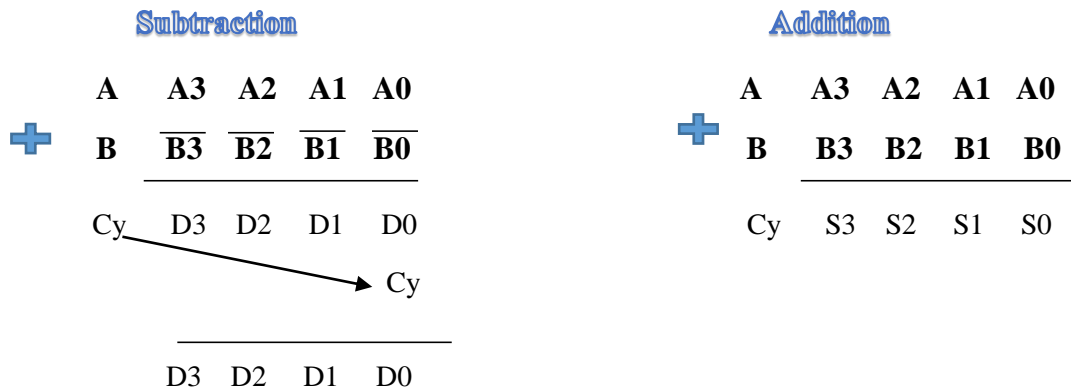Design a logic circuit to Add/subtract two 4-bit numbers using Adders and logic gates:



X = 0 Addition A + B

X = 1 Subtraction A + \overline{B} (1's complement Subtraction)

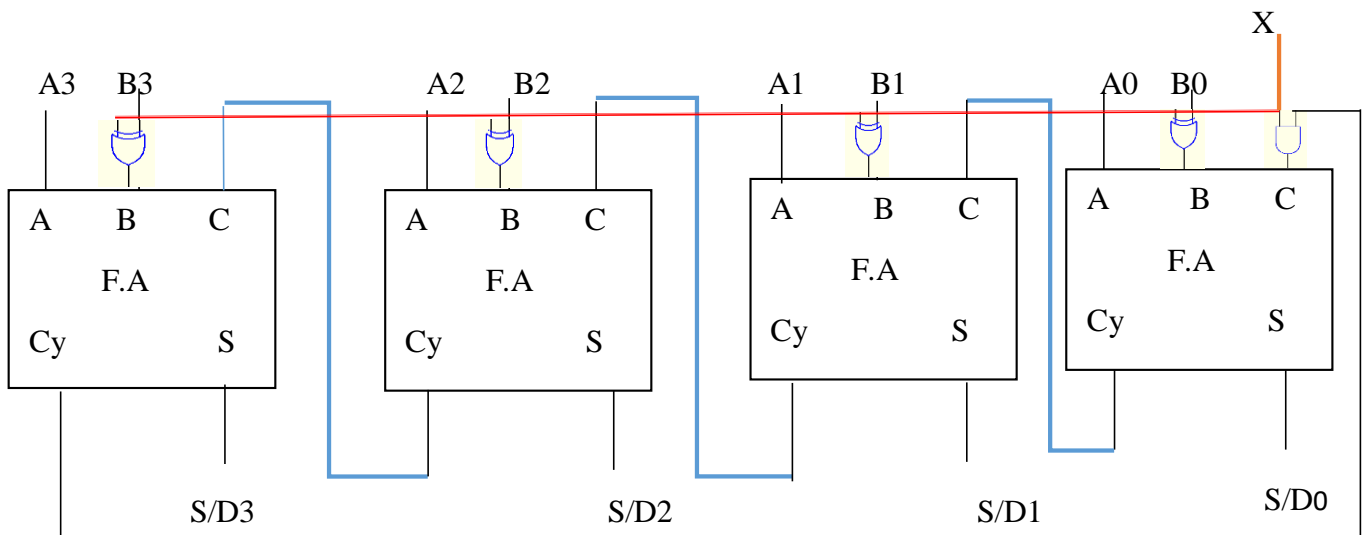

Ex6:

Convert a subtraction of 4-bit numbers to comparator:

