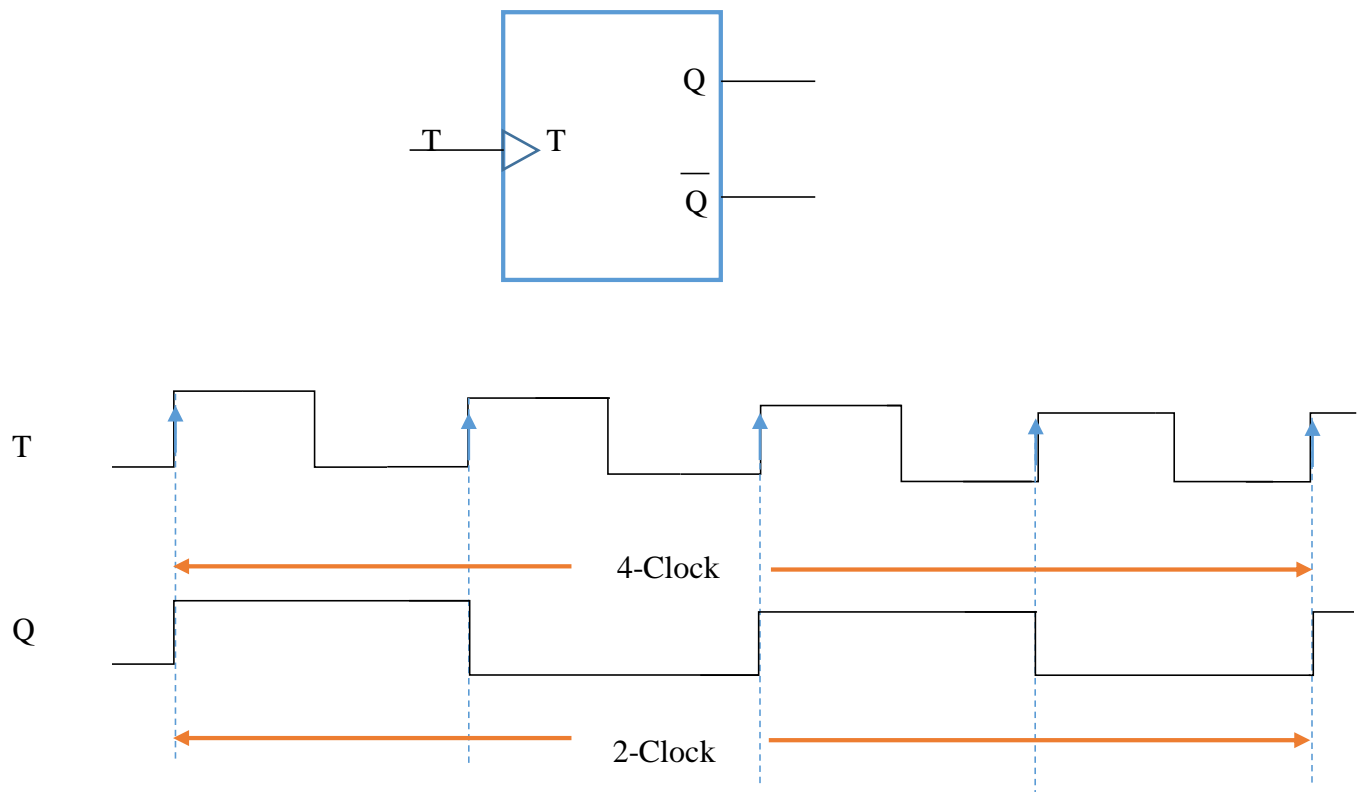


Counter


A counter is a device which can count any particular event on the basis of how many times the particular event(s) is occurred.

Asynchronous Counters:



The term asynchronous refers to events that do not have a fixed time relationship with each other and, generally, do not occur at the same time. An asynchronous counter is one in which the flip-flops (FF) within the counter do not change states at exactly the same time because they do not have a common clock pulse.




*T-Flip Flop is use to divide the input frequency of digital signal by 2.

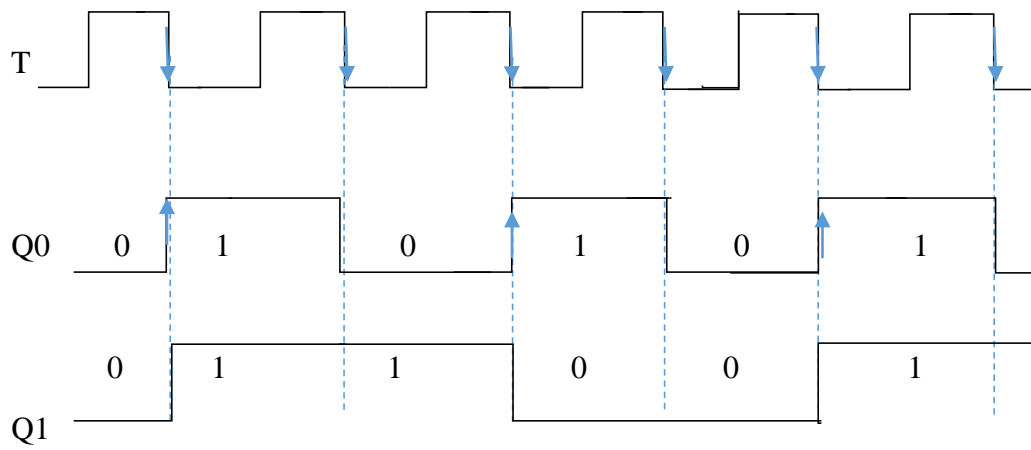

Ex1: Design 3-bit binary asynchronous down counter and draw timing diagram.

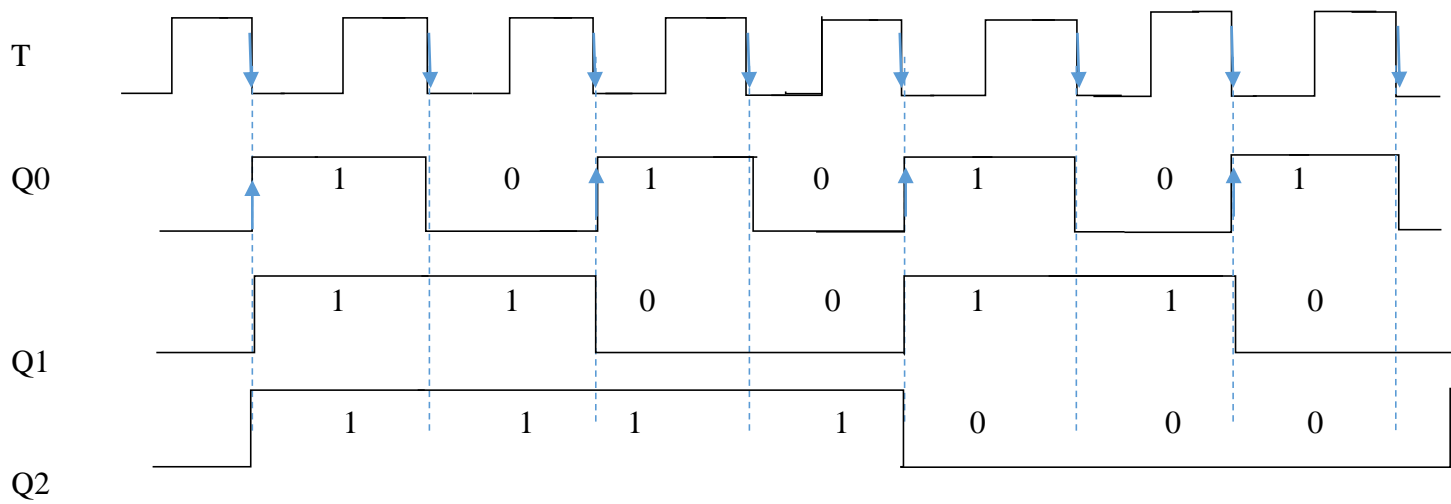 

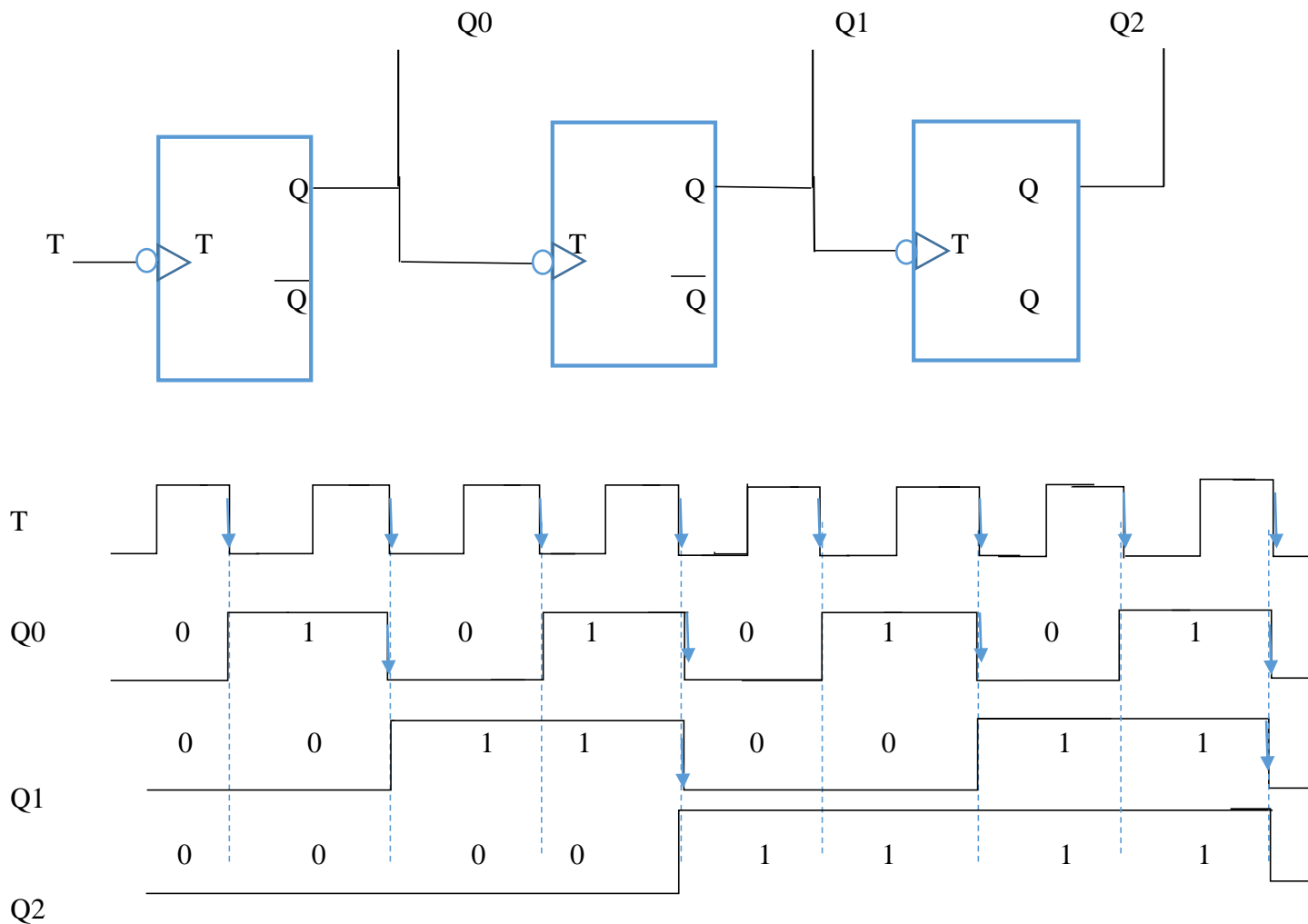
Ex2: Design 3-bit binary asynchronous up counter and draw timing diagram.



Counter Modification: When the **preset** input is activated, the flip-flop will be set ($Q=1$, $\text{not-}Q=0$) regardless of any of the synchronous inputs or the clock. When the clear input is activated, the flip-flop will be reset ($Q=0$, $\text{not-}Q=1$), regardless of any of the synchronous inputs or the clock.


Preset and clear inputs find use when multiple flip-flops are ganged together to perform a function on a multi-bit binary word, and a single line is needed to set or reset them all at once. Asynchronous inputs can be engineered to be active-high or active-low. If they're active-low, there will be an inverting bubble at that input lead on the block symbol, just like the negative edge-trigger clock inputs.


Sometimes the designations "PRE" and "CLR" will be shown with inversion bars above them, to further denote the negative logic of these inputs:

 

Ex3: Design “Asynchronous” BCD up counter, count from (0 to 9)


Q3	Q2	Q1	Q0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1


 


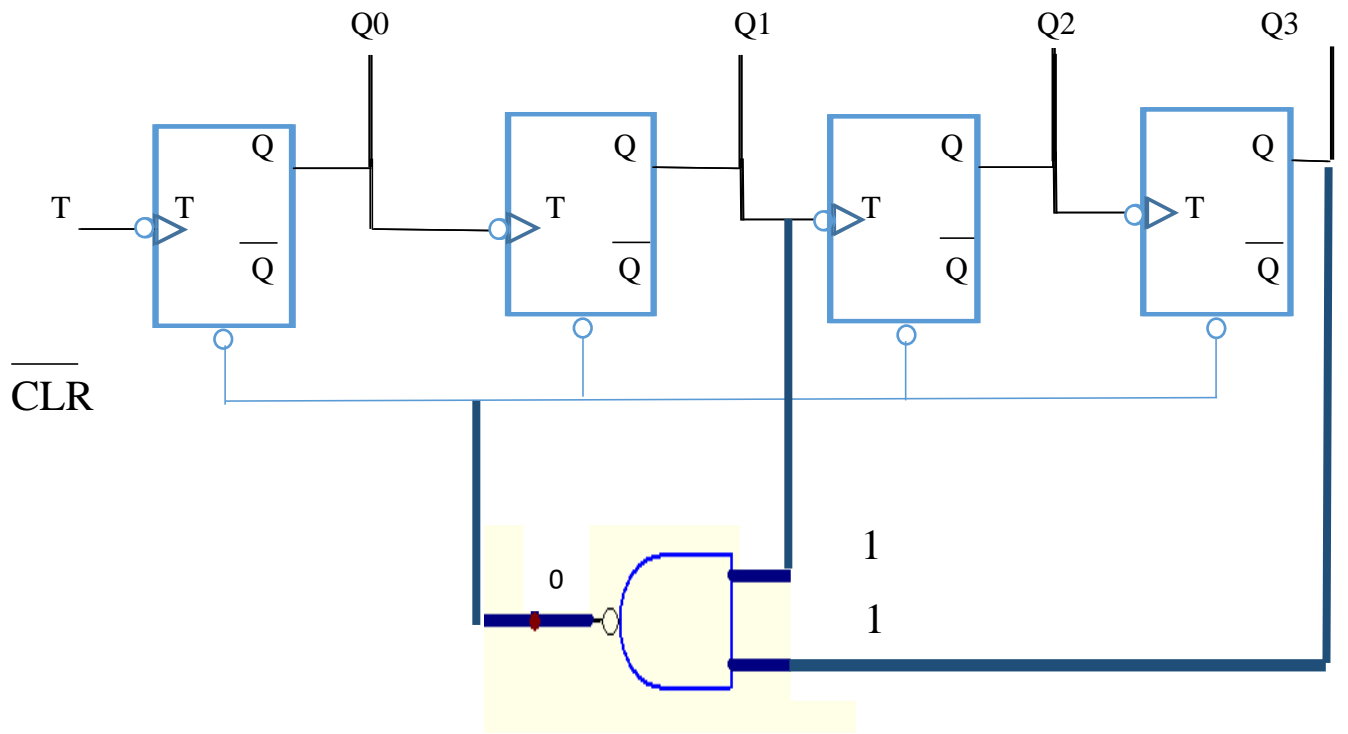

Ex4: Design “Asynchronous” up counter, to count from (0 to 5) and draw timing digram.



Q2	Q1	Q0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1

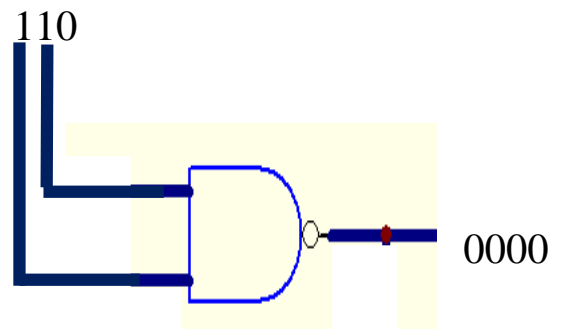

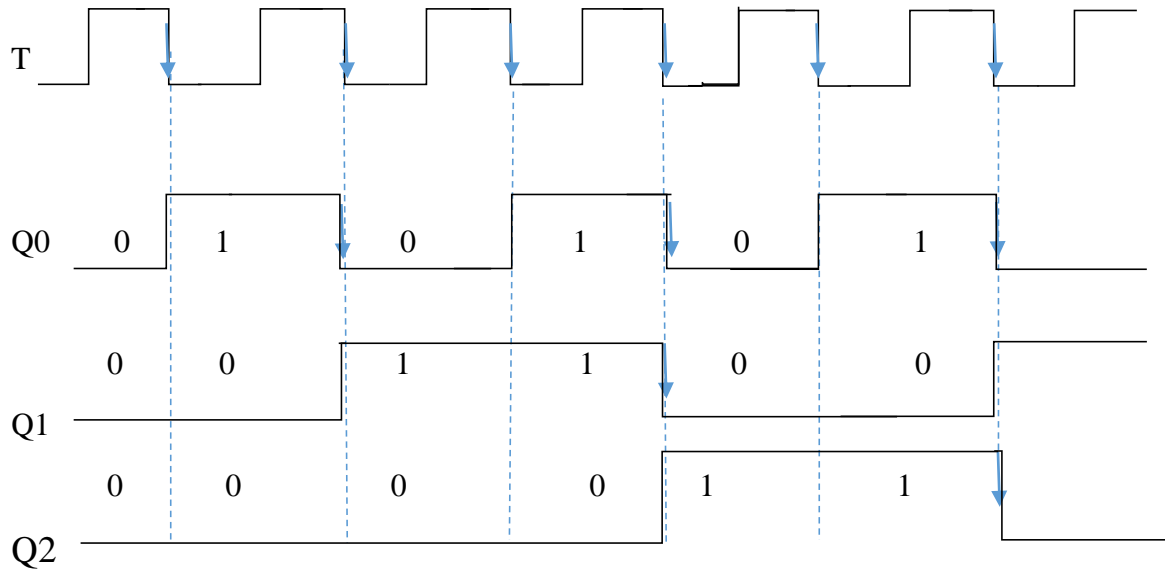
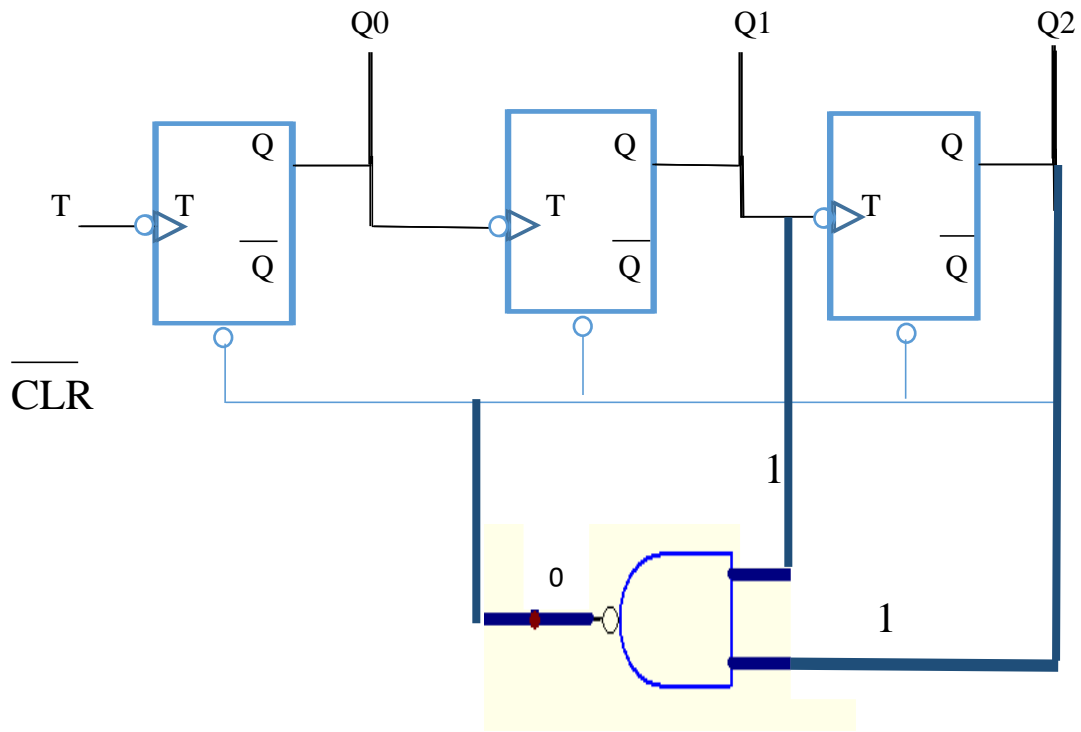


Ex5: Design “Asynchronous” BCD down counter, count from (9 to 0)

Q3	Q2	Q1	Q0
1	0	0	1
1	0	0	0
0	1	1	1
0	1	1	0
0	1	0	1
0	1	0	0
0	0	1	1
0	0	1	0
0	0	0	1
0	0	0	0

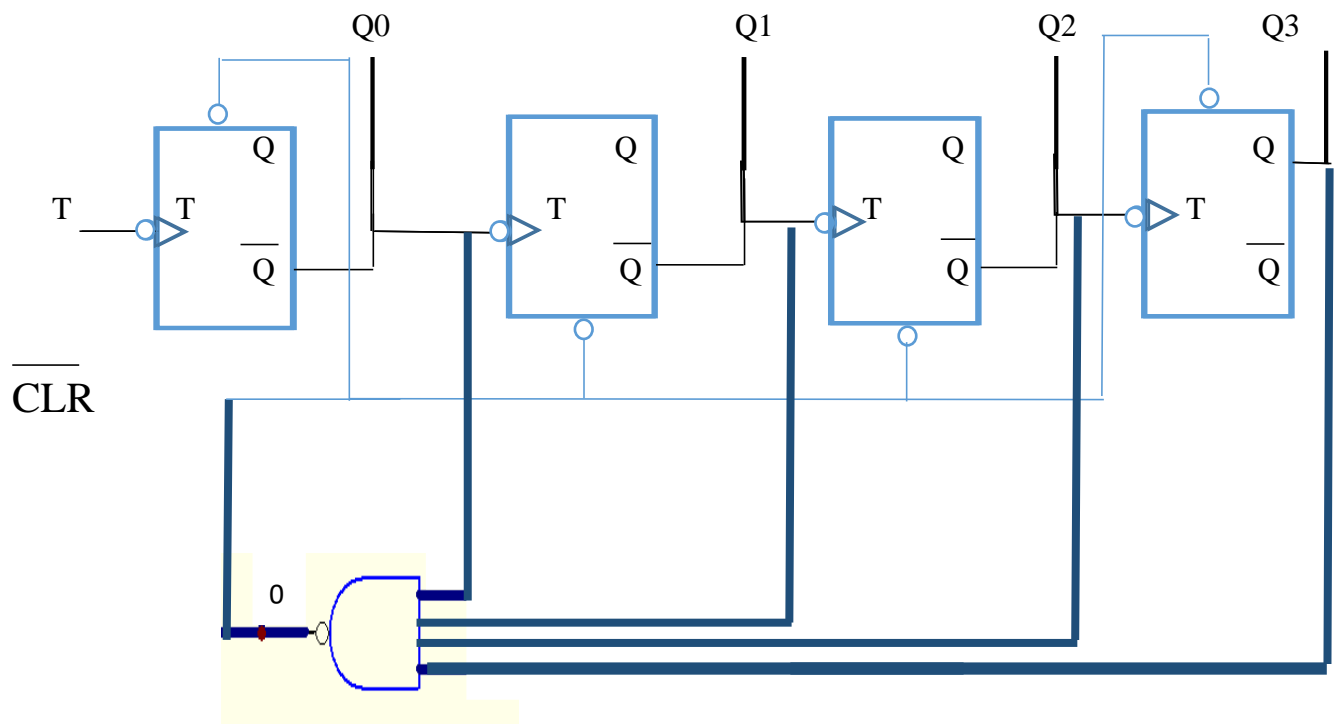 

6. XOR (Exclusive OR)gate:

 
 


Truth table:

INPUTS		OUTPUT
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Boolean expression:
 $Y = A'B + AB' = A \oplus B$

7. XNOR(Exclusive NOR)gate:

  

Truth table:

INPUTS		OUTPUT
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

Boolean expression:
 $Y = A'B' + AB = (A \oplus B)'$