
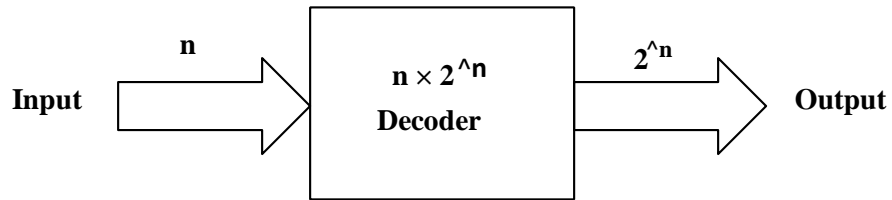



1. Decoders: is a Combinational Logic Circuit that convert Binary information from (n) input line to a maximum of 2^n unique output line.

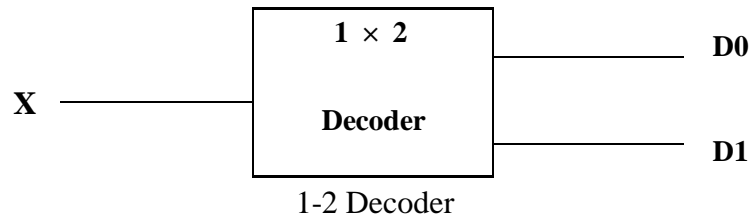

EX1: Design One to two Decoder




X	D0	D1
0	1	0
1	0	1

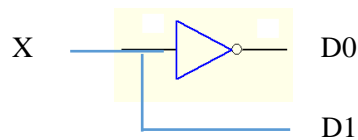

$$D0 = \overline{X}$$

$$D1 = X$$

EX2: Design Two to Four Decoder

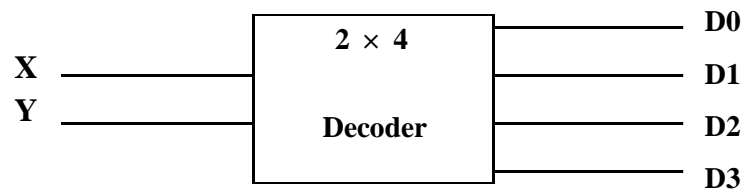

X	Y	D ₀	D ₁	D ₂	D ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1


Two to Four Decoder Truth Table

$$D_0 = \overline{X} \overline{Y}$$

$$D_1 = \overline{X} Y$$

$$D_2 = X \overline{Y}$$



$$D_3 = X Y$$

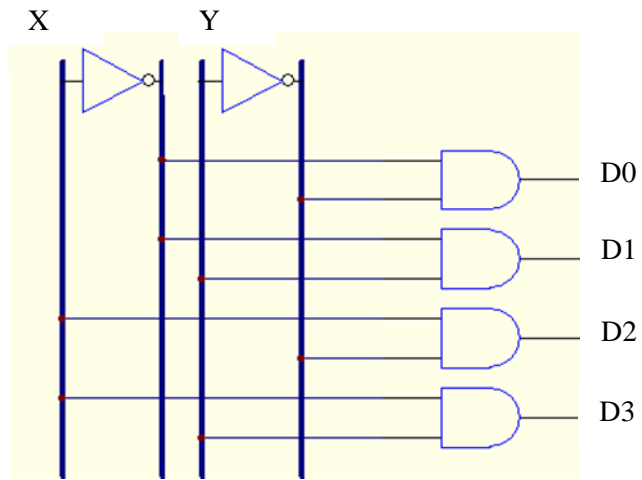

Ex3: Design 3-8 Decoder

C	B	A	y ₀	y ₁	y ₂	y ₃	y ₄	y ₅	y ₆	y ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

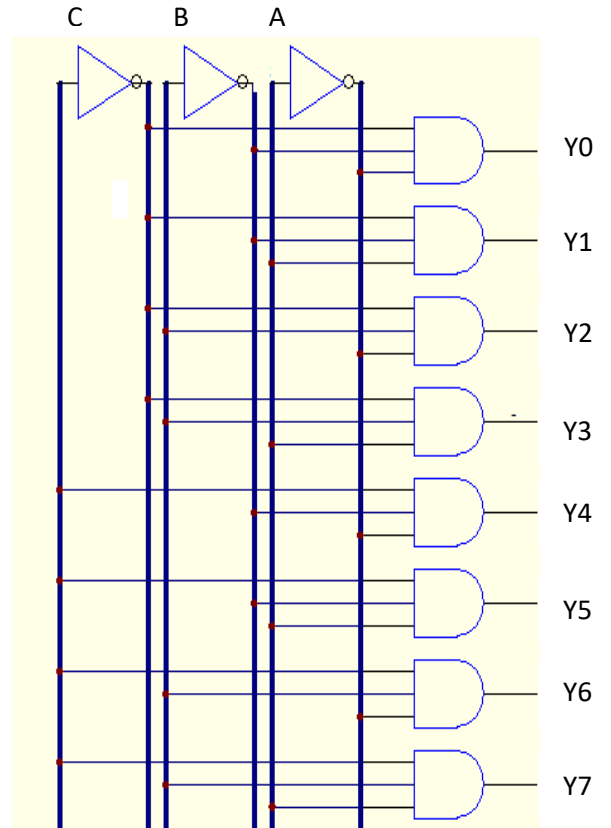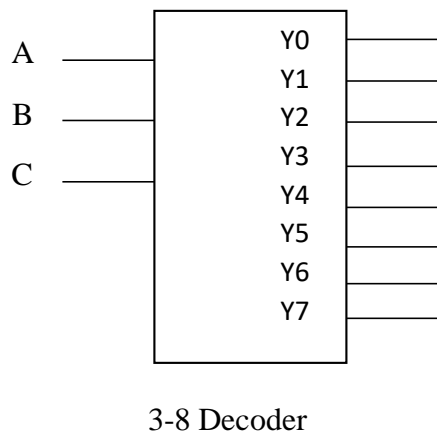
$y_0 = \overline{C} \overline{B} \overline{A}$
 $y_1 = \overline{C} \overline{B} A$
 $y_2 = \overline{C} B \overline{A}$
 $y_3 = \overline{C} B A$
 $y_4 = C \overline{B} \overline{A}$
 $y_5 = C \overline{B} A$
 $y_6 = C B \overline{A}$
 $y_7 = C B A$



* Note: all the previous decoders are active high outputs but the most popular decoders are active low outputs.

Ex4: Design 3-8 decoder using 2 of (2-4 decoders)and one (1-2 decoder), with active low output.

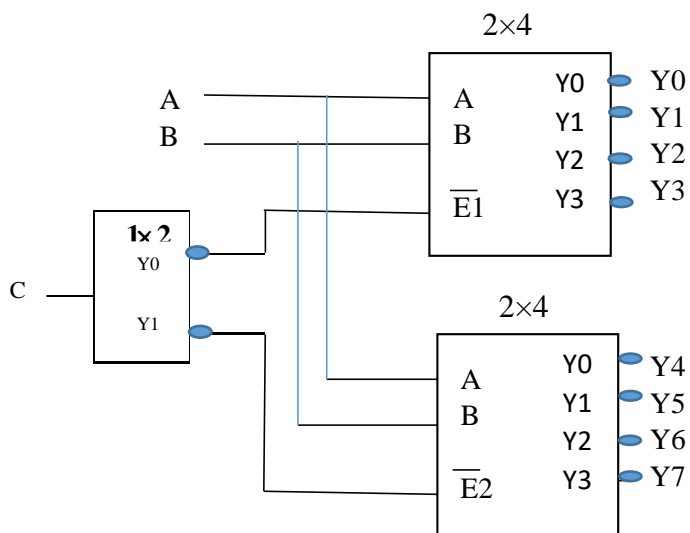Important note: We use Enable input to expanded decoders.



C	E2	E1	B	A	Y4	Y5	Y6	Y7	Y0	Y1	Y2	Y3
0	0	1	0	0	0	1	1	1	1	1	1	1
0	0	1	0	1	1	0	1	1	1	1	1	1
0	0	1	1	0	1	1	0	1	1	1	1	1
0	0	1	1	1	1	1	1	0	1	1	1	1
1	1	0	0	0	1	1	1	1	0	1	1	1
1	1	0	0	1	1	1	1	1	1	0	1	1
1	1	0	1	0	1	1	1	1	1	1	0	1
1	1	0	1	1	1	1	1	1	1	1	1	0