

Electrical Engineering Fundamentals

EEI

① Basic Concepts & Basic Laws

1.1 Basic Concepts

1.1.1 System of Units

The basic SI units

Quantity	Basic unit	Symbol
Length	meter	m
Mass	kilogram	kg
Time	second	s
Electric current	ampere	A
Thermodynamic temperature	kelvin	K
Luminous intensity	candela	cd

The SI prefixes

Multiplier	Prefix	Symbol
10^{18}	exa	E
10^{15}	peta	P
10^{12}	tera	T
10^9	giga	G
10^6	mega	M
10^3	kilo	k
10	deca	da
10^{-1}	deci	d
10^{-2}	centi	c
10^{-3}	milli	m
10^{-6}	micro	μ
10^{-9}	nano	n
10^{-12}	pico	p
10^{-15}	femto	f
10^{-18}	atto	a

Examples

$$10 \text{ MHz} \Rightarrow 10 \times 10^6 \text{ Hz}$$

$$2 \text{ mA} = 2 \times 10^{-3} = 0.002 \text{ A}$$

$$5 \mu\text{s} = 5 \times 10^{-6} \text{ s}$$

1.1.2 Charge and Current


EE1

The electric charge is an electrical property of the atomic particles of which matter consists, measured in coulombs (C). The charge of an electron is $(-1.602 \times 10^{-19} \text{ C})$.

Electric Current


is the rate of change of charge, measured in amperes (A). The current (I) is defined mathematically as:

$$i = \frac{dq}{dt}$$

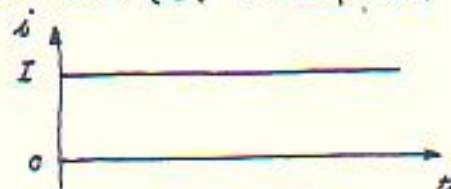

d.c. current

$$\therefore q = \int_{t_1}^{t_2} i dt$$

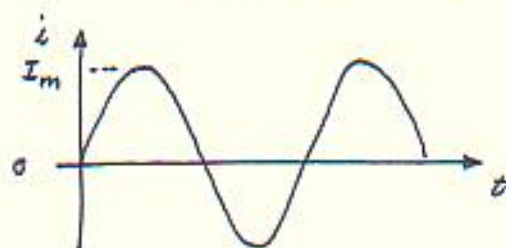

a.c. current

- * A direct current (dc) is current that remains constant with time. The symbol (I) is usually used to represent such a constant current.
- * An alternating current (ac) is a current that is varying sinusoidally with time. A time varying current is represented by the symbol (i).

Example

Determine the total charge entering a terminal between $t = 1 \text{ s}$ and $t = 2 \text{ s}$, if the current passing the terminal is $i = (3t^2 - t) \text{ A}$.


Solution

$$\begin{aligned} q &= \int_{t_1}^{t_2} i dt \\ &= \int_1^2 (3t^2 - t) dt = \left(t^3 - \frac{t^2}{2} \right) \Big|_1^2 \\ &= (8 - 2) - \left(1 - \frac{1}{2} \right) = \underline{\underline{5.5 \text{ C}}} \end{aligned}$$

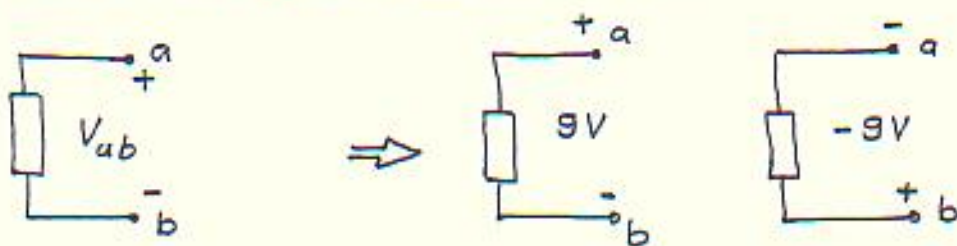1.1.3 Voltage

EE1

 : The voltage (or potential difference) is the energy required to move a unit charge through an element, measured in volts (V).



Polarity of Voltage
 V_{ab}

* For the voltage $V_{ab} \Rightarrow$ This means that the potential of point a is higher than that of point b

$$V_{ab} = V_a - V_b$$

1.1.4 Power and Energy

* Power: is the time rate of expending or absorbing energy, measured in watts (W)

$$\Rightarrow p = \frac{dw}{dt}$$

where p is the power in watts (W), w is the energy in joules (J), and t is the time in seconds (s)

$$\text{We have; } p = \frac{dw}{dt} \Rightarrow p = \frac{dw}{dq} \cdot \frac{dq}{dt}$$

$$\Rightarrow p = \frac{dw}{dq} \cdot \frac{dq}{dt} = v \cdot i$$

$$\therefore p = vi$$

* The energy absorbed or supplied by an element

from time t_0 to time t is :

EE1

$$w = \int_{t_0}^t p dt = \int_{t_0}^t v i dt$$

Energy is the capacity to do work, measured in joules (J)

* The electric power utility companies measure energy in watt-hour (Wh), where

$$1 \text{ Wh} = 3,600 \text{ J}$$

Example

: How much energy does a 100 W electric bulb consume in 2 hours?

Solution

$$w = pt = 100 \times 2 = 200 \text{ Wh}$$

or


$$\begin{aligned} w &= pt = (100 \text{ W})(2 \times 60 \times 60) \\ &= 720000 \text{ J} \\ &= 720 \text{ kJ} \end{aligned}$$

which is the same result (if you convert from joules to watts or vice-versa).

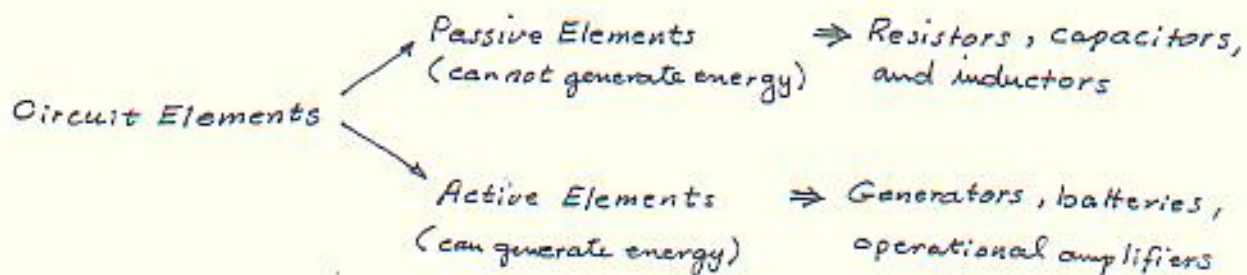1.1.5 Circuit Elements

: An electric circuit is an interconnection of electrical elements.

* Circuit analysis is the process of determining voltages across (or the currents through) the elements of the circuit.



- * The most important active elements are voltage or current EE1 sources that generally deliver power to the circuit connected to them.

Voltage (or current) sources $\left\{ \begin{array}{l} \text{Independent sources} \\ \text{Dependent sources} \end{array} \right.$

- * An ideal independent source is an active element that provides a specified voltage or current that is completely independent of other circuit variables.
- * Dependent sources (or controlled sources) are active elements in which the source quantity is controlled by another voltage or current. (It will be discussed later.)


1.2 Basic Laws

1.2.1 Ohm's Law

(1826) : Ohm's Law states that the voltage V across a resistor is directly proportional to the current I flowing through the resistor.

$$V \propto I$$

$$\Rightarrow V = IR$$

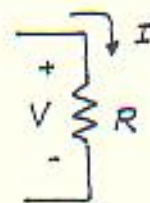

where R is the resistance. The resistance R denotes the ability of an element to resist the flow of electric current, it is measured in ohms (Ω).


For any material, the resistance R depends on its physical dimensions as follows:

$$R = \rho \frac{l}{A}$$

where ρ is the resistivity of the material.

\Rightarrow Good conductors have low resistivities (such as copper, aluminum, etc..)

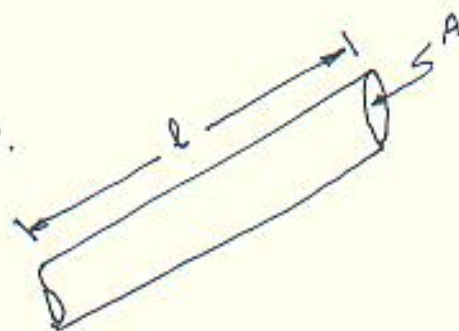\Rightarrow Insulators have high resistivities (such as mica, paper, etc...)




المعلومات

Resistivities of Common Materials


EE1

Material	Resistivity ($\Omega \cdot m$)	Usage
Silver	1.64×10^{-8}	Conductor
Copper	1.72×10^{-8}	"
Aluminum	2.80×10^{-8}	"
Gold	2.45×10^{-8}	"
Carbon	4.00×10^{-5}	Semiconductor
Germanium	47.0×10^{-2}	"
Silicon	6.40×10^{-2}	"
Paper	10^{10}	Insulator
Mica	5×10^{11}	"
Glass	10^{12}	"
Teflon	3×10^{12}	"

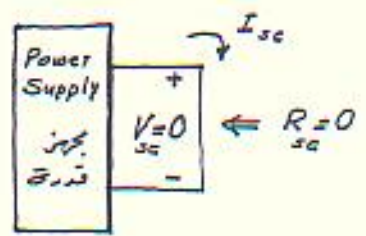- * The resistance of a short circuit element is approaching zero
- * The resistance of an open circuit is approaching infinity.



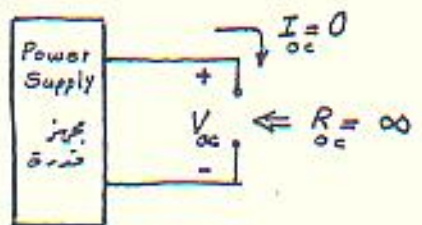Short circuit with $R_{sc} = 0$
 $V_{sc} = 0$



Open circuit with $R_{oc} = \infty$
 $I_{oc} = 0$

* Conductance (G)

A useful quantity in circuit analysis is the reciprocal of resistance (R), is called the conductance (G);

$$G = \frac{1}{R} = \frac{i}{v}$$

The conductance can be explained as the ability of an element to conduct electric current, it is measured in mhos (\mathcal{U}) or in siemens (S).

$$\therefore i = Gv$$

and:


$$P = vi = i^2 R = \frac{v^2}{R} \quad \text{watts (W)}$$

OR

$$P = vi = v^2 G = \frac{i^2}{G}$$

Example

 : In the circuit shown, calculate the current I , the conductance G , and the power P

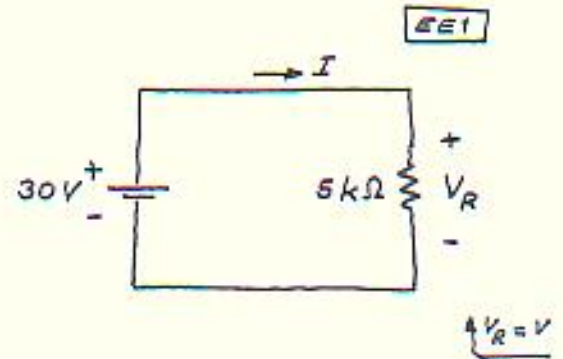Solution

- the current $I = \frac{V_R}{R} = \frac{30}{5 \times 10^3} = 6 \times 10^{-3} = \underline{6 \text{ mA}}$

- the conductance $G = \frac{1}{R} = \frac{1}{5 \times 10^3} = 0.2 \times 10^{-3} = 0.2 \text{ mS}$

- the power $P = V_R I = 30 (6 \times 10^{-3}) = \underline{180 \text{ mW}}$

or

$P = I^2 R = (6 \times 10^{-3})^2 (5 \times 10^3) = \underline{180 \text{ mW}}$

or

$P = V_R^2 G = (30)^2 (0.2 \times 10^{-3}) = \underline{180 \text{ mW}}$

1.2.2 Nodes, branches and loops


* A branch represents a single element in the electric circuit, such as a voltage source or a resistor etc...

* A node represents the point of connection between two or more branches.

* A loop is any closed path in a circuit.

Example

 : For the circuit shown, determine the number of branches, nodes and the independent loops.

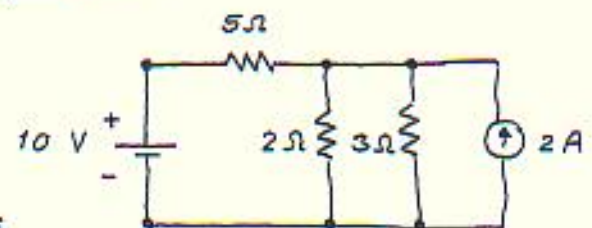Solution


 Since there are 5 elements

\Rightarrow Number of branches = 5 10V, 5Ω, 2Ω, 3Ω, and 2A

Number of nodes = 3 (as shown in the figure).
3 nodes

تمرین حل بنائے

⇒ There are 3 nodes :
a, b and c

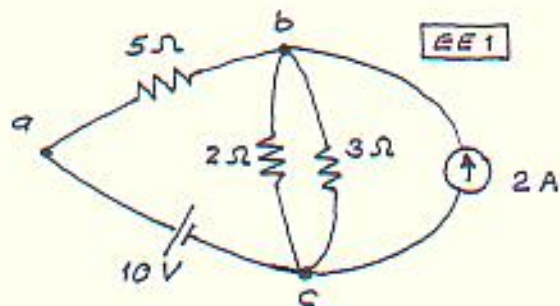


* The number of the independent loops = 3

⇒ loop 1 or loop abc:
contains (10V, 5Ω, 2Ω)

⇒ loop 2 or loop bcb:
contains (2Ω, 3Ω)

⇒ loop 3 or loop bcb:
contains (3Ω, 2A)

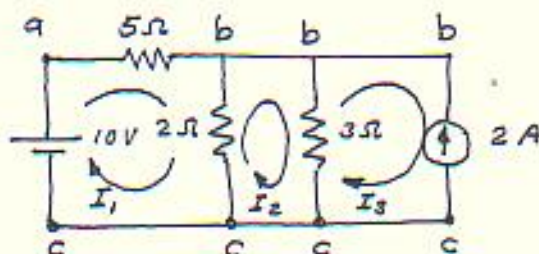

Notes

— : There are more than 3 (dependent) loops in this example, we had only calculated the INDEPENDENT loops which are only 3.

IN GENERAL; Any circuit with b branches, n nodes and l independent loops, the following fundamental theorem of network topology:

$$b = l + n - 1$$

* Two or more elements are in SERIES if they are cascaded sequentially and consequently carry the SAME current.

* Two or more elements are in PARALLEL if they are connected to the same two nodes and have consequently the same VOLTAGE across them.

1.2.3 Kirchoff's Laws (1847)

* Kirchoff's current law (KCL); states that the algebraic sum of all current entering a node is zero or: The sum of currents entering a node is equal to the sum of currents leaving that node.

$$\sum_{n=1}^N I_n = 0$$


or

$$\sum_{m=1}^M I_{mi} = \sum_{n=1}^N I_{no}$$

where I_{mi} are the currents entering the node and I_{no} are the currents leaving the node.

Example

For the network shown, calculate the total current I_T

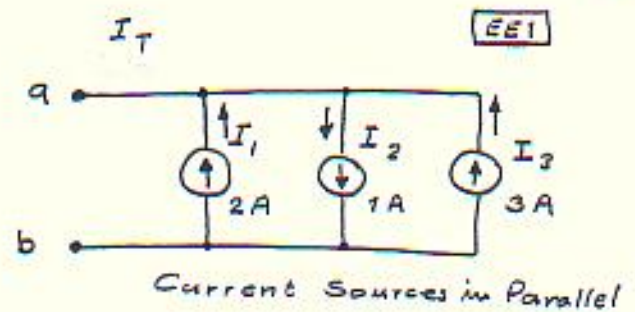
Solution

According to KCL;

$$I_T = I_1 - I_2 + I_3$$

$$= 2 - 1 + 3 = \underline{5A}$$

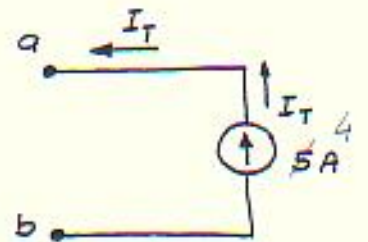∴ The equivalent circuit for the network can be as shown ⇒



* Kirchoff's Voltage Law (KVL); states that the algebraic sum of all voltages around a closed path (or loop) is zero.
 قانون كيرشوف للجهد


∴ Mathematically KVL states that:

$$\sum_{m=1}^M V_m = 0$$

where M is the number of voltages in the loop (or the number of branches in the loop), and V_m is the m th voltage.

Example

For the circuit shown, find the voltages V_1 and V_2

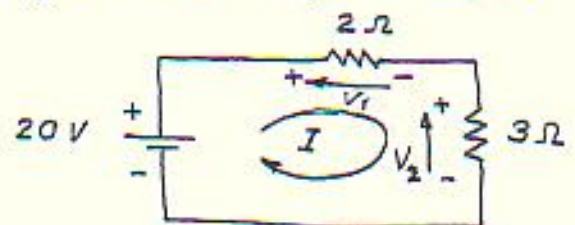Solution

$$V_1 = 2I$$

$$V_2 = 3I$$

From KVL:

$$\sum V = 0 \Rightarrow 20 - V_1 - V_2 = 0 \Rightarrow 20 = 3I + 2I$$

$$\Rightarrow 5I = 20 \Rightarrow I = 4A$$


$$\therefore V_1 = 2I = \underline{8V} \quad \text{and} \quad V_2 = 3I = \underline{12V}$$

Tutorial Sheet No 1

Basic Concepts & Basic Laws

TSI

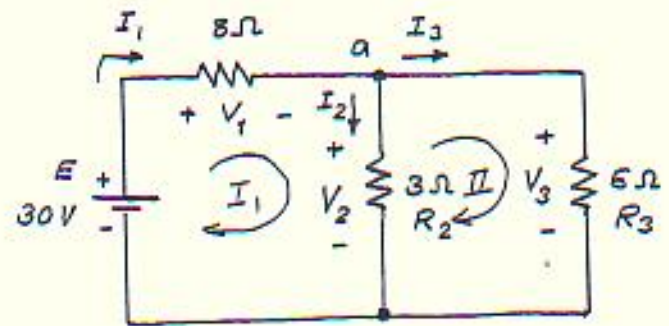Example
Using Kirchoff's laws,
find the currents and voltages in
the circuit shown.



Solution

ملاحظة : المطلوب في المثال إيجاد كل من :
 $I_1, I_2, I_3, V_1, V_2, V_3$
باستخدام قانون كيرشوف

* Using Ohm's law :

$$\begin{aligned} V_1 &= I_1 R_1 = 8 I_1 \\ V_2 &= I_2 R_2 = 3 I_2 \\ V_3 &= I_3 R_3 = 6 I_3 \end{aligned}$$

* Applying KCL at node a :

$$I_1 = I_2 + I_3 \Rightarrow I_1 - I_2 - I_3 = 0$$

Eq(1)

* Applying KVL to loop 1 :

$$\begin{aligned} E - V_1 - V_2 &= 0 \Rightarrow 30 - V_1 - V_2 = 0 \\ \Rightarrow 30 - 8 I_1 - 3 I_2 &= 0 \\ \therefore I_1 &= \frac{30 - 3 I_2}{8} \end{aligned}$$

Eq(2)

* Applying KVL to loop 2 :

$$\begin{aligned} V_2 - V_3 &= 0 \Rightarrow V_2 = V_3 \\ \therefore 3 I_2 &= 6 I_3 \\ \therefore I_3 &= \frac{I_2}{2} \end{aligned}$$

Eq(3)

هنا دافع تارة
توازنا $R_2 \neq R_3$

⇒ From Eq(1), Eq(2) & Eq(3)

$$\frac{30 - 3 I_2}{8} - I_2 - \frac{I_2}{2} = 0 \Rightarrow I_2 = \underline{\underline{2 A}}$$

$$\text{and } I_1 = \frac{30 - 3 I_2}{8} = \frac{30 - 3(2)}{8} = \underline{\underline{3 A}}$$

$$I_3 = \frac{I_2}{2} = \frac{2}{2} = 1 A$$

$\Rightarrow \therefore V_1 = 8I_1 \Rightarrow \therefore V_1 = 8(3) = 24V$ T51

Similarly $V_2 = 3I_2 = 3(2) = 6V$

and $V_3 = 6I_3 = 6(1) = 6V$

للتأكد من صحة الحل :

$I_1 = I_2 + I_3$
 $3 = 2 + 1 \Rightarrow \underline{\underline{3 = 3}}$


كذلك فان تطبيعها قانون كيرشوف للتيار على المسار المغلقة رقم 1 ينتج ما يلي :

$E = V_1 + V_2$
 $\therefore 30 = 24 + 6$

$\therefore 30 = 30$ ← كل صحيح

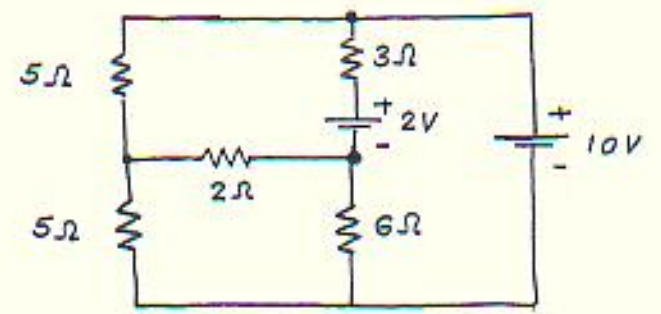Example

—: Determine the number of branches, nodes and independent loops in the circuit shown.



Solution:


* There are 7 element \Rightarrow no. of branches = 7
 $\Rightarrow \underline{\underline{b = 7}}$

a, b, c, d, e \Leftarrow * There are 5 nodes as shown in the figure:
 $\Rightarrow n = 5$

I, II, III \Leftarrow * There are 3 independent loops:
 $\Rightarrow l = 3$


$\therefore b = l + n - 1$ is satisfied

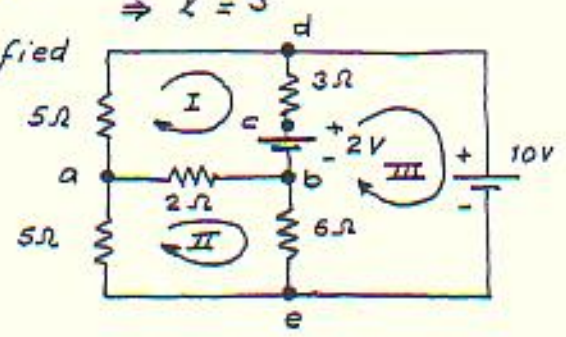since $7 = 3 + 5 - 1$
 $\Rightarrow 7 = 7$



Practice Problem

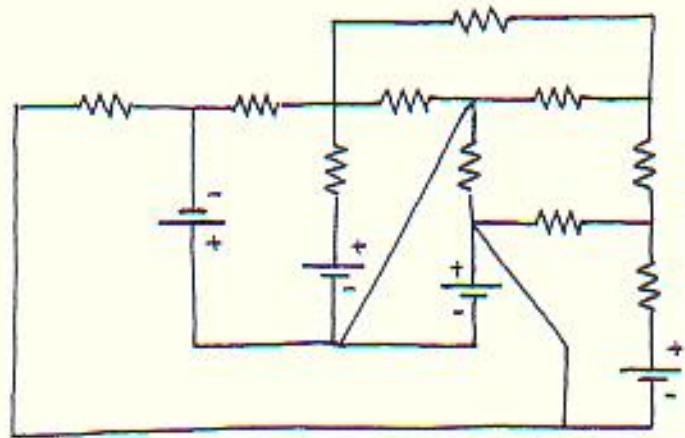Identify all nodes, branches and independent loops in the circuit shown in the figure.



Answer


no. of nodes = 8	$n = 8$
no. of branches = 14	$b = 14$
no. of independent loops = 7	$l = 7$

Check. Does this satisfy the fundamental theorem of network topology?

$$b = l + n - 1 = 7 + 8 - 1 = 14 \quad \underline{\text{YES}}$$

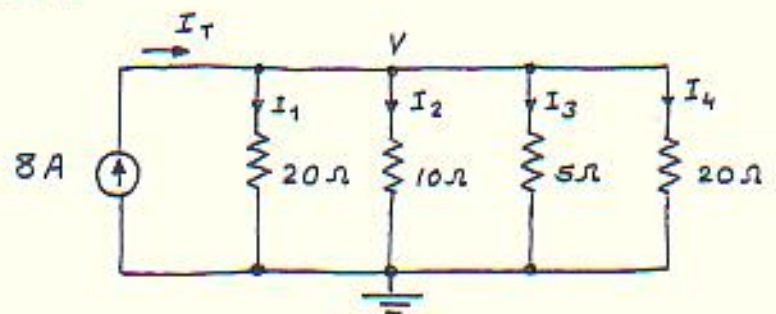Example

Determine all currents and voltages in the circuit of the figure shown.



Solution

KCL \Rightarrow

$$I_T = I_1 + I_2 + I_3 + I_4 \quad \Rightarrow \quad 8 = I_1 + I_2 + I_3 + I_4$$

Ohm's law

$V = 20 I_1$	$\Rightarrow I_1 = V/20$
$= 10 I_2$	$I_2 = V/10$
$= 5 I_3$	$I_3 = V/5$
$= 20 I_4$	$I_4 = V/20$

Substituting in the current equation;

$$\Rightarrow 8 = \frac{V}{20} + \frac{V}{10} + \frac{V}{5} + \frac{V}{20}$$

$$\therefore 160 = V + 2V + 4V + V$$

$$160 = 8V$$

$$\therefore \underline{V = 20 \text{ Volts}}$$

$$\therefore I_1 = \frac{V}{20} = \frac{20}{20} = 1 \text{ A}$$

$$I_2 = \frac{V}{10} = \frac{20}{10} = 2 \text{ A}$$

$$I_3 = \frac{V}{5} = \frac{20}{5} = 4 \text{ A}$$

$$I_4 = \frac{V}{20} = \frac{20}{20} = 1 \text{ A}$$

check

$$I_T = I_1 + I_2 + I_3 + I_4$$

$$8 = 1 + 2 + 4 + 1$$

$$8 = 8 \quad \checkmark$$

Fundamentals of Electrical Engineering

①

1. Circuit Variables & Circuit Elements

1.1 - System of Units

- The English System
- The metric System {
 - MKS System
 - CGS System
- The International System of Units (SI)

The (SI) system is the commonly used by all the major engineering societies.

The (SI) system of units

Quantity	Basic unit	Symbol
Length	Meter	m
Mass	Kilogram	kg
Time	Second	s
Electric current	Ampere	A
Temperature	Degree Kelvin	K
Luminous intensity	Candela	cd

Some scientific notations: In many cases, the SI units is either too small or too large to use conveniently. Standard prefixes correspond to the power of 10 are applied to the basic unit as shown in the table.

Prefix	Symbol	Power
pico	p	10^{-12}
nano	n	10^{-9}
micro	μ	10^{-6}
milli	m	10^{-3}
centi	c	10^{-2}
deci	d	10^{-1}
kilo	k	10^3
mega	M	10^6
giga	G	10^9

Examples

$$1000000 \text{ W} = 10^6 \text{ W} = 1 \text{ MW}$$

$$0.000001 \text{ F} = 10^{-6} \text{ F} = 1 \mu\text{F}$$

1.2 Voltage and Current

* Voltage

_____ In general the potential difference between two points is defined as:

$$V = \frac{W}{Q} \quad \text{volts (V)}$$

where: Q is the charge moving between the two points in Coulombs (C)

W is the energy expended to do this motion in Joules (J)

From the above equation, we have:

$$W = QV \quad \text{joules (J)}$$

and

$$Q = \frac{W}{V}$$

Example

_____ : Determine the energy expended in moving a charge of $50 \mu\text{C}$ through a potential difference of 6V .

Solution:

$$\begin{aligned} W &= QV = (50 \times 10^{-6})(6) \\ &= 300 \times 10^{-6} \text{ J} \\ &= 300 \mu\text{J} \end{aligned}$$

★ Current

It is the rate of charge moving in a certain metal, and can be given by:

$$I = \frac{\Delta Q}{\Delta t}$$

or

$$I = \frac{Q}{t}$$

amperes (A)

then

$$Q = It$$

in Coulombs (C)

and

$$t = \frac{Q}{I}$$

in seconds (s)

Example

_____ : A charge of 0.16 C is flowing every 64 ms. Determine the resulting current

Solution

$$\begin{aligned} \text{_____ : } I &= \frac{Q}{t} = \frac{0.16}{64 \times 10^{-3}} \\ &= 2.5 \text{ A} \end{aligned}$$


1.3 Circuit Elements

- Voltage sources
- Current sources
- Resistors
- Capacitors
- Inductors

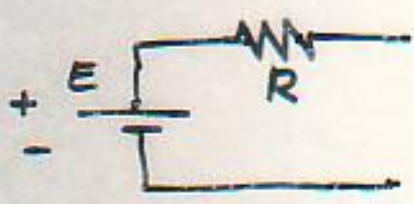1.4 Voltage and Current Sources

- Voltage Source

_____ : It is a device which supplies a fixed terminal voltage even though the current drain may vary



voltage source




Ideal

V.S (with $R=0$)




- Current Source

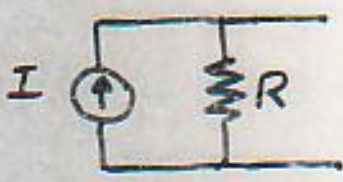_____ It is a device which supplies a constant current to a load even though there will be variations in the terminal voltage as determined by the load.



Current source

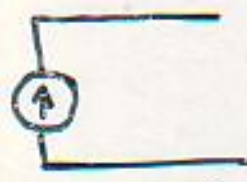

Ideal



1.5 Electrical Resistance


$$R = \rho \frac{l}{A}$$

where R is the resistance in Ω

ρ is the resistivity of the material $\Omega \cdot m$

l is the length of the conductor in m

A is the cross-sectional area in m^2

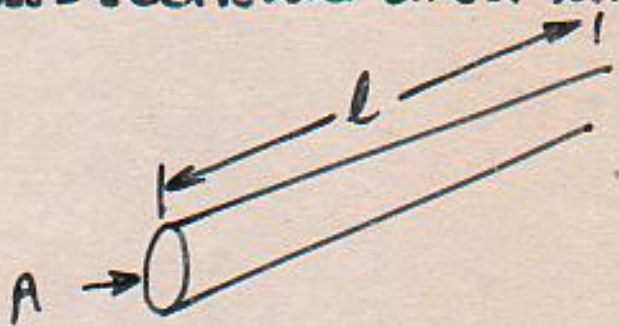

Example

_____ : Determine the resistance of 100 ft of a copper wire if the diameter is 0.0126 in, given that the resistivity of copper is $1.724 \times 10^{-6} \Omega \cdot cm$.

Solution

$$R = \rho \frac{l}{A}$$

$$\rho = 1.724 \times 10^{-6} \Omega \cdot cm$$

$$l = 100 \text{ ft} = 1200 \text{ in}$$

$$= 1200 \times 2.54$$

$$= 3048 \text{ cm}$$

$$\therefore R = \frac{(1.724 \times 10^{-6})(3048)}{8.04 \times 10^{-4}}$$

$$= \underline{\underline{6.5 \Omega}}$$

$$d = 0.0126 \text{ in}$$

$$= 0.032 \text{ cm}$$

$$A = \frac{\pi d^2}{4} = 8.04 \times 10^{-4} \text{ cm}^2$$


Temperature Effects on Resistance

The effect of rise of temp. is :

- to increase the resistance of pure metals.
- to increase the resistance of alloys.
- to decrease R of insulators and partial

conductors such as carbon.

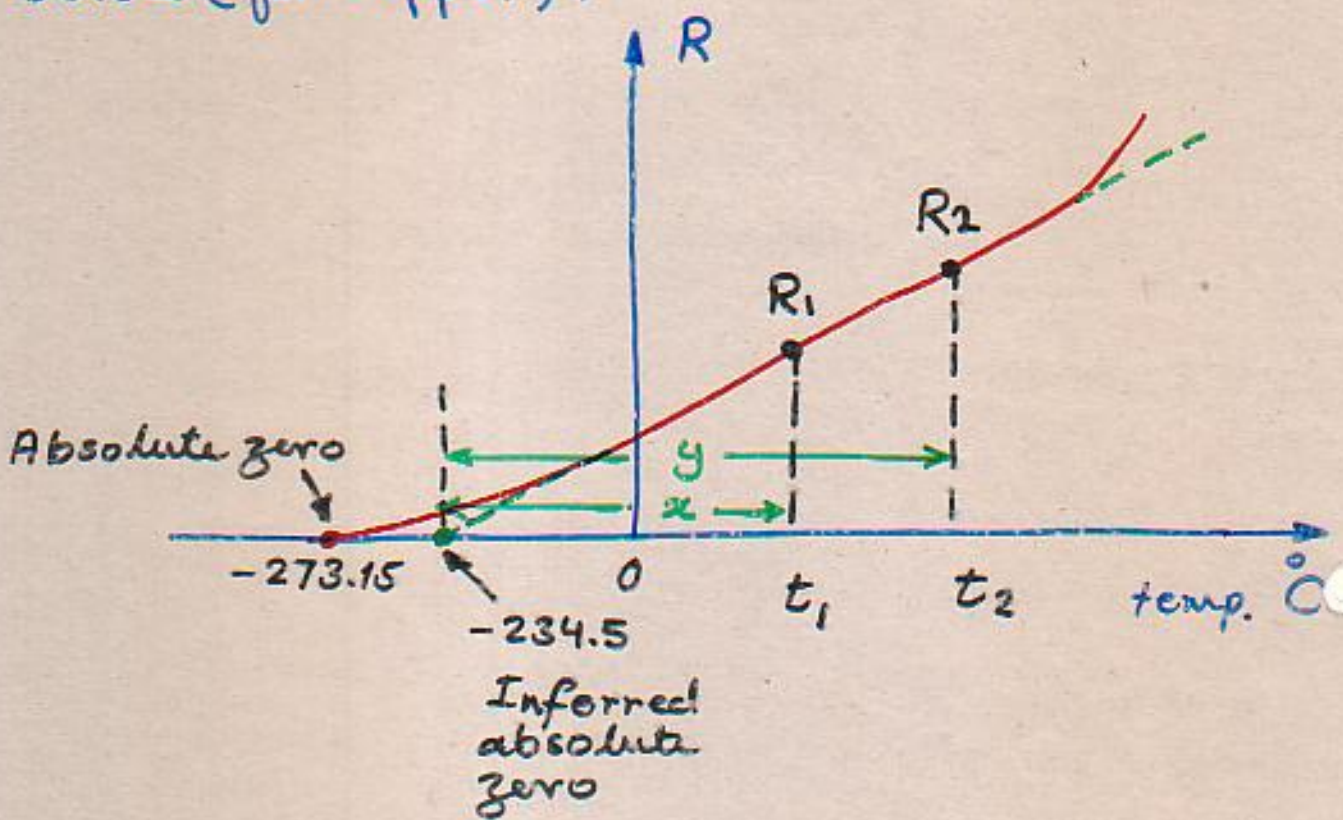Typical variation of R with temp. is shown below (for copper).



From the graph $\Rightarrow \frac{x}{R_1} = \frac{y}{R_2}$

or $\frac{t_1 + 234.5}{R_1} = \frac{t_2 + 234.5}{R_2}$

In general, for any material

$$\frac{|T| + t_1}{R_1} = \frac{|T| + t_2}{R_2}$$

where |T| is the inferred absolute zero of the material (°C).

Example

: If the resistance of a copper wire is 50 Ω at 20 °C, what is its resistance at 100 °C?

Solution:

$$\frac{234.5 + 20}{50} = \frac{234.5 + 100}{R_2}$$

$$\Rightarrow R_2 = 65.72 \Omega$$

Another relation for the temp. effect on R is given as

$$R_2 = R_1 [1 + \alpha_1 (t_2 - t_1)]$$


where α_1 is the temperature coefficient of resistance

1.6 Ohm's & Kirchoff's Laws


- Ohm's Law

_____ : It is an equation that establishes a relationship among the current (I), voltage (V) and the resistance (R) of an electrical circuit. It is given by:

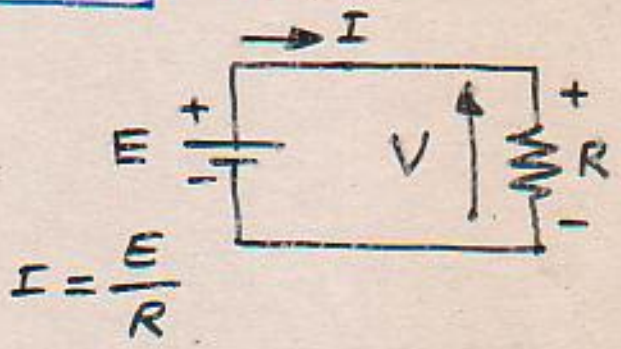in amperes (A) $I = \frac{V}{R}$ in volts (V) in Ω



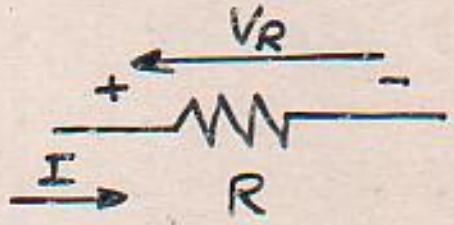For resistive element, the polarity of the voltage drop as show for the indicated current directions




A reversal in current will reverse the polarity.

$$I = \frac{V}{R} \Rightarrow V = IR$$

$$\text{slope} = \frac{1}{R} = \frac{\Delta I}{\Delta V}$$
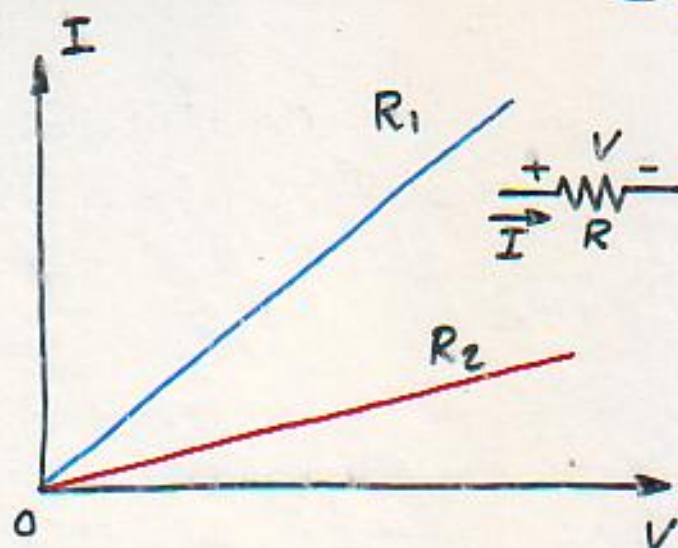
$$\Rightarrow R = \frac{\Delta V}{\Delta I}$$




$$R_2 > R_1$$

For non-linear resistor the resistance can be determined graphically as:

$$R = \frac{\Delta V}{\Delta I}$$

from the I-V graph.

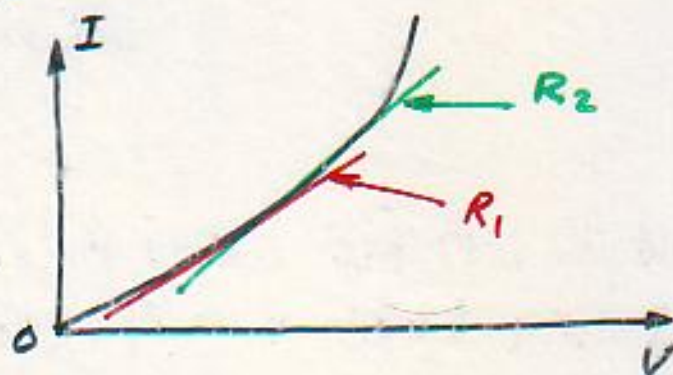

Kirchoff's Laws


* Kirchoff's Current Law (KCL)

It states that "in any electrical network, the algebraic sum of the currents meeting at a point (or junction) is zero. or in other words; it simply means that the total currents leaving a junction is equal to the total currents entering that junction."


Example

$$I_1 + (-I_2) + (-I_3) = 0$$

$$\Rightarrow I_1 = I_2 + I_3$$

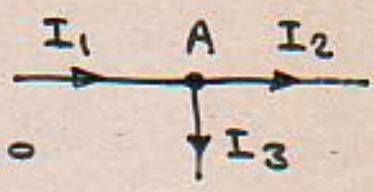

Example

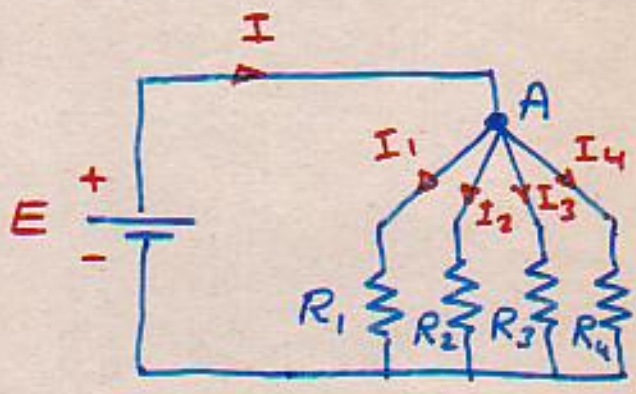

at junction A

$$\sum I = 0$$

$$I + (-I_1) + (-I_2) + (-I_3) + (-I_4) = 0$$


$$\Rightarrow I = I_1 + I_2 + I_3 + I_4$$

* Kirchhoff's Voltage Law (KVL)

_____ : It states that "the algebraic sum of all potentials around any closed path (loop) is zero, i.e.,

$$\sum V = 0$$

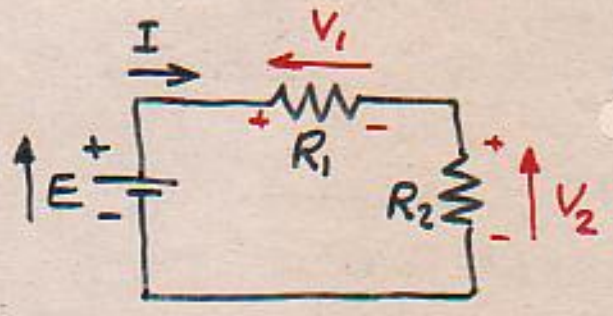Moving **CW** around the loop shown, then :



$$E + (-V_1) + (-V_2) = 0$$

or

$$E = V_1 + V_2$$

1.7 Power and Energy

* Power: It is defined as the rate of doing work, i.e.,

$$P = \frac{W}{t} \quad \text{Watts (W)} \\ \text{or joules/sec (J/s)}$$

From the earliest analysis, we have:

$$W = QV$$

$$\Rightarrow P = \frac{QV}{t}$$

$$\Leftarrow \frac{Q}{t} = I$$

$$\therefore P = VI$$

Since $I = \frac{V}{R}$

Ohm's law \Rightarrow

$$P = \frac{V^2}{R}$$

or

$$P = I^2 R$$

$$1 \text{ Watt} = 1 \text{ J/s}$$

$$1 \text{ horsepower} = 746 \text{ W}$$

* Energy

It is a quantity represents the product of the power (P) and the period (t), i.e.

$$W = Pt$$

Watt.sec. W.s
or Joules

$$\text{Energy (kWh)} = \frac{\text{Power (W)} \times \text{time (h)}}{1000}$$


2. Circuit Transformations

2.1 Series Circuits

Two elements are in series if they have only one point in common that is not connected to other current carrying elements of the network.

For the series ckt. shown, using KVL we have:
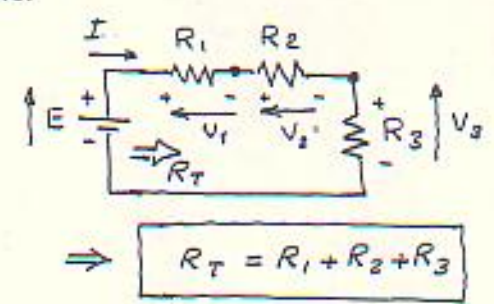
$$\begin{aligned}
 E &= V_1 + V_2 + V_3 \\
 &= IR_1 + IR_2 + IR_3 \\
 &= I(R_1 + R_2 + R_3) \\
 &= IR_T
 \end{aligned}$$




$$\therefore I = \frac{E}{R_T}$$

In general, for a series ckt. consisting N resistors, then the total resistance of such a ckt. R_T is given as

$$R_T = R_1 + R_2 + R_3 + \dots + R_N$$

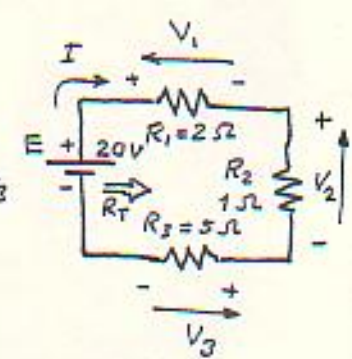Example

- For the ckt. shown;
- Find the total resistance
 - Calculate the current I
 - Determine the voltages V_1 , V_2 and V_3



Solution


- $R_T = R_1 + R_2 + R_3 = 2 + 1 + 5 = 8 \Omega$
- $I = \frac{E}{R_T} = \frac{20}{8} = 2.5 \text{ A}$
- $V_1 = IR_1 = (2.5)(2) = 5 \text{ V}$
 $V_2 = IR_2 = (2.5)(1) = 2.5 \text{ V}$
 $V_3 = IR_3 = (2.5)(5) = 12.5 \text{ V}$

ملاحظة
 $V_1 + V_2 + V_3 = E$
 $5 + 2.5 + 12.5 = 20 \text{ V}$
 $\therefore 20 \text{ V} = 20 \text{ V}$

2.1.1 Voltage Sources in Series

The net voltage will be the algebraic sum of all sources that are connected in series.

Example

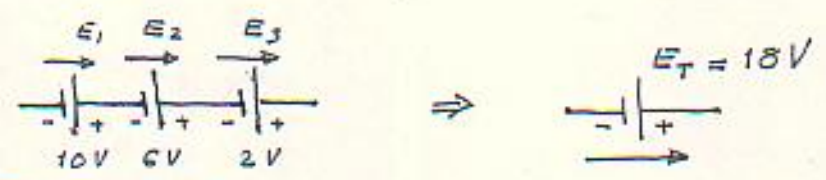

$$\begin{aligned}
 E_T &= E_1 + E_2 + E_3 \\
 &= 10 + 6 + 2 = 18 \text{ V}
 \end{aligned}$$

ملاحظة: لا يمكن ربط مصادر التيار في التوالي معاً ذلك مخالف لقانون كيرشوف للتيار.

2.1.2 Voltage Divider Rule

EE2


Consider the series ckt. shown.

we have:

$$R_T = R_1 + R_2$$

and $I = \frac{E}{R_T}$
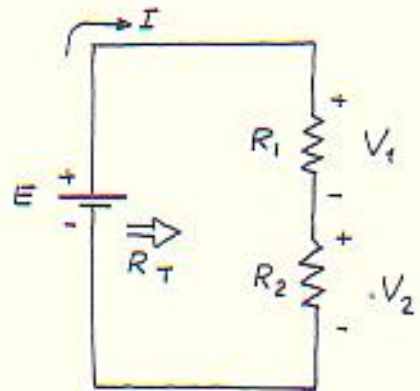
$$V_1 = IR_1 = \left(\frac{E}{R_T}\right) \cdot R_1 = \frac{E \cdot R_1}{R_T}$$



Similarly;

$$V_2 = IR_2 = \left(\frac{E}{R_T}\right) \cdot R_2 = \frac{E \cdot R_2}{R_T}$$

Hence, we can write:

$V_x = \frac{E \cdot R_x}{R_T}$ ← Voltage divider rule

This means that "the voltage divider rule" can be understood to state that:

The voltage across a resistor in a series circuit is equal to the value of that resistor times the the total applied voltage across the series elements divided by the total resistance of the series elements.


Example

Determine the voltages V_1 , V_3 , and V' for the ckt. shown.

Solution:

Using the voltage divider rule:
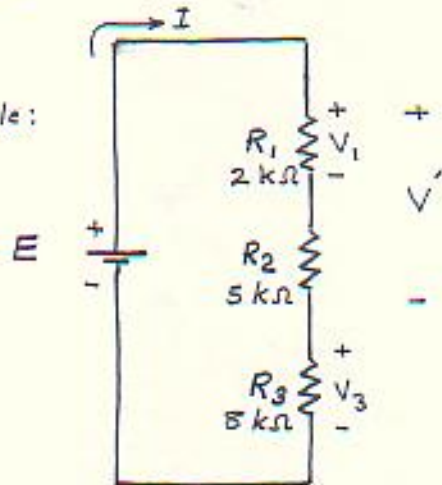
$$V_1 = \frac{E \cdot R_1}{R_T} = \frac{(45) \cdot (2 \times 10^3)}{(2+5+8) \times 10^3} = 6V$$
$$V_3 = \frac{E \cdot R_3}{R_T} = \frac{(45)(8 \times 10^3)}{(2+5+8) \times 10^3} = 24V$$



$$V' = \frac{E \cdot R'}{R_T}$$

$$= \frac{(45) \cdot (7 \times 10^3)}{(2 + 5 + 8) \times 10^3}$$

$$= \underline{21 \text{ V}}$$

$$R' = (2 + 5) \times 10^3 \Omega$$

$$= 7 \times 10^3 \Omega$$

EE2

لحفظ ان :

$$E = V_3 + V'$$


$$45 \text{ V} = 24 \text{ V} + 21 \text{ V}$$

$$45 \text{ V} = 45 \text{ V}$$

نلاحظ ان فرقة الجهد بين طرفي اي عنصر من عناصر دائرة الترانزستور تتناسب مع مقاومة ذلك العنصر ، أي ان المقاومة الكبيرة يقابلها فرقة جهد كبير والمقاومة الصغيرة يقابلها فرقة جهد صغيرة ، وفي جميع الاحوال يجب ان يكون مجموع فروق الجهد مساوياً الى كل من قيمة المصدر .


NOTATION ground potential

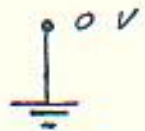It is common, for safety purposes and as a reference to ground electrical and electronic systems. The symbol for the ground connection is :



with its defined potential level (zero volts). As a consequence, the cct. might need to be redrawn in the ordinary form so as to be analyzed.


Example : For the cct. shown ; with ground potentials connected for the source and to elements ; this cct. can be redrawn to make it easy analyzing it.

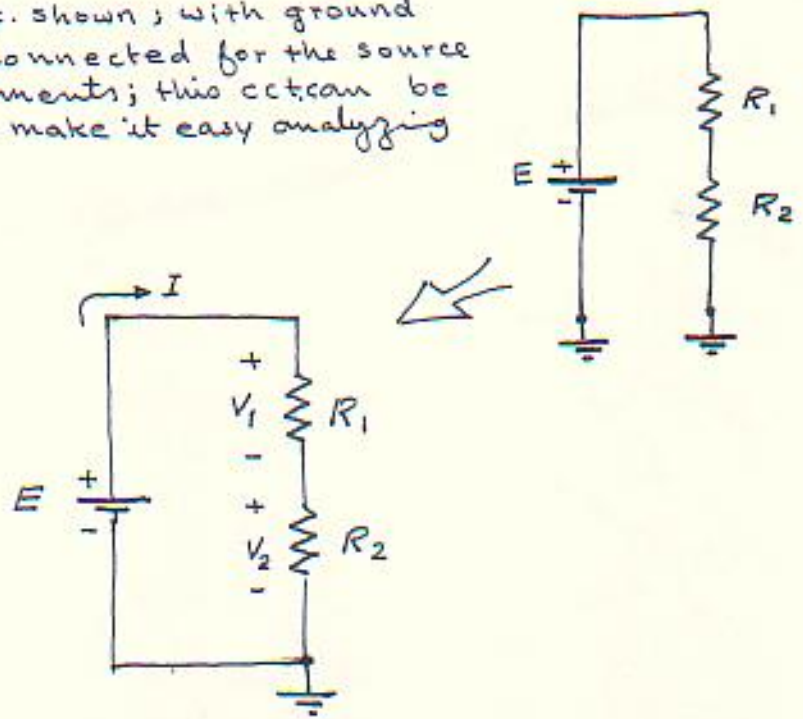

EE2

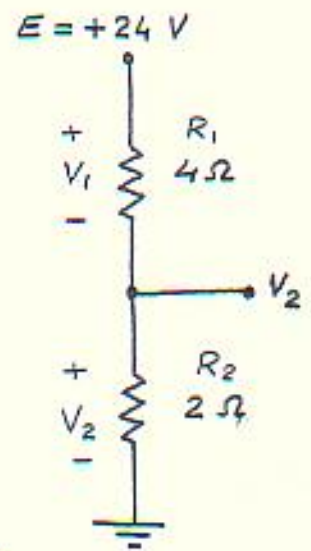Example

: Using the voltage divider rule, determine the voltages V_1 and V_2 for the cct shown:




Solution

: Redrawing the cct. with the standard battery symbol, then the cct. will be as shown below:

$$\therefore V_1 = \frac{R_1 E}{R_T} = \frac{(4) \cdot (24)}{4 + 2} = \underline{16\text{ V}}$$


and
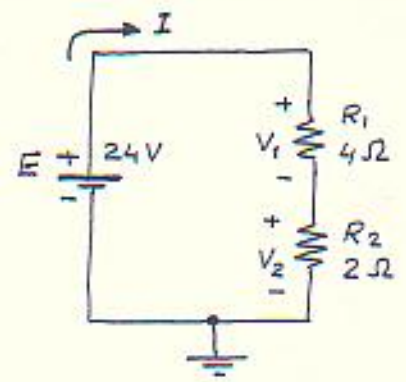
$$V_2 = \frac{R_2 E}{R_T} = \frac{(2) \cdot (24)}{4 + 2} = \underline{8\text{ V}}$$



Example

: For the cct. shown, determine V_{ab} , V_{cb} and V_b .

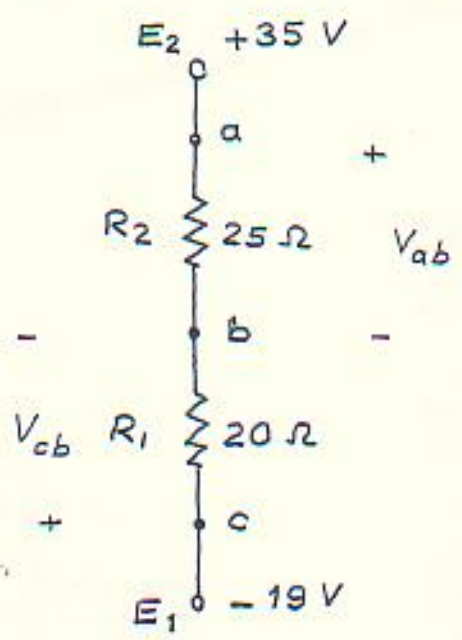

EE2

Solution


The cct. is redrawn as shown;

$$\therefore I = \frac{E_1 + E_2}{R_T} = \frac{19 + 35}{20 + 25} = 1.2 \text{ A}$$

$$V_{ab} = IR_2 = (1.2)(25) = 30 \text{ V}$$

$$\text{and } V_{cb} = -V_{bc} = -IR_1 = -(1.2)(20) = -24 \text{ V}$$

$$V_c = -E_1 = -19 \text{ V}$$

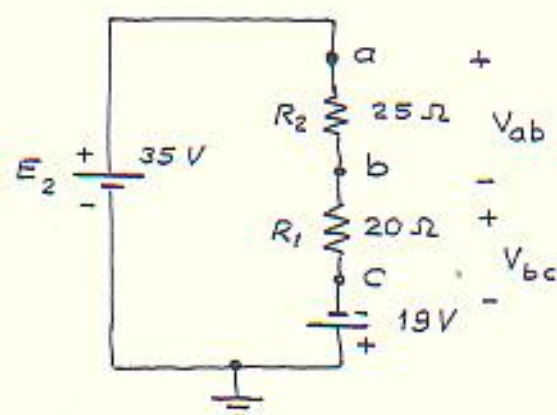


ملاحظة ١ / يمكنه الحل باستخدام voltage divider rule مع ملاحظة ان $V_{cb} = -V_{bc}$


ملاحظة ٢ / ان V_{ab} تعني فرق جهد النقطة a عن النقطة b ، فاذا كانت V_{ab} موجبة فان V_b اكبر من V_a والعكس صحيح .

ملاحظة ٣ / ان V_a تعني جهد النقطة a بالنسبة الى الارض .


Internal Resistance of Voltage Sources

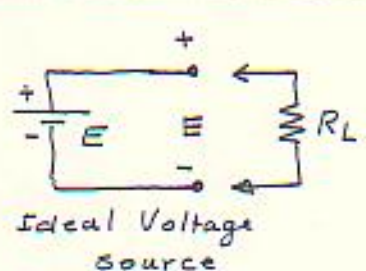

①

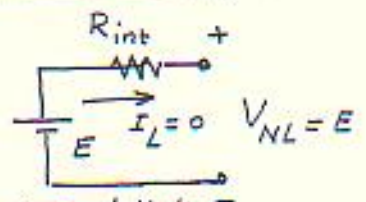

②

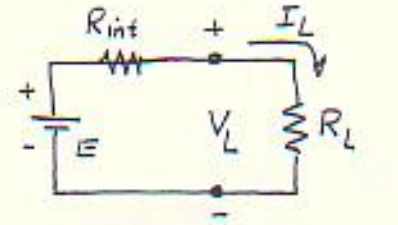

③

- Applying KVL on figure ③ :

$$E - I_L R_{in} - V_L = 0$$

- Applying KVL on figure ② :

$$E = V_{NL}$$

Substituting, then :

$$V_{NL} - I_L R_{in} - V_L = 0$$

$$\therefore V_L = V_{NL} - I_L R_{in}$$

2.2 Parallel Circuits

EE2

: Two branches or elements or networks are in parallel if they have two points in common.

For the parallel cct. shown ; using KCL, we have:

$$I = I_1 + I_2 + I_3$$


$$= \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$

since $V_1 = V_2 = V_3 = E = V$

$$\therefore I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\therefore \frac{V}{R_T} = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$
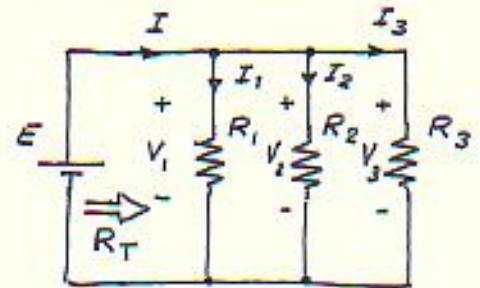
$$\therefore \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



$$E = V_1 = V_2 = V_3$$

$$I = \frac{E}{R_T} = \frac{V}{R_T}$$

In general, for N resistors connected in parallel, then:

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}$$

Notation

Conductance G

For parallel networks, it is common to use the idea of conductance in the cct. analysis. The conductance (G) is defined as:

$$G = \frac{1}{R} \quad \text{Siemens (S)}$$

So, we can write the total conductance G_T for the parallel cct shown, as:

$$G_T = G_1 + G_2 + G_3$$

$$\Rightarrow R_T = \frac{1}{G_T}$$



NOTE that, the total resistance R_T of parallel resistors is always less than the value of the smallest resistor.

Special Cases

EE2

The general relation for the total resistance of parallel resistors is:

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}$$

* Case 1

For equal resistors in parallel, ie, when

$$R_1 = R_2 = R_3 \dots R_N = R$$

then;
$$\frac{1}{R_T} = \underbrace{\frac{1}{R} + \frac{1}{R} + \frac{1}{R} + \dots + \frac{1}{R}}_N$$

$$\therefore \frac{1}{R_T} = N \left(\frac{1}{R} \right) \Rightarrow \boxed{R_T = \frac{R}{N}}$$

* Case 2

For two resistors in parallel, then R_T is given as:

$$\boxed{R_T = \frac{R_1 R_2}{R_1 + R_2}}$$

This means that, the total resistance of the two parallel resistors is the product of the two divided by their sum.


* Case 3

For three resistors in parallel, then R_T is given as:

$$\boxed{R_T = \frac{R_1 R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}}$$

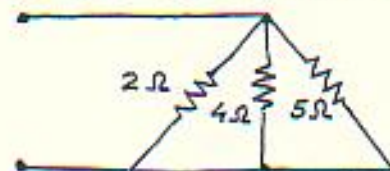Example


Determine the total resistance for the network shown:



Solution

Redraw the ckt. to be as shown;
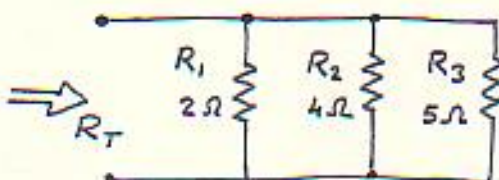
$$\begin{aligned} \frac{1}{R_T} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \\ &= \frac{1}{2} + \frac{1}{4} + \frac{1}{5} \\ &= 0.5 + 0.25 + 0.2 \\ &= 0.95 \end{aligned}$$




$$\Rightarrow \therefore R_T = \frac{1}{0.95} = \underline{1.053 \Omega}$$

Example

For the parallel network shown;

- Calculate R_T
- Determine I_T
- Calculate I_1 and I_2
- Determine the power to each resistive load.
- Determine the power delivered by the source and compare it with the total power dissipated by the resistive elements.

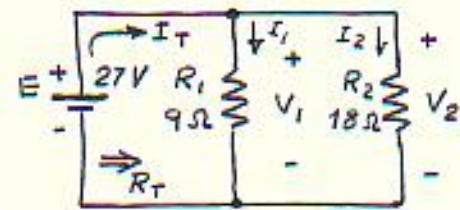Solution

$$a. \quad R_T = \frac{R_1 R_2}{R_1 + R_2} = \frac{(9)(18)}{9 + 18} = \frac{162}{27} = \underline{6 \Omega}$$

$$b. \quad I_T = \frac{E}{R_T} = \frac{27}{6} = \underline{4.5 A}$$

$$c. \quad I_1 = \frac{V_1}{R_1} = \frac{E}{R_1} = \frac{27}{9} = \underline{3 A}$$

and

$$I_2 = \frac{V_2}{R_2} = \frac{E}{R_2} = \frac{27}{18} = \underline{1.5 A}$$

ملاحظة: $I_T = I_1 + I_2$

$$d. \quad P_1 = I_1 V_1 = E I_1 = (27)(3) = \underline{81 W}$$

$$P_2 = I_2 V_2 = E I_2 = (27)(1.5) = \underline{40.5 W}$$

$$e. \quad P_s = E I_T = (27)(4.5) = 121.5 W$$

$$P_s = P_1 + P_2 = 81 + 40.5 = 121.5 W$$

* لاحظ ان مجموع القدرة المستهلكة في المقاومتين R_1 و R_2 يساوي القدرة التي يجهزها المصدر E


2.2.1 Current Divider Rule

Consider the parallel ckt. shown;

$$\text{We have; } I = \frac{V}{R_T} \Rightarrow V = I R_T$$

$$\text{and } R_T = \frac{R_1 R_2}{R_1 + R_2}$$
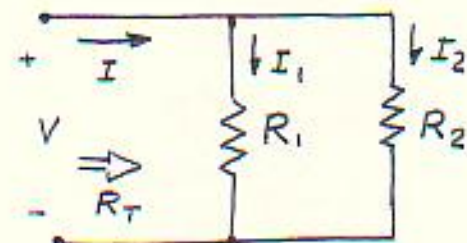
$$\text{but } I_1 = \frac{V}{R_1} = \frac{I R_T}{R_1} = I \cdot \frac{R_1 R_2}{R_1 + R_2} \cdot \frac{1}{R_1}$$



$$\therefore \boxed{I_1 = I \cdot \frac{R_2}{R_1 + R_2}}$$


Similarly, for I_2 , we have:

$$I_2 = \frac{V}{R_2} = \frac{I R_T}{R_2} = I \cdot \frac{R_1 R_2}{R_1 + R_2} \quad \boxed{EE1}$$

$$\therefore I_2 = I \cdot \frac{R_1}{R_1 + R_2}$$

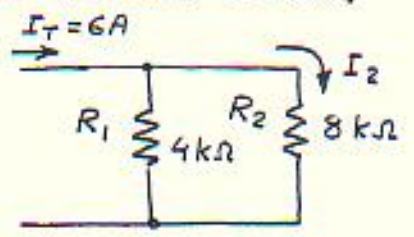Example

: Determine the current I_2 for the network shown;




solution:
$$I_2 = I_T \cdot \frac{R_1}{R_1 + R_2}$$

$$= 6 \frac{4 \times 10^3}{(4 + 8) \times 10^3} = 6 \cdot \frac{4}{12} = \underline{2 \text{ A}}$$

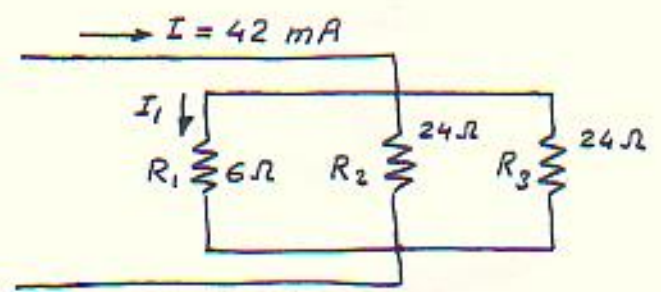Example

: Find the current I_1 for the network shown;



Solution

$$I_1 = I \cdot \frac{R_T}{R_1}$$

$$R_T = \frac{R_1 R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

or

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{6} + \frac{1}{24} + \frac{1}{24}$$


$$\Rightarrow R_T = 4 \Omega$$

$$\therefore I_1 = 42 \times 10^{-3} \frac{4}{6}$$

$$= 28 \times 10^{-3} = \underline{28 \text{ mA}}$$

2.2.2 Voltage Sources in Parallel :

EE2

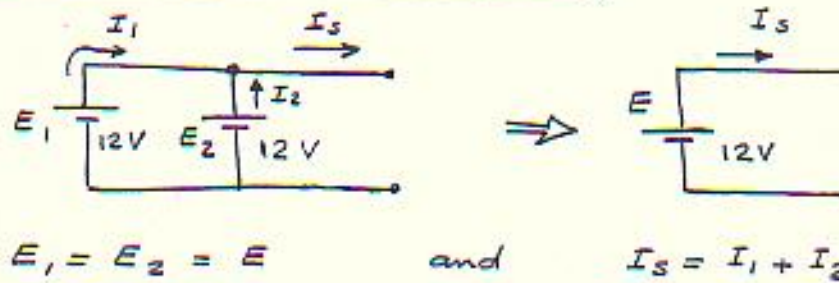

To increase the current rating of the source, two or more batteries in parallel of the same terminal voltage would be used.

2.3 Open and Short Circuits


: We often need to apply the open and short circuits in the analysis of electric networks.

* Open Circuit

: An open circuit is simply two isolated terminals not connected by an element of any kind.

Consider the circuit shown; with open circuit terminals a and b.

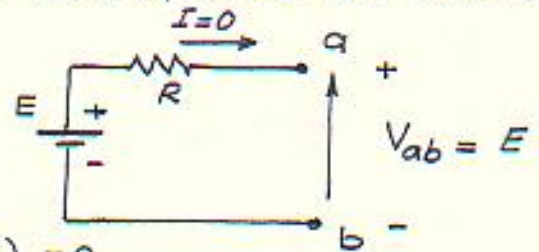$V_{open\ circuit} = V_{OC} = V_{ab} = E$



since I (in the open circuit) = 0


In general

: An open circuit CAN HAVE a potential difference (voltage) across its terminals but the current is always ZERO.

* Short Circuit

: A short circuit is a direct connection of zero ohms across an element or combination of elements.

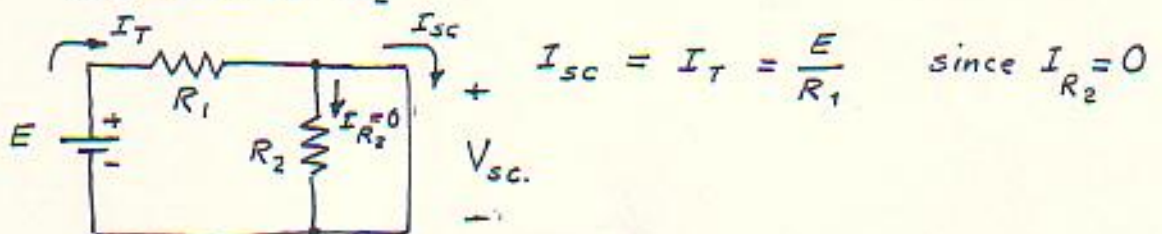Consider the circuit shown, with a short circuit across the resistor R_2



$V_{short\ ckt.} = V_{sc} = \underline{\underline{0}}$


EE2

In general

: A short circuit CAN CARRY a current of any level but the potential difference (voltage) across its terminals is always ZERO.

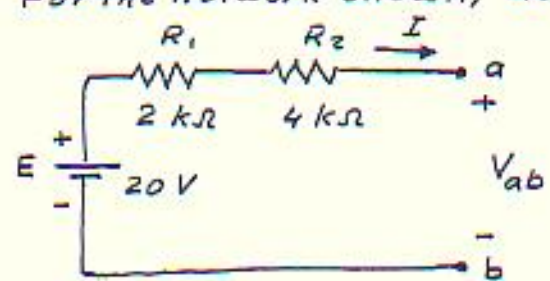Examples

: (a). For the network shown, determine V_{ab} .




Solution: - We have an open cct across the terminal a and b, the

$I = 0 \Rightarrow V_1 = 0$ and $V_2 = 0$

- Applying KVL $\Rightarrow V_{ab} = E = 20V$

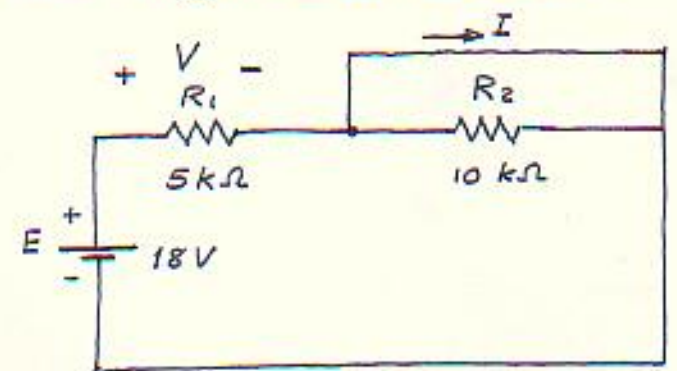(b). Calculate I and V for the network shown;



Solution: - We have a short cct. across R_2


\Rightarrow No current through R_2

$\Rightarrow I = \frac{E}{R_T} = \frac{E}{R_1 + 0} = \frac{18}{5k\Omega}$

$= \underline{3.6 \text{ mA}}$

$\therefore V = I R_1 = E = \underline{18V}$

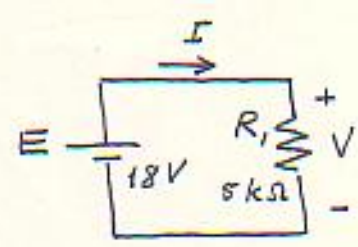Note: the cct can be redrawn to be as shown



2.4 Source Transformation :

EE2

It is often necessary or convenient to have a voltage source rather than a current source or a current source rather than a voltage source.

In the ckt. shown, we have a voltage source connected to a load resistance R_L

We have :


$$I_L = \frac{E}{R_T} = \frac{E}{R_S + R_L}$$

Multiplying the numerator by $(R_S/R_S = 1)$, we have :

$$I_L = \frac{(R_S/R_S)E}{R_S + R_L} = \frac{R_S(E/R_S)}{R_S + R_L}$$


$$\therefore I_L = \frac{R_S \cdot I}{R_S + R_L}$$

$$I = \frac{E}{R_S}$$

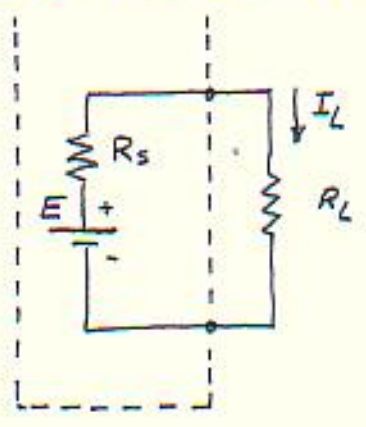

Voltage Source


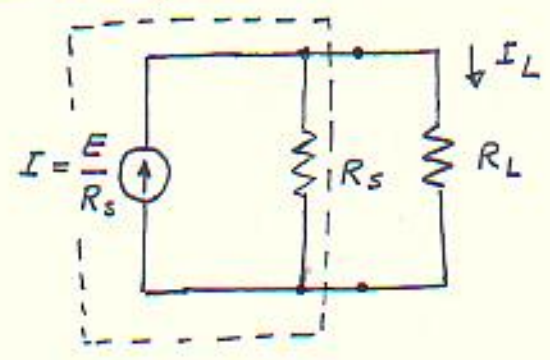
This is a current divider equation, which can be represented by the circuit below; which is the equivalent ckt. of the voltage source.



Current source

In general

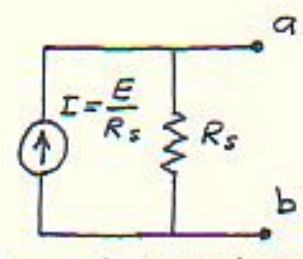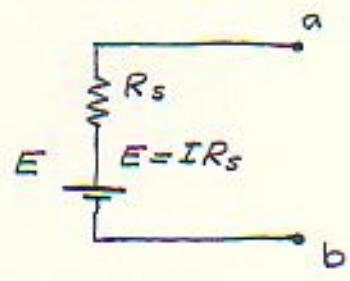A voltage source with voltage E and series resistor R_S can be replaced by a current source with a current I and parallel resistor R_S as shown:




← current to voltage source

voltage source to current source →

EE2

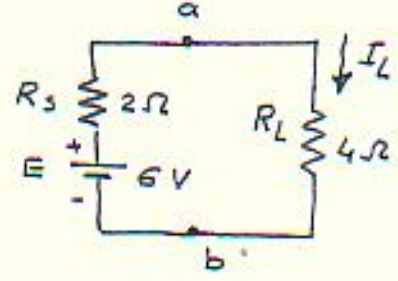Example

Convert the voltage source, in the cct below, to a current source, then calculate the current through the load for each source.




Solution

* For the voltage source cct;

$$I_L = \frac{E}{R_s + R_L} = \frac{6}{2 + 4} = \underline{\underline{1 A}}$$

* For the current source cct;

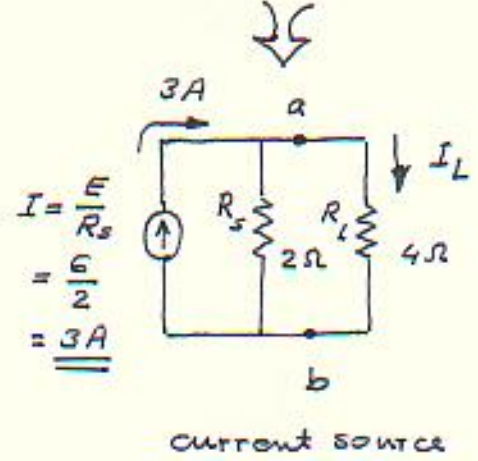
$$I_L = \frac{I R_s}{R_s + R_L} = \frac{(3)(2)}{2 + 4} = \underline{\underline{1 A}}$$



نصف ان I_L متاثر في الحالتين وهذا صحيح.

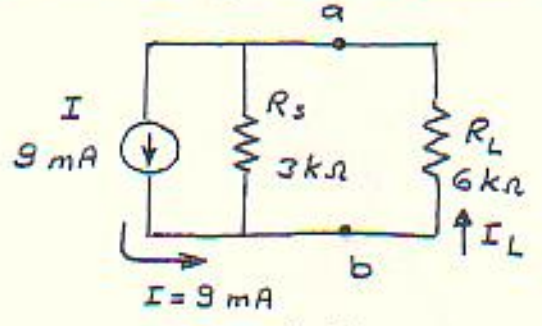Example

Convert the current source, in the cct. shown, to a voltage source and determine I_L for each source.



Solution


* For the current source cct;

$$I_L = \frac{I \cdot R_s}{R_s + R_L} = \frac{(9 \times 10^{-3})(3 \times 10^3)}{(3 + 6) \times 10^3} = 3 \times 10^{-3} = \underline{\underline{3 mA}}$$

* For the voltage source cct;

$$I_L = \frac{E}{R_T} = \frac{E}{R_s + R_L} = \frac{27}{(3 + 6) \times 10^3} = 3 \times 10^{-3} = \underline{\underline{3 mA}}$$

current divider rule →

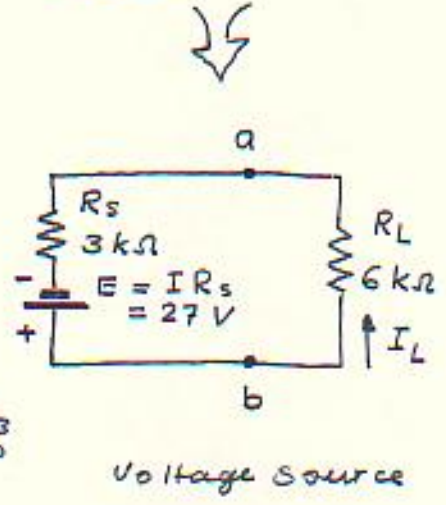


2.3 Series-Parallel Circuits

EE2

Example

: For circuit shown,

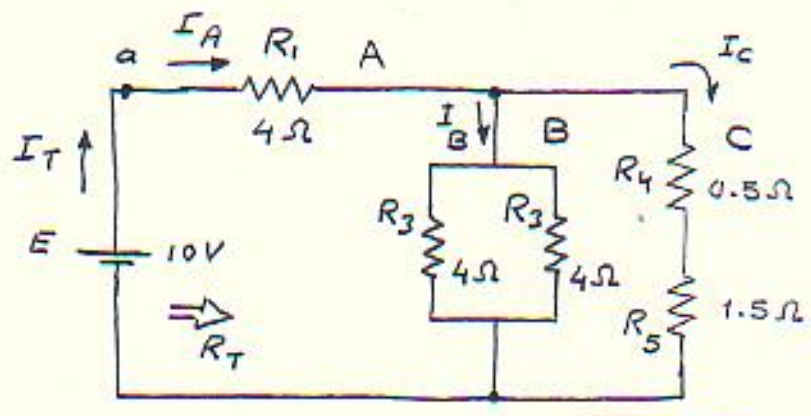


Fig(1)

Solution

$$R_1 = R_A = 4\Omega$$


$$R_B = R_2 // R_3 = \frac{R_N}{N} = \frac{4}{2} = 2\Omega$$
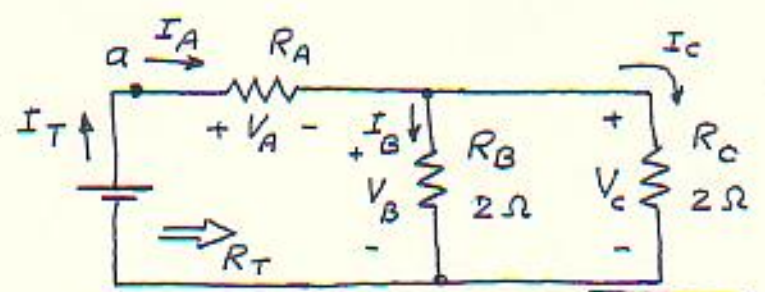
$$R_C = R_4 + R_5 = 0.5 + 1.5 = 2\Omega$$



Fig(2)

$$R_{B||C} = \frac{R_N}{N} = \frac{2}{2} = 1\Omega$$

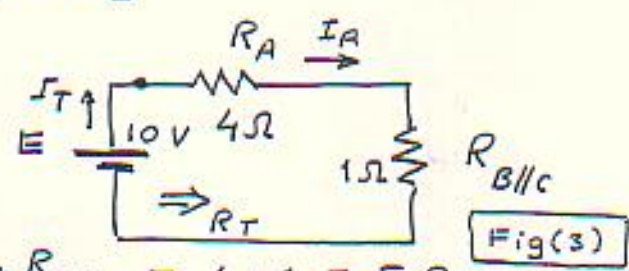

Fig(3)

From Fig. 3 $\Rightarrow \therefore R_T = R_A + R_{B||C} = 4 + 1 = 5\Omega$

$\hookrightarrow \therefore I_T = \frac{E}{R_T} = \frac{10}{5} = 2A$

From Fig(2) $I_B = I_C = \frac{I_A}{2} = \frac{2}{2} = 1A$

From Fig(1) $\Rightarrow I_{R_4} = I_{R_5} = I_C = 1A$

From fig(2) $\Rightarrow V_A = I_A R_A = (2)(4) = 8V$

$V_B = I_B R_B = (1)(2) = 2V$

$V_C = I_C R_C = (1)(2) = 2V$


For check

KVL $\sum V = 0 \Rightarrow E - V_A - V_B = 0 \Rightarrow 10 = 8 + 2 \Rightarrow 10V = 10V$

Wye - Delta Transformation


EE2

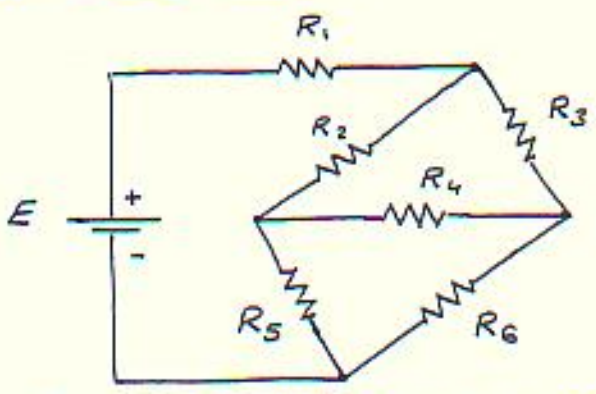There are some cases often arises in circuit analysis, when the resistors are neither in parallel nor in series. For example, consider the circuit shown:




In this circuit, $R_1, R_2, R_3 \dots R_6$ are neither in series nor in parallel

* Wye (Y or star) connection

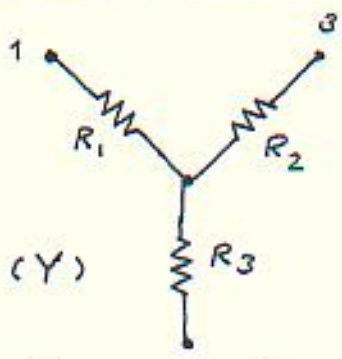

Y or star circuit connection


Equivalent

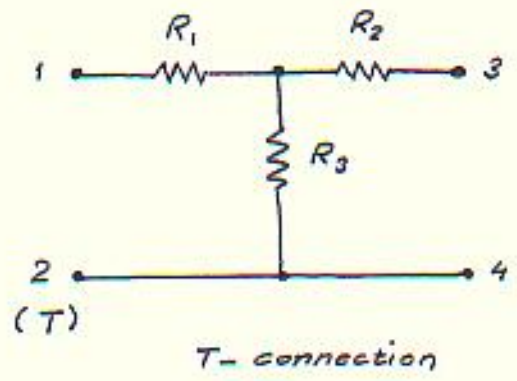

T-connection


Y and T connections

* Delta (Δ or π) circuit connection

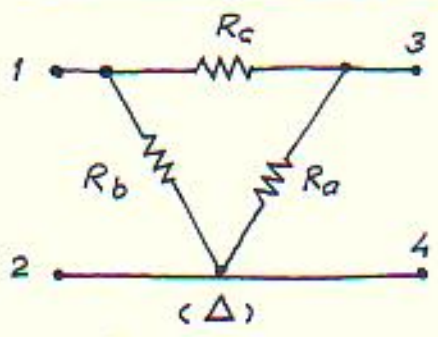

Delta circuit connection

Equivalent

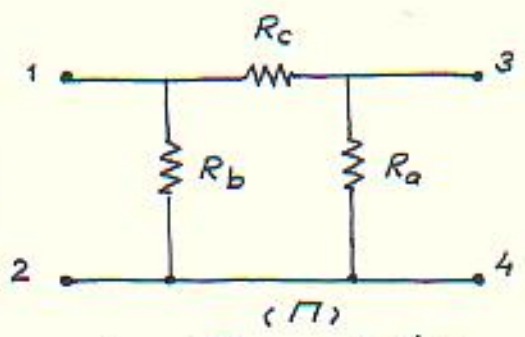

(Π)

Delta circuit connection & its equivalent Π -connection

Δ Y
* Delta to Wye Transformation :



- We have Δ and want to get its equivalent star circuit

- Consider the Δ circuit shown; to be transformed into its equivalent star shown below:

$$R_{12} = \frac{R_b (R_a + R_c)}{R_a + R_b + R_c}$$

$$R_{13} = \frac{R_c (R_a + R_b)}{R_a + R_b + R_c}$$
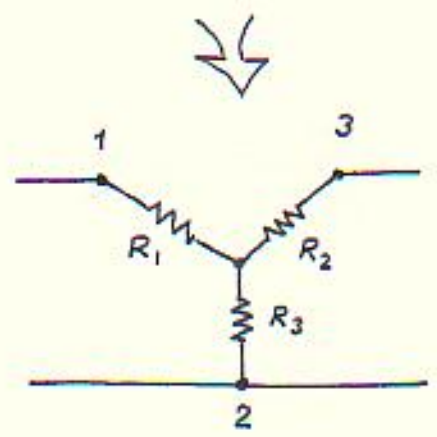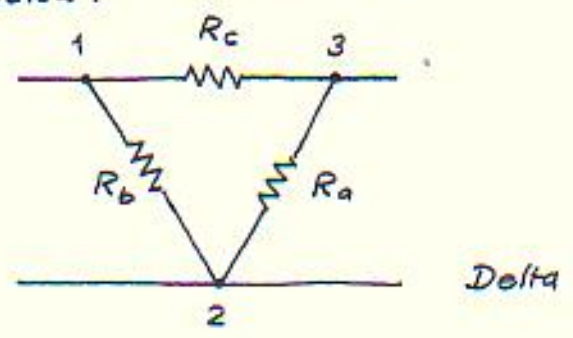
$$R_{23} = \frac{R_a (R_b + R_c)}{R_a + R_b + R_c}$$



$$R_{12} = R_1 + R_3$$

$$R_{13} = R_1 + R_2$$

$$R_{23} = R_2 + R_3$$

$$\therefore R_1 + R_3 = \frac{R_b (R_a + R_c)}{R_a + R_b + R_c} \dots (1)$$

and $R_1 + R_2 = \frac{R_c (R_b + R_c)}{R_a + R_b + R_c} \dots (2)$

$$R_2 + R_3 = \frac{R_a (R_b + R_c)}{R_a + R_b + R_c} \dots (3)$$

Subtraction Eq.(3) from Eq.(1) and adding the resulting equation to Eq.(1) results in:

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

Similarly;

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

and;

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

IN GENERAL

Each resistor in the Y network is the product of the resistors in the two adjacent Δ branches, divided by the sum of the three resistors

* Wye to Delta Transformation

- We have Y connected circuit and want to get its equivalent Δ.
- Consider the Y circuit shown, its equivalent Δ is shown below;

Using the previous sets of equations, then we have:


$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3}$$

and

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2}$$

IN GENERAL

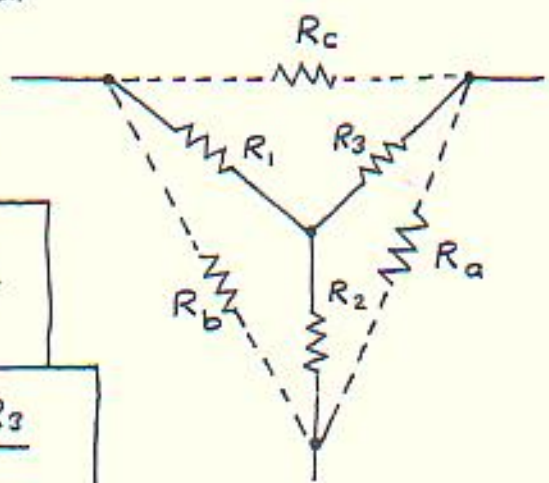

Each resistor in the Δ network is the sum of all possible products of Y resistors taken two at a time, divided by the opposite Y resistor.

Notes

* The Y and Δ networks are said to be balanced when:

$$R_1 = R_2 = R_3 = R_Y$$

and

$$R_a = R_b = R_c = R_\Delta$$

* Under balance condition, the conversion equations become:


$$R_Y = \frac{R_\Delta}{3}$$

or

$$R_\Delta = 3R_Y$$

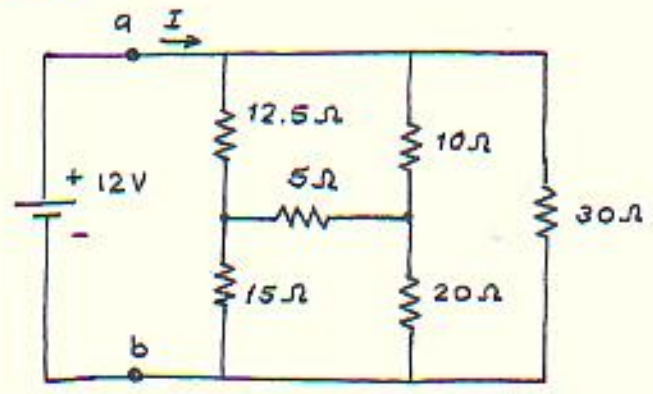Example

Obtain the equivalent resistance R_{ab} for the circuit shown and use it to find the current I



Solution

- * We can't use the relations of series connected or parallel connected resistors to obtain R_{ab} .
- * We try to use Δ-Y transformations or Y-Δ to get R_{ab} .


* If we transform the Y consisting of :

$$R_1 = 10 \Omega$$

$$R_2 = 20 \Omega$$

and $R_3 = 5 \Omega$

∴ the equivalent Δ circuit contains :

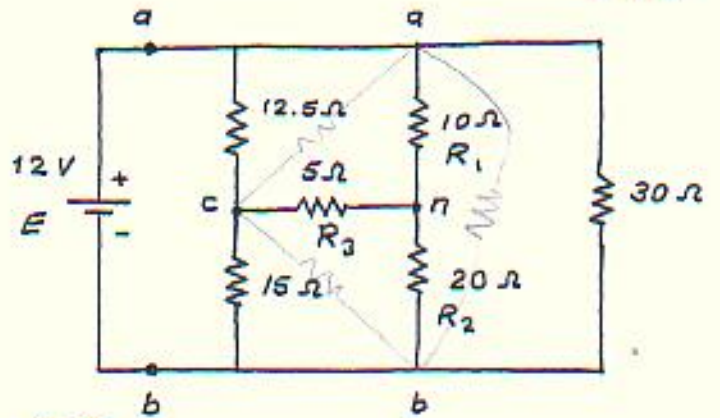

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$$

$$= \frac{10 \times 20 + 20 \times 5 + 5 \times 10}{10} = \frac{350}{10}$$

$$= 35 \Omega$$

Similarly;

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2} = \frac{350}{20} = 17.5 \Omega$$

and:

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3} = \frac{350}{5} = 70 \Omega$$

$$\therefore R_{ab} = (7.3 + 10.5) \parallel 30$$



$$= \frac{17.8 \times 21}{17.8 + 21}$$

$$\Rightarrow R_{ab} = \underline{9.632 \Omega}$$

$$\therefore I = \frac{E}{R_{eq}} = \frac{E}{R_{ab}}$$

$$= \frac{12}{9.632}$$
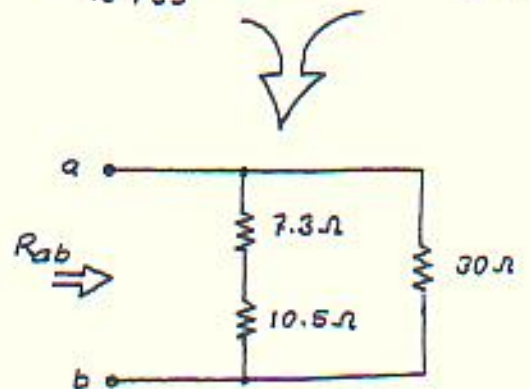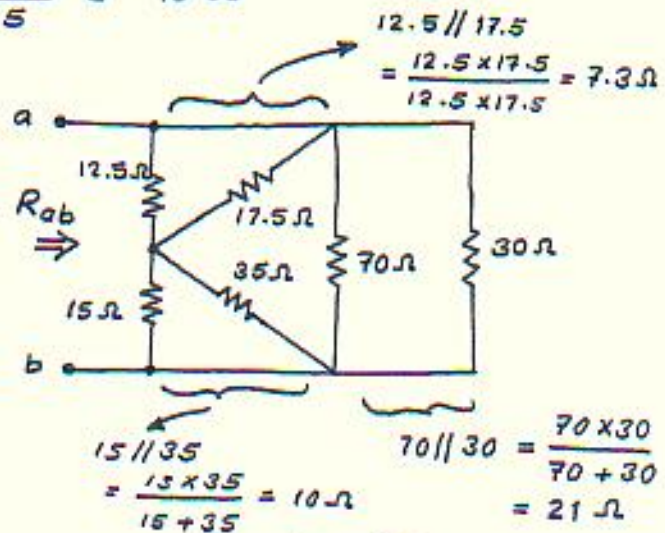
$$\Rightarrow I = \underline{1.246 \text{ A}}$$



ملاحظة: جميع أسئلة الكتاب والأدلة المحلولة فيه مطلوبة

Example 1

Three resistors are connected in series across a 12 V battery. The first resistor has a value of 1Ω , the second has a voltage drop of 4 V, and the third has a power dissipation of 12 W.

Calculate the value of the circuit current.

Solution

We have

$$P_3 = I^2 R_3 = 12 \text{ W} \quad \text{--- (1)}$$

and

$$V_2 = I R_2 = 4 \text{ V} \quad \text{--- (2)}$$


From (2)

$$\therefore I = \frac{4}{R_2}$$

From (1) & (2)

$$\left(\frac{4}{R_2}\right)^2 R_3 = 12$$

$$\therefore R_3 = \frac{3}{4} R_2^2$$

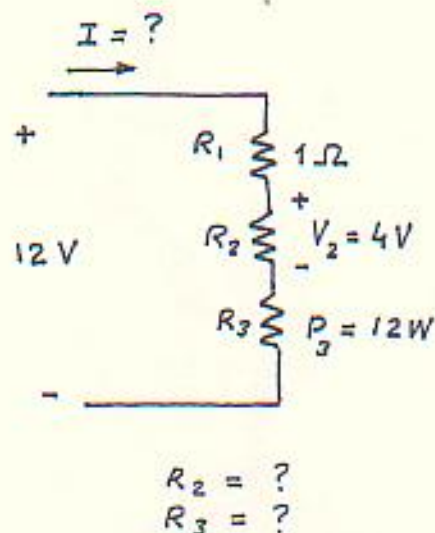

From the circuit shown, we have:

$$12 = I (R_1 + R_2 + R_3) = I (1 + R_2 + R_3)$$

Substituting for I and R_3 , we have:

$$12 = \frac{4}{R_2} \left(1 + R_2 + \frac{3}{4} R_2^2\right)$$

$$\therefore 3R_2^2 - 8R_2 + 4 = 0$$

$$\therefore R_2 = \frac{8 \pm \sqrt{64 - 48}}{6} = 2\Omega \quad \text{or} \quad \frac{2}{3}\Omega$$

$$\therefore R_3 = \frac{3}{4} R_2^2 \Rightarrow R_3 = 3\Omega \quad \text{or} \quad \frac{1}{3}\Omega$$


$$\therefore I = \frac{12}{R_1 + R_2 + R_3} = \frac{12}{1 + 2 + 3} = \underline{2 \text{ A}}$$

or

$$I = \frac{12}{1 + \left(\frac{2}{3}\right) + \left(\frac{1}{3}\right)} = \underline{6 \text{ A}}$$

Practice Problem

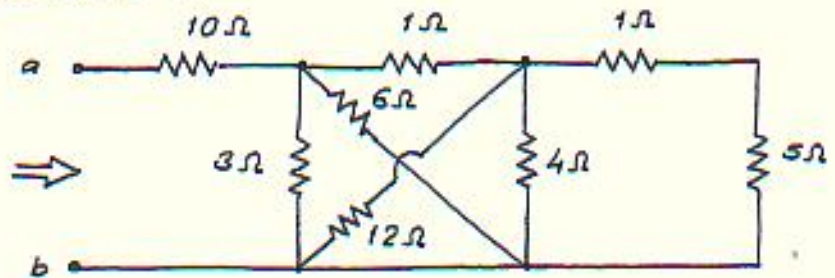_____ : Calculate the equivalent resistance R_{ab} in the circuit shown.




Answer

_____ : $R_{ab} = 11.2 \Omega$

Practice Problem

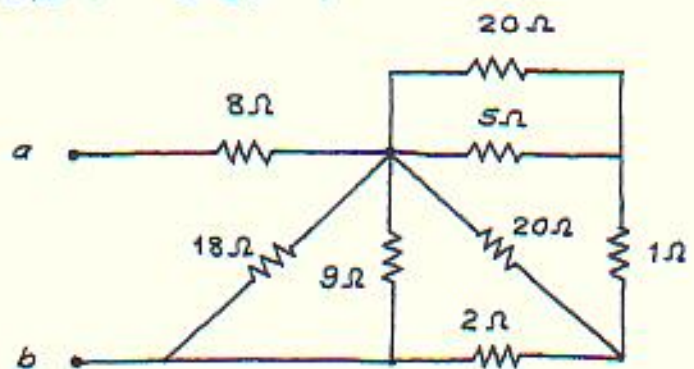_____ : Find R_{ab} for the circuit shown:



Answer

_____ : $R_{ab} = 11 \Omega$

Practice Problem

_____ : Find V_1 and V_2 in the circuit shown. Also calculate I_1 and I_2 and the power dissipated in the 12Ω and 40Ω resistors.


Answer

_____ :

$$V_1 = 5V, \quad V_2 = 10V$$


$$I_1 = 416.7 \text{ mA}, \quad I_2 = 250 \text{ mA}$$
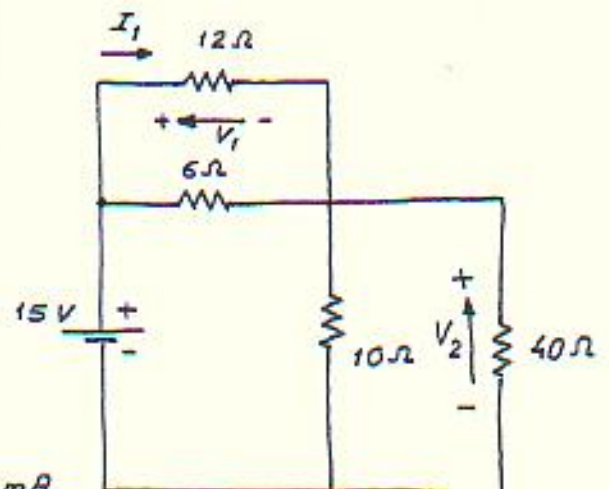
$$P_1 = 2.083 \text{ W}, \quad P_2 = 2.5 \text{ W}$$



Practice Problem

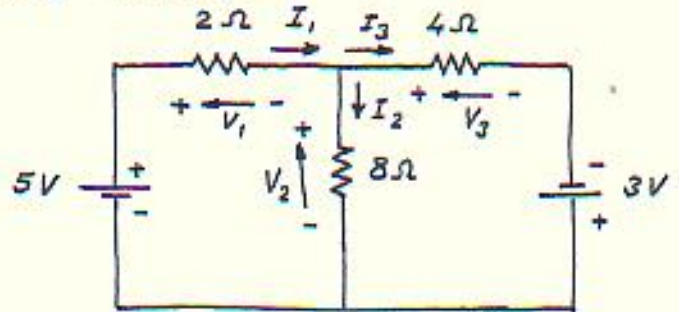Find the currents and voltages in the circuit shown, using Kirchoff's laws.




Answer

$V_1 = 3V$, $V_2 = 2V$, $V_3 = 5V$


$I_1 = 1.5A$, $I_2 = 0.25A$, $I_3 = 1.25A$

Example

Find Req for the circuit shown.

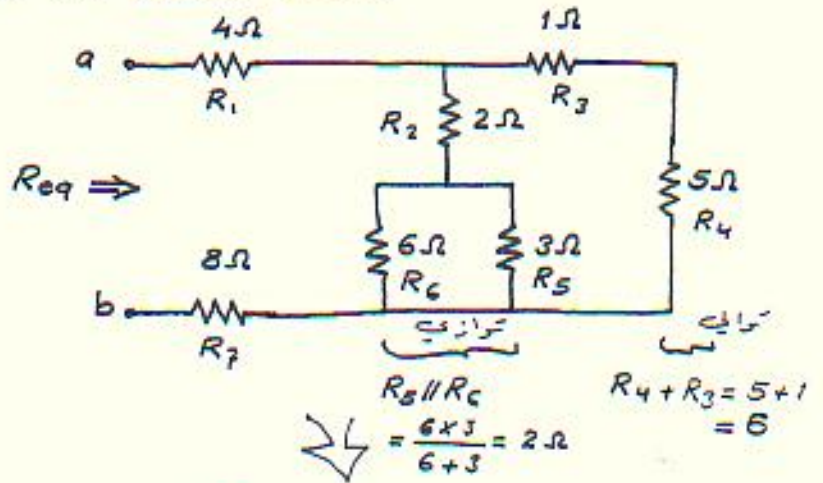

Solution

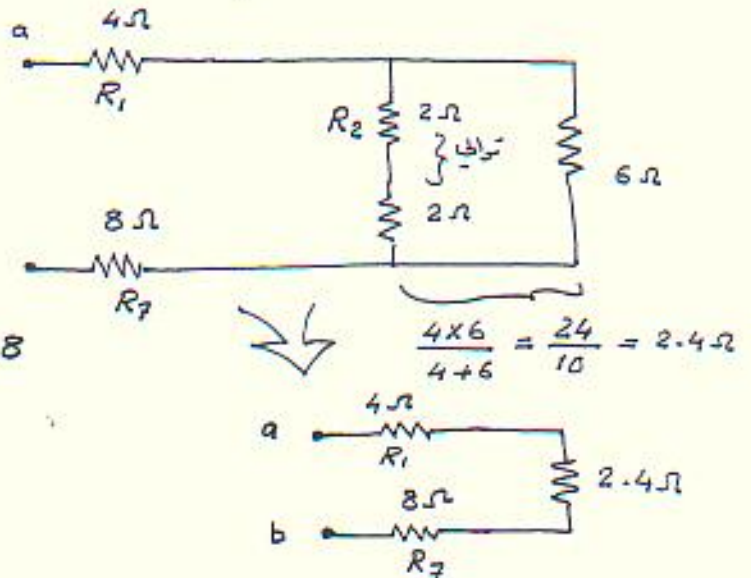


$\therefore R_{eq} = R_{ab} = 4 + 2.4 + 8$
 $= \underline{14.4 \Omega}$

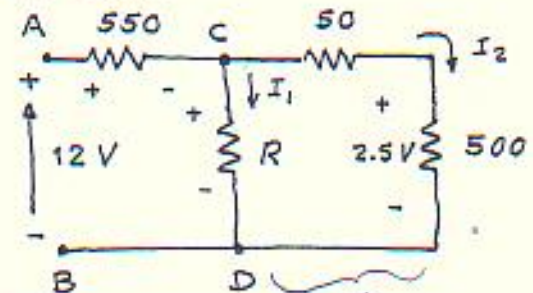Example

TS2

: What is the value of the unknown resistor R in the circuit shown, if the voltage drop across the $500\ \Omega$ resistor is 2.5 V ? All resistors are in Ohms.




Solution

Using the voltage divider rule;


* The voltage drop across the $50\ \Omega$ resistor is:
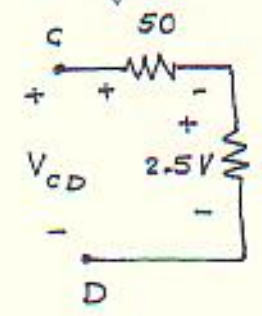
$$V_{50\ \Omega} = 2.5 \times \frac{50}{500} = 0.25\text{ V}$$



$$\therefore V_{CD} = 2.5 + 0.25 = 2.75\text{ V}$$
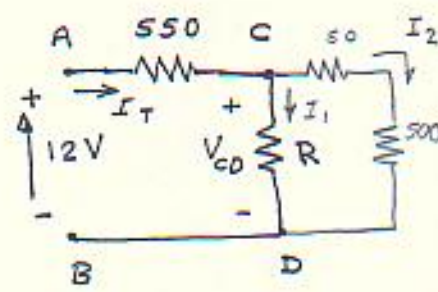
$$* V_{550\ \Omega} = 12 - V_{CD} = 12 - 2.75 = 9.25\text{ V}$$



$$\therefore I_T = \frac{V_{550\ \Omega}}{550} = \frac{9.25}{550} = 0.0168\text{ A}$$

$$I_2 = \frac{V_{500}}{500} = \frac{2.5}{500} = 0.005\text{ A}$$


$$\therefore I_1 = I - I_2 = 0.0168 - 0.005 = 0.0118\text{ A}$$

$$\therefore R = \frac{V_{CD}}{I_1} = \frac{2.75}{0.0118} = 233\ \Omega$$

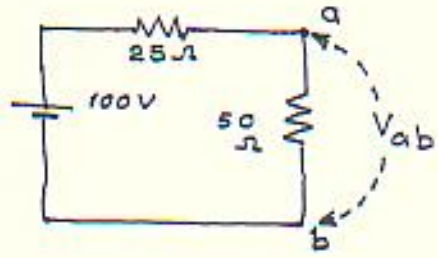
Example

TS2


For the networks shown, find V_{ab} (with polarity).




(a)

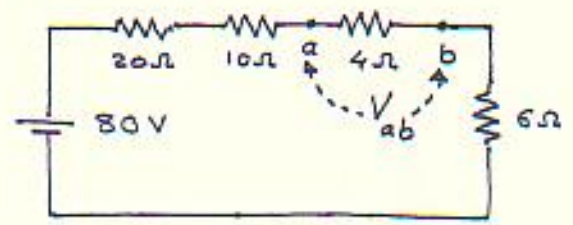

(b)

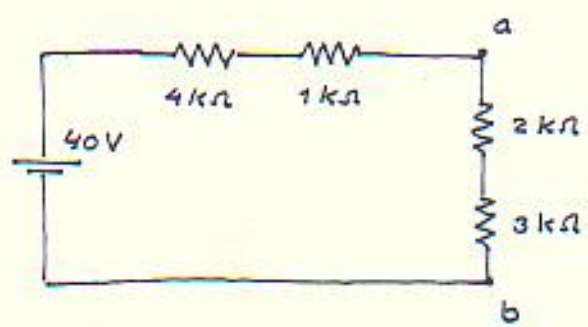

(c)

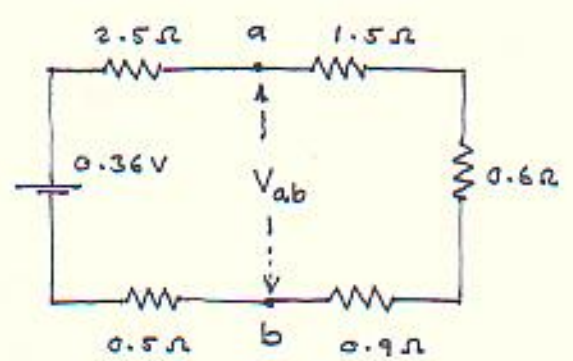


Solution

(a). Using the voltage divider rule; then

$$\therefore V_{ab} = 100 \cdot \frac{50}{25+50}$$


$$= 66.67 \text{ V}$$

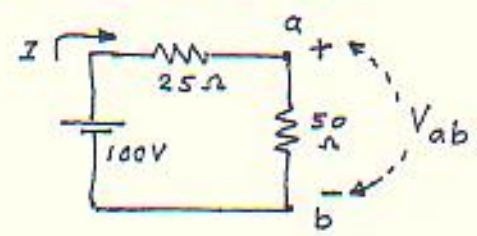

(b). Using the voltage divider rule, then:

$$\therefore V_{ab} = 80 \cdot \frac{4}{20+10+4+6}$$


$$= 8 \text{ V}$$

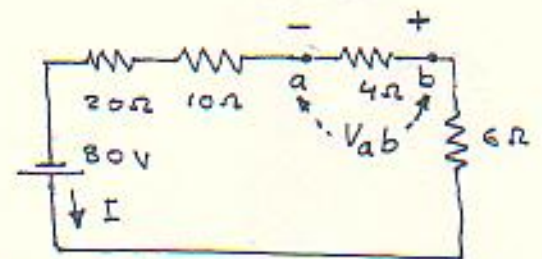

(c). Using the voltage divider rule, then:

$$V_{ab} = \frac{(2+3) \times 10^3}{(4+1+2+3) \times 10^3}$$

$$= 20 \text{ V}$$

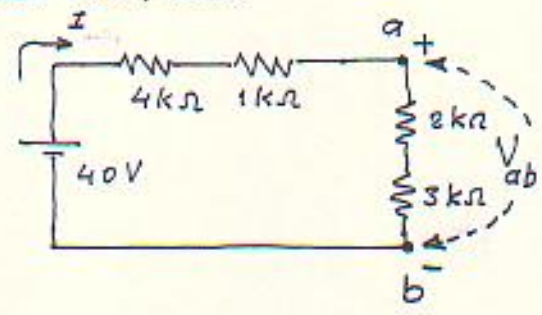


(d). Using the voltage divider rule, then;

TS2


$$V_{ab} = 0.36 \frac{(1.5 + 0.6 + 0.9)}{2.5 + 1.5 + 0.6 + 0.9 + 0.5}$$

$$= 0.18 \text{ V}$$

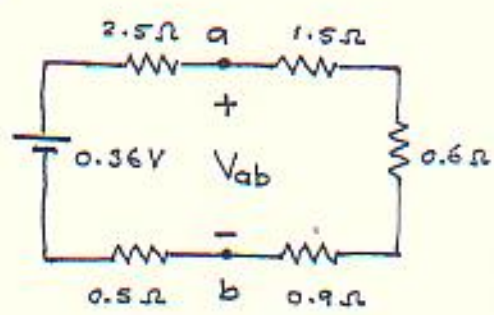

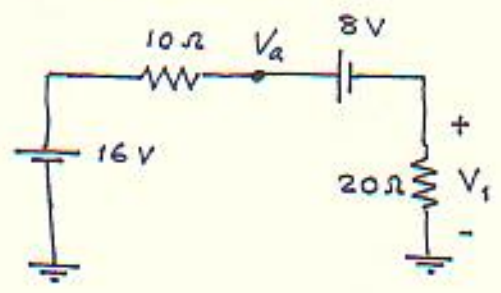Example

: Determine the voltage V_a and V_1 , for the network shown.



Solution

: Redraw the circuit to be as shown;

using KVL

$$V_a = 8 + V_1$$

$$= 8 + I(20)$$


$$I = ?$$

$$I = \frac{16 - 8}{20 + 10}$$

$$= \frac{8}{30}$$

$$\therefore V_a = 8 + \frac{8}{30}(20) = 8 + \frac{16}{3} = \frac{40}{3} \text{ V}$$

$$= \underline{13.33 \text{ V}}$$

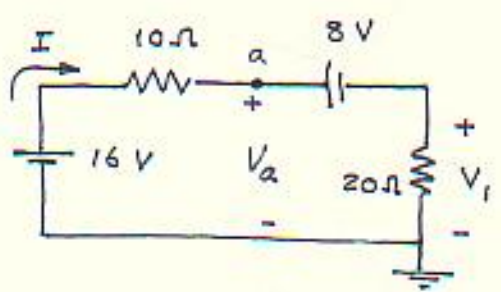

OR


using KVL

$$16 = I(10) + V_a \Rightarrow 16 = \frac{8}{30}(10) + V_a$$

$$\therefore V_a = 16 - \frac{8}{3} = \frac{40}{3} = \underline{13.33 \text{ V}}$$


$$V_1 = I(20) = \frac{8}{3}(20) = \frac{16}{3} = \underline{5.33 \text{ V}}$$

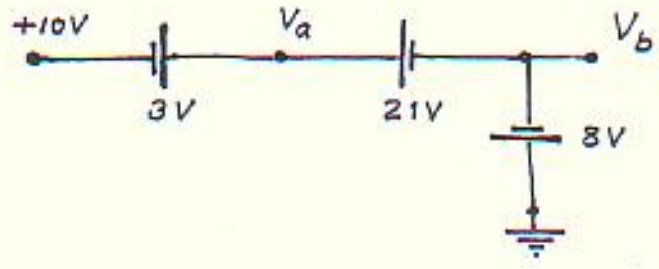Example : Determine the voltage V_{ab} for the network shown; TS2



Solution : Redraw the cct. to be as shown;

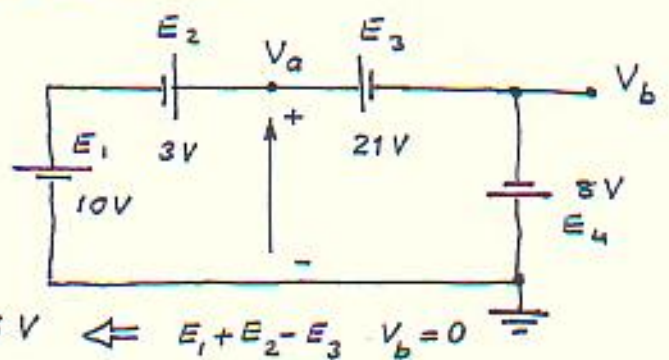$V_b = -8V$
 $V_b = -E_4$ directly the drop of point b with respect to the ground.



OR
 using KVL


$$V_b = 10 + 3 - 21 = -8V$$

KVL $V_a = 10 + 3 = 13V$ $\leftarrow E_1 + E_2 - V_a = 0$

$$\therefore V_{ab} = V_a - V_b = 13 - (-8) = 21V$$

OR
 $V_a - E_3 + E_4 = 0$
 $\therefore V_a = E_3 - E_4 = 21 - 8 = 13V$

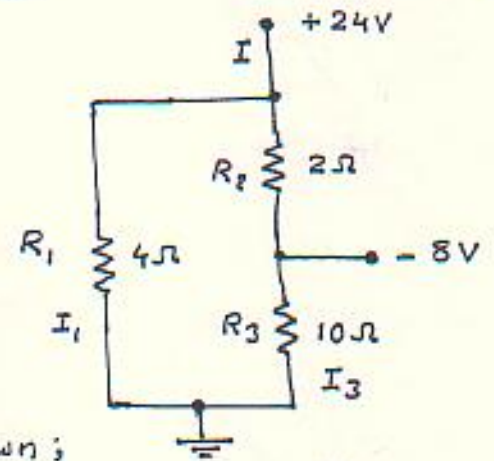Example : For the network shown, find the currents I , I_1 , and I_3 and indicate their directions.



Solution : Redraw the cct to be as shown;

$$I_3 = \frac{V_b}{R_3} = \frac{-8}{10} = -0.8A$$

$$I_1 = \frac{V_a}{R_1} = \frac{24}{4} = 6A$$

$$I_2 = \frac{V_a - V_b}{R_2} = \frac{24 + 8}{2} = 16A$$

$$I = I_1 + I_2 = 6 + 16 = 24A$$

