

The voltage and current divider circuits

*Ministry of higher education and
scientific research
Al-Mustaqbal University
Department of Medical
Instrumentation Techniques
Engineering
Lecturer: MSC. Shahlaa yaseen*

Lecture Four

The voltage and current divider circuits

4.1 The voltage-divider circuit

Voltage-divider circuit, shown in Fig.4.1. We analyze this circuit by directly applying Ohm's law and Kirchhoff's laws. To aid the analysis we introduce the current I as shown in Fig.4.1 (b).

From Kirchhoff's current law R_1 and R_2 , carry the same current. Applying **Kirchhoff's voltage law** around the closed loop yields

$$V_s = I R_1 + I R_2,$$

Now we can use Ohm's law to calculate v_1 and, v_2 :

$$v_1 = \frac{R_1 v_s}{R_1 + R_2}, \quad v_2 = \frac{R_2 v_s}{R_1 + R_2} \quad (4.1)$$

In general, if a voltage divider has N resistors (R_1, R_2, \dots, R_N) in series with the source voltage v_s , the N th resistor (R_N) will have a voltage drop of

$$v_N = \frac{R_N v_s}{R_1 + R_2 + \dots + R_N} = \frac{R_N v_s}{R_{eq}} \quad (4.2)$$

4.2 The current-divider circuit

The **current-divider circuit** shown in Fig. 4.2. The current divider is designed to divide the current i_s between R_1 and R_2 . We find the relationship between the current i_s , and the current in each resistor (that is, i_1 and i_2) by directly applying **Ohm's law and Kirchhoff's current law**.

The voltage across the parallel resistors is

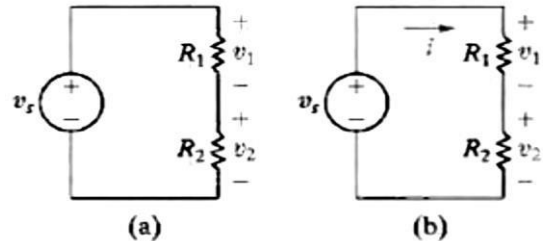


Figure 4.1 (a) A voltage-divider circuit and (b) The voltage-divider circuit with current i indicated

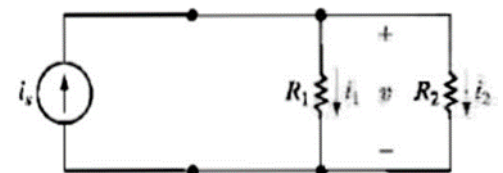


Figure 4.2 the current-divider circuit.

$$V = i_1 R_1 = i_2 R_2 = \frac{R_1 R_2}{R_1 + R_2} i_s$$

$$i_1 = \frac{R_2 i_s}{R_1 + R_2}, \quad i_2 = \frac{R_1 i_s}{R_1 + R_2} \quad (4.3)$$

If we divide both the numerator and denominator by $R_1 R_2$, Eq. (2.16) become

$$i_1 = \frac{G_1 i_s}{G_1 + G_2}, \quad i_2 = \frac{G_2 i_s}{G_1 + G_2} \quad (4.4)$$

Thus, in general, if a current divider has N conductors (G_1, G_2, \dots, G_N) in parallel with the source current i , the n th conductor (G_N) will have current

$$i_N = \frac{G_N i_s}{G_1 + G_2 + \dots + G_N} = \frac{R_{eq} i_s}{R_N} \quad (4.5)$$

Example 2.3: Find i_o and v_o in the circuit shown in Fig. 4.3(a). Calculate the power dissipated in the 3- Ω resistor.

Solution: The 6- Ω and 3- Ω resistors are in parallel, so their combined resistance is

$$6 \Omega \parallel 3 \Omega = 6 \times 3 / (6 + 3) = 2 \Omega$$

By apply voltage division, since the 12 V in Fig. 4.3(b) is divided between the 4- Ω and 2- Ω resistors. Hence,

$$v_o = 2(12 \text{ V}) / (2 + 4) = 4 \text{ V}$$


Apply current division to the circuit in Fig. 4.3(a) now that we know i , by writing

$$i = 12 / 4 + 2 = 2 \text{ A}$$

$$i_o = 6 i / (6 + 3) = 4 / 3 \text{ A}$$

The power dissipated in the 3- Ω resistor is
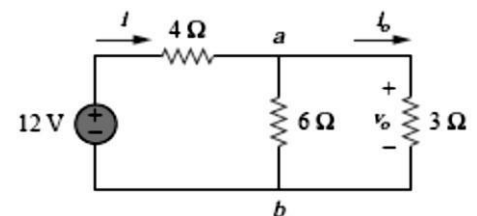
$$p_o = v_o i_o = 4(4/3) = 5.333 \text{ W}$$



(a)

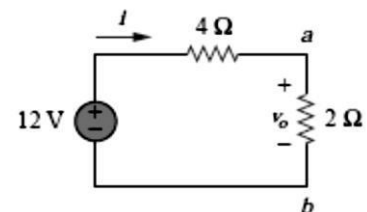


Figure 4.3 (a) Original circuit, (b) Its equivalent circuit.

Example 4.2: Find the voltage drop at the resistor 4Ω in the circuit shown in Fig.4.4

Solution:

$$V(4\Omega) = \frac{24 \times 4\Omega}{2\Omega + 4\Omega + 6\Omega} = 8 \text{ v}$$

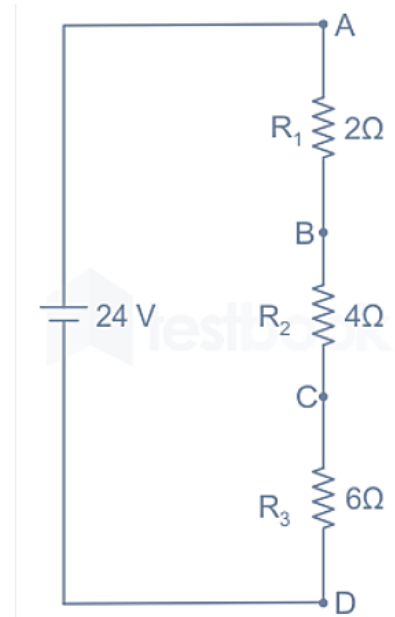


Figure. 4.4

Example 4.3: Find the current through the resistor 8Ω in the circuit shown in Fig.4.5

Solution:

The 8Ω and 4Ω resistors are in parallel, so their combined resistance is

$$8\Omega \parallel 4\Omega = 8 \times 4 / (8 + 4) = 2.667 \Omega$$

By using the voltage divider rule the voltage at (2.667Ω) is

$$V(2.667\Omega) = \frac{16 \times 2.667\Omega}{2\Omega + 2.667\Omega} = 9.143 \text{ v}$$

The voltage at 8Ω is 9.143v (parallel connected)

The current through 8Ω is

$$i(8\Omega) = \frac{9.143}{8} = 1.14 \text{ A}$$


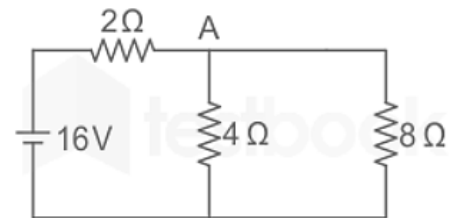


Figure. 4.5

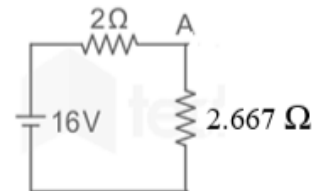

Thank You