

**D.C Voltmeter:**

A voltmeter is always connect in parallel with the element being measured, and measures the voltage between the points across which its' connected. Most d.c voltmeter employ PMMC meter with series resistor as shown. The series resistance should be much larger than the impedance of the circuit being measured, and they are usually much larger than  $R_m$ .

$$R_s = \frac{R_T - R_m}{I_m}$$

$$R_s = \frac{V_{range}}{I_m} - R_m$$


$I_m = I_{FSD}$   
 The ohm/volt sensitivity of a voltmeter  
 Is given by:

$$S_V = \frac{R_m}{V_{FSD}} = \frac{1}{I_{FSD}} = \frac{\Omega}{V} \text{ rating}$$

$$S_{Range} = \frac{R_m + R_s}{V_{Range}} = \frac{1}{I_{Range}} = \frac{\Omega}{V}$$

So the internal resistance of voltmeter or the input resistance of voltmeter is
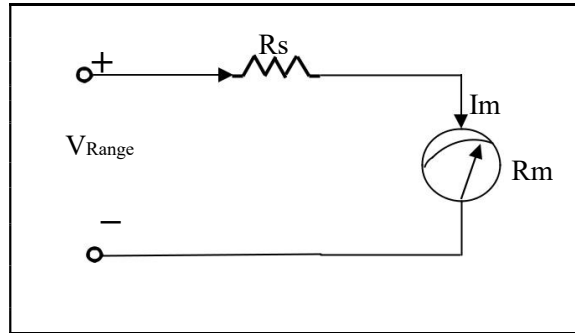
$$R_v = V_{FSD} \times \text{sensitivity}$$



**Example:**

We have a micro ammeter and we wish to adapted it so as to measure 1volt full scale, the meter has internal resistance of  $100\Omega$  and  $I_{FSD}$  of  $100\mu A$ .

**Sol.:**

$$R_s = \frac{V}{I_m} - R_m \qquad R_s = \frac{1}{0.0001} - 100 = 9900\Omega = 9.9K\Omega$$


So we connect with PMMC meter a series resistance of  $9.9K\Omega$  to convert it to voltmeter

**Extension of Voltmeter Range:**

Voltage range of d.c voltmeter can be further extended by a number of series resistance selected by a range switch; such a voltmeter is called multirange voltmeter.

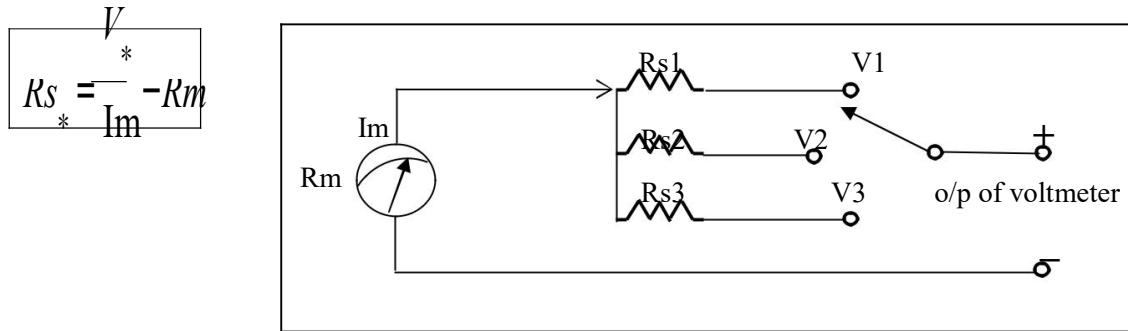**a) Direct D.c Voltmeter Method:**

In this method each series resistance of multirange voltmeter is connected in direct with PMMC meter to give the desired range.




**b) Indirect D.c Voltmeter Method:**

In this method one or more series resistances of multirange voltmeter is connected with PMMC meter to give the desired range.

$$R_{s1} = \frac{V1 - R_m}{I_m}$$

$$R_{s2} = \frac{V2 - V1}{I_m}$$

$$R_{s3} = \frac{V3 - V2}{I_m}$$

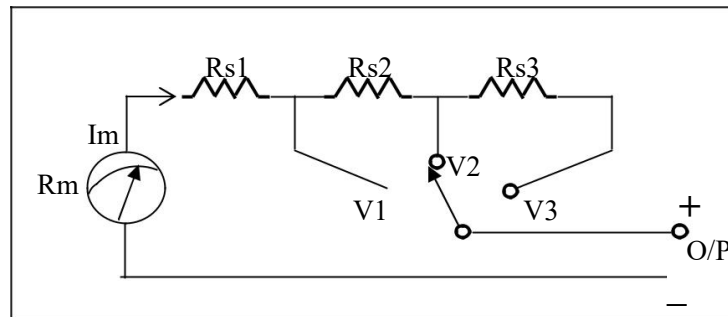

**Example (1):**

A basic d'Arsonval movement with internal resistance of 100Ω and half scale current deflection of 0.5 mA is to be converted by indirect method into a multirange d.c voltmeter with volages ranges of 10V, 50V, 250V, and 500V.

**Sol:**

$$I_{FSD} = I_{HSD} \times 2$$

$$I_{FSD} = 0.5\text{mA} \times 2 = 1\text{mA}$$

$$R_{s1} = \frac{V1 - R_m}{I_m}$$


$$R_{s1} = \frac{10}{1\text{mA}} - 100 = 9.9\text{K}\Omega$$

$$R_{s2} = \frac{V_2 - V_1}{I_m}$$

$$R_{s2} = \frac{50 - 10}{1 \times 10^{-3}} = 40K\Omega$$

$$R_{s3} = \frac{250 - 50}{1 \times 10^{-3}} = 200K\Omega$$
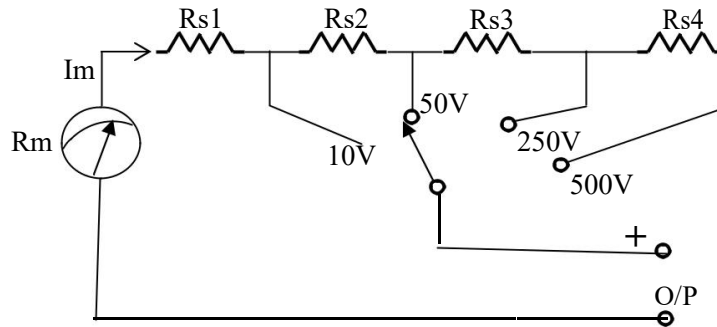
$$R_{s4} = \frac{500 - 250}{1 \times 10^{-3}} = 250K\Omega$$



**Example (2):**

Design d.c voltmeter by using direct method with d'Arsonval meter of  $100\Omega$  and full scale deflection of  $100\mu A$  to give the following ranges: 10mV, 1V, and 100V.

**Sol:**

$$R_{s*} = \frac{V}{I_m} - R_m$$

$$R_{s1} = \frac{10mV}{100\mu A} - 100 = 0\Omega$$

$$R_{s2} = \frac{1}{100 \times 10^{-6}} - 100 = 9.9K\Omega$$

$$R_{s3} = \frac{100}{100 \times 10^{-6}} - 100 = 99.9K\Omega$$

