



COLLEGE OF ENGINEERING AND TECHNOLOGIES
ALMUSTAQBAL UNIVERSITY

Electronics

CTE 207

Lecture 20

- FET Biasing -

(2023 - 2024)


Dr. Zaidoon AL-Shammari

Lecturer / Researcher

zaidoon.waleed@mustaqbal-college.edu.iq

- The p-channel JFET is constructed in exactly the same manner as the n-channel device, but with a reversal of the p and n type materials as shown in Figure below.


P - Channel Devices

 


p-Channel JFET.

- The defined current directions are reversed, as are the actual polarities for the voltages V_{GS} and V_{DS} .
- For the p-channel device, the channel will be constricted by increasing positive voltages from gate to source and the double-subscript notation for V_{DS} will result in negative voltages for V_{DS} on the characteristics of Figure below.

P - Channel Devices

 

 p-Channel JFET characteristics with $I_{DSS} = 6\text{ mA}$ and $V_P = +6\text{ V}$.



JFET symbols: (a) n-channel; (b) p-channel.

Transfer Characteristics

The relationship between I_D and V_{GS} is defined by *Shockley's equation*:

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

control variable

constants

- The squared term of the equation will result in a nonlinear relationship between I_D and V_{GS} , producing a curve that grows exponentially with decreasing magnitudes of V_{GS} .

- The transfer characteristics defined by Shockley's equation are unaffected by the network in which the device is employed.
- By using basic algebra we can obtain an equation for the resulting level of VGS for a given level of ID.

$$V_{GS} = V_P \left(1 - \sqrt{\frac{I_D}{I_{DSS}}} \right)$$

- In the Figure below two graphs are provided, with the vertical scaling in milliamperes for each graph.
- One is a plot of I_D versus V_{DS} , while the other is I_D versus V_{GS} .

IMPORTANT RELATIONSHIPS:

<i>JFET</i>		<i>BJT</i>
$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$	\Leftrightarrow	$I_C = \beta I_B$
$I_D = I_S$	\Leftrightarrow	$I_C \cong I_E$
$I_G \cong 0 \text{ A}$	\Leftrightarrow	$V_{BE} \cong 0.7 \text{ V}$


In review:

When $V_{GS} = 0 V$, $I_D = I_{DSS}$, and when $V_{GS} = V_P$, $I_D = 0 mA$.

The total device dissipation at 25°C (room temperature) is the maximum power the device can dissipate under normal operating conditions and is defined by

$$P_D = V_{DS} I_D$$

Transfer Characteristics

 

Obtaining the transfer curve from the drain characteristics.

- The general relationships that can be applied to the dc analysis of all FET amplifiers are

$$I_G \approx 0 \text{ A} \quad \text{and} \quad I_D = I_S$$

- The simplest of biasing arrangements for the n-channel JFET appears in the Figure below.
- Referred to as the fixed-bias configuration, it is one of the few FET configurations that can be solved just as directly using either a mathematical or graphical approach.

Fixed - Bias Configuration


$$I_G = 0 \text{ A} \quad \text{and} \quad V_{RG} = I_G R_G = (0 \text{ A})R_G = 0 \text{ V}$$

Applying Kirchhoff's voltage law in the clockwise direction of the indicated loop of Fig. will result in

$$-V_{GG} - V_{GS} = 0 \quad \text{and} \quad V_{GS} = -V_{GG}$$

The drain-to-source voltage of the output section can be determined by applying Kirchhoff's voltage law as follows:
 
$$+V_{DS} + I_D R_D - V_{DD} = 0 \quad \text{and} \quad V_{DS} = V_{DD} - I_D R_D$$



Network for dc analysis.

Fixed - Bias Configuration

For the configuration of Fig

$$V_S = 0$$

Using double-subscript notation:

$$V_{DS} = V_D - V_S \text{ or } V_D = V_{DS} + V_S = V_{DS} + 0V \text{ and } V_D = V_{DS}$$

In addition, $V_{GS} = V_G - V_S \text{ or } V_G = V_{GS} + V_S = V_{GS} + 0V \text{ and } V_G = V_{GS}$

Fixed - Bias Configuration

The drain-to-source voltage of the output section can be determined by applying Kirchhoff's voltage law as follows:

$$+V_{DS} + I_D R_D - V_{DD} = 0$$

and

$$V_{DS} = V_{DD} - I_D R_D$$

Recall that single-subscript voltages refer to the voltage at a point with respect to ground. For the configuration of Fig.

$$V_S = 0 \text{ V}$$

Using double-subscript notation, we have

$$V_{DS} = V_D - V_S$$

or

$$V_D = V_{DS} + V_S = V_{DS} + 0 \text{ V}$$

and

$$V_D = V_{DS}$$

In addition,

$$V_{GS} = V_G - V_S$$

or

$$V_G = V_{GS} + V_S = V_{GS} + 0 \text{ V}$$

and

$$V_G = V_{GS}$$

