



COLLEGE OF ENGINEERING AND TECHNOLOGIES
ALMUSTAQBAL UNIVERSITY

Electronics

CTE 207

Lecture 16

- DC Biasing of BJT -

(2023 - 2024)

Dr. Zaidoon AL-Shammari


Lecturer / Researcher

zaidoon.waleed@mustaqbal-college.edu.iq

- The fixed-bias circuit of Figure below provides a relatively straight forward and simple introduction to transistor DC bias analysis.
- Even though the network employs an NPN transistor, the equations and calculations apply equally well to a PNP transistor configuration merely by changing all current directions and voltage polarities.

- For the DC analysis the network can be isolated from the indicated AC levels by replacing the capacitors with an open circuit equivalent.
- In addition, the DC supply VCC can be separated into two supplies (for analysis purposes only) as shown in Figure below.
- The separation is valid, as we note in Figure below that VCC is connected directly to RB and RC just as in Figure below.

Fixed Bias Circuit

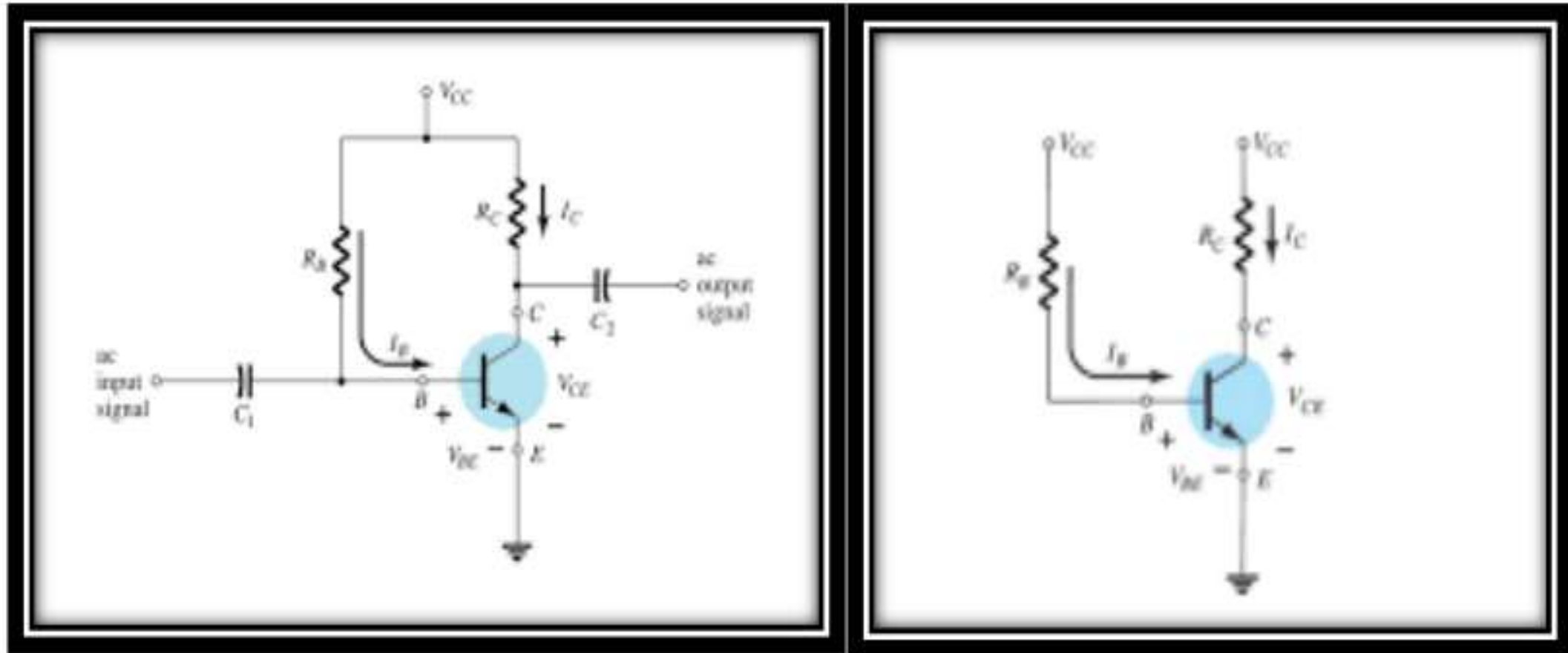

- The analysis or design of a transistor amplifier requires a knowledge of both the DC and AC response of the system.
- The analysis or design of any electronic amplifier therefore has two components: the DC portion and the AC portion.
- Fortunately, the superposition theorem is applicable and the investigation of the DC conditions can be separated from the AC response.



- To analysis any network in following these rules are true:

$$V_{BE} \cong 0.7 \text{ V}$$

$$I_E = (\beta + 1)I_B \cong I_C$$

$$I_C = \beta I_B$$

Base - Emitter loop

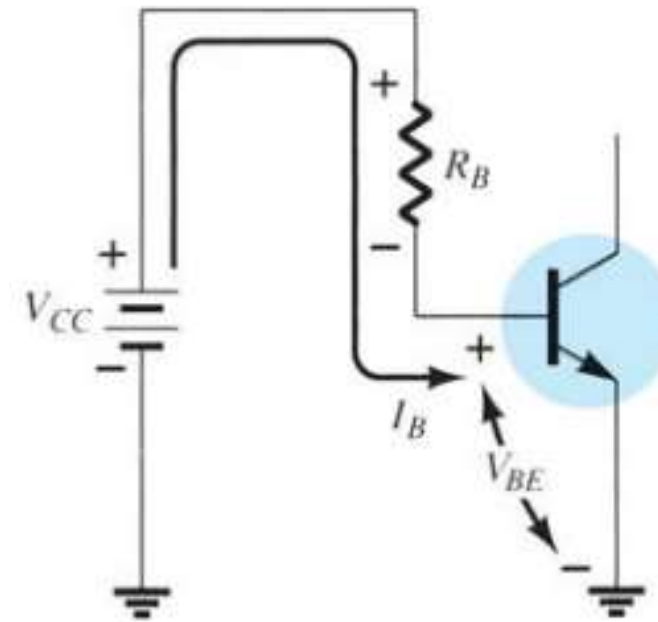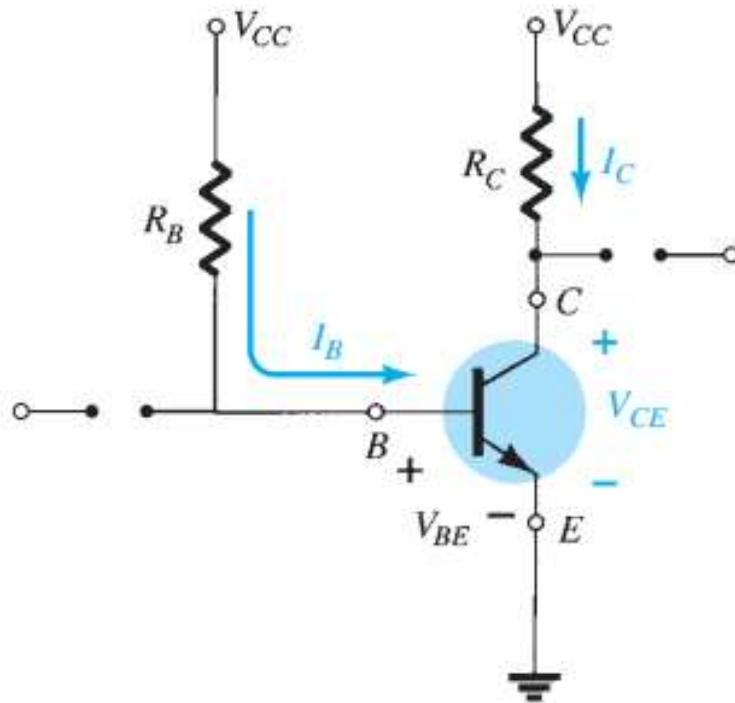



Consider first the base–emitter circuit loop of Fig. 4.4. Writing Kirchhoff’s voltage equation in the clockwise direction for the loop, we obtain

$$+V_{CC} - I_B R_B - V_{BE} = 0$$

Note the polarity of the voltage drop across R_B as established by the indicated direction of I_B . Solving the equation for the current I_B results in the following:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

Collector - Emitter Loop

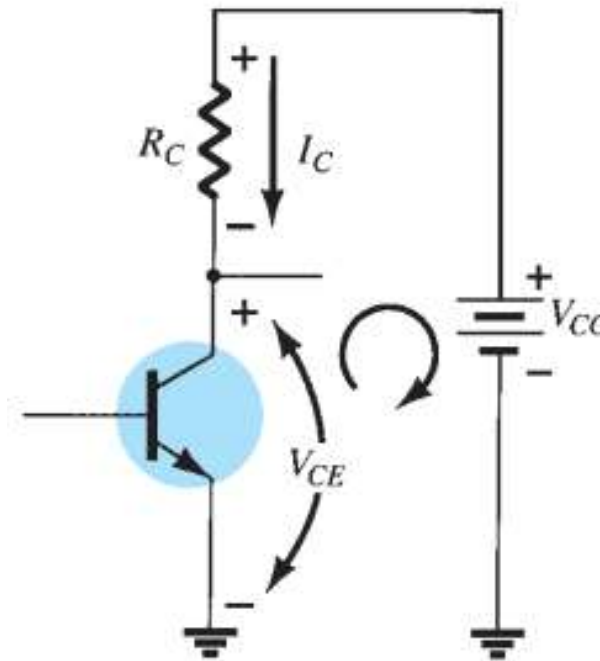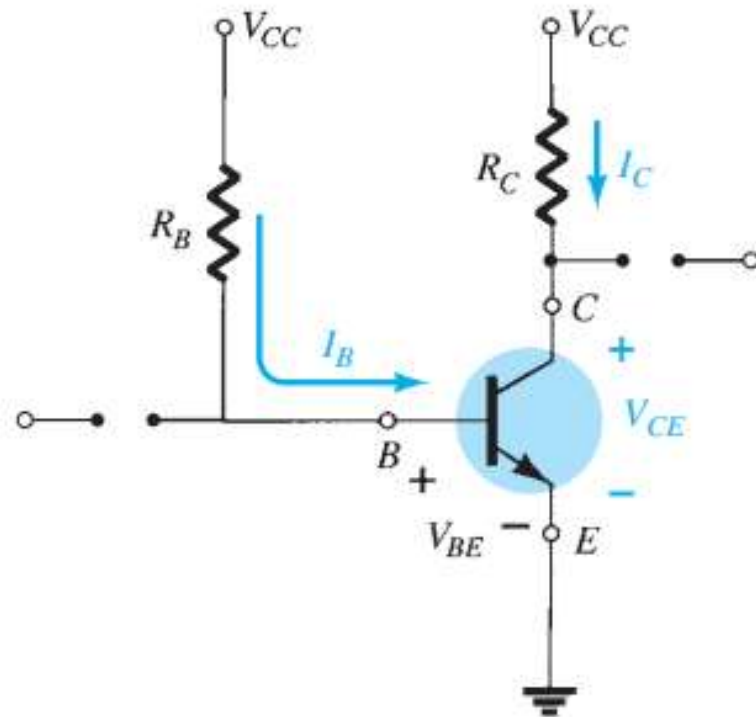

The collector–emitter section of the network appears in Fig. 4.5 with the indicated direction of current I_C and the resulting polarity across R_C . The magnitude of the collector current is related directly to I_B through

$$I_C = \beta I_B$$

It is interesting to note that because the base current is controlled by the level of R_B and I_C is related to I_B by a constant β , the magnitude of I_C is not a function of the resistance R_C . Changing R_C to any level will not affect the level of I_B or I_C as long as we remain in the active region of the device. However, as we shall see, the level of R_C will determine the magnitude of V_{CE} , which is an important parameter.

Applying Kirchhoff's voltage law in the clockwise direction around the indicated closed loop of Fig. 4.5 results in the following:

$$V_{CE} + I_C R_C - V_{CC} = 0$$

and

$$V_{CE} = V_{CC} - I_C R_C$$

which states that the voltage across the collector-emitter region of a transistor in the fixed-bias configuration is the supply voltage less the drop across R_C .

As a brief review of single- and double-subscript notation recall that

$$V_{CE} = V_C - V_E$$

Collector - Emitter Loop

where V_{CE} is the voltage from collector to emitter and V_C and V_E are the voltages from collector and emitter to ground, respectively. *In this case*, since $V_E = 0$ V, we have

$$V_{CE} = V_C$$

In addition, because

$$V_{BE} = V_B - V_E$$


and $V_E = 0$ V, then

$$V_{BE} = V_B$$

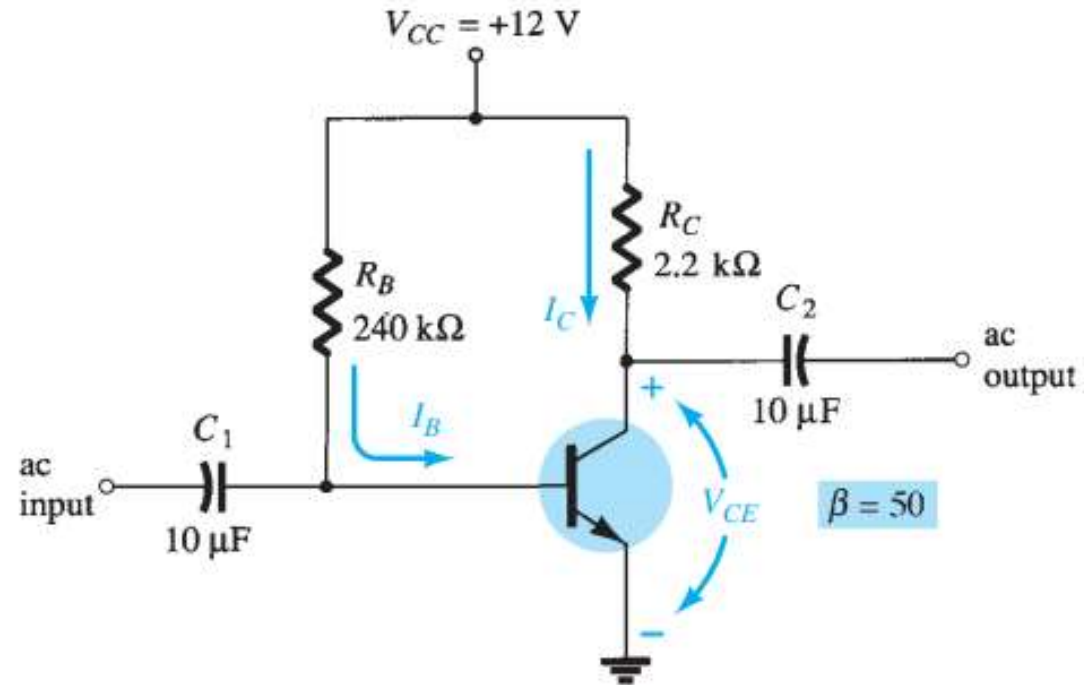Example

Determine the following for the fixed-bias configuration of Figure below

- I_{BQ} and I_{CQ} .
- V_{CEQ} .
- V_B and V_C .
- V_{BC} .



a. Eq. (4.4):
$$I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 \text{ V} - 0.7 \text{ V}}{240 \text{ k}\Omega} = \mathbf{47.08 \mu\text{A}}$$

Eq. (4.5):
$$I_{CQ} = \beta I_{BQ} = (50)(47.08 \mu\text{A}) = \mathbf{2.35 \text{ mA}}$$

b. Eq. (4.6):
$$\begin{aligned} V_{CEQ} &= V_{CC} - I_C R_C \\ &= 12 \text{ V} - (2.35 \text{ mA})(2.2 \text{ k}\Omega) \\ &= \mathbf{6.83 \text{ V}} \end{aligned}$$

c.
$$\begin{aligned} V_B &= V_{BE} = \mathbf{0.7 \text{ V}} \\ V_C &= V_{CE} = \mathbf{6.83 \text{ V}} \end{aligned}$$

d. Using double-subscript notation yields

$$\begin{aligned} V_{BC} &= V_B - V_C = 0.7 \text{ V} - 6.83 \text{ V} \\ &= \mathbf{-6.13 \text{ V}} \end{aligned}$$

