



COLLEGE OF ENGINEERING AND TECHNOLOGIES
ALMUSTAQBAL UNIVERSITY

Electronics

CTE 207

Lecture 15

**- Bipolar Junction Transistors (BJT) II -
(2023 - 2024)**

Dr. Zaidoon AL-Shammari





Lecturer / Researcher

zaidoon.waleed@mustaqbal-college.edu.iq

- The transistor is a three-layer semiconductor device consisting of either two n- and one p-type layers of material or two p- and one n-type layers of material.
- The former is called an npn transistor, while the latter is called a pnp transistor.
- In Fig. below both biasing potentials have been applied to a pnp transistor, with the resulting majority- and minority-carrier flow indicated.



- The most frequently encountered transistor configuration appears in Figure below for the pnp and npn transistors.
- It is called the common emitter configuration since the emitter is common or reference to both the input and output terminals (in this case common to both the base and collector terminals).

Common-Emitter Configuration

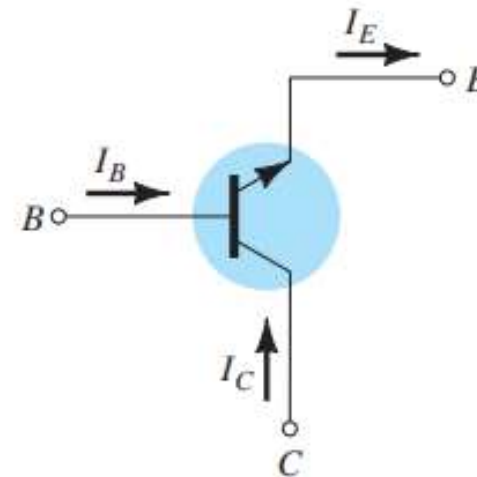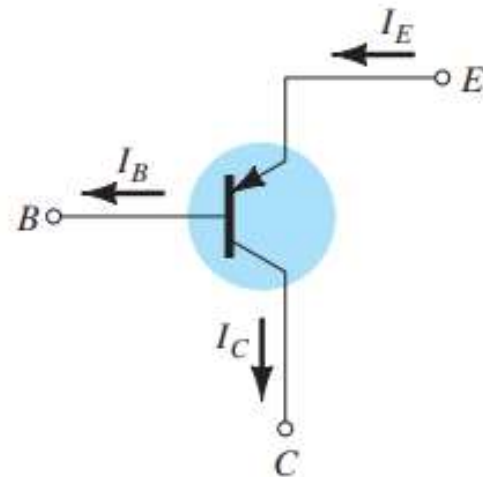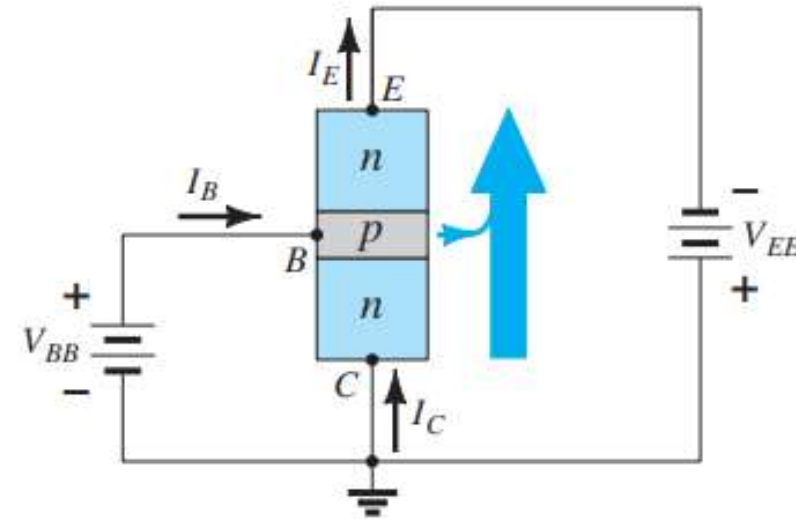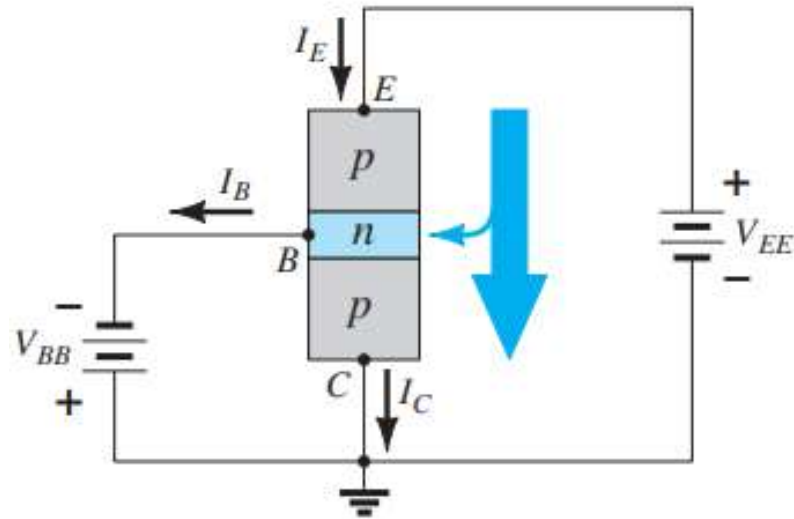

- For the common-emitter configuration, the output characteristics are a plot of the output current (I_C) versus output voltage (V_{CE}) for a range of values of input current (I_B).
- The input characteristics are a plot of the input current (I_B) versus the input voltage (V_{BE}) for a range of values of output voltage (V_{CE}).

Common-Emitter Configuration

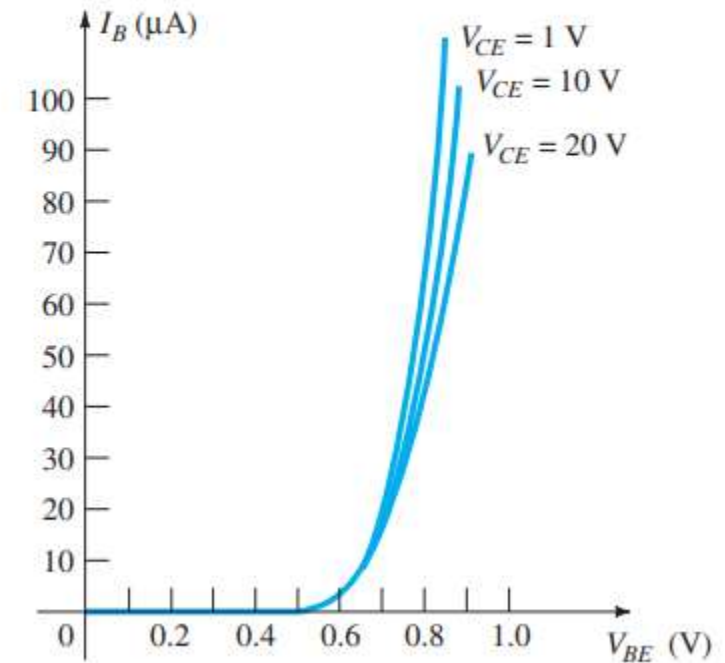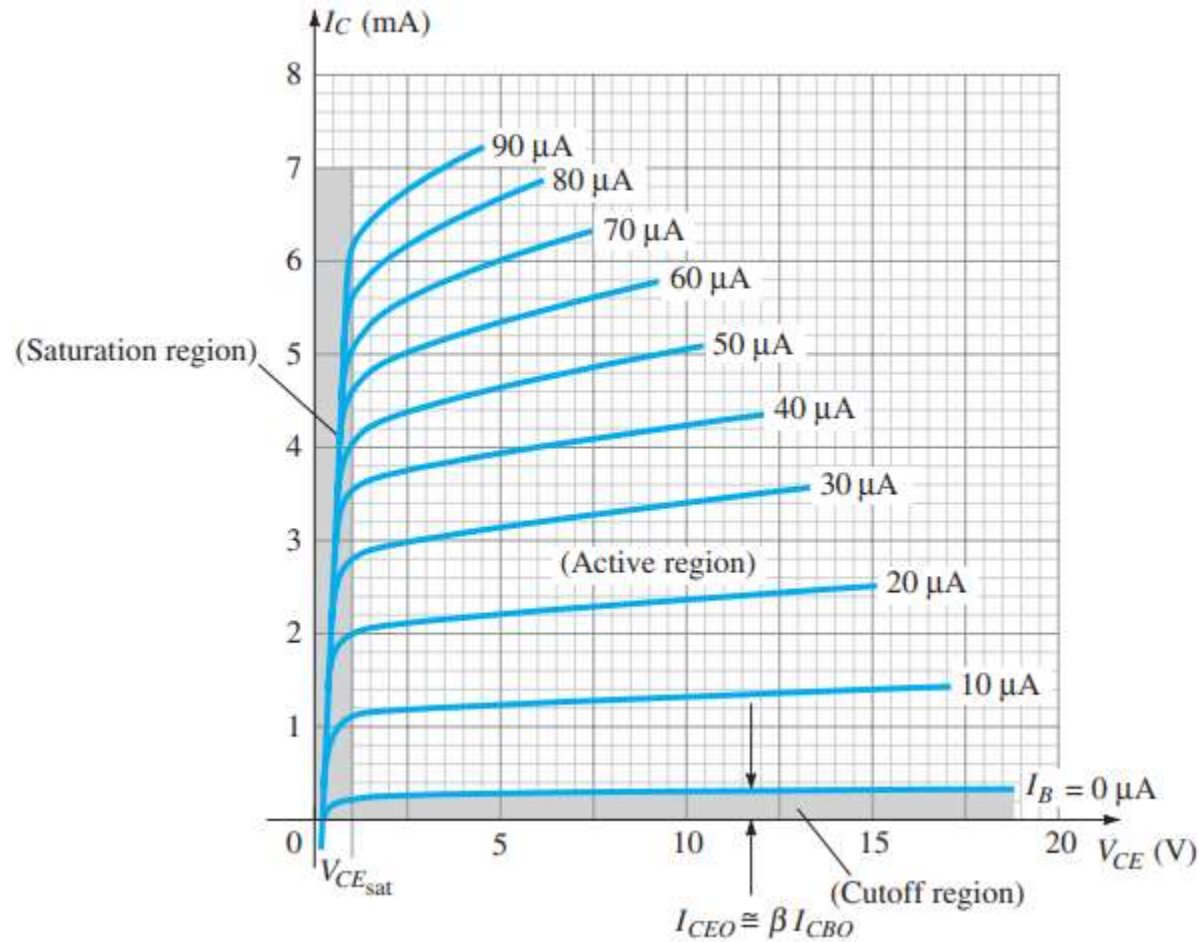

Common-Emitter Configuration

In the dc mode the levels of I_C and I_B are related by a quantity called beta and defined by the following equation:


$$\beta_{dc} = \frac{I_C}{I_B}$$

For practical devices the level of typically ranges from about 50 to over 400, with most in the midrange.

A relationship can be developed between β and α using the basic relationships introduced thus far. Using $\beta = I_C/I_B$ we have $I_B = I_C/\beta$, and from $\alpha = I_C/I_E$ we have

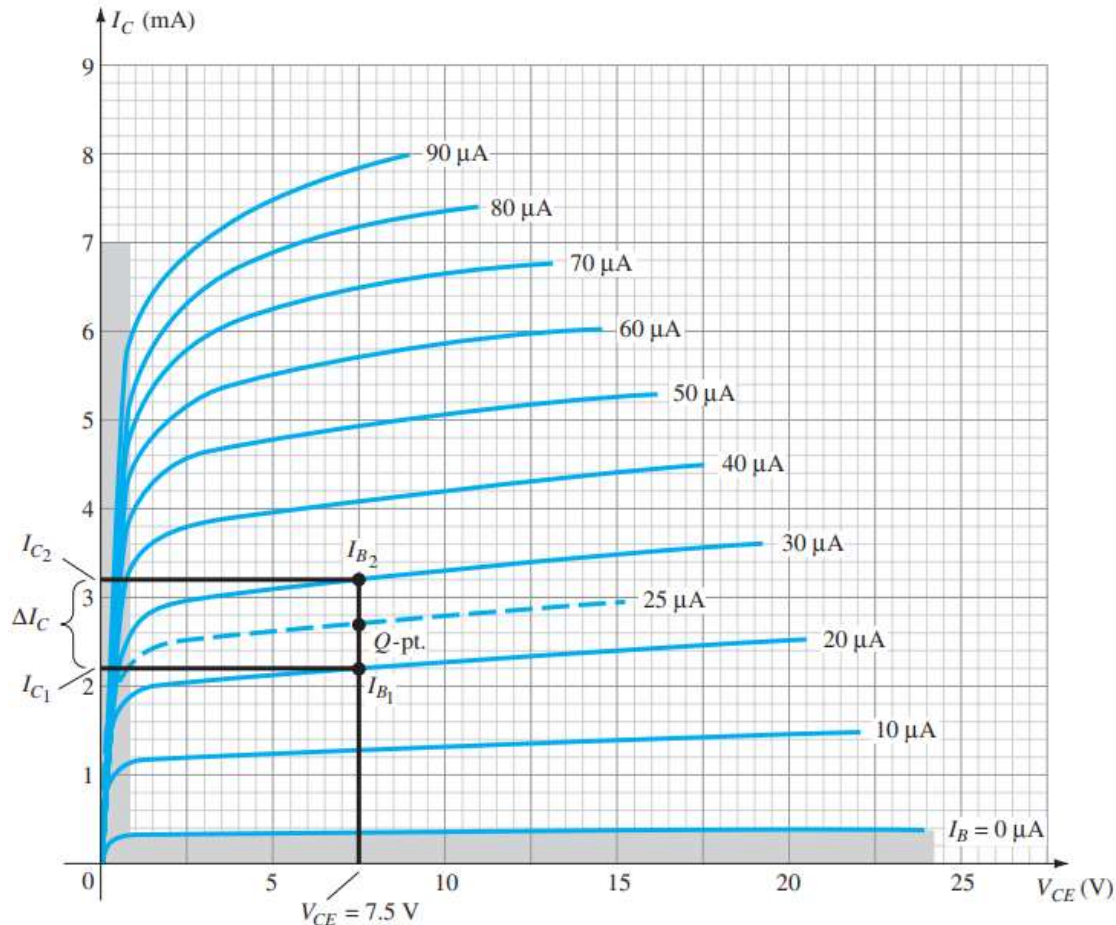Example

Determining β_{ac} and β_{dc} from the collector characteristics.




$$\beta_{ac} = \left. \frac{\Delta I_C}{\Delta I_B} \right|_{V_{CE}=\text{constant}}$$

$$\begin{aligned} \beta_{ac} &= \left. \frac{\Delta I_C}{\Delta I_B} \right|_{V_{CE}=\text{constant}} = \frac{I_{C2} - I_{C1}}{I_{B2} - I_{B1}} \\ &= \frac{3.2 \text{ mA} - 2.2 \text{ mA}}{30 \mu\text{A} - 20 \mu\text{A}} = \frac{1 \text{ mA}}{10 \mu\text{A}} \\ &= \mathbf{100} \end{aligned}$$

$$\beta_{dc} = \frac{I_C}{I_B} = \frac{2.7 \text{ mA}}{25 \mu\text{A}} = \mathbf{108}$$

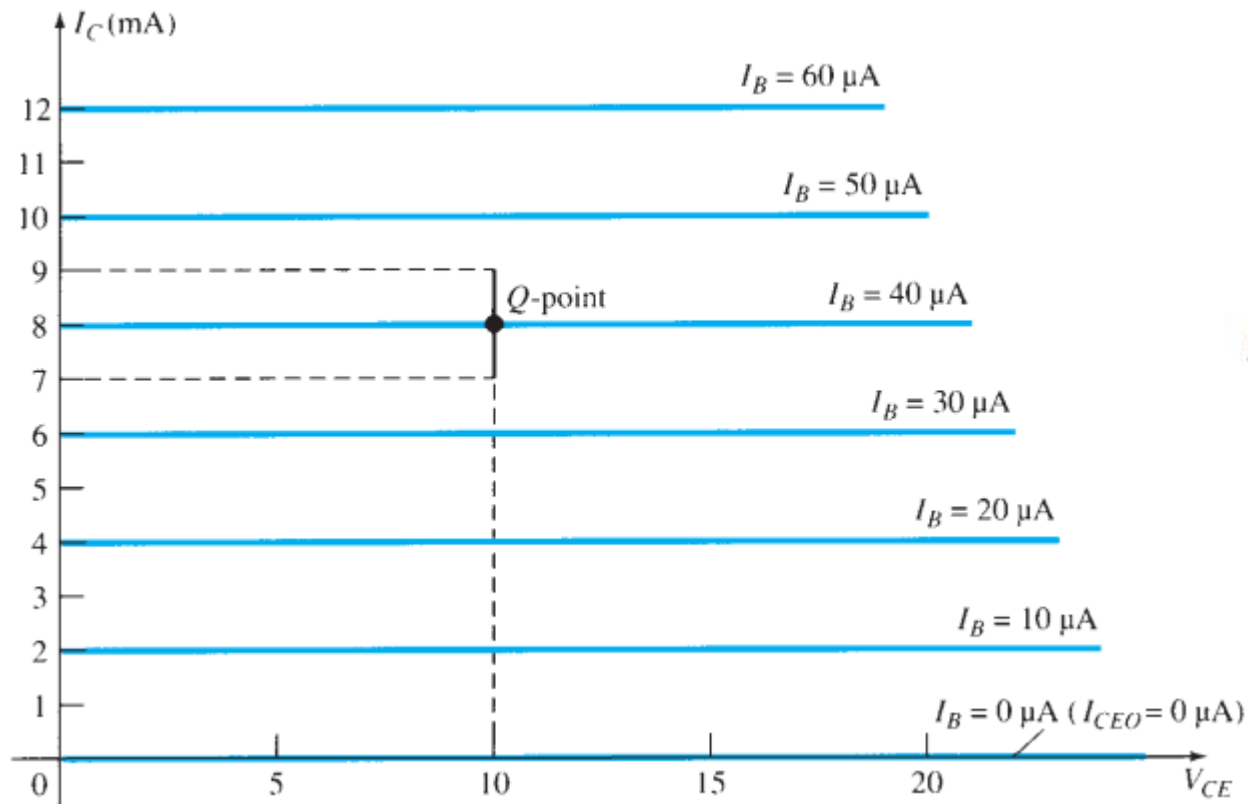Example

Determining β_{ac} and β_{dc} from the collector characteristics.



$$\beta_{ac} = \left. \frac{\Delta I_C}{\Delta I_B} \right|_{V_{CE} = \text{constant}}$$

$$\beta_{ac} = \left. \frac{\Delta I_C}{\Delta I_B} \right|_{V_{CE} = \text{constant}} = \frac{9 \text{ mA} - 7 \text{ mA}}{45 \mu\text{A} - 35 \mu\text{A}} = \frac{2 \text{ mA}}{10 \mu\text{A}} = 200$$

$$\beta_{dc} = \frac{I_C}{I_B} = \frac{8 \text{ mA}}{40 \mu\text{A}} = 200$$

Common-Emitter Configuration

$I_E = I_C/\alpha$. Substituting into

we have

$$I_E = I_C + I_B$$

$$\frac{I_C}{\alpha} = I_C + \frac{I_C}{\beta}$$

and dividing both sides of the equation by I_C will result in

$$\frac{1}{\alpha} = 1 + \frac{1}{\beta}$$

or

$$\beta = \alpha\beta + \alpha = (\beta + 1)\alpha$$

so that

$$\alpha = \frac{\beta}{\beta + 1}$$

or

$$\beta = \frac{\alpha}{1 - \alpha}$$

Common-Emitter Configuration

and since

$$I_C = \beta I_B$$

$$\begin{aligned} I_E &= I_C + I_B \\ &= \beta I_B + I_B \end{aligned}$$

we have

$$I_E = (\beta + 1)I_B$$

- The common-collector configuration is used primarily for impedance-matching purposes since it has a high input impedance and low output impedance, opposite to that of the common-base and common-emitter configurations.

- For all practical purposes, the output characteristics of the common collector configuration are the same as for the common-emitter configuration.
- For the common-collector configuration the output characteristics are a plot of I_E versus V_{CE} for a range of values of I_B .
- The input current, therefore, is the same for both the common-emitter and common-collector characteristics.

Common-Collector Configuration

