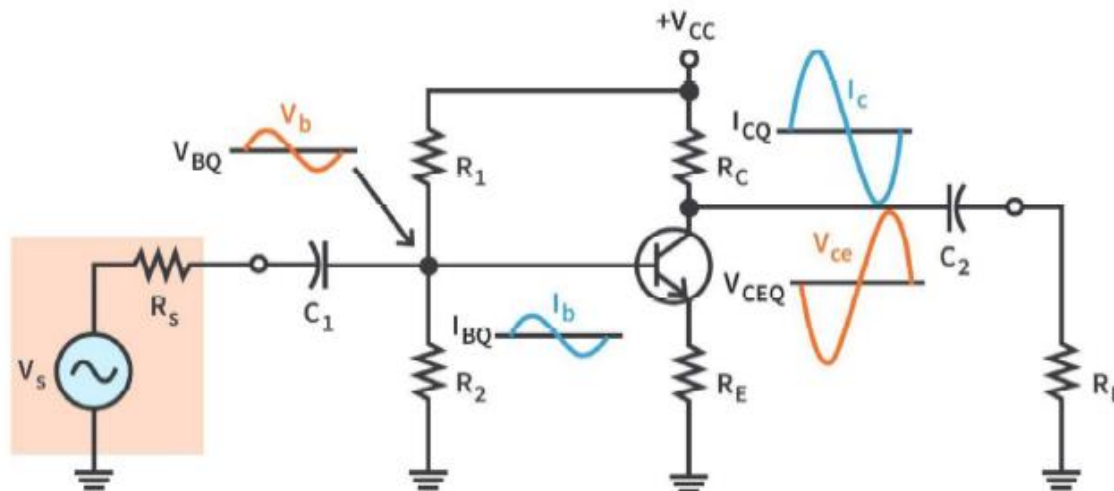


## Small-Signal Amplifier




The basic construction, appearance, and characteristics of the transistor were introduced in Chapter 3. We now begin to examine the ac response of the BJT amplifier by reviewing the *models* most frequently used to represent the transistor in the sinusoidal ac domain.

One of our first concerns in the sinusoidal ac analysis of transistor networks is the magnitude of the input signal. It will determine whether *small-signal* or *large-signal* techniques should be applied. There is no set dividing line between the two, but the application—and the magnitude of the variables of interest relative to the scales of the device characteristics will usually make it quite clear which method is appropriate. The small-signal technique is introduced in this Lecture.

There are three models commonly used in the small-signal ac analysis of transistor networks: the ***re* model**, the **hybrid *p* model**, and the **hybrid equivalent model**.


the ac equivalent of a transistor network is obtained by:

1. Setting all dc sources to zero and replacing them by a short-circuit equivalent
2. Replacing all capacitors by a short-circuit equivalent
3. Removing all elements bypassed by the short-circuit equivalents introduced by steps 1 and 2
4. Redrawing the network in a more convenient and logical form

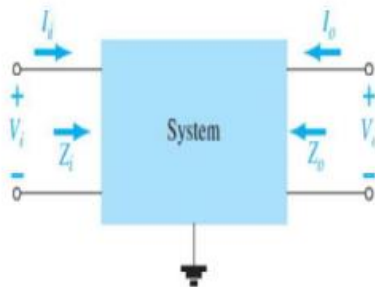


**FIG. 5.5**

*Defining the important parameters of any system.*

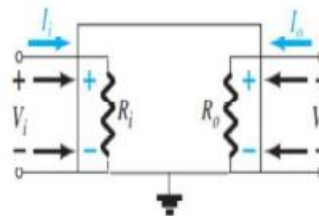

**FIG. 5.6**

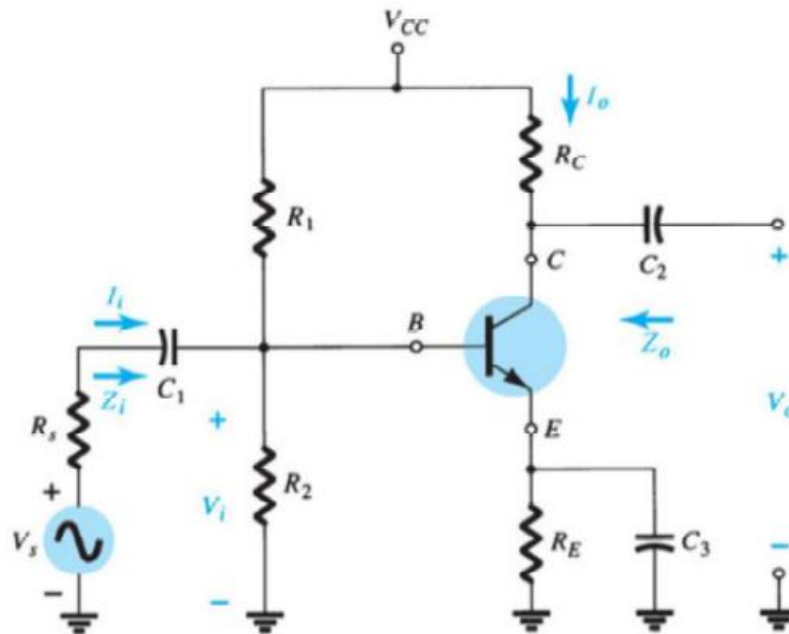
*Demonstrating the reason for the defined directions and polarities.*



## re model:


The re model for the CE, CB, and CC BJT transistor configurations will now be introduced with a short description of why each is a good approximation to the actual behavior of a BJT transistor.

## Common-Emitter Configuration

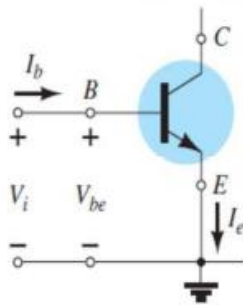

**FIG. 5.8**

*Finding the input equivalent circuit for a BJT transistor.*

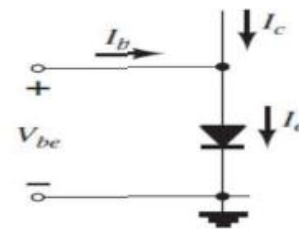

**FIG. 5.10**

*Equivalent circuit for the input side of a BJT transistor.*

Now, for the input side:

$$Z_i = \frac{V_i}{I_b} = \frac{V_{be}}{I_b}$$


Solving for  $V_{be}$ :

$$\begin{aligned}
 V_{be} &= I_e r_e = (I_c + I_b) r_e = (\beta I_b + I_b) r_e \\
 &= (\beta + 1) I_b r_e
 \end{aligned}$$

and

$$Z_i = \frac{V_{be}}{I_b} = \frac{(\beta + 1) I_b r_e}{I_b}$$

$$Z_i = (\beta + 1) r_e \cong \beta r_e$$

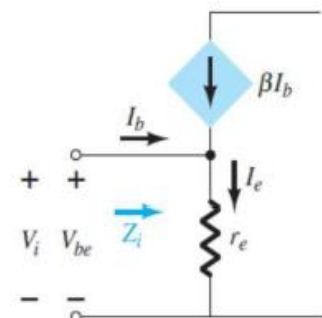


**FIG. 5.13**

*Defining the level of  $Z_i$ .*

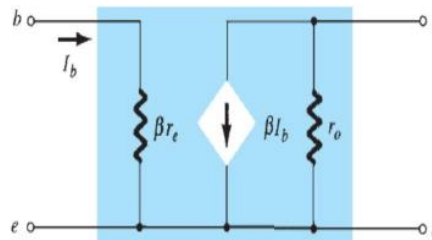
### output impedance

$$r_o \cong \frac{V_A}{I_{CQ}}$$


$$r_o = \frac{\Delta V_{CE}}{\Delta I_C}$$



### Common-Base Configuration

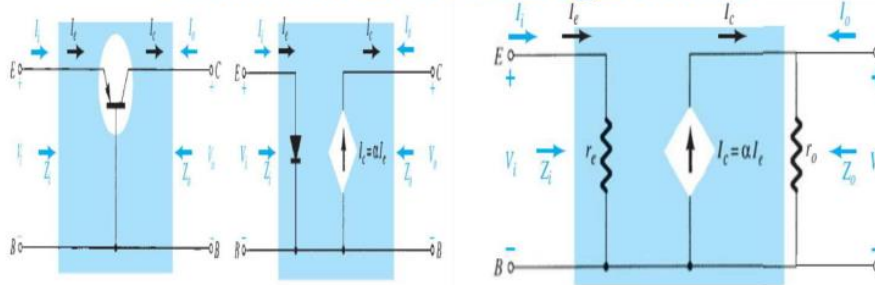


### COMMON-EMITTER FIXED-BIAS CONFIGURATION

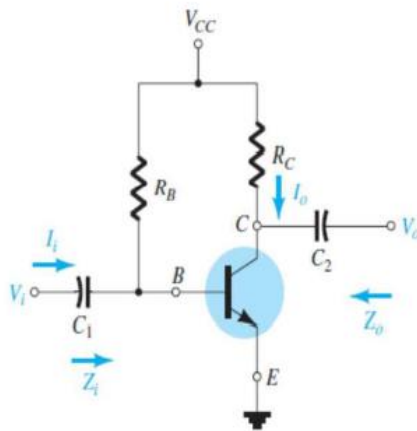

**FIG. 5.20**


Common-emitter fixed-bias configuration.

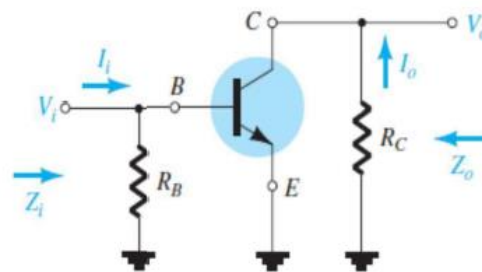

**FIG. 5.21**

Network of Fig. 5.20 following the removal of the effects of  $V_{CC}$ ,  $C_1$ , and  $C_2$ .

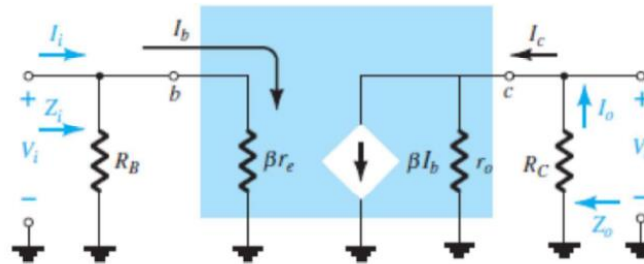The equivalent network of common-emitter fixed bias can be redrawn as the following



**Z<sub>i</sub>** Figure 5.22 clearly shows that

$$Z_i = R_B \parallel \beta r_e \quad \text{ohms} \quad (5.5)$$

For the majority of situations  $R_B$  is greater than  $\beta r_e$  by more than a factor of 10 (recall from the analysis of parallel elements that the total resistance of two parallel resistors is always less than the smallest and very close to the smallest if one is much larger than the other), permitting the following approximation:


$$Z_i \cong \beta r_e \quad R_B \geq 10\beta r_e \quad \text{ohms} \quad (5.6)$$

**Z<sub>o</sub>** Recall that the output impedance of any system is defined as the impedance  $Z_o$  determined when  $V_i = 0$ . For Fig. 5.22, when  $V_i = 0$ ,  $I_i = I_b = 0$ , resulting in an open-circuit equivalence for the current source. The result is the configuration of Fig. 5.23. We have

$$Z_o = R_C \parallel r_o \quad \text{ohms} \quad (5.7)$$

If  $r_o \geq 10R_C$ , the approximation  $R_C \parallel r_o \cong R_C$  is frequently applied, and

$$Z_o \cong R_C \quad r_o \geq 10R_C \quad (5.8)$$

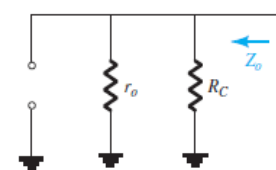

**FIG. 5.23**  
Determining  $Z_o$  for the network of Fig. 5.22.

**A<sub>v</sub>** The resistors  $r_o$  and  $R_C$  are in parallel, and

$$V_o = -\beta I_b (R_C \parallel r_o)$$

but

$$I_b = \frac{V_i}{\beta r_e}$$

so that

$$V_o = -\beta \left( \frac{V_i}{\beta r_e} \right) (R_C \parallel r_o)$$

and

$$A_v = \frac{V_o}{V_i} = -\frac{(R_C \parallel r_o)}{r_e} \quad (5.9)$$


If  $r_o \geq 10R_C$ , so that the effect of  $r_o$  can be ignored,

$$A_v = -\frac{R_C}{r_e} \quad r_o \geq 10R_C \quad (5.10)$$

Note the explicit absence of  $\beta$  in Eqs. (5.9) and (5.10), although we recognize that  $\beta$  must be utilized to determine  $r_e$ .

**EXAMPLE 5.1** For the network of Fig. 5.25:

- Determine  $r_e$ .
- Find  $Z_i$  (with  $r_o = \infty \Omega$ ).
- Calculate  $Z_o$  (with  $r_o = \infty \Omega$ ).
- Determine  $A_v$  (with  $r_o = \infty \Omega$ ).
- Repeat parts (c) and (d) including  $r_o = 50 \text{ k}\Omega$  in all calculations and compare results.

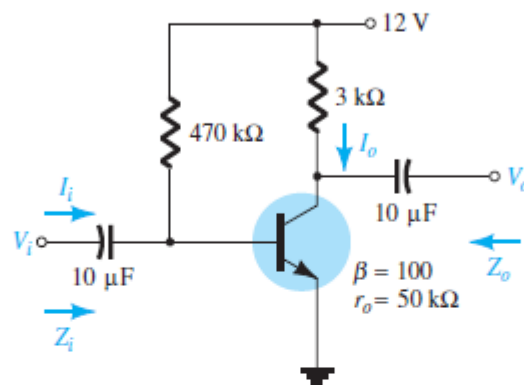

**FIG. 5.25**  
Example 5.1.

**Solution:**

- a. DC analysis:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 \text{ V} - 0.7 \text{ V}}{470 \text{ k}\Omega} = 24.04 \mu\text{A}$$

$$I_E = (\beta + 1)I_B = (101)(24.04 \mu\text{A}) = 2.428 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{2.428 \text{ mA}} = 10.71 \Omega$$

- b.  $\beta r_e = (100)(10.71 \Omega) = 1.071 \text{ k}\Omega$

$$Z_i = R_B \parallel \beta r_e = 470 \text{ k}\Omega \parallel 1.071 \text{ k}\Omega = 1.07 \text{ k}\Omega$$

- c.  $Z_o = R_C = 3 \text{ k}\Omega$


d.  $A_v = -\frac{R_C}{r_e} = -\frac{3 \text{ k}\Omega}{10.71 \Omega} = -280.11$

e.  $Z_o = r_o \parallel R_C = 50 \text{ k}\Omega \parallel 3 \text{ k}\Omega = 2.83 \text{ k}\Omega$  vs.  $3 \text{ k}\Omega$

$$A_v = -\frac{r_o \parallel R_C}{r_e} = \frac{2.83 \text{ k}\Omega}{10.71 \Omega} = -264.24$$
 vs.  $-280.11$



**VOLTAGE-DIVIDER BIAS**

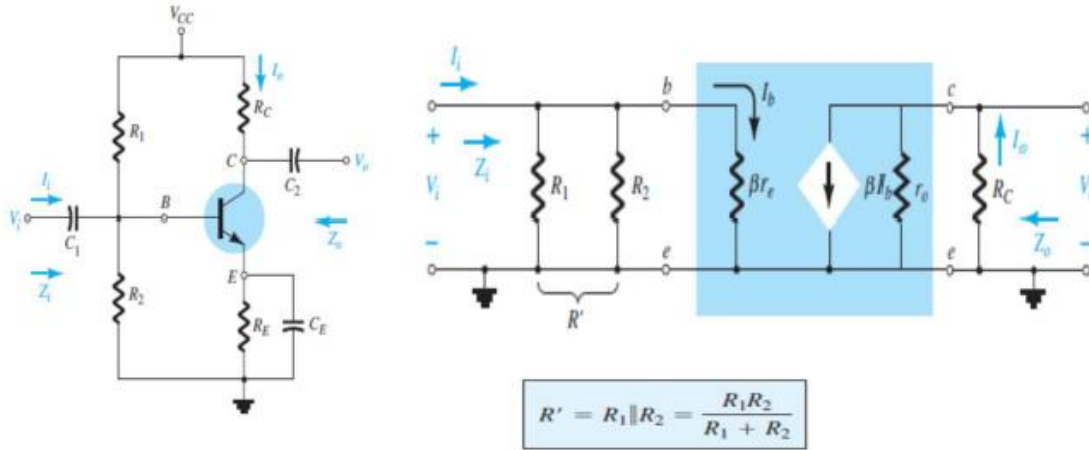

**Input impedance**

$$R' = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

$$Z_i = R' \parallel \beta r_e$$

17

**Zo From Fig below with Vi set to 0 V, resulting in Ib = 0 mA and βIb = 0 mA**

$$Z_o = R_C \parallel r_o \tag{5.13}$$

If  $r_o \geq 10R_C$ ,

$$Z_o \cong R_C \quad r_o \geq 10R_C \tag{5.14}$$

**Av** Because  $R_C$  and  $r_o$  are in parallel,

$$V_o = -(\beta I_b)(R_C \parallel r_o)$$

and

$$I_b = \frac{V_i}{\beta r_e}$$

so that

$$V_o = -\beta \left( \frac{V_i}{\beta r_e} \right) (R_C \parallel r_o)$$

and

$$A_v = \frac{V_o}{V_i} = \frac{-R_C \parallel r_o}{r_e} \tag{5.15}$$


which you will note is an exact duplicate of the equation obtained for the fixed-bias configuration.

For  $r_o \geq 10R_C$ ,

$$A_v = \frac{V_o}{V_i} \cong -\frac{R_C}{r_e} \quad r_o \geq 10R_C \tag{5.16}$$

**EXAMPLE 5.2** For the network of Fig. 5.28, determine:

- a.  $r_e$ .
- b.  $Z_i$ .
- c.  $Z_o$  ( $r_o = \infty \Omega$ ).
- d.  $A_v$  ( $r_o = \infty \Omega$ ).
- e. The parameters of parts (b) through (d) if  $r_o = 50 \text{ k}\Omega$  and compare results.

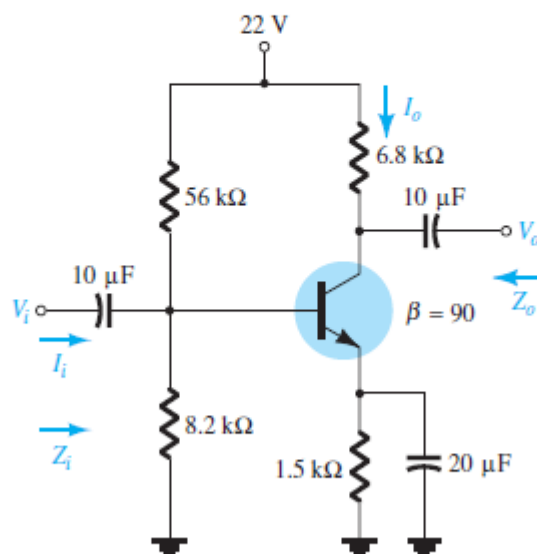

**FIG. 5.28**  
Example 5.2.

**Solution:**

a. DC: Testing  $\beta R_E > 10R_2$ ,

$$(90)(1.5 \text{ k}\Omega) > 10(8.2 \text{ k}\Omega)$$

$$135 \text{ k}\Omega > 82 \text{ k}\Omega \text{ (satisfied)}$$

Using the approximate approach, we obtain

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{(8.2 \text{ k}\Omega)(22 \text{ V})}{56 \text{ k}\Omega + 8.2 \text{ k}\Omega} = 2.81 \text{ V}$$

$$V_E = V_B - V_{BE} = 2.81 \text{ V} - 0.7 \text{ V} = 2.11 \text{ V}$$

$$I_E = \frac{V_E}{R_E} = \frac{2.11 \text{ V}}{1.5 \text{ k}\Omega} = 1.41 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{1.41 \text{ mA}} = 18.44 \Omega$$





Al-Mustaqbal University  
College of Engineering and Technologies  
Medical Instrumentation Technique Engineering Department  
Class: 2<sup>nd</sup>  
Subject: Electronic Circuits  
Lecturer: Dr. Rami Qays Malik  
Lecture: 11- Small-Signal Amplifier



b.  $R' = R_1 \parallel R_2 = (56 \text{ k}\Omega) \parallel (8.2 \text{ k}\Omega) = 7.15 \text{ k}\Omega$   
 $Z_i = R' \parallel \beta r_e = 7.15 \text{ k}\Omega \parallel (90)(18.44 \text{ }\Omega) = 7.15 \text{ k}\Omega \parallel 1.66 \text{ k}\Omega$   
 $= 1.35 \text{ k}\Omega$

c.  $Z_o = R_C = 6.8 \text{ k}\Omega$

d.  $A_v = -\frac{R_C}{r_e} = -\frac{6.8 \text{ k}\Omega}{18.44 \text{ }\Omega} = -368.76$

e.  $Z_i = 1.35 \text{ k}\Omega$   
 $Z_o = R_C \parallel r_o = 6.8 \text{ k}\Omega \parallel 50 \text{ k}\Omega = 5.98 \text{ k}\Omega$  vs.  $6.8 \text{ k}\Omega$   
 $A_v = -\frac{R_C \parallel r_o}{r_e} = -\frac{5.98 \text{ k}\Omega}{18.44 \text{ }\Omega} = -324.3$  vs.  $-368.76$

There was a measurable difference in the results for  $Z_o$  and  $A_v$ , because the condition  $r_o \geq 10R_C$  was *not* satisfied.