

# *Electrical Engineering Fundamentals*

*First class*

**AC**

**Lecture 2 & 3**

*Dr. Saad Mutashar Abbas*

*2024-2025*

## EFFECTIVE (RMS) VALUES

The effective value (or the rms value) of an alternating waveform is given by the steady (dc) current which when flowing through a given circuit, for a given time produces the same heat produced by the alternating current when flowing the same circuit for the same time.

Effective value of the **sinusoidal** is:

$$I_{\text{eff}} = 0.707I_m$$


$$E_{\text{eff}} = 0.707E_m$$

The effective value of any quantity plotted as a function of time can be found by using the following equation:

$$I_{\text{eff}} = \sqrt{\frac{\int_0^T i^2(t) dt}{T}}$$

$$I_{\text{eff}} = \sqrt{\frac{\text{area}(i^2(t))}{T}}$$

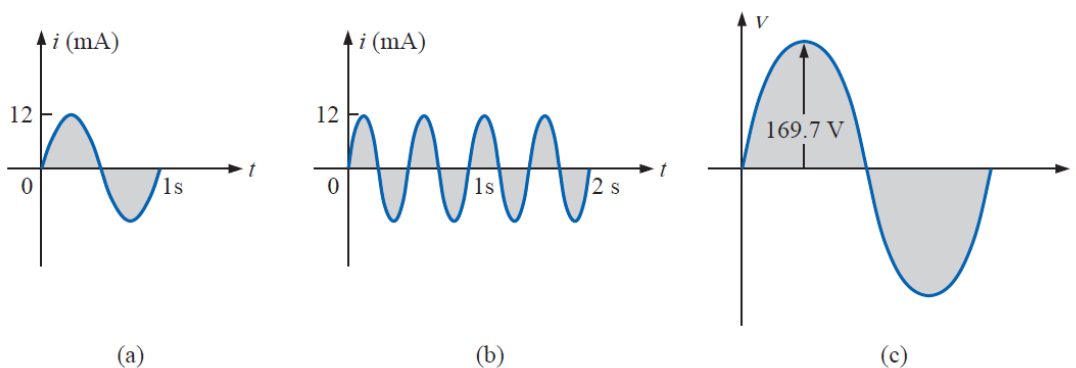**EXAMPLE:** Find the **rms** values of the sinusoidal waveform




**Solution:**

For part (a),  $I_{\text{rms}} = 0.707(12 * 10^{-3} \text{ A}) = \mathbf{8.484 \text{ mA}}$ . For part (b), again  $I_{\text{rms}} = \mathbf{8.484 \text{ mA}}$ . Note that frequency did not change the effective value

in (b) above compared to (a). For part (c),  $V_{\text{rms}} = 0.707(169.73 \text{ V}) \cong 120 \text{ V}$ .

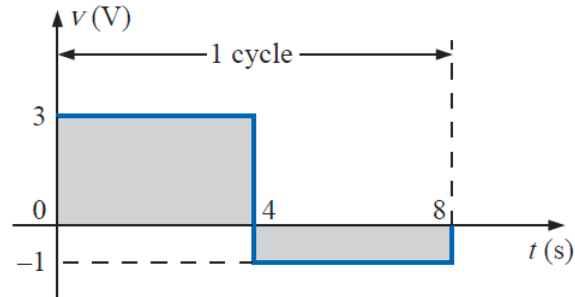
**EXAMPLE:** Find the effective or rms value of the waveform



**Solution:**

$$V_{\text{rms}} = \sqrt{\frac{(9)(4) + (1)(4)}{8}} = \sqrt{\frac{40}{8}} = 2.236 \text{ V}$$

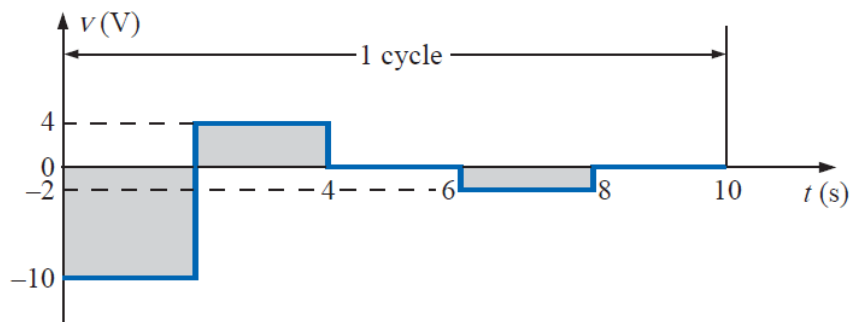**EXAMPLE:** Calculate the rms value of the voltage




**Solution:**

$$V_{\text{rms}} = \sqrt{\frac{(100)(2) + (16)(2) + (4)(2)}{10}} = \sqrt{\frac{240}{10}}$$

$$= 4.899 \text{ V}$$

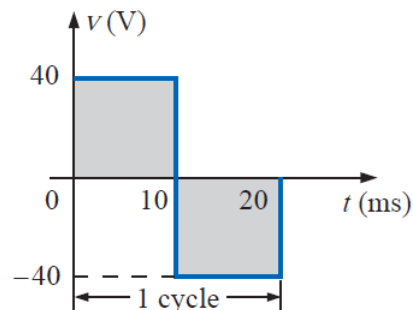**EXAMPLE:** Determine the average and rms values of the square wave.



**Solution:**

$$V_{\text{rms}} = \sqrt{\frac{(1600)(10 \times 10^{-3}) + (1600)(10 \times 10^{-3})}{20 \times 10^{-3}}}$$

$$= \sqrt{\frac{32,000 \times 10^{-3}}{20 \times 10^{-3}}} = \sqrt{1600}$$

$$V_{\text{rms}} = 40 \text{ V}$$

**Problem 3**

Determine the effective values of

a)  $i = 50\sin(\omega t + 20) \text{ mA}$

b)  $v = 10\cos 2\omega t \text{ V}$

**Problem 4**


The 120-V dc source delivers 3.6 W to the load. Determine the peak value of the applied voltage ( $V_m$ ) and the current ( $I_m$ ) if the ac source is to deliver the same power to the load.

### **RESPONSE OF BASIC R, L, AND C ELEMENTS TO A SINUSOIDAL VOLTAGE OR CURRENT**

R, L, and C circuit elements each have quite different electrical properties. Resistance, for example, opposes current, while inductance opposes changes in current, and capacitance opposes changes in voltage.
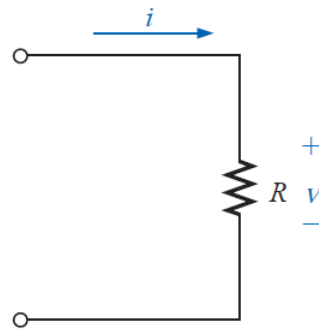
#### 1) **Resistor**

For a purely resistive element, the voltage across and the current through the element are in phase, with their peak values related by Ohm's law.



For  $v = V_m \sin \omega t$ ,


$$i = \frac{v}{R} = \frac{V_m \sin \omega t}{R} = \frac{V_m}{R} \sin \omega t = I_m \sin \omega t$$

$$I_m = \frac{V_m}{R}$$

Or

$$v = iR = (I_m \sin \omega t)R = I_m R \sin \omega t = V_m \sin \omega t$$


$$V_m = I_m R$$

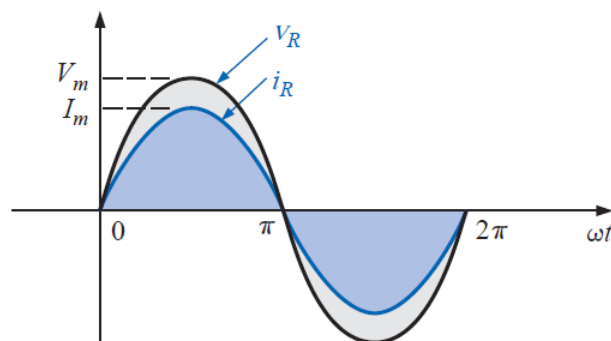

## 2) Inductor

For an inductor,  $v_L$  leads  $i_L$  by  $90^\circ$ , or  $i_L$  lags  $v_L$  by  $90^\circ$ .

$$v_L = L \frac{di_L}{dt}$$

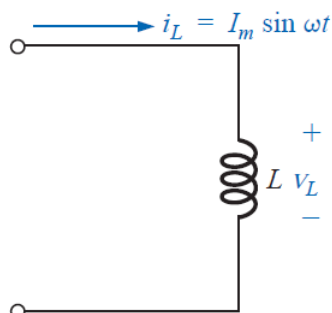

$$\frac{di_L}{dt} = \frac{d}{dt}(I_m \sin \omega t) = \omega I_m \cos \omega t$$


$$v_L = L \frac{di_L}{dt} = L(\omega I_m \cos \omega t) = \omega L I_m \cos \omega t$$

$$v_L = V_m \sin(\omega t + 90^\circ)$$

$$V_m = \omega L I_m$$

$$i_L = I_m \sin(\omega t \pm \theta)$$
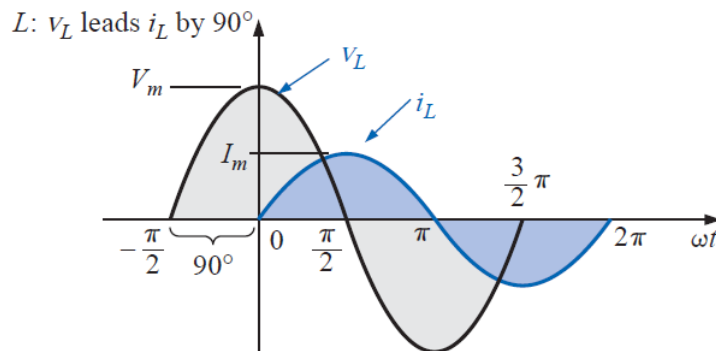
$$v_L = \omega L I_m \sin(\omega t \pm \theta + 90^\circ)$$



The quantity  $\omega L$ , called the **reactance** (from the word *reaction*) of an inductor, is symbolically represented by  $X_L$  and is measured in ohms; that is,

$$X_L = \omega L \quad (\text{ohms, } \Omega)$$


$$X_L = \frac{V_m}{I_m} \quad (\text{ohms, } \Omega)$$

$$X_L = \omega L = 2\pi f L = 2\pi L f$$

### 3) Capacitor

For a particular capacitance, the greater the rate of change of voltage across the capacitor, the greater the capacitive current.

$$i_C = C \frac{dv_C}{dt}$$

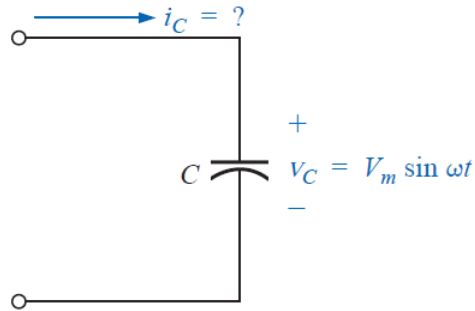

$$\frac{dv_C}{dt} = \frac{d}{dt}(V_m \sin \omega t) = \omega V_m \cos \omega t$$

$$i_C = C \frac{dv_C}{dt} = C(\omega V_m \cos \omega t) = \omega C V_m \cos \omega t$$

$$i_C = I_m \sin(\omega t + 90^\circ)$$

$$I_m = \omega C V_m$$

For a capacitor,  $i_C$  leads  $v_C$  by  $90^\circ$ , or  $v_C$  lags  $i_C$  by  $90^\circ$ .

$$v_C = V_m \sin(\omega t \pm \theta)$$


$$i_C = \omega C V_m \sin(\omega t \pm \theta + 90^\circ)$$

The quantity  $1/\omega C$ , called the **reactance** of a capacitor, is symbolically represented by  $X_C$  and is measured in ohms; that is,

$$X_C = \frac{1}{\omega C} \quad (\text{ohms, } \Omega)$$

$$X_C = \frac{V_m}{I_m} \quad (\text{ohms, } \Omega)$$

$$X_C = \frac{1}{2\pi f C}$$

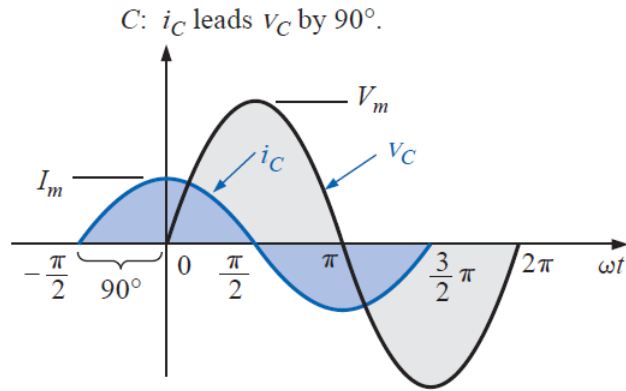

**EXAMPLE:** The voltage across a resistor is indicated. Find the sinusoidal expression for the current if the resistor is  $10\ \Omega$ . Sketch the curves for  $v$  and  $i$ .

a)  $v = 100 \sin 377t$

b)  $v = 25 \sin(377t + 60^\circ)$


**Solutions:**

a)

$$I_m = \frac{V_m}{R} = \frac{100\text{ V}}{10\ \Omega} = 10\text{ A}$$

( $v$  and  $i$  are in phase)

$$i = 10 \sin 377t$$

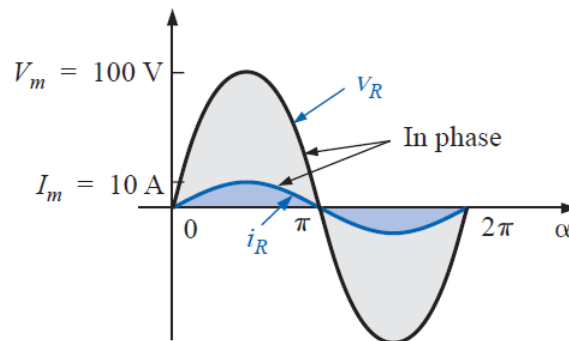


b)

$$I_m = \frac{V_m}{R} = \frac{25\text{ V}}{10\ \Omega} = 2.5\text{ A}$$

( $v$  and  $i$  are in phase)

$$i = 2.5 \sin(377t + 60^\circ)$$

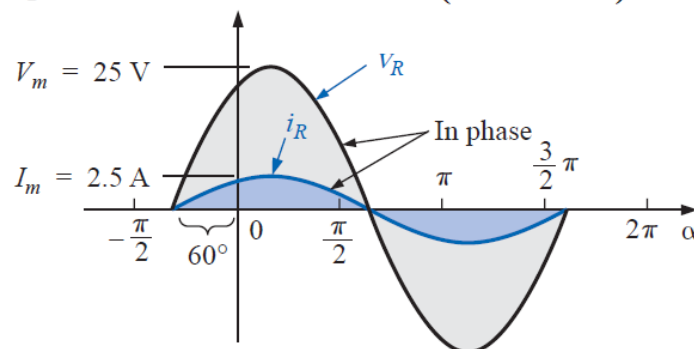



**EXAMPLE:** The current through a 0.1-H coil is provided. Find the sinusoidal expression for the voltage across the coil. Sketch the  $v$  and  $i$  curves.

a)  $i = 10 \sin 377t$

b)  $i = 7 \sin(377t - 70^\circ)$

**Solutions:**


a)

$$X_L = \omega L = (377 \text{ rad/s})(0.1 \text{ H}) = 37.7 \Omega$$

$$V_m = I_m X_L = (10 \text{ A})(37.7 \Omega) = 377 \text{ V}$$

$v$  leads  $i$  by  $90^\circ$

$$v = 377 \sin(377t + 90^\circ)$$

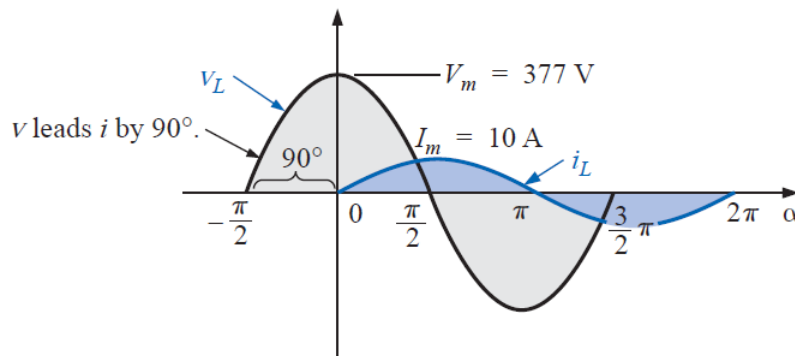


b)

$$V_m = I_m X_L = (7 \text{ A})(37.7 \Omega) = 263.9 \text{ V}$$

$v$  leads  $i$  by  $90^\circ$

$$v = 263.9 \sin(377t - 70^\circ + 90^\circ)$$

$$v = 263.9 \sin(377t + 20^\circ)$$

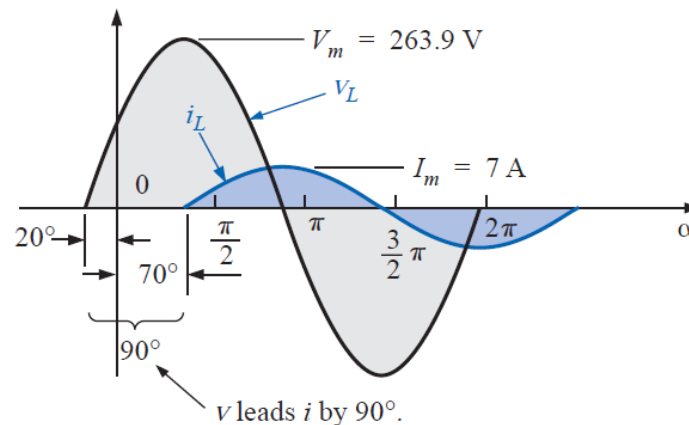


**EXAMPLE:** The voltage across a  $1\text{-}\mu\text{F}$  capacitor is provided below. What is the sinusoidal expression for the current? Sketch the  $v$  and  $i$  curves.  
 $v = 30 \sin 400t$

**Solutions:**

$$X_C = \frac{1}{\omega C} = \frac{1}{(400 \text{ rad/s})(1 \times 10^{-6} \text{ F})} = \frac{10^6 \Omega}{400} = 2500 \Omega$$

$$I_m = \frac{V_m}{X_C} = \frac{30 \text{ V}}{2500 \Omega} = 0.0120 \text{ A} = 12 \text{ mA}$$

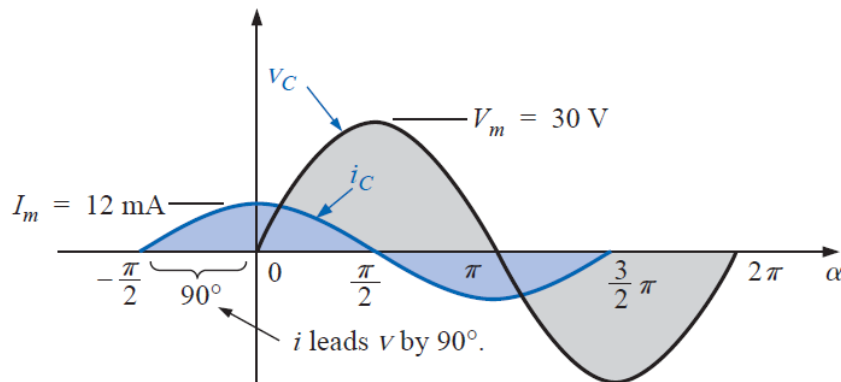$i$  leads  $v$  by  $90^\circ$        $i = 12 \times 10^{-3} \sin(400t + 90^\circ)$



**EXAMPLE:** At what frequency will the reactance of a  $200\text{-mH}$  inductor match the resistance level of a  $5\text{-k}\Omega$  resistor?

**Solutions:**

$$\begin{aligned} 5000 \Omega &= X_L = 2\pi fL = 2\pi Lf \\ &= 2\pi(200 \times 10^{-3} \text{ H})f = 1.257f \end{aligned}$$

$$f = \frac{5000 \text{ Hz}}{1.257} \cong 3.98 \text{ kHz}$$