



Class: 1st
Subject: Electrical Technology
Lecturer: Omar A. Alkawak
E-mail: OmarAhmed@mustaqbal-college.edu.iq



Lecture No. 29-30


“Rectifiers”



Rectifier

Half – wave rectifier :

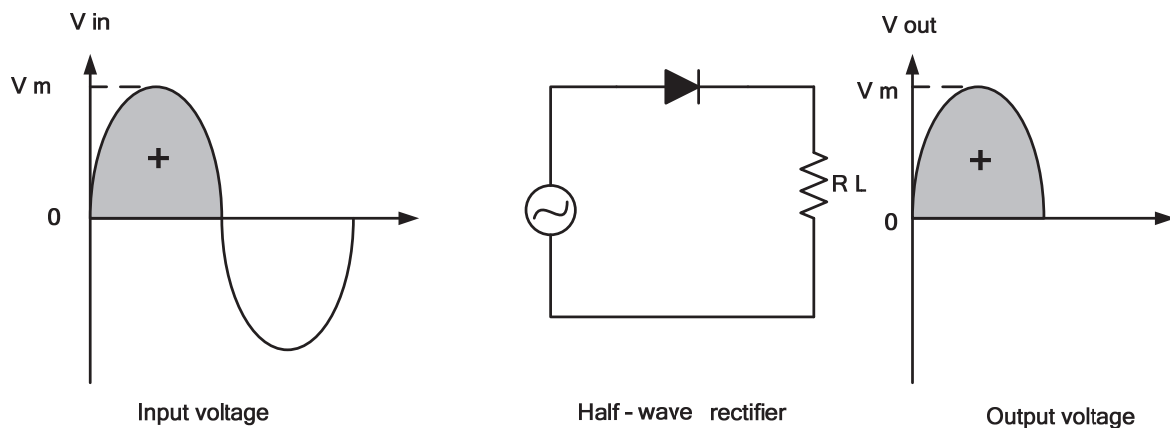A diode is connected to A.C source and load resistance as shown in figure below.



When the sinusoidal input voltage goes positive , the diode is forward biased and conducts current through the load resistor . The current produces an output voltage across R_L , which has the same shape as the positive half – cycle of the input voltage .

When the input voltage goes negative during the second half of its cycle the diode is reversed biased . There is no current , so the voltage across R_L is zero . The net result is that only the positive half – cycle of A.C input voltage appears across the load .

We can calculate the output voltage and output current as below :

$$V_{av} = \frac{V_m}{\pi} \quad (\text{if barrier potential is neglected})$$



$$V_{av} = \frac{V_m - 0.7}{\pi} \quad (\text{if the barrier potential is not neglected})$$

$$V_{r.m.s} = \frac{V_m}{2}$$

$$I_{r.m.s} = \frac{I_m}{2}$$

Input maximum voltage (V_m) = input r.m.s voltage $\times \sqrt{2}$

Efficiency of half – wave rectifier :

The ratio of D.C output power to the applied input A.C power is known as rectifier efficiency .

$$\eta = \frac{\text{D.C output power}}{\text{A.C input power}}$$

The output current is pulsating direct current , therefore in order to find D.C power , average current ($I_{d.c}$) has to be find out .

$$I_{av} = I_{d.c} = \frac{I_m}{\pi}$$

$$P_{d.c} = (I_{d.c})^2 \times R_L$$

$$P_{d.c} = (I_m / \pi)^2 \times R_L$$

The A.C input power has to be find out as :



$P_{a.c} = I_{r.m.s}^2 \times (R_f + R_L)$ where R_f is the forward resistance of the diode .

$$I_{r.m.s} = \frac{I_m}{2}$$

$$P_{a.c} = (I_m/2)^2 \times (R_f + R_L)$$

$$\eta = \frac{(I_m / \pi)^2 \times R_L}{(I_m / 2)^2 \times (R_f + R_L)}$$

$$\eta = \frac{0.406 R_L}{R_f + R_L}$$


$$\eta = \frac{0.406}{1 + (R_f / R_L)}$$

The efficiency will be maximum if R_f is negligible as compared to R_L

Maximum efficiency $\eta_{max.} = 40.6 \%$

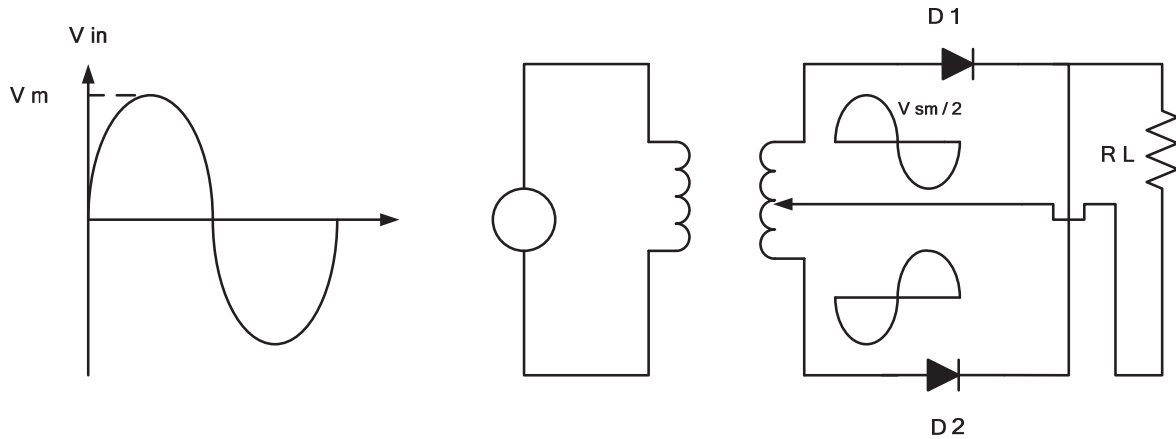2. Center – tapped full wave rectifier :

A center – tapped full wave rectifier uses two diodes connected to the secondary of a center – tapped transformer as shown in figure below .



Half of the total secondary voltage appears between the center tap and each diode . For positive half – cycle of the input voltage , the positive of the secondary voltage will make diode D1 forward biased and diode D2 reverse biased (D1 ON , D2 OFF).

For negative half – cycle an opposite condition occurs (D1 OFF , D2 ON).

Because the output current during both the positive and negative portion of the input cycle is in the same direction through the load resistor , we shall obtain full wave rectified D.C voltage .


$$V_{\text{out}} = \frac{V_{\text{m(sec)}}}{2} - 0.7 \quad \text{volt}$$

$$V_{\text{d.c}} = V_{\text{av}} = \frac{2 V_{\text{out}}}{\pi}$$



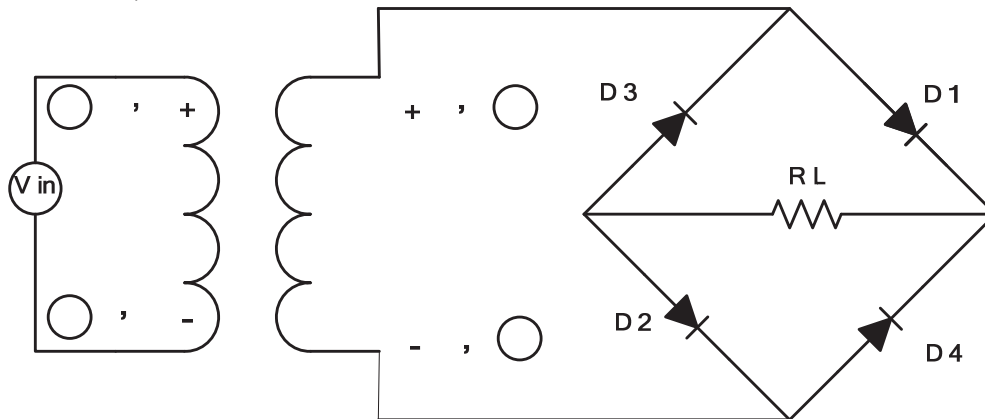3. Bridge full wave rectifier :

The bridge rectifier uses four diodes connected as shown in figure below . When the input voltage is positive , diodes D1 and D2 are forward biased and conduct current and voltage developed across the load . During this time D3 and D4 are reverse biased .When the input voltage is negative D3 and D4 are forward biased and conduct current , while D1 and D2 are reversed biased .



+ , - (D1 , D2) Forward biased

(+) (-) (D3 , D4) Reversed biasd

$V_{out} = V_{m(sec)} - 1.4$ (because two diodes conduct at the same time)

$$V_{av} = \frac{2V_{out}}{\pi}$$



Efficiency of full wave rectifier :

$$\eta = \frac{\text{D.C output power}}{\text{A.C input power}}$$

Find out D.C output power:

$$P_{d.c} = I_{d.c}^2 \times R_L$$

$$I_{av} = I_{d.c} = \frac{2 I_m}{\pi}$$

$$P_{d.c} = (2 I_m / \pi)^2 \times R_L$$

Find out A.C input power:

$$P_{a.c} = I_{r.m.s}^2 \times (R_f + R_L)$$

$$I_{r.m.s} = \frac{I_m}{\sqrt{2}}$$

$$P_{a.c} = (I_m / \sqrt{2})^2 \times (R_f + R_L)$$

$$\eta = \frac{(2 I_m / \pi)^2 \times R_L}{(I_m / \sqrt{2})^2 \times (R_f + R_L)}$$

$$\eta = \frac{4 I_m^2 \times R_L}{\pi^2} \times \frac{2}{I_m^2 (R_f + R_L)}$$



Class: 1st
Subject: Electrical Technology
Lecturer: Omar A. Alkawak
E-mail: OmarAhmed@mustaqbal-
college.edu.iq



$$\eta = \frac{8 R_L}{\pi^2 (R_f + R_L)}$$

$$\eta = \frac{0.812}{1 + (R_f / R_L)}$$

Therefore maximum efficiency = 81.2 %